

Chapter 3- Exercise 7

Exercise 7. (a). The critical path of one multiply-add time can be achieved by using the transpose FIR filter structure as shown in Figure 3.7(a).

(b). The block filter with block size 3 can be described by

$$\begin{aligned} y(3k) &= ax(3k) + bx(3k-4) + cx(3k-6) & (3.7) \\ y(3k+1) &= ax(3k+1) + bx(3k-3) + cx(3k-5) \\ y(3k+2) &= ax(3k+2) + bx(3k-2) + cx(3k-4). \end{aligned}$$

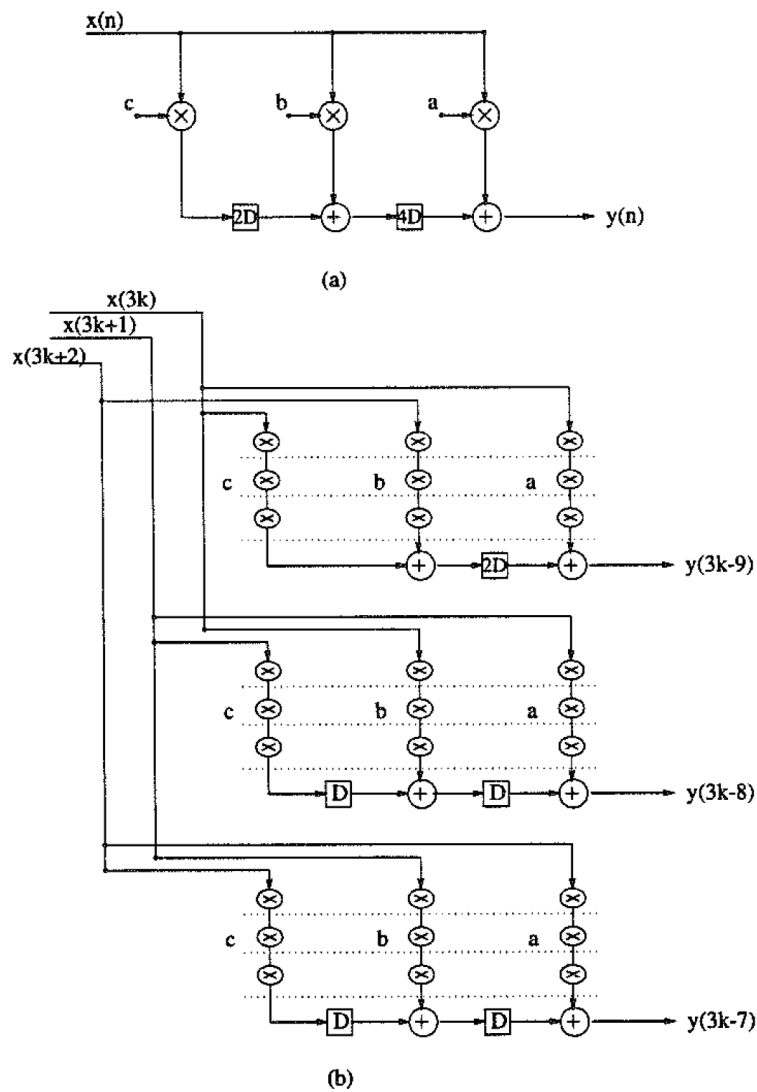


Fig. 3.7 (a):Transpose FIR filter for Exercise 7; (b):Pipelined Block Filter for Exercise 7

Chapter 4- Exercise 1


(a)

$$T_{I_{bound}} = \frac{T_m + 2T_a}{2} = 18ns \quad (4.1)$$

(b)

$$T_{critical} = 2(T_m + 3T_a) = 88ns \quad (4.2)$$


(c)

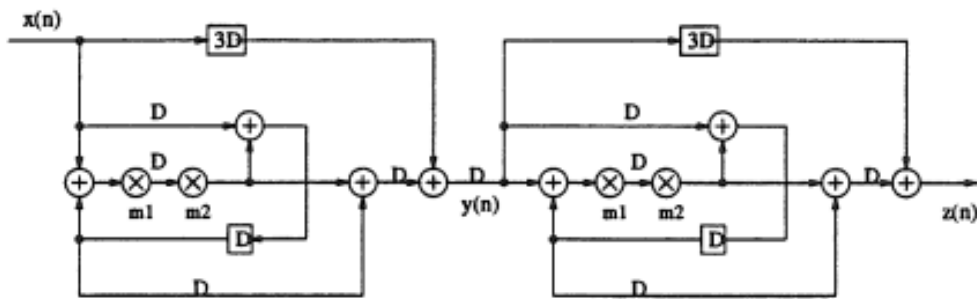

Chapter 4- Exercise 4

$$T_{\infty} = 2T \quad (4.5)$$

$$T_{critical} = 7T \quad (4.6)$$

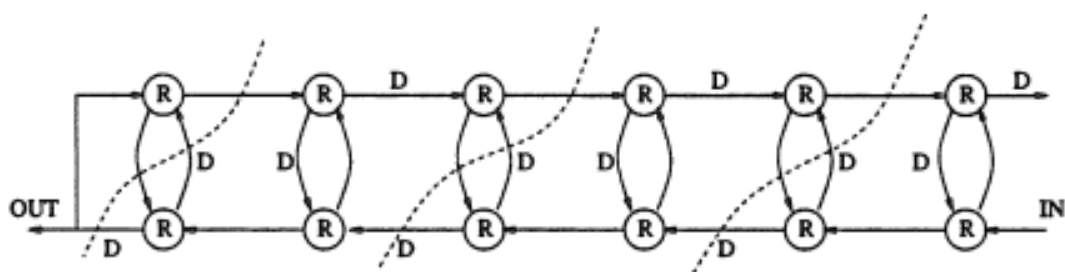


Chapter 4- Exercise 5


$$T_{\infty} = 4 \quad (4.7)$$

$$T_{critical} = 7 \quad (4.8)$$

(b) The minimum achievable clock period obtained with pipelining and retiming is the iteration bound of the DFG, which equals to $4u.t.$ in this problem.

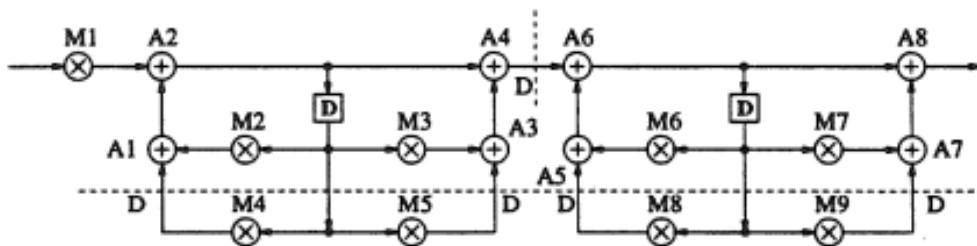

Chapter 4- Exercise 10

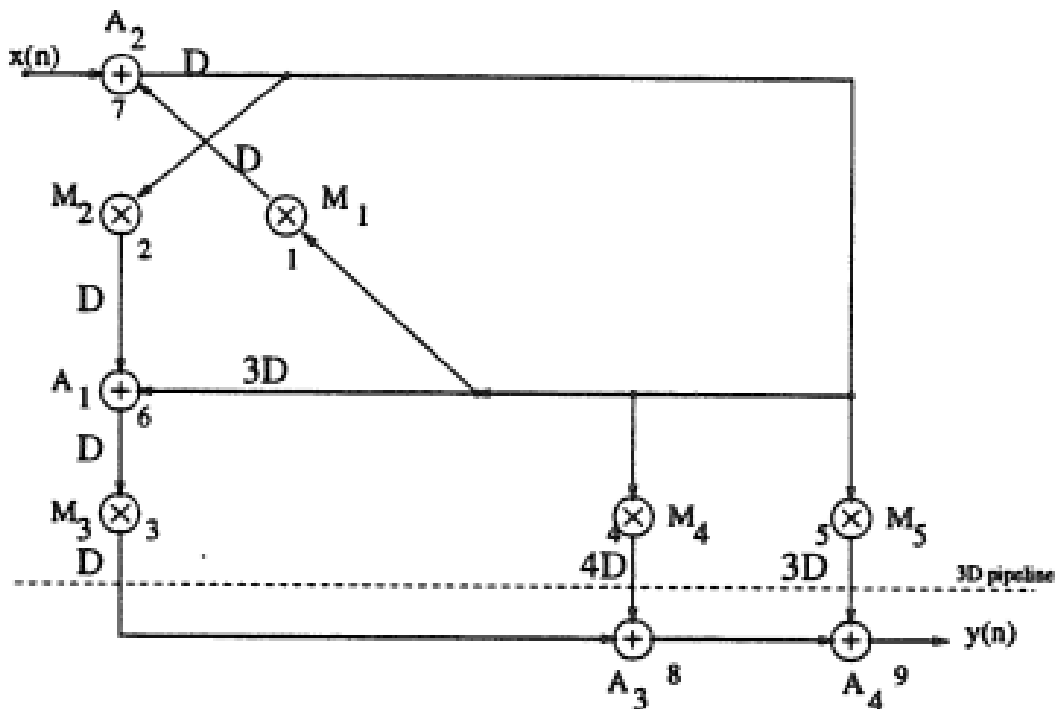

Chapter 5- Exercise 1

(a). The 3-unfolded DFG is as shown in Figure 4.1.


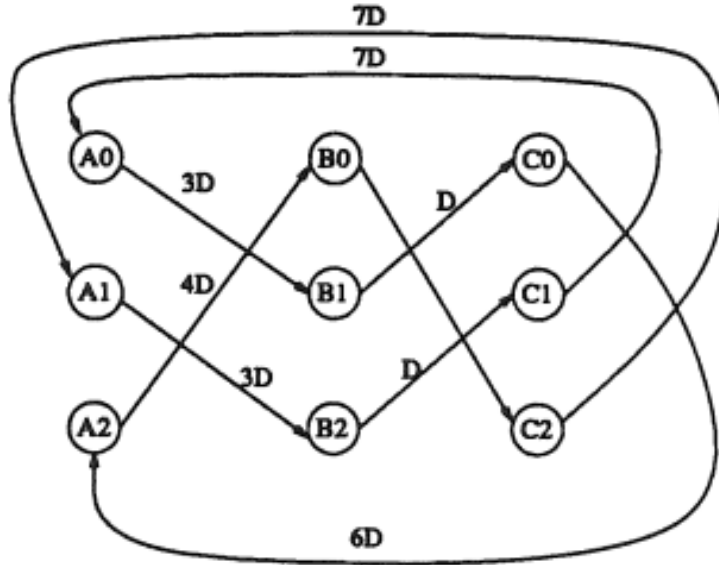


Fig. 4.1 The 3-unfolded DFG for Problem 1(a).

(b). The 4-unfolded DFG is as shown in Figure 4.2.

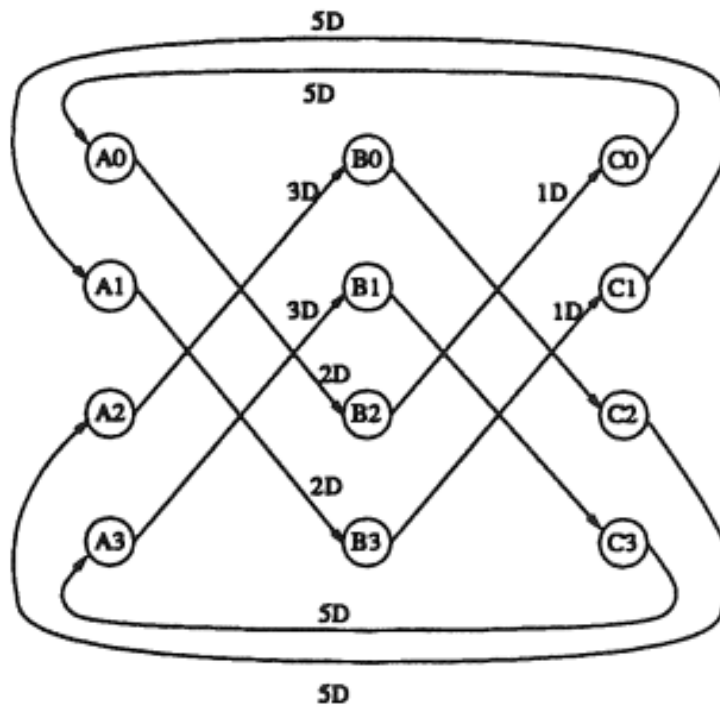

Chapter 5- Exercise 14

Exercise 14. The DFGs of the direct-form and data broadcast form FIR filter are shown in Figure 4.11(a) and (b), respectively.

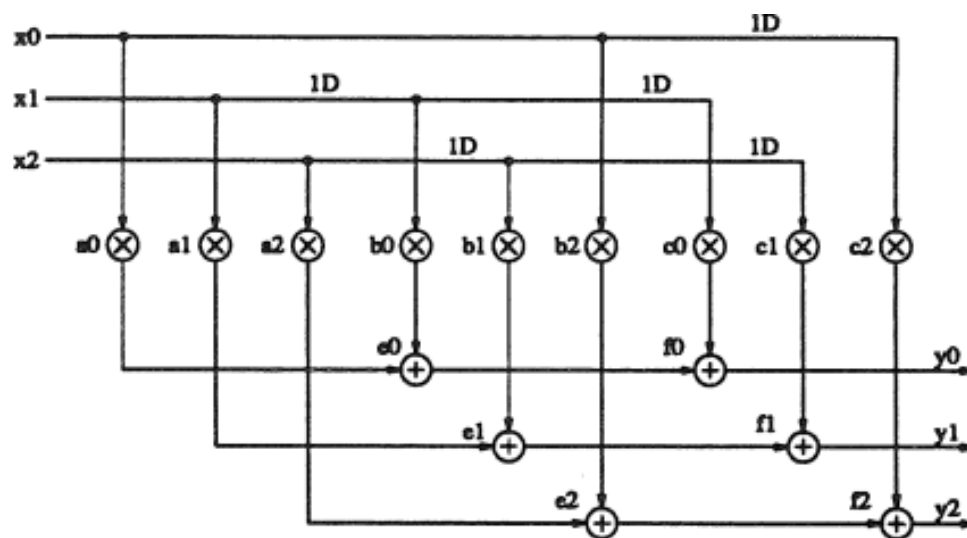
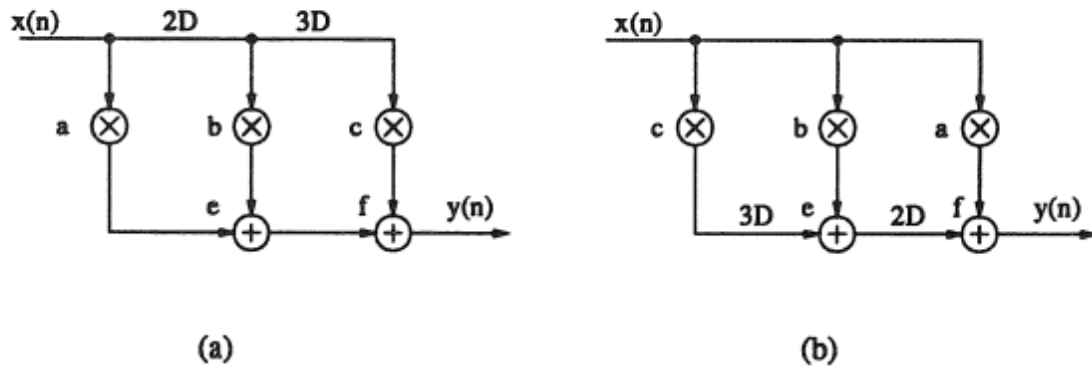


Fig. 4.12 The 3-unfolded DFG for the direct-form FIR filter in Problem 13.

Chapter 6- Exercise 1

Assuming each MA is pipelined by 1 stage,

$$D_F(x \rightarrow MA0) = 2 \times 0 + 0 - 0 - 0 = 0 \quad (6.1)$$

$$D_F(x \rightarrow MA1) = 1 \quad (6.2)$$

$$D_F(MA0 \rightarrow MA1) = 2 \times 1 + 1 - 0 - 1 = 2 \quad (6.3)$$

$$D_F(MA1 \rightarrow MA2) = 2 \times 1 + 0 - 1 - 1 = 0 \quad (6.4)$$

$$D_F(MA2 \rightarrow MA3) = 2 \times 1 + 1 - 0 - 1 = 2 \quad (6.5)$$

$$D_F(MA3 \rightarrow MA4) = 2 \times 1 + 0 - 1 - 1 = 0 \quad (6.6)$$

$$D_F(MA4 \rightarrow MA5) = 2 \times 1 + 1 - 0 - 1 = 2 \quad (6.7)$$

$$D_F(MA5 \rightarrow MA6) = 2 \times 1 + 0 - 1 - 1 = 0 \quad (6.8)$$

$$(6.9)$$

The folded structure is as following:

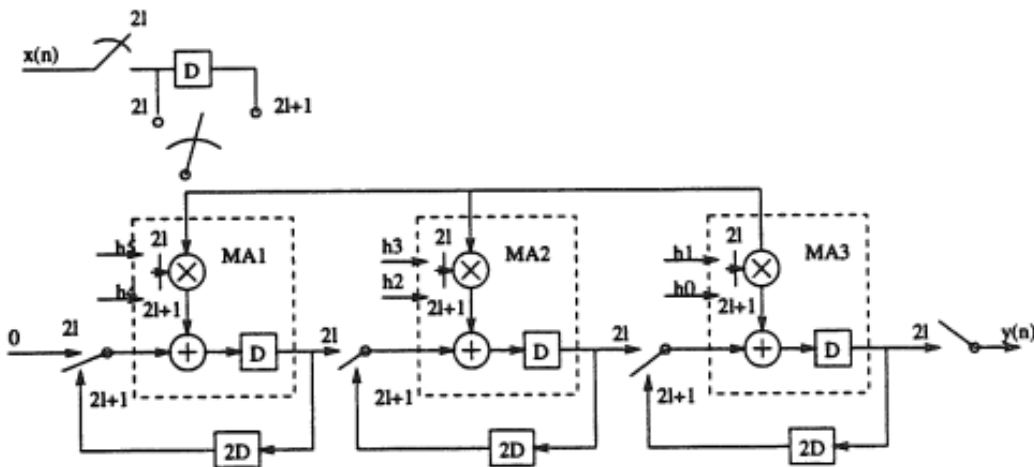


Fig. 6.1 The folded graph for problem 1(a).

(b).

Cycle	Out In	MA1/2	MA3/4	MA5/6
0	x0	$h5x0$	$h3x0$	$h1x0$
1	x0	$h4x0+h4x(-1)$	$h2x0+h3x(-1)$	$h0x0+h1x(-1)$
2	x1	$h5x1$	$h3x1+h4x0+h5x(-1)$	$h1x1+h2x0+h3x(-1)$
3	x1	$h4x1+h5x0$	$h2x1+h3x0$	$h0x1+h1x0$
4	x2	$h5x2$	$h3x2+h4x1+h5x0$	$h1x2+h2x1+h3x0$
5	x2	$h4x2+h5x1$	$h2x2+h3x1+h4x0+h5x(-1)$	$h0x2+h1x1+h2x0+h3x(-1)$
6	x3	$h5x3$	$h3x3+h4x2+h5x1$	$h1x3+h2x2+h3x1+h4x0+h5x(-1)$
7	x3	$h4x3+h5x2$	$h2x3+h3x2+h4x1+h5x0$	$h0x3+h1x2+h2x1+h3x0$
8	x4	$h5x4$	$h3x4+h4x3+h5x2$	$h1x4+h2x3+h3x2+h4x1+h5x0$
9	x4	$h4x4+h5x3$	$h2x4+h3x3+h4x2+h5x1$	$h0x4+h1x3+h2x2+h3x1+h4x0+h5x(-1)=y4$
10	x5	$h5x5$	$h3x5+h4x4+h5x3$	$h1x5+h2x4+h3x3+h4x2+h5x1$
11	x5	$h4x5+h5x4$	$h2x5+h3x4+h4x3+h5x2$	$h0x5+h1x4+h2x3+h3x2+h4x1+h5x0=y5$

Chapter 6- Exercise 18

Exercise 18 The golded delay edges are as in the following table:

$$\begin{aligned}
 D_{A1 \rightarrow A2} &= 0 - 1 + 3 - 2 = 0 \\
 D_{A2 \rightarrow A4} &= 4 \times 1 - 1 + 1 - 3 = 1 \\
 D_{A2 \rightarrow M1} &= 4 \times 1 - 1 + 0 - 3 = 0 \\
 D_{A2 \rightarrow M3} &= 4 \times 1 - 1 + 2 - 3 = 2 \\
 D_{A2 \rightarrow M2} &= 4 \times 1 - 1 + 1 - 3 = 1 \\
 D_{A2 \rightarrow M4} &= 4 \times 1 - 1 + 3 - 3 = 3 \\
 D_{A3 \rightarrow A4} &= 0 - 1 + 1 - 0 = 0 \\
 D_{M1 \rightarrow A1} &= 0 - 2 + 2 - 0 = 0 \\
 D_{M2 \rightarrow A1} &= 4 \times 1 - 2 + 2 - 1 = 3 \\
 D_{M3 \rightarrow A3} &= 4 \times 1 - 2 + 2 - 1 = 0 \\
 D_{M4 \rightarrow A3} &= 4 \times 1 - 2 + 2 - 1 = 3
 \end{aligned}$$

The folded architecture is shown in Figure 6.40. Unfold it, we get the delay element numbers and switch intervals in Table 6.7. Unfolded structure is the same as original one.

