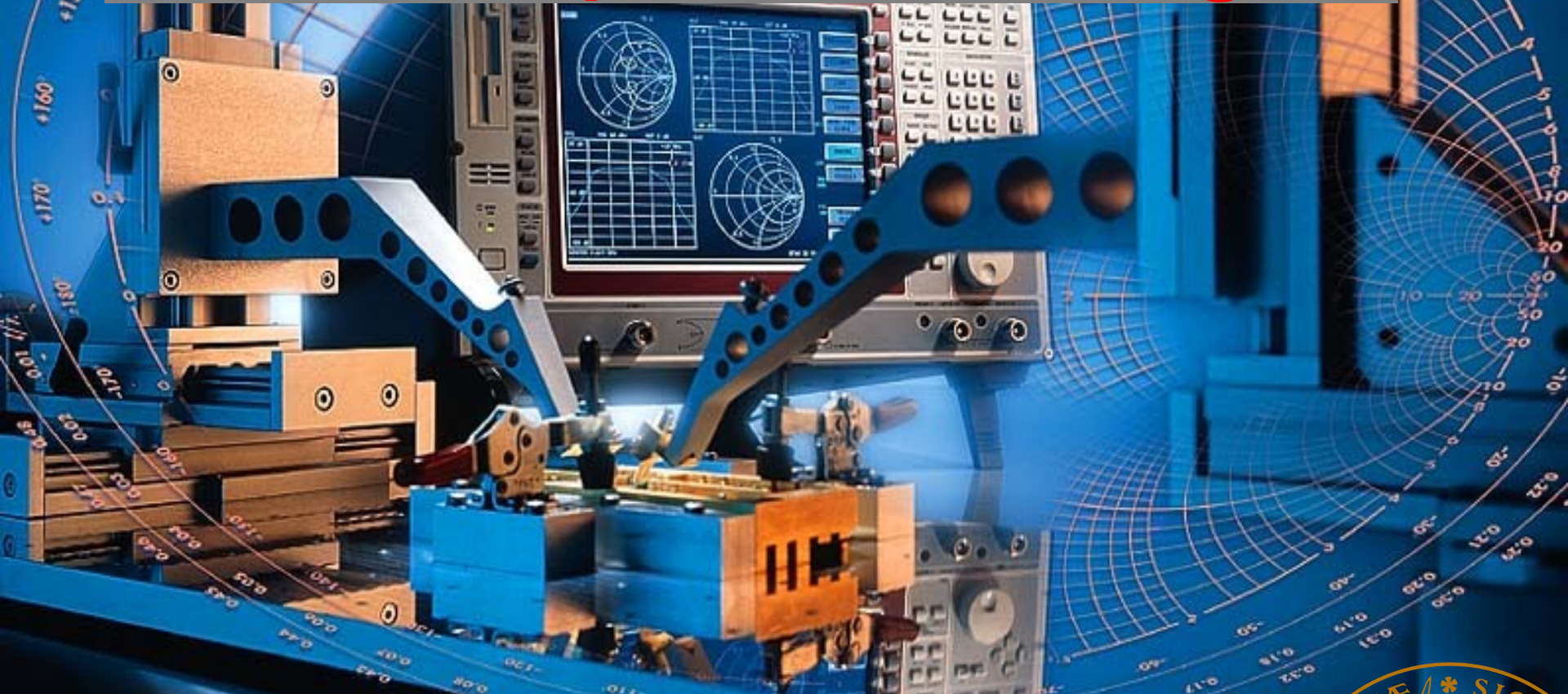


2019-11-04

# Welcome to RF Amplifier Design



Lars Ohlsson Fhager  
Electrical and Information Technology




# Lecture 1

- Introduction to RF Amplifier Design
- Information About the Course
- Resonant Circuits

# RF Amplifier Design

- Objective
  - Analysis and design of radio- and microwave amplifiers by using
    - discrete, passive and active components
    - lumped and distributed components
  - Knowledge about components
  - Measurement technique


# Some Applications

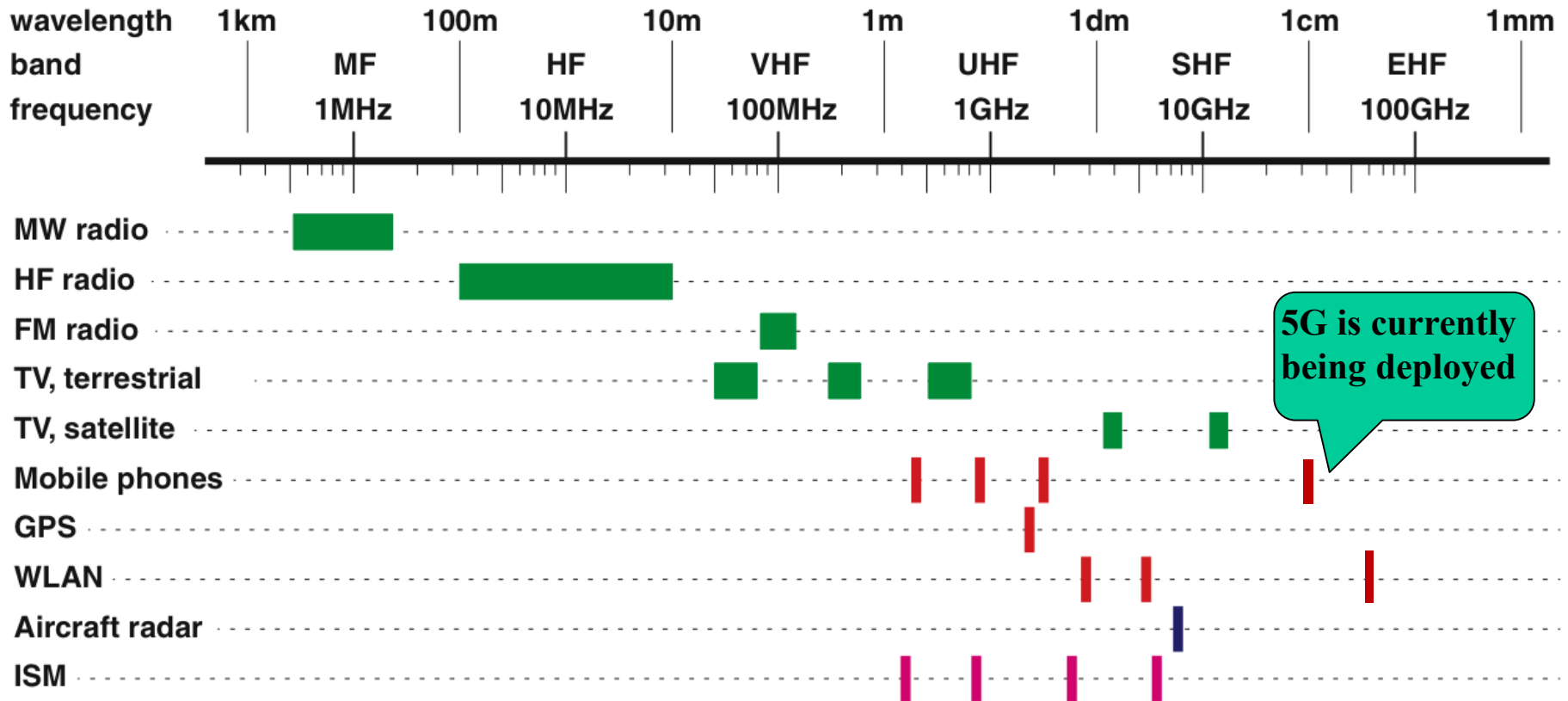


# IEEE Microwave Bands

• Band	Frequency range (GHz)
• HF	0.003 - 0.030
• VHF	0.030 - 0.300
• UHF	0.300 - 1.000
• L band	1.000 - 2.000
• S band	2.000 - 4.000
• C band	4.000 - 8.000
• X band	8.000 - 12.000
• Ku band	12.000 - 18.000
• K band	18.000 - 27.000
• Ka band	27.000 - 40.000
• Millimetre	40.000 - 300.000
• Sub millimetre	> 300.000

# Find the differences:

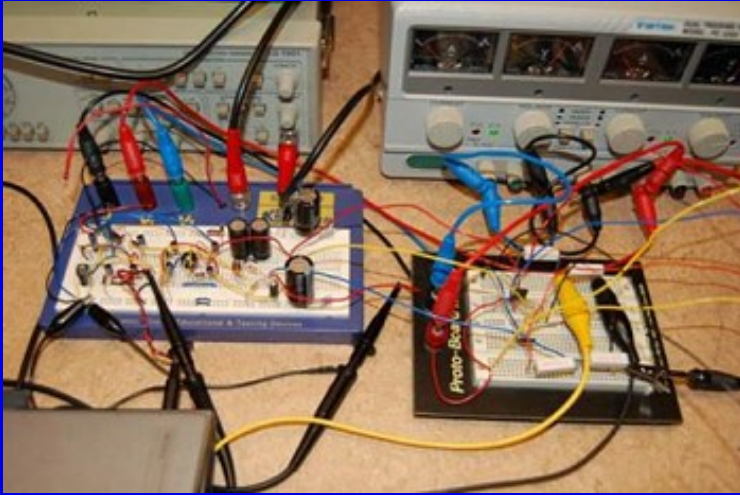


**Low Frequency**

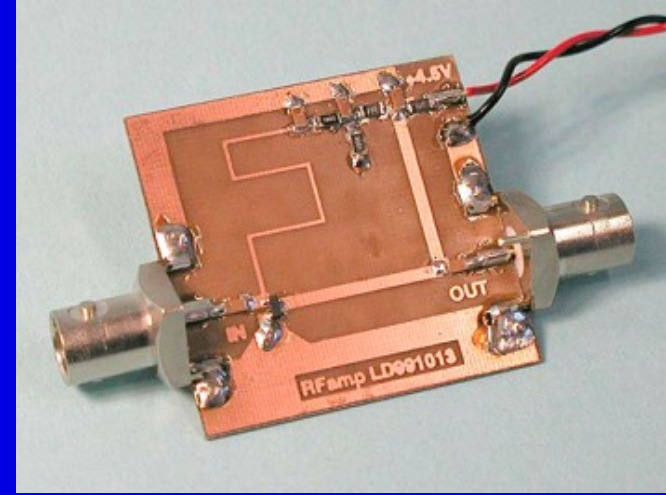

**Radio Frequency**

**Millimetre Wave**

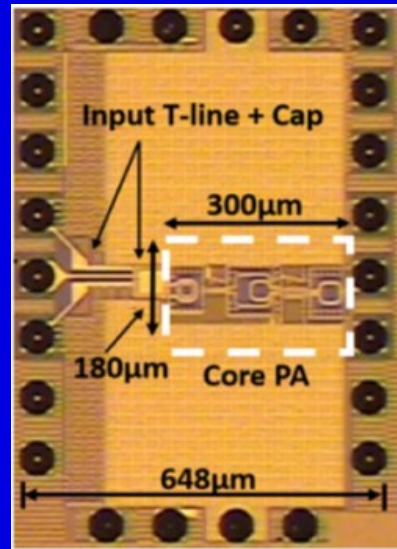

**Electronics**

*Callender et al. 2018  
75 GHz FinFET PA*

# Comparison

## Low frequency electronics


1. voltage or current interface between stages, “voltage matching” or “current matching”
2. small and large impedances are feasible
3. reactive components are often avoided - broadband circuits
4. parasitic reactance's in components limits the performance
5. the length of wires is in most cases uncritical

## Radio (or mmWave) frequency electronics

1. voltage or current interfaces are not possible due to parasitics
2. small and large impedances are difficult to produce due to parasitics
3. reactive components are usable - band-pass circuits are used to improve the performance
4. parasitic reactance's in components does not necessarily limit the performance
5. the length and width of wires is in most cases critical
6. reactive components may be implemented by transmission lines
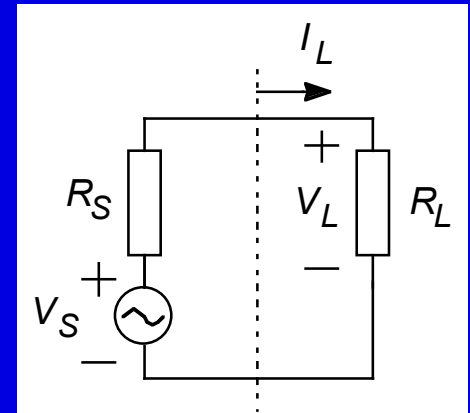
# Power Instead of Voltage and Current (1)


- Voltage matching
  - at low frequencies it is possible to realize a **high load resistance** relative to the source,  
 $R_S \ll R_L$   
i.e. the **“available voltage”** ends up at the load
- Current matching
  - at low frequencies it is possible to realize a **low load resistance** relative to the source,  
 $R_S \gg R_L$   
i.e. the **“available current”** ends up through the load
- Power matching
  - A source has besides an available voltage or current also an **“available power”**...




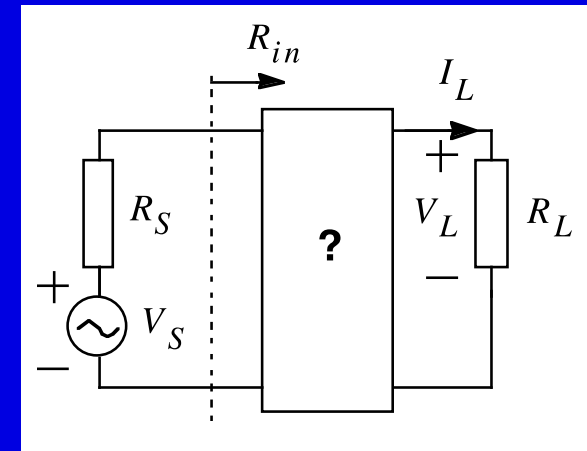
# Power Instead of Voltage and Current (2)

- Power matching
  - Instead of transferring available voltage or current to the load:  
**transfer available power**
  - From circuit theory:  
the transfer of power is maximized when  
 $R_S = R_{in}$
  - or generally at **complex conjugate matching**  
 $Z_S = Z_{in}^*$
  - If both  $R_S$  and  $R_L$  are fixed we may maximize the transfer of power and accordingly optimize the voltage and the current.
- We need a lossless matching network between  $R_S$  and  $R_L$ .




# Power Instead of Voltage and Current (3)

- reactive elements → no or low losses
  - available power may be preserved and transferred to the load, by that also the transfer of voltage and current optimized.
- drawback: not a broadband solution

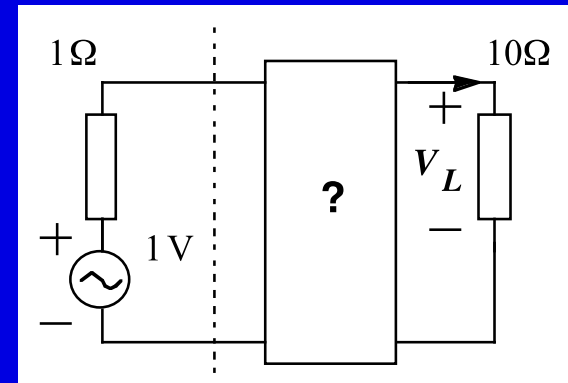- **example:**

- without matching:  $V_L = 0.9 \text{ V}$   
 $P_L = 0.08 \text{ W}$
- with matching:  $V_L = 1.6 \text{ V}$   
 $P_L = 0.25 \text{ W}$
- **x4 with matching**



# RF Amplifier Design Compared to Traditional (low frequency) Analog Electronics

- **Transmission of power** rather than voltage or current
- **Reactive circuit elements** - lumped or distributed
- New design methods
- Device models where parasitics must be considered
- Interesting measurements equipment

# RF Amplifier Design ETIN50 Facts

- ECTS: 7.5
- Level A
- open for E4, N4, EEE, COM, etc.
- Literature: L. Sundström, G. Jönsson and H. Börjeson, “Radio Electronics”
- Teaching in period ht 2:
  - 9 lectures and 8 exercise slots
  - 4 compulsory laboratory exercises
  - 2 compulsory hand-in assignments
- Examination:
  - passed written exam
  - passed hand-in exercises
  - passed laboratory exercises

# RF Amplifier design ETIN50 Contents

- Resonant circuits
- Transmission lines
- The Smith chart
- Matching
- IF amplifiers
- RF amplifiers
  - Z-, Y- and S-parameters
  - stability
  - power gain
  - noise properties
  - DC design
- Oscillators

ETIN50 – RF Amplifier Design - 2018 Ht2						
Johan Wernehag		The course replaces Radio Elektronik ETIO32				
week	day	date	time	room	activity	contents
1	mån	2018-11-05	13-15	E:3139	L1	Introduction, resonant circuits
	ons	2018-11-07	10-12	E:2311	L2	Waves on transmission lines
	ons	2018-11-07	13-15	E:4119	E1	Resonant circuits Ex: all in Exercises 1
2	mån	2018-11-12	13-15	E:3139	L3	The Smith chart, matching
	ons	2018-11-14	10-12	E:4119	E2	Transmission lines Ex: all in Exercises 2 except 2.6 and 2.9
	ons	2018-11-14	13-15	E:4119	E3	The Smith chart Ex: all in Exercises 4
	tor	2018-11-15	*	E:2427	Lab1	Resonant circuit and transmission line resonator
3	mån	2018-11-19	13-15	E:3139	L4	Matching (cont.), passive components
	ons	2018-11-21	10-12	E:2311	L5	Transistors, HF amplifiers, amplifier design (z, y, ABCD): 2-port representation of transistors, power gain definitions, stability
	ons	2018-11-21	13-15	E:4119	E4	Matlab demo, matching Ex: all in Exercises 5 except 5.5
fre	2018-11-23	Hand in of the solution to hand-in assignment 1				Analysis of a network in the Smith chart and calculations in Matlab and deslilb
4	mån	2018-11-26	13-15	E:3139	L6	Amplifier design: S-parameters, gain definitions, stability, RF measurements
	ons	2018-11-28	10-12	E:2311	L7	Amplifier design: design methodologies, noise optimization
	ons	2018-11-28	13-15	E:4119	E5	Matching, medium frequency amplifiers Ex: all in Exercises 6
fre	2018-11-30	*	E:2427	Lab2		RF measurement techniques, S-parameter measurements on a transistor
5	mån	2018-12-03	13-15	E:3139	L8	Amplifier design: DC design
	ons	2018-12-05	10-12	E:4119	E6	2-port, S-parameters DC design, hand-in assignment 2 Ex: Exercises 9.1, 9.2 and 9.4
	ons	2018-12-05	13-15	E:4119	E7	Stability, design of RF amplifiers Ex: all in Exercises 8 except 8.3, 8.5, 8.6, 8.7, 8.9, 8.10, 8.12 and 8.14
	fre	2018-12-07	Hand in of the solution to hand-in assignment 2			
6	mån	2018-12-10	13-15	E:3139	L9	Oscillators
	tis	2018-12-11	*	E:4119	Lab3	RF amplifiers
	ons	2018-12-12	13-15	E:4119	E9	Analysis of IF amplifiers, oscillators Ex: all in Exercises 10 except 10.3
fre	2018-12-14	*	E:2427	Lab4		Oscillators
7	mån	2018-12-17	13-15	E:3139	Q1	Preparation for the exam. Answering students questions
8	fre	2018-01-05	8-13	E:2311		Examination

\* separate registration L = Lecture, E = Exercise, Lab = Lab exercise, Q = Question hour

# Prerequisites

- Circuit Theory
- Analog Electronics
- Introduction to wireless systems EITF50  
(or ETI031, ETIF05)

# Course Materials

- Textbook: “Radio Electronics” (the blue book) (available as pdf at LU Canvas)
- Study materials (the green book) (available as pdf)
  - Exercises and solutions
  - Laboratory experiments
- Formulas and Tables (the red book)
- The complete package is sold at KFS
- Smith charts
- Deslib, toolbox for Matlab (available at LU Canvas)
- Example exam (available at the LU Canvas)

# Schedule

Course facts

Course Description

Course Information

Course Material

Laboratory Lessons

Schedule

Lectures

Messages

Sign up

Results

ETIN50 RF Amplifier Design  
Schedule  
2018/2019

Link to "[Schemageneratorn](#)"

**ETIN50 – RF Amplifier Design - 2018 Ht2**  
Johan Wernehag      The course replaces Radio Electronics ETI032

week	day	date	time	room	activity	contents
1	mån	2018-11-05	13-15	E:3139	L1	Introduction, resonant circuits
	ons	2018-11-07	10-12	E:2311	L2	Waves on transmission lines
	ons	2018-11-07	13-15	E:4119	E1	Resonant circuits Ex: all in Exercises 1
2	mån	2018-11-12	13-15	E:3139	L3	The Smith chart, matching
	ons	2018-11-14	10-12	E:4119	E2	Transmission lines Ex: all in Exercises 2 except 2.6 and 2.9
	ons	2018-11-14	13-15	E:4119	E3	The Smith chart Ex: all in Exercises 4
	tor	2018-11-15	*	E:2427	Lab1	Resonant circuit and transmission line resonator
3	mån	2018-11-19	13-15	E:3139	L4	Matching (cont.), passive components

- Lectures and lessons
- Four compulsory laboratory exercises
- Two compulsory hand-in assignments
- Continuous assessment
- Written exam
- Home page: [www.eit.lth.se/course/etin50](http://www.eit.lth.se/course/etin50)
- LU Canvas: <https://canvas.education.lu.se/> > ETIN50




# Resonant Circuits


- Concepts
  - resonant circuit
  - resonant frequency
  - circuit Q
  - bandwidth
- Basic circuits
  - series resonant circuit
  - parallel resonant circuit
  - series-to-parallel conversion
  - capacitive and inductive taps
  - transformer
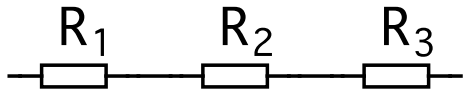
# Resonant Circuits

- Series circuits are handled by summing the **impedances**



$$R_{tot} = R_1 + R_2 + R_3$$

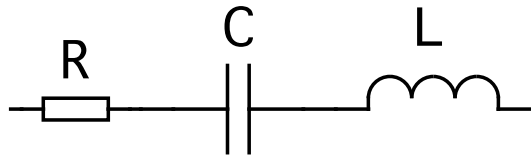

**Series resonance**


$$Z_{tot}(\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

The frequency that leaves a purely resistive impedance is called **the resonant frequency**:


$$\omega_0 L - \frac{1}{\omega_0 C} = 0 \Rightarrow f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$
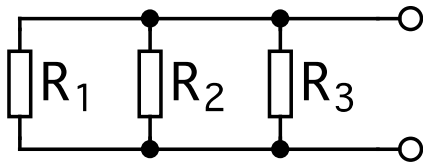
# Resonant Circuits

- Parallel circuits are handled by summing the **admittances**


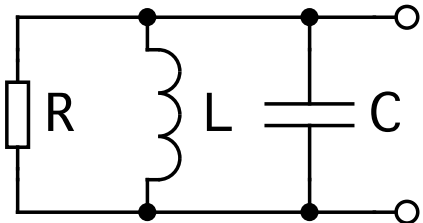
$$Y = \frac{1}{R_{tot}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



**Parallel resonance**

$$Y_{tot}(\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

The frequency that leaves a purely resistive admittance is called **the resonant frequency**:

$$\omega_0 C - \frac{1}{\omega_0 L} = 0 \Rightarrow f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$


# Circuit Q - Quality Factor

$$Q = 2\pi \frac{\text{maximum energy stored in the circuit}}{\text{energy dissipated per cycle}}$$

- is a measure of the maximum instantaneous stored energy related to the total energy dissipated in the circuit
  - Max. reactive energy / active energy
- is dimensionless
- is called “Q-värde” (“godhetstal” in Swedish)
- is also used for non-electronic systems
- is also applicable to non-resonant circuits such as
  - RC-circuit or
  - individual components such as a coil
- is equal to the ratio between the resonance frequency and the 3dB bandwidth:

$$Q = \frac{f_0}{B_{3dB}}$$


# Quality Factor - Some Comparisons

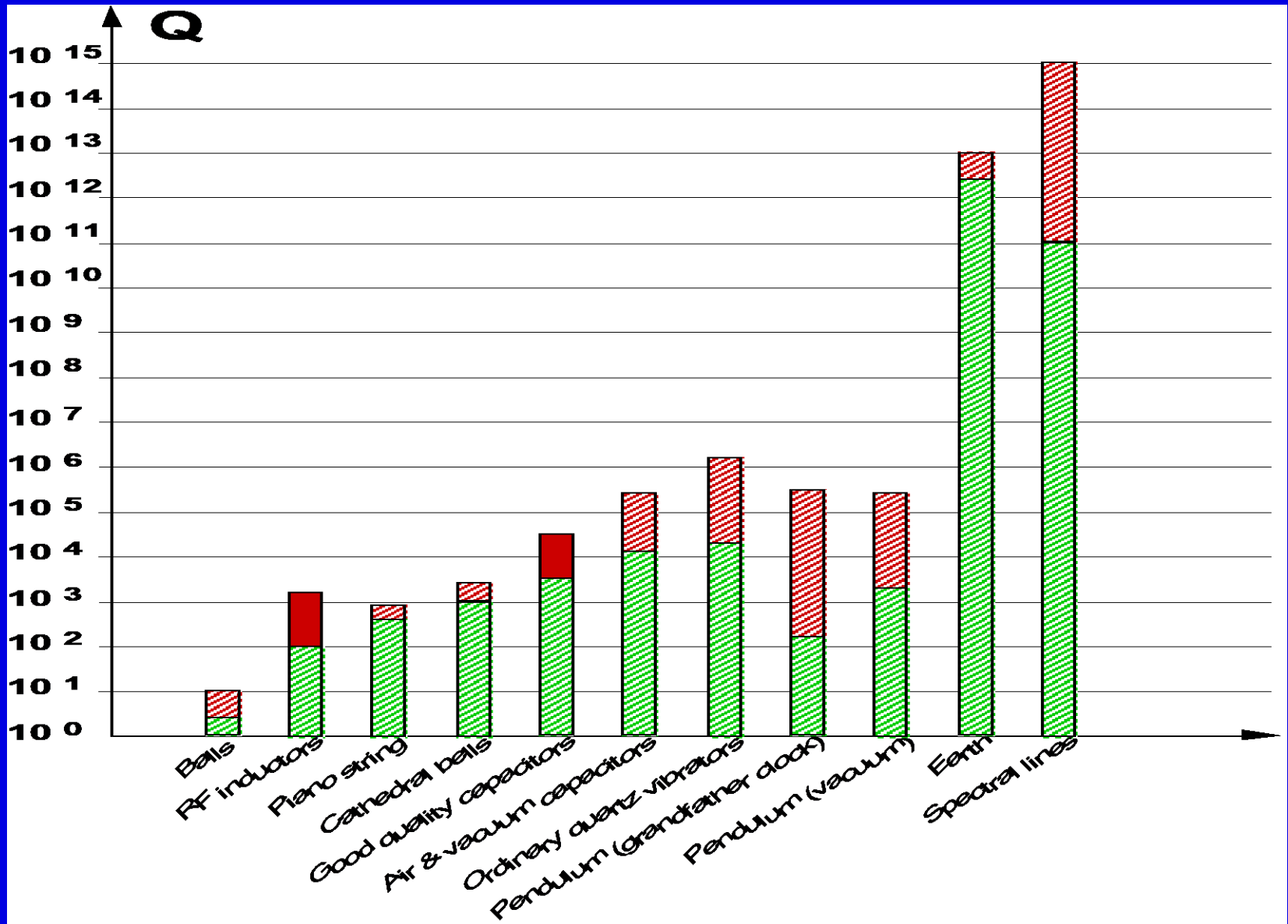

# Circuit Q


## Series circuit Q

$$Q = \frac{|X|}{R_s} = \frac{\omega_0 L_s}{R_s} = \frac{1}{R_s \omega_0 C_s} = \frac{\sqrt{L_s / C_s}}{R_s}$$

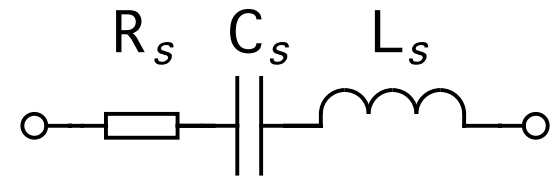

## Parallel circuit Q



$$Q = \frac{R_p}{|X|} = R_p \omega_0 C_p = \frac{R_p}{\omega_0 L_p} = \frac{R_p}{\sqrt{L_p / C_p}}$$

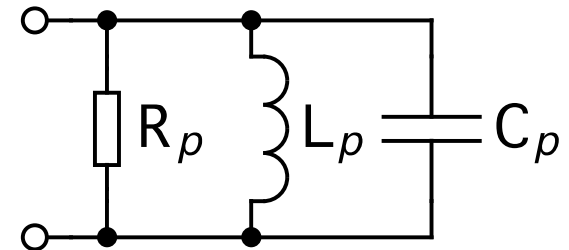

- Characteristic impedance  $Z_0 = \sqrt{L/C}$  ohms
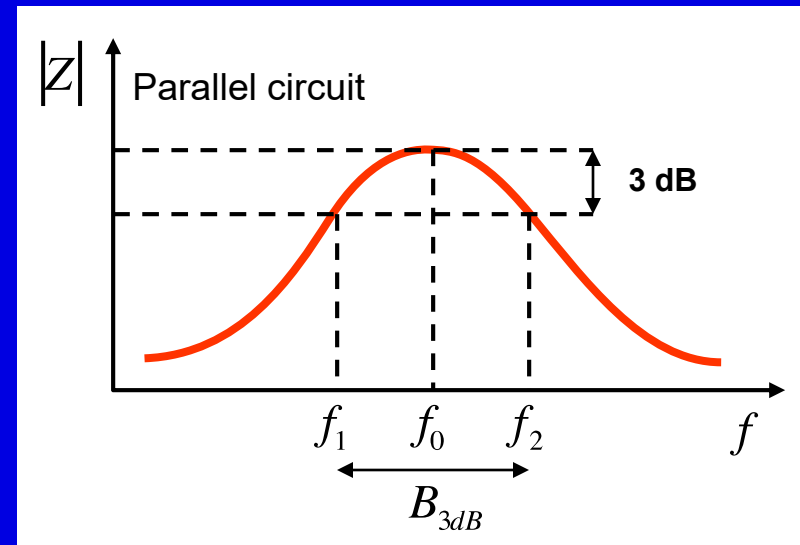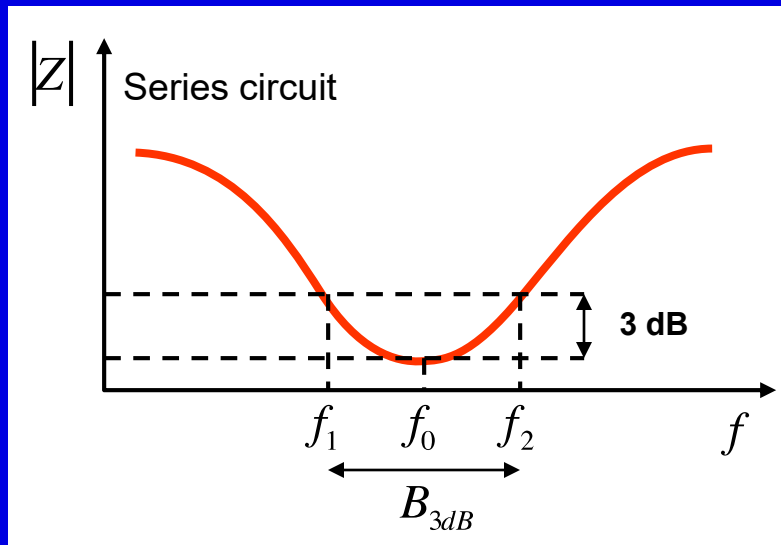
# Bandwidth

- The **3dB-bandwidth** is defined as the frequency range where the circuit impedance or admittance has changed 3dB.



$$B_{3dB} = f_2 - f_1 = \frac{f_0}{Q}$$

# Bandwidth

- regarding the parallel circuit

$$Y(\omega) = G + j \left( \omega C - \frac{1}{\omega L} \right) = G + \frac{j}{\omega L} (\omega^2 LC - 1)$$

- set  $\omega = \omega_0 + \Delta\omega$  and  $\omega_0 = 1/\sqrt{LC}$ :

$$\begin{aligned} Y(\omega) &= G + \frac{j}{\omega L} \left( \left[ \left( \frac{1}{\sqrt{LC}} \right)^2 + 2\Delta\omega\omega_0 + (\Delta\omega)^2 \right] LC - 1 \right) = \\ &= G + \frac{j}{\omega L} (2\Delta\omega\omega_0 + (\Delta\omega)^2) LC \end{aligned}$$

$$Y(\omega) \approx G + j2\Delta\omega C$$

- Compare to a parallel RC-link with  $R = 1/G$ ,  $C' = 2C$  and  $\omega = \Delta\omega$




# Bandwidth (cont.)

- for small  $\Delta\omega$  the circuit behaves like a parallel RC-link:

$$Y(\omega) \approx G + j2\Delta\omega C$$

- the bandwidth of an RC-link  $= 1/RC$

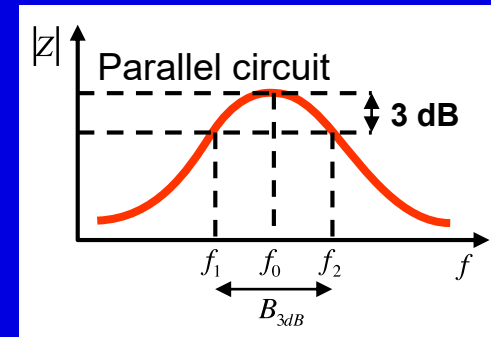


- the one-sided bandwidth of parallel resonant circuit  $= 1/2RC$

- the double-sided bandwidth:  $B_{3dB} = \omega_2 - \omega_1 = 1/RC$

$$\rightarrow \frac{B_{3dB}}{\omega_0} = \frac{1}{R\omega_0 C} = \frac{1}{Q}$$

# Properties in the frequency domain


- Parallel resonant circuit

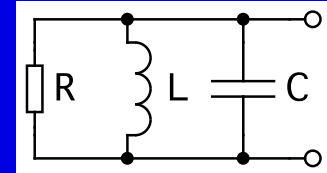

$$Y_p(\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) = \\ = \frac{1}{R} \left( 1 + jQ_p \left[ \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right] \right)$$


- where  $Q_p = \frac{R}{\omega_0 L} = R\omega_0 C = \frac{f_0}{f_2 - f_1} = \frac{f_0}{B_{3dB}}$

# Parallel Resonance - an Example

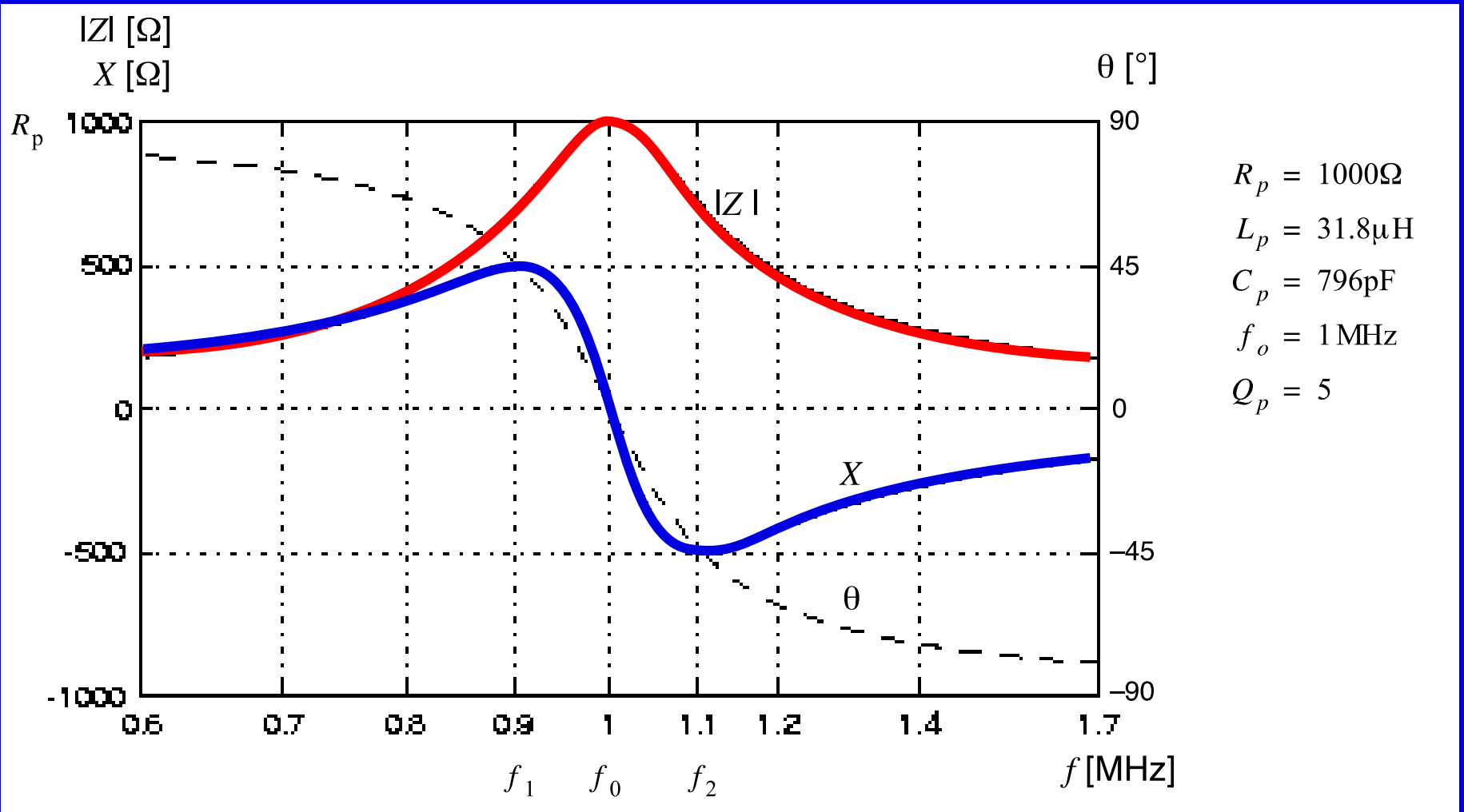

# Properties in the Frequency Domain

- Series resonant circuit

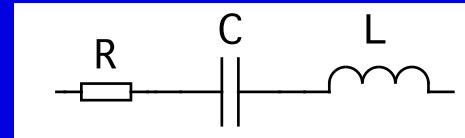


$$Z_s(\omega) = R + \frac{1}{j\omega C} + j\omega L = R + j\left(\omega L - \frac{1}{\omega C}\right) = \\ = R\left(1 + jQ_s\left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right]\right)$$

- where

$$Q_s = \frac{\omega_0 L}{R} = \frac{1}{R\omega_0 C} = \frac{f_0}{f_2 - f_1} = \frac{f_0}{B_{3dB}}$$


# Series Resonance - an Example

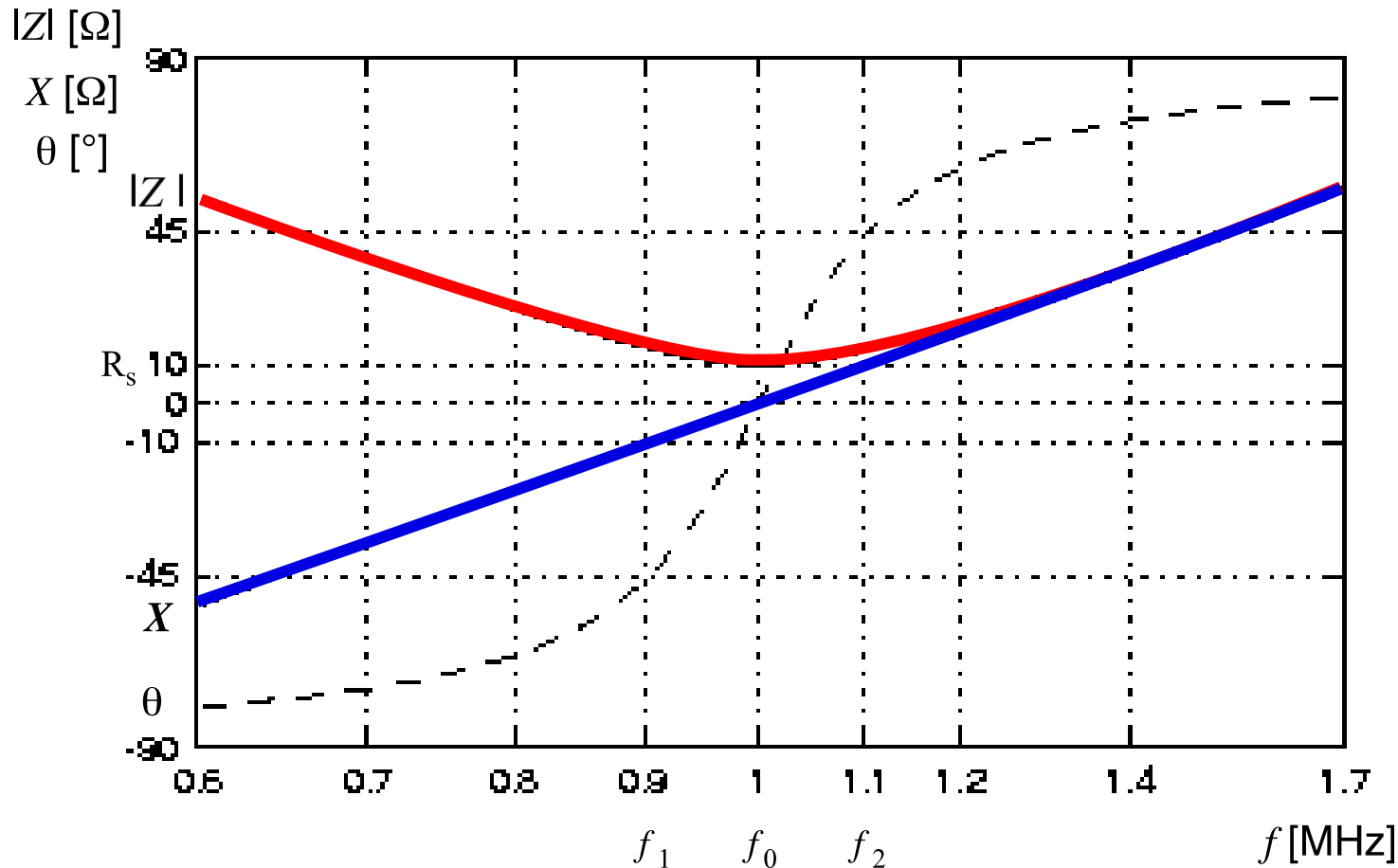

$R_s = 10\Omega$   
 $L_s = 7.96\text{nH}$   
 $C_s = 31.8\mu\text{F}$   
 $f_o = 1\text{MHz}$   
 $Q_s = 5$

# The Current through Reactive Elements in Parallel Resonant Circuits

- at resonance  $Z_P = R_P$

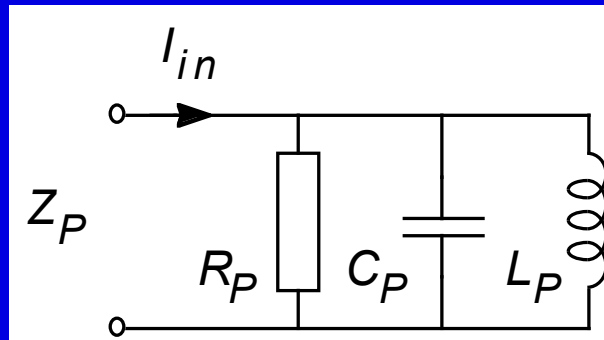


$$|I_L| = |I_C| = \frac{|V|}{Z} = \frac{I_{in} R_P}{\omega_0 L_P} = Q |I_{in}|$$

@  $\omega_0$

- example:  $I_{in} = 1 \text{ A}, Q = 200 \Rightarrow |I_L| = |I_C| = 200 \text{ A}$

# The Voltage at Reactive Elements in Series Resonant Circuits

- at resonance  $Z_S = R_S$

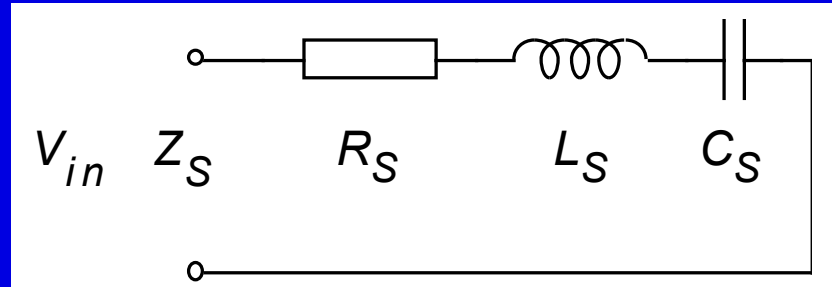


$$|V_L| = |V_C| = Z|I| = \omega_0 L_S \frac{V_{in}}{R_S} = Q|V_{in}| \quad @ \omega_0$$

- example:  $V_{in} = 1 \text{ V}, Q = 200 \Rightarrow |V_L| = |V_C| = 200 \text{ V}$

# Series-to-Parallel Conversion

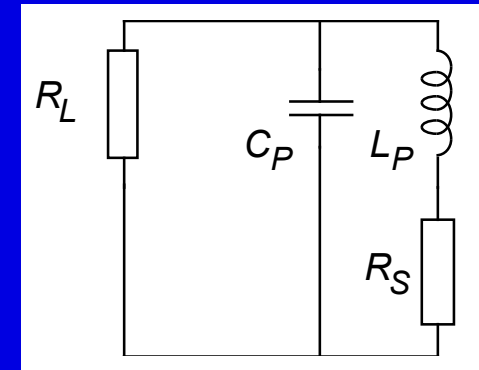
- Example of usage:
  - the circuit is loaded by a parallel resistance  $R_L$
  - the loss in the coil is specified as series resistance  $R_S$
- What is the overall circuit Q?
- Solution:
  - convert the series resistance  $R_S$  to an equivalent parallel resistance  $R_P$
  - calculate the parallel connection to  $R_L$
  - calculate the circuit Q





# Series-to-Parallel Conversion (cont.)

- Coil with losses

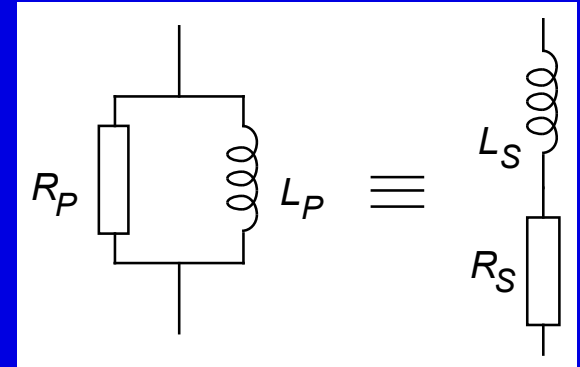

$$R_S + j\omega_0 L_S = R_P || j\omega_0 L_P = \frac{(\omega_0 L_P)^2 R_P + j\omega_0 L_P R_P^2}{R_P^2 + (\omega_0 L_P)^2} \quad *$$

$$Q = Q_S = \frac{\omega_0 L_S}{R_S} = Q_P = \frac{R_P}{\omega_0 L_P}$$

- solve:  $R_P = R_S(1 + Q^2), L_P = L_S \left( \frac{1 + Q^2}{Q^2} \right)$  (valid only close to  $\omega_0$ )

# Series-to-Parallel Conversion (cont.)

- Inductance

- $R_P = R_S(1 + Q^2), L_P = L_S \left( \frac{1 + Q^2}{Q^2} \right)$  (valid only close to  $\omega_0$ )

- Capacitance



- $R_P = R_S(1 + Q^2), C_P = C_S \left( \frac{Q^2}{1 + Q^2} \right)$  (valid only close to  $\omega_0$ )

- or generally

- $R_P = R_S(1 + Q^2), X_P = X_S \left( \frac{1 + Q^2}{Q^2} \right)$  (valid only close to  $\omega_0$ )

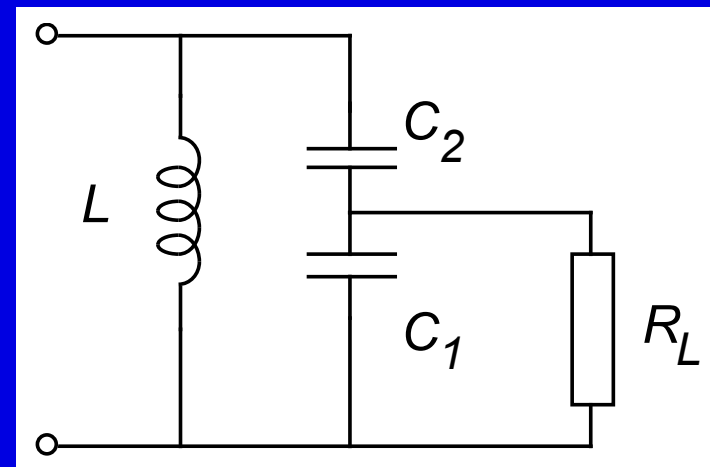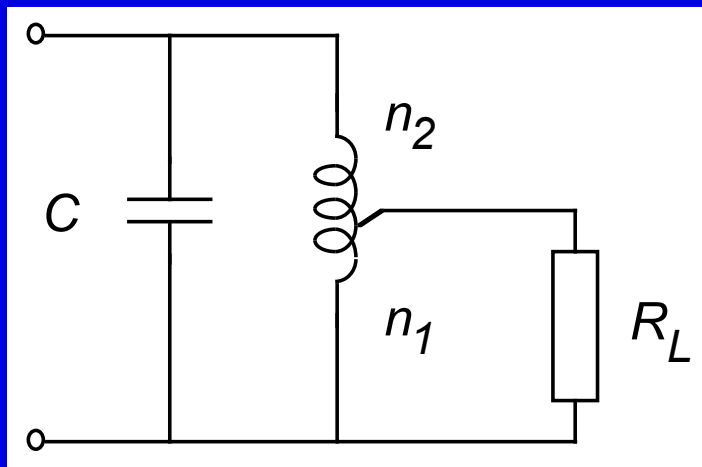
# Capacitive and Inductive Tap

- The properties of basic resonant circuits are limited as the bandwidth and circuit Q are determined by the losses and the load.
- By a capacitive or inductive tap in the resonant circuit the bandwidth is set independently from the load value.
- Example:



# Capacitive Tap

- Equivalent model

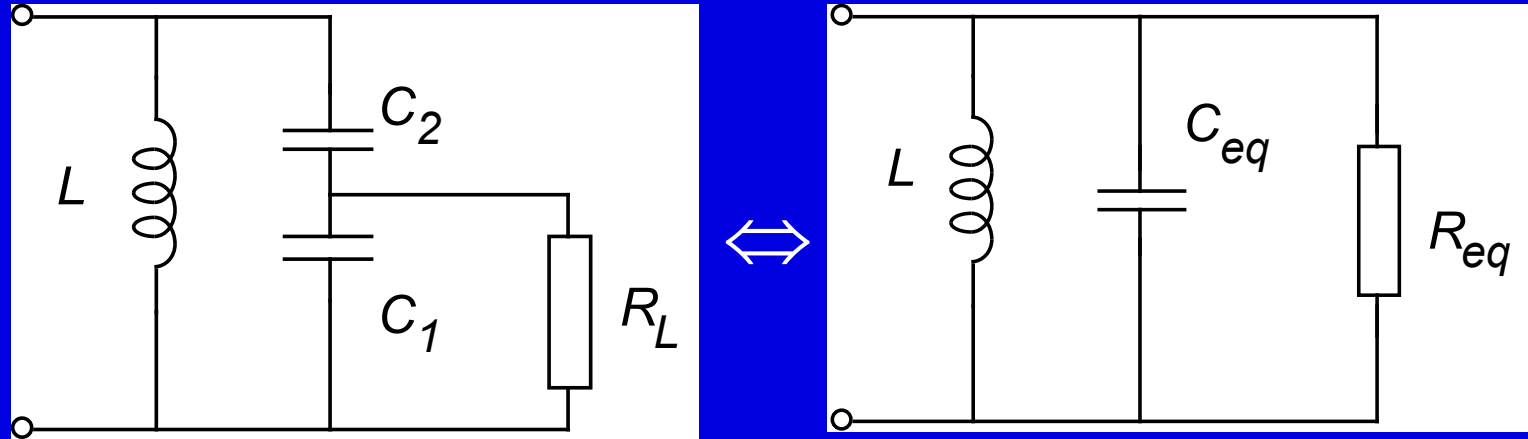


- $$R_{eq} = R_L \left( \frac{C_1 + C_2}{C_2} \right)^2, C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$
 if  $R_L \gg X_{C1}$  (unloaded circuit)

- if the tap is considered as loaded the conversion has to be performed in several steps by successive parallel  $\rightarrow$  series  $\rightarrow$  parallel conversion

# Inductive Tap

- Equivalent model

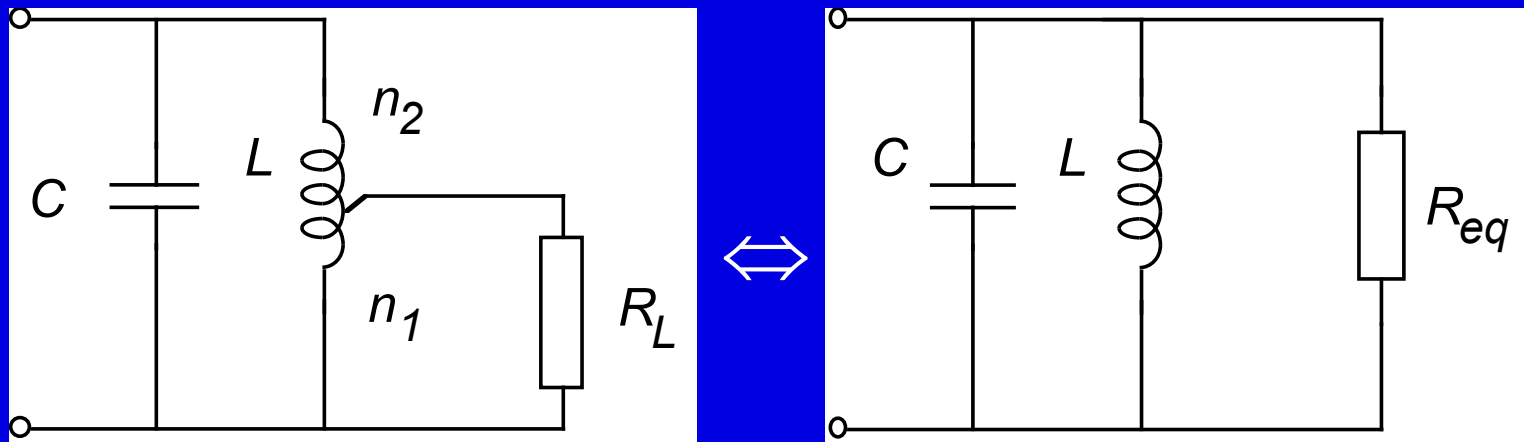


$$R_{eq} = R_L \left( \frac{n_1 + n_2}{n_1} \right)^2$$

- valid if the tap may be considered as unloaded i.e.  $Q \geq 10$  and with unity coupling  $k = 1$

# Transformer


- Equivalent model

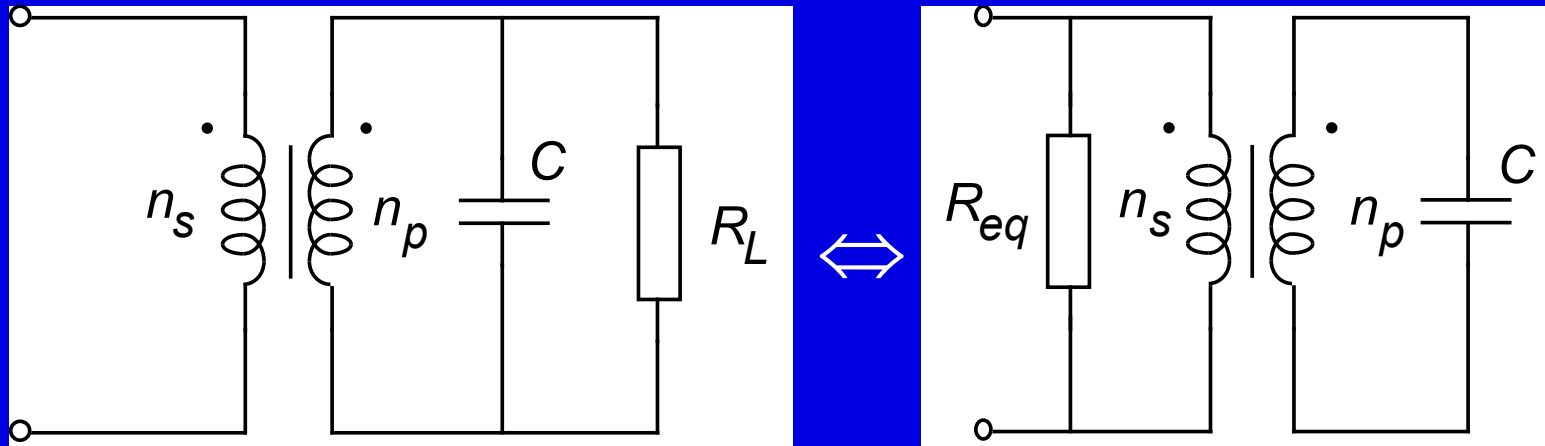

$$R_{eq} = R_L \left( \frac{n_s}{n_p} \right)^2$$

- valid if the transformer may be considered as unloaded i.e.  $Q \geq 10$ , and with unity coupling  $k = 1$
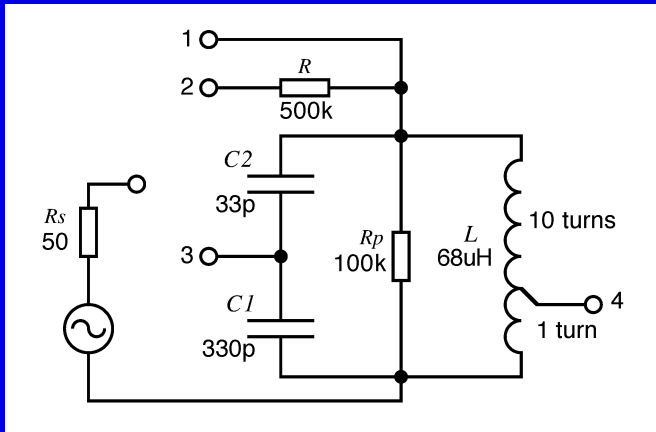
# How to connect the parallel resonant circuit



The unloaded circuit:

- Resonant frequency

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC_{eq}}} = \frac{1}{2\pi} \sqrt{\frac{1}{68 \times 10^{-6} \times 30 \times 10^{-12}}} = 3.5 \text{ MHz}$$

- Circuit Q

$$Q = \frac{R_p}{|X|} = \frac{R_p}{\omega_0 L} = \frac{100 \times 10^3}{2\pi \times 3.5 \times 10^6 \times 68 \times 10^{-6}} = 67$$

- Bandwidth

$$B_{3dB} = \frac{f_0}{Q} = \frac{3.5 \times 10^6}{67} = 52 \text{ kHz}$$

Connect the external load or source:

- Direct

$$Q = \frac{R_p // 50 \Omega}{|X|} = 0.03 \Rightarrow B_{3dB} = 105 \text{ MHz}$$

- Series R

$$Q = \frac{R_p // 500 \text{ k}\Omega}{|X|} = 56 \Rightarrow B_{3dB} = 63 \text{ kHz}$$

The voltage decreases by a factor  $10^4$

- Capacitive tap

$$Q = \frac{R_p // R_s'}{|X|}$$

$f_0$  decreases due to loading of  $C1$

The voltage increases

AC coupled

- Inductive tap

as capacitive tap but

$f_0$  increases due to loading of  $nI$

DC coupled