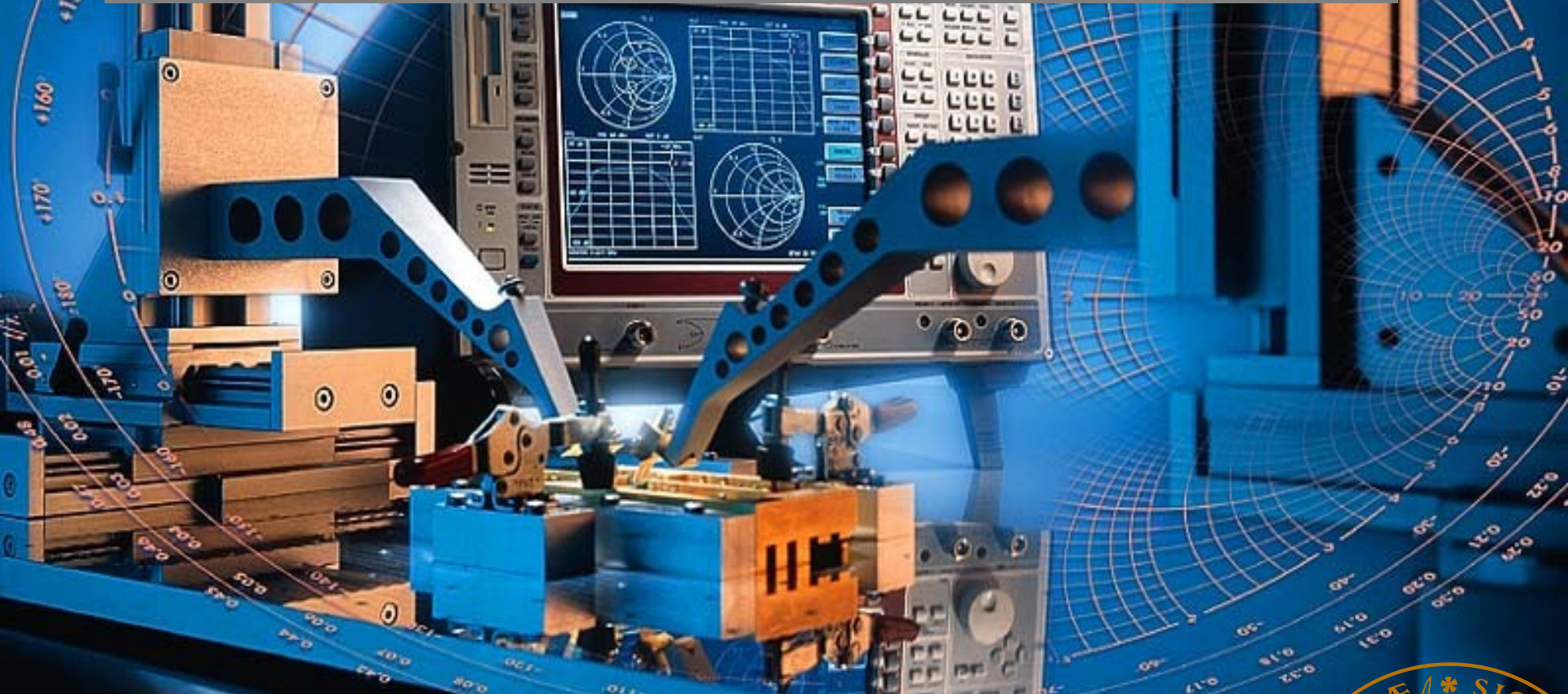


Radio Electronics



Lars Ohlsson Fhager
Electrical and Information Technology




Lecture 5

- RF Amplifier Analysis and Design
 - The hybrid- π -model
 - transistor configurations
 - amplifier classes
 - example of a tuned amplifier
 - Two-Port Network Representation
 - y , z , and ABCD parameters, definition and applications
 - measurement of parameters
 - power gain definitions
 - stability


Transistor Models

Physical model

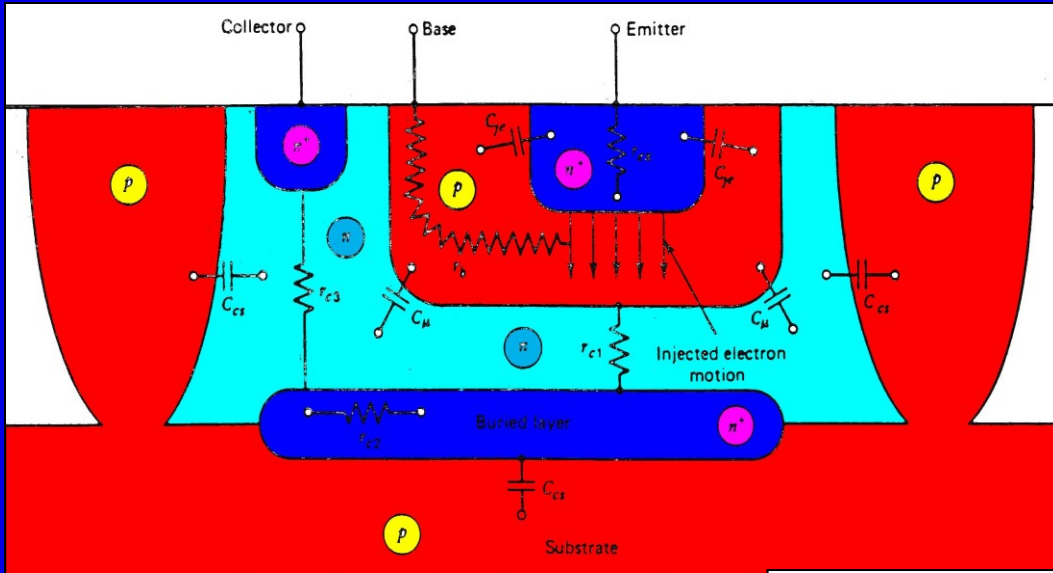



PINNING

PIN	DESCRIPTION
Code: N28	
1	base
2	emitter
3	collector

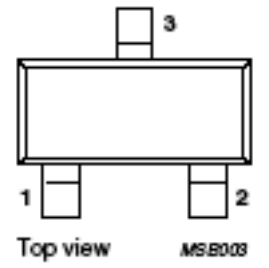


Simplified hybrid- π -model

S-Parameter model

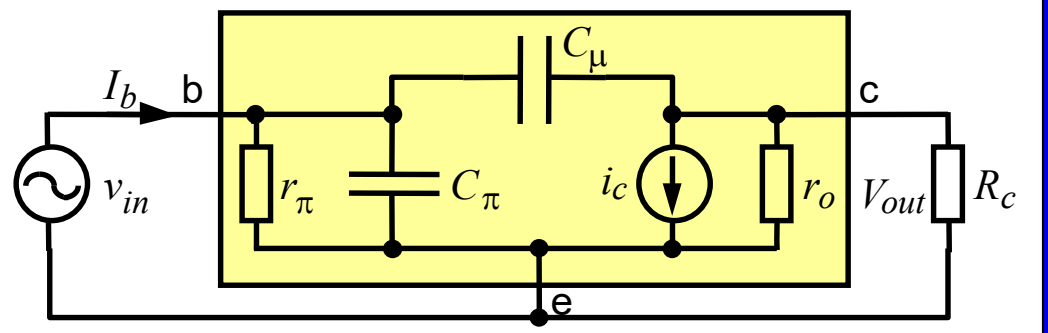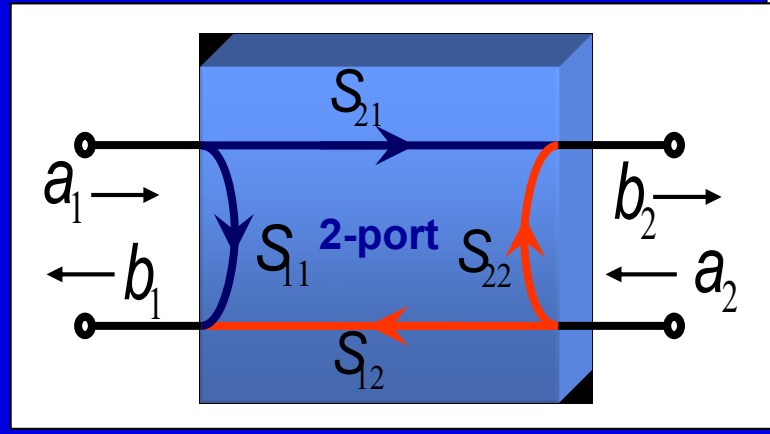

Transistors

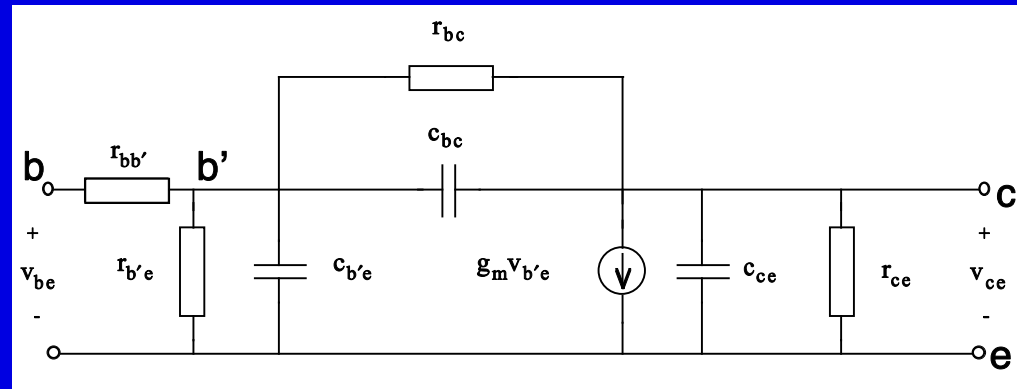The hybrid- π model for bipolar transistors



$$r_{b'e} = r_{\pi}$$

$$C_{b'e} = C_{\pi}$$

$$r_{bc} = r_{\mu}$$

$$C_{bc} = C_{\mu}$$

$$r_{ce} = r_o$$


- Example:

$$C_{b'c} = 0.5 \text{ pF} \quad C_{b'e} = 9 \text{ pF} \quad C_{ce} = 1 \text{ pF}$$

$$r_{b'b} = 10 \Omega \quad \beta = 300 \quad V_A = 50 \text{ V} \quad I_C = 1 \text{ mA}$$

DC:

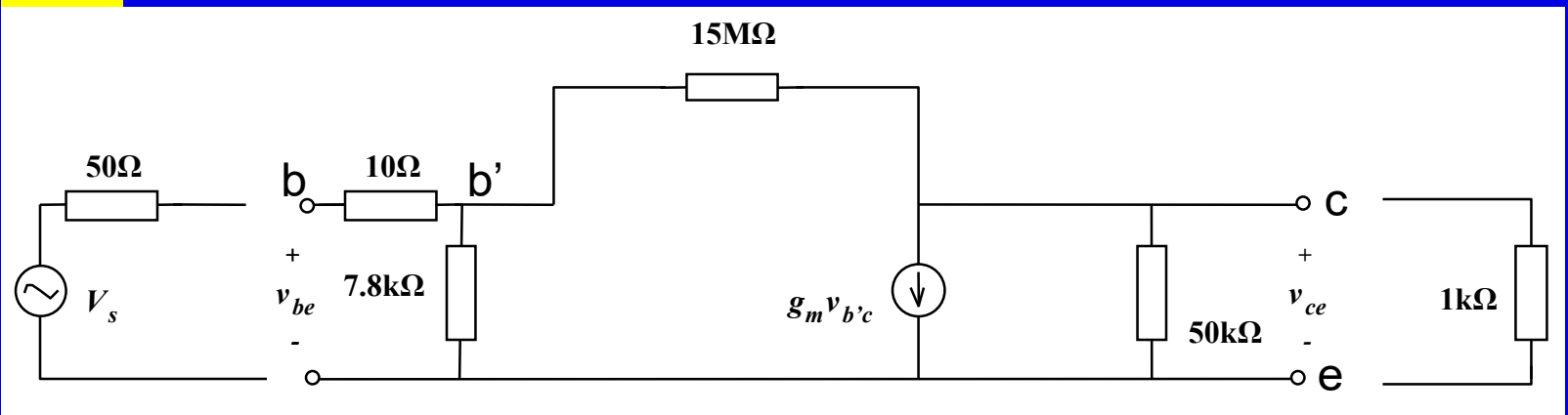
What happens when the frequency increases from 0 to 1 GHz?




Transistors (cont.)

You will use these models in the labs/exam/exercise


1 MHz:

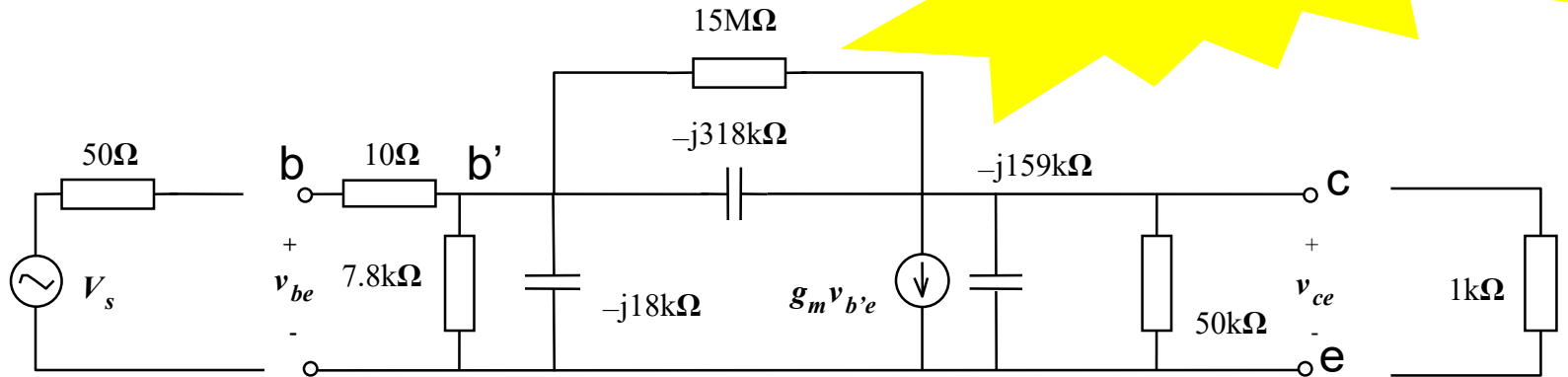

1 GHz:

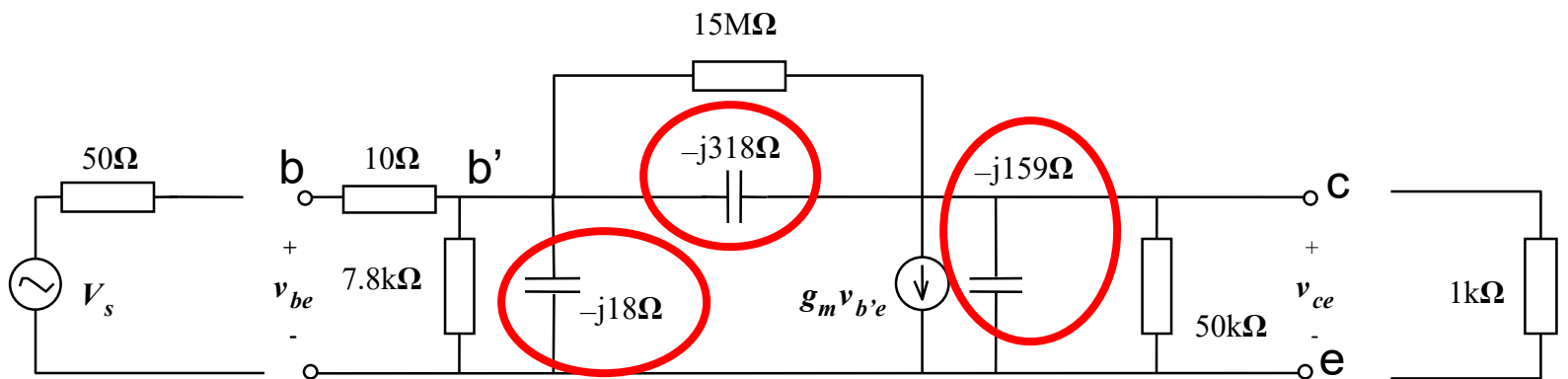

Voltage Gain

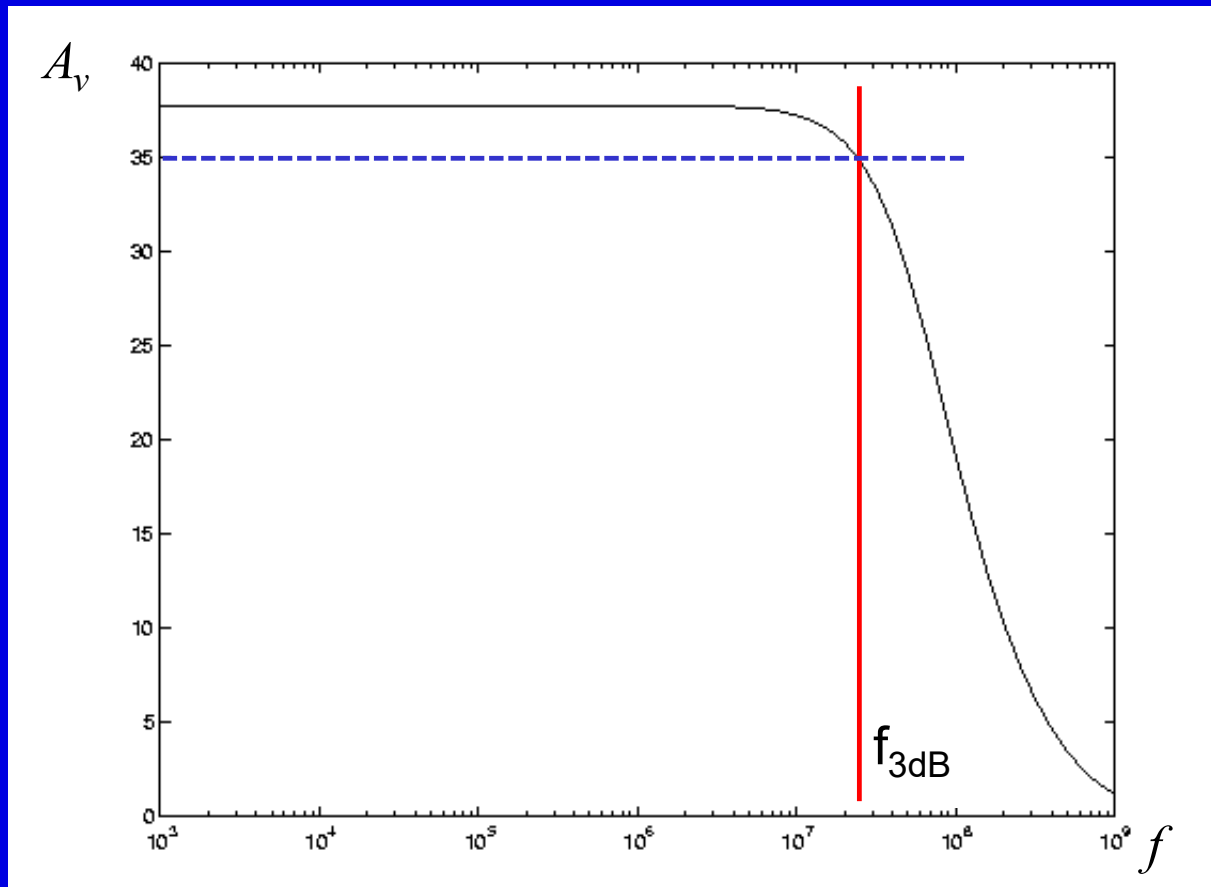


Tuned Amplifiers

- Conventional design of amplifiers results in low-pass behaviour due to intrinsic device capacitances and this causes problems at higher frequencies
- By neutralizing the problematic capacitances the high-frequency behaviour can be improved
 - with preserved bandwidth!
- How to? Connect an inductor in parallel to the capacitance to form a resonant circuit tuned to the operation frequency.

The rest of the amplifier is designed by conventional low-frequency methods

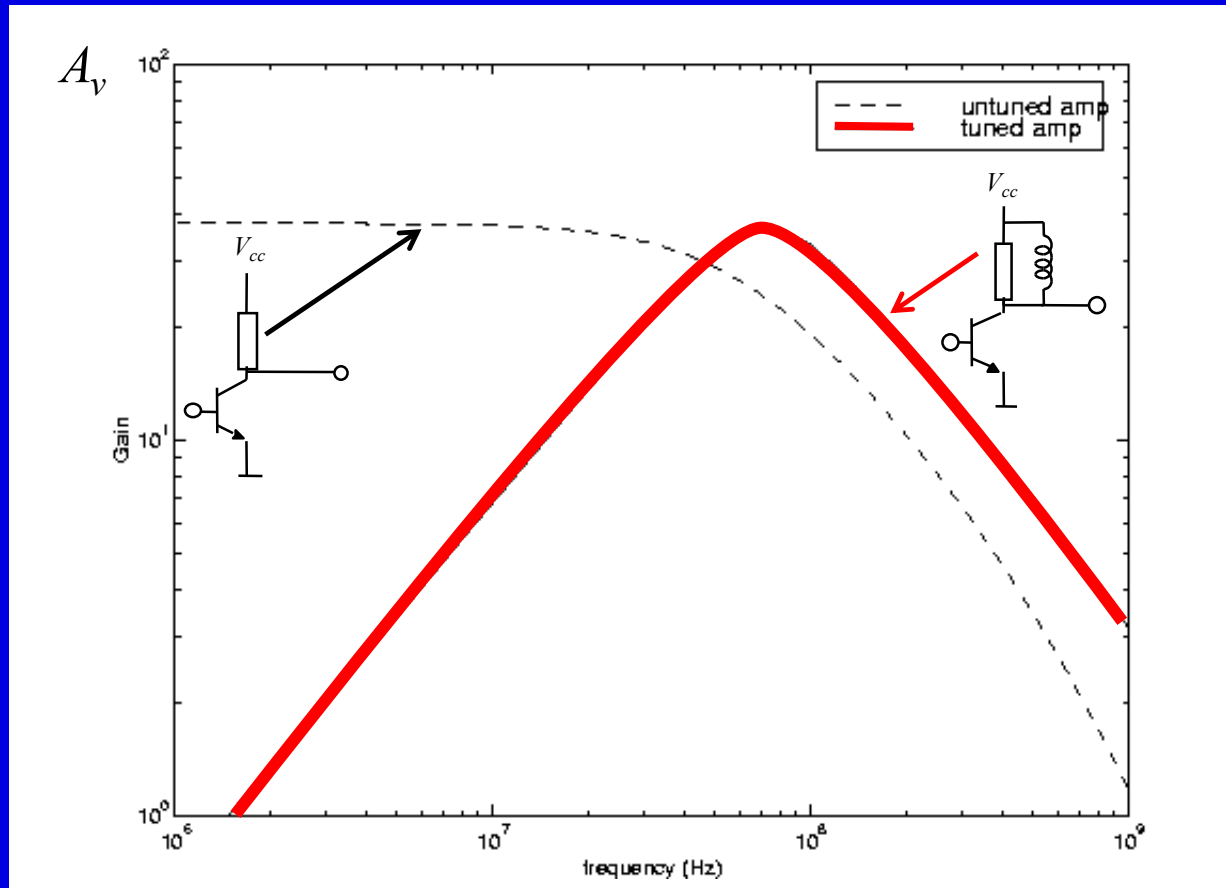Result of Neutralization (Inductive Peaking)




Both amplifiers have the same bandwidth, don't let the log-scale fool you.

$$Q = f_0/B_{3dB} = R/X_L = R/X_C = R\omega_0 C \Rightarrow B_{3dB} = 1/2\pi RC$$


Example of a Tuned Amplifier

Cf. lab 3,
task 3.2

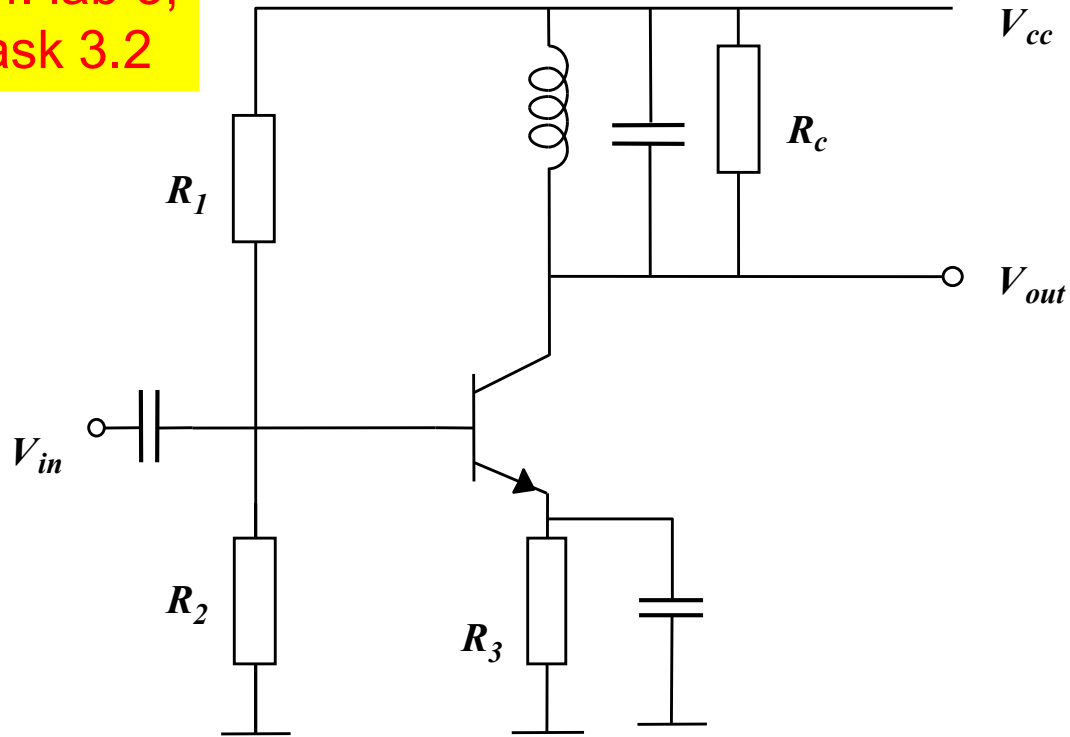

Note the Signal Notation

Cf. lab 3,
task 3.2

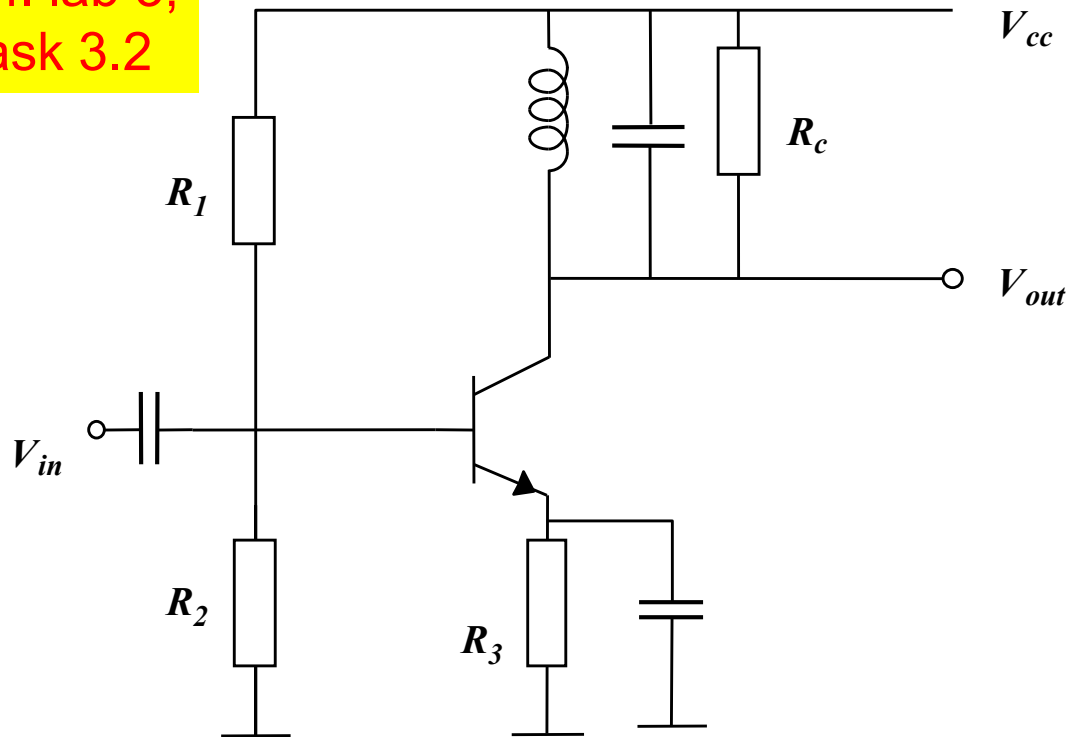


Small-signal component at carrier (operation)
frequency often implied:

$$V_{in}(f_0) = \mathcal{F}\{v_{IN}(t)\}(f_0), \quad v_{IN}(t) = V_{IN} + v_{in}(t)$$
$$V_{out}(f_0) = \mathcal{F}\{v_{OUT}(t)\}(f_0), \quad v_{OUT}(t) = V_{OUT} + v_{out}(t)$$


Small Signal Model of Bipolar Junction Transistor (BJT)

Circuit diagram

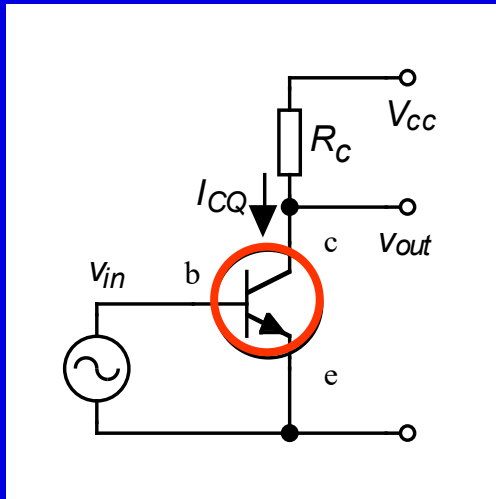

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

Simplified hybrid- π -model

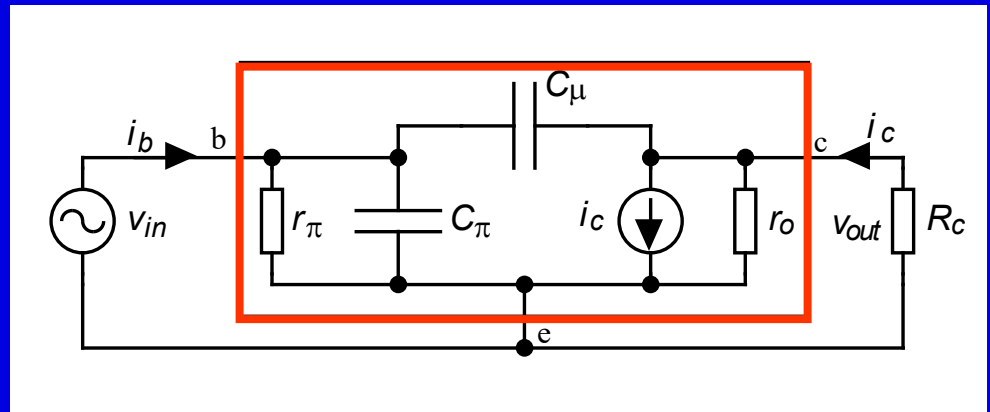

$$i_c = \beta i_b = g_m v_{in} = g_m r_{\pi} i_b$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

The BJT model is fitted at a quiescent point and only valid at small-signal input:

$$V_{in} \ll V_T = \frac{kT}{q} \approx 25.0 \text{ mV at } T = T_0 = 290 \text{ K}$$

Common Emitter (CE) Transistor Configuration

- High voltage gain

$$A_v = -g_m R_c$$

- High input resistance and capacitance

$$R_{in} = \frac{\beta}{g_m} = (\beta + 1)r_e$$


$$C_{in} = C_{\pi} + (1 - A_v)C_{\mu}$$

Result of Miller's theorem
(Miller approximation)

- High output resistance and low output capacitance

$$R_{out} = r_o || R_c$$

$$C_{out} \approx C_{\mu}$$

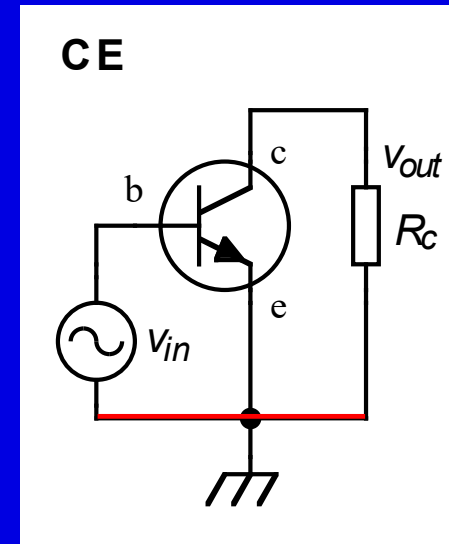

Common Base (CB) Transistor Configuration

- High voltage gain

$$A_v = g_m R_c$$

- Low input resistance and capacitance


$$R_{in} = r_e \approx \frac{1}{g_m}$$

$$C_{in} = C_{\pi}$$

- High output resistance and low output capacitance

$$R_{out} = r_o || R_c$$

$$C_{out} = C_{\mu}$$

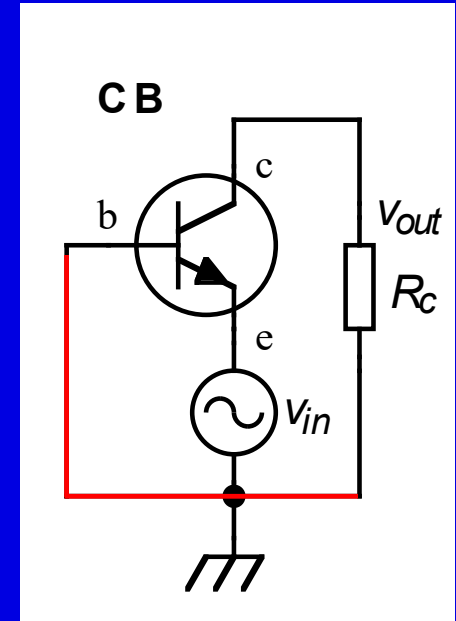

Common Collector (CC) Transistor Configuration

- Low voltage gain

$$A_v \approx 1$$

- High input resistance and low input capacitance


$$R_{in} = \beta \left(\frac{1}{g_m} + R_e \right) \approx \beta (r_e + R_e)$$

$$C_{in} = C_{\mu}$$

- Low output resistance and capacitance

$$R_{out} = r_e \parallel R_e$$


$$C_{out} \approx 0$$

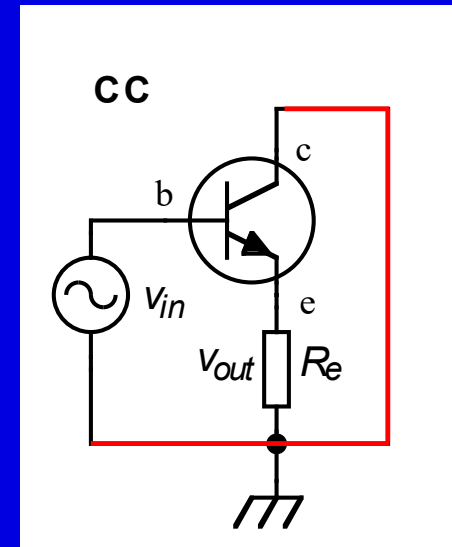

Amplifier Classes

- Class A

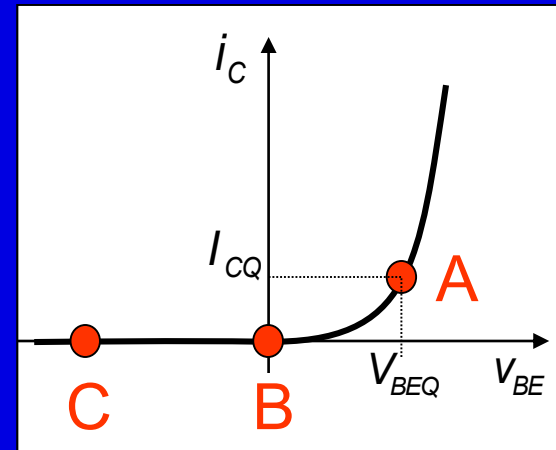- linear
- suitable for all signals
- efficiency $\eta \leq 50\%$




- Class B

- non-linear
- only signals at high and constant amplitude
- efficiency $\eta \leq 78\%$

- Class C

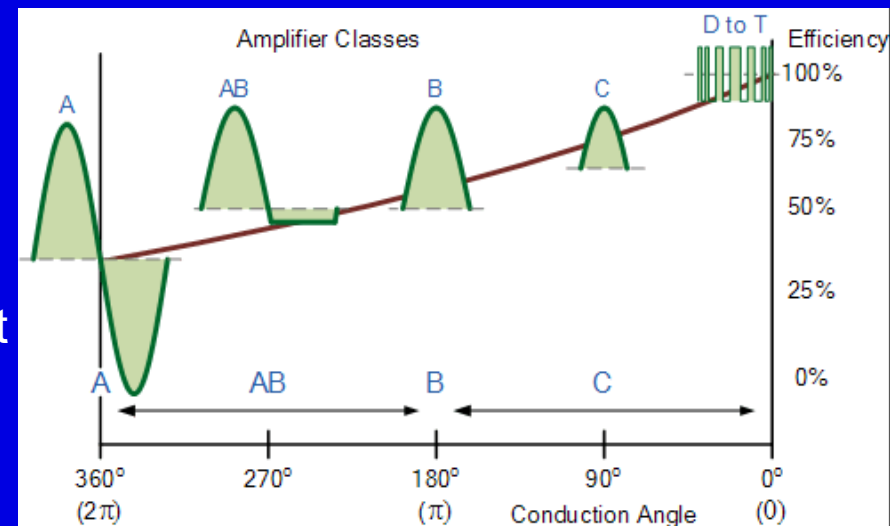- non-linear
- only signals at high and constant amplitude (e.g. FM)
- efficiency $\eta \leq 90\%$





When the Frequency Increases Further...

- Only simple neutralization (inductive peaking) is not efficient
 - more reactive elements affects the properties of the transistor
 - more elements generally affect the properties and therefore the rough hybrid- π -model must be further refined, or other data required
- Important to consider **power** to “preserve” available performance
- Design at high frequencies by lumped components therefore utilizes **two-port models** of devices, described by S-parameters
 - sometimes easier to measure than to calculate...
- Two-port models describe total response of the device
 - Careful measurements and modelling needed

Two-Port Network Representations

- voltage and current
 - z, impedance parameters
 - y, admittance parameters
 - ABCD, chain parameters
 - ...

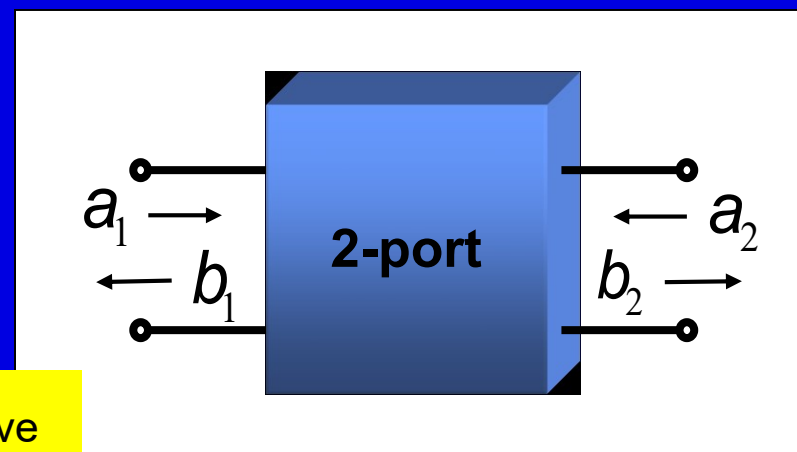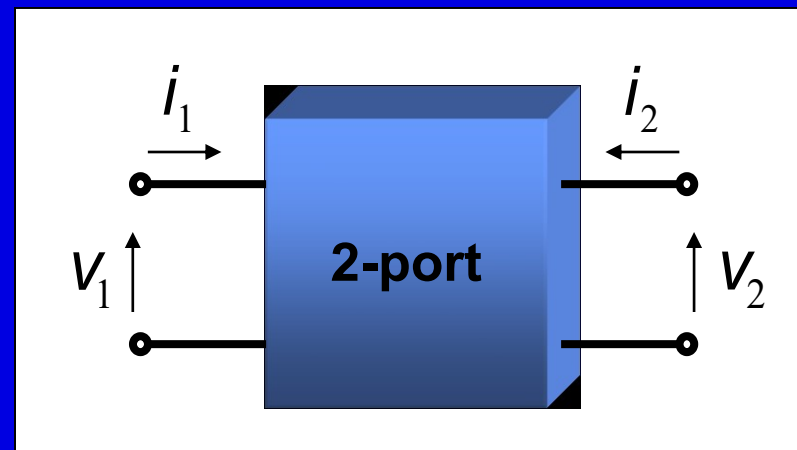
- waves
 - S, scattering parameters
 - T, transmission parameters
 - X, large signal scattering parameters



a_x = incident wave

b_x = reflected wave

Two-Port

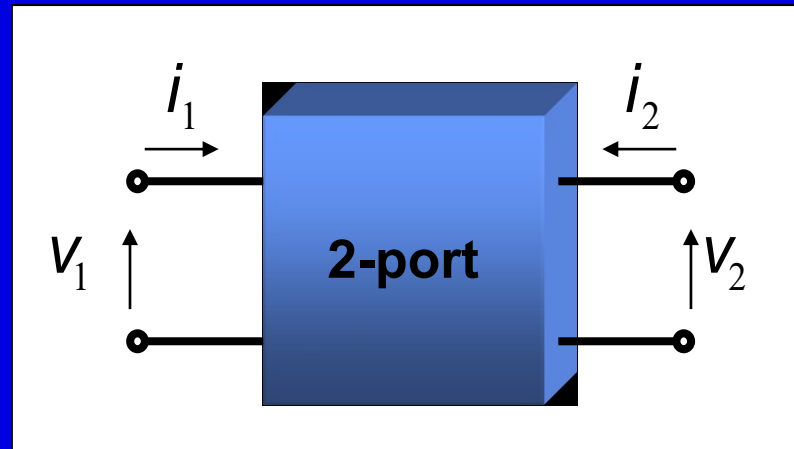


- If
 - the two-port is linear and
 - port signals (voltages and currents) are complex quantities (phasors)

the small signal properties must be characterized by four complex parameters

- these are only valid at the specified frequency and
- at the specific bias conditions

Admittance (y) Parameters

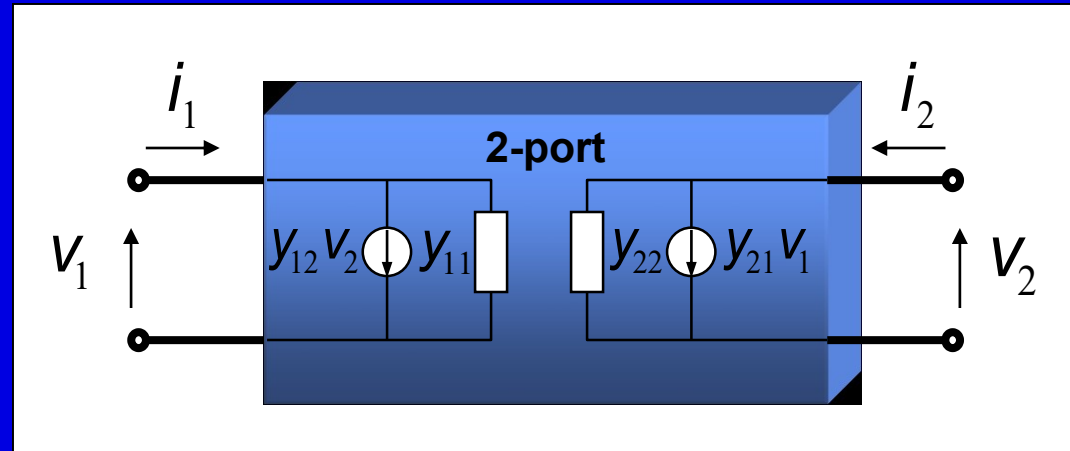Two-port schematic
(transadmittance,
controlled Norton)



or in matrix format:


Definition

$$\begin{cases} i_1 = y_{11} \cdot v_1 + y_{12} \cdot v_2 \\ i_2 = y_{21} \cdot v_1 + y_{22} \cdot v_2 \end{cases}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Impedance (z) Parameters

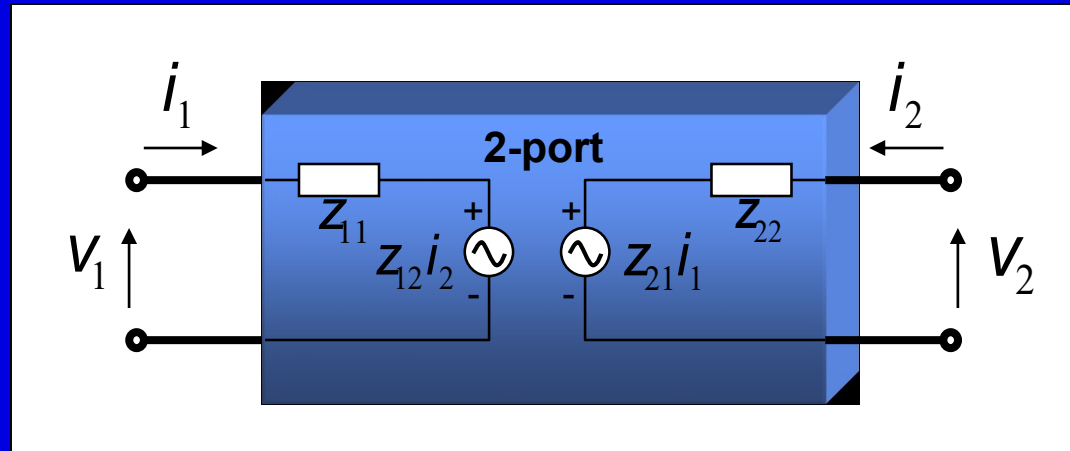Two-port schematic
(transimpedance,
controlled Thevenin)



or in matrix format:


Definition

$$\begin{cases} v_1 = z_{11} \cdot i_1 + z_{12} \cdot i_2 \\ v_2 = z_{21} \cdot i_1 + z_{22} \cdot i_2 \end{cases}$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Chain (ABCD, Cascade) Parameters

Two-port schematic
(just ideal sources)

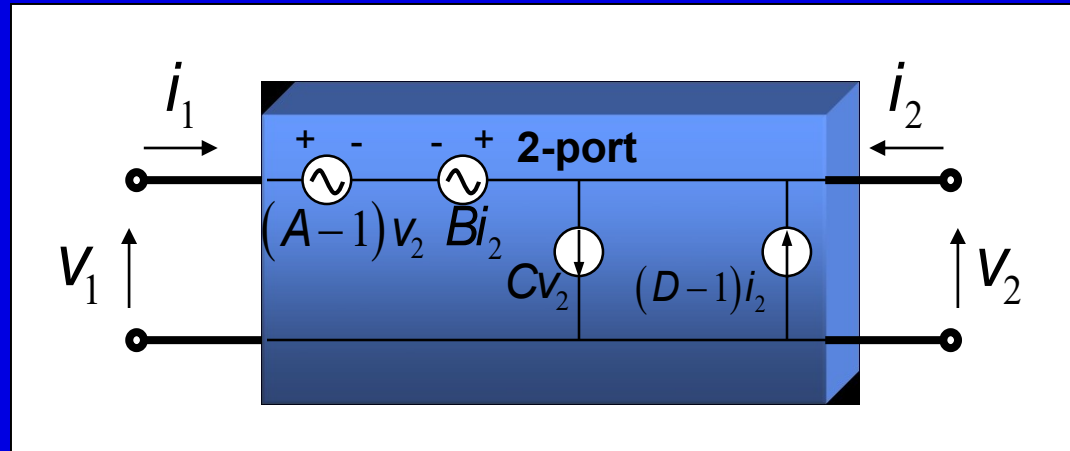

or in matrix format:

Definition

$$\begin{cases} v_1 = A \cdot v_2 + B \cdot (-i_2) \\ i_1 = C \cdot v_2 + D \cdot (-i_2) \end{cases}$$


$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

Measuring Two-Port Parameters

ex. y parameters

$$\begin{cases} i_1 = y_{11} \cdot v_1 + y_{12} \cdot v_2 \\ i_2 = y_{21} \cdot v_1 + y_{22} \cdot v_2 \end{cases}$$

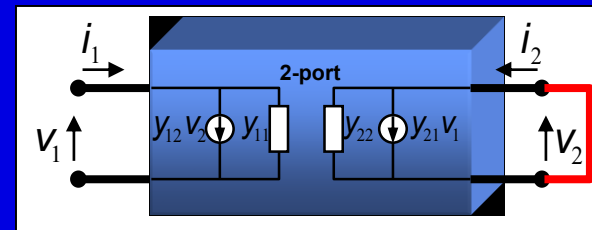- Parameters are simply derived when a port voltage is turned to zero, i.e. a port is short-circuited:



- at the same time as port 2 is short-circuited a signal is applied to port 1. The current voltage ratio at port 1 is then:
- repeat from other side for full matrix


$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}$$
$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0}$$

Measuring Two-Port Parameters (cont.)

- Two-port parameters in z/y/ABCD-format are generally (mathematically) measured by means of **open** ($i = 0$) or **short-circuited** ($v = 0$) ports.
- Open or short-circuited terminations are however **hard to achieve in reality and more so at high frequencies**, especially close to the device.
- Open or short-circuited terminations may also **cause instability and self-oscillation** when measurements are performed on active components.
- At high frequency there is obviously a need for a model (e.g. S parameters) that doesn't require open or short-circuited device ports.
- **y, z and ABCD parameters are still valid and useful for calculations at higher frequencies as well, but cannot be directly measured.**


Circuit Analysis by Two-Port Parameters

- parallel connection:
use y parameters

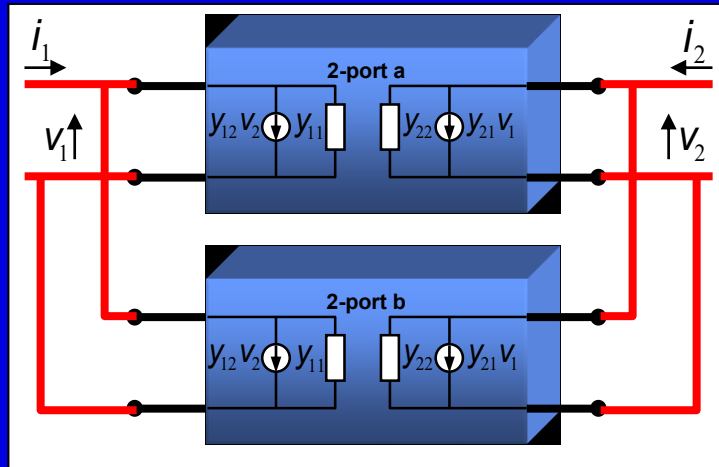

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} i_1^a + i_1^b \\ i_2^a + i_2^b \end{bmatrix} = \begin{bmatrix} y_{11}^a + y_{11}^b & y_{12}^a + y_{12}^b \\ y_{21}^a + y_{21}^b & y_{22}^a + y_{22}^b \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

- series connection:
use z parameters

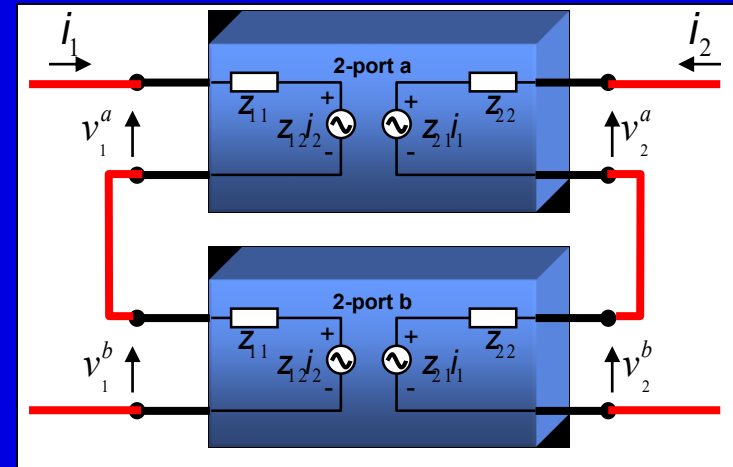


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} v_1^a + v_1^b \\ v_2^a + v_2^b \end{bmatrix} = \begin{bmatrix} z_{11}^a + z_{11}^b & z_{12}^a + z_{12}^b \\ z_{21}^a + z_{21}^b & z_{22}^a + z_{22}^b \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

Be careful, however, because some connections can disrupt the port condition implied for each device, yielding invalid results.


Circuit Analysis by Two-Port Parameters (cont.)

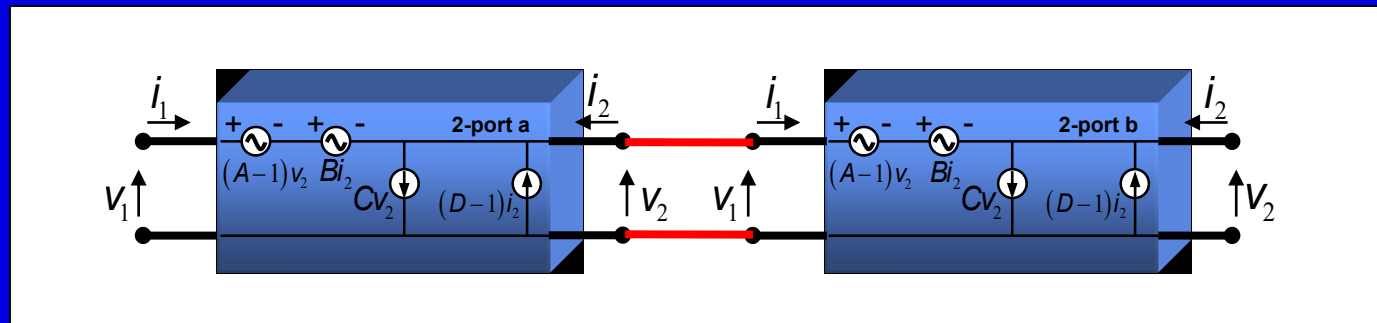- **cascade connection:** use ABCD parameters




$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} V_1^a \\ i_1^a \end{bmatrix} = \begin{bmatrix} A^a & B^a \\ C^a & D^a \end{bmatrix} \begin{bmatrix} V_2^a \\ -i_2^a \end{bmatrix} = \begin{bmatrix} A^a & B^a \\ C^a & D^a \end{bmatrix} \begin{bmatrix} A^b & B^b \\ C^b & D^b \end{bmatrix} \begin{bmatrix} V_2^b \\ -i_2^b \end{bmatrix}$$

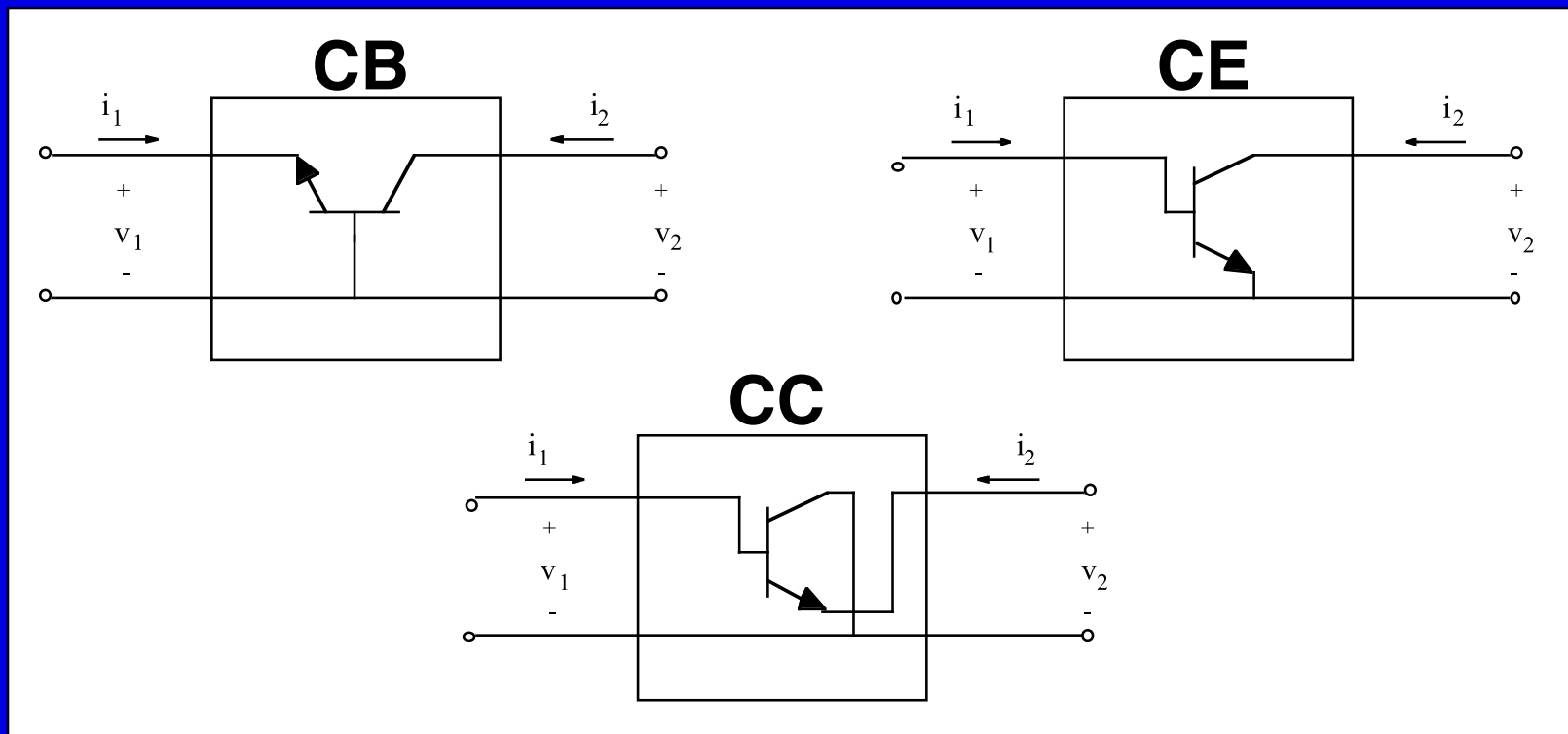Parameters for Various Transistor Configurations




- The parameters may easily be converted between different configurations without any loss of information. (Table 8.1 in the textbook)

Power Gain Definitions

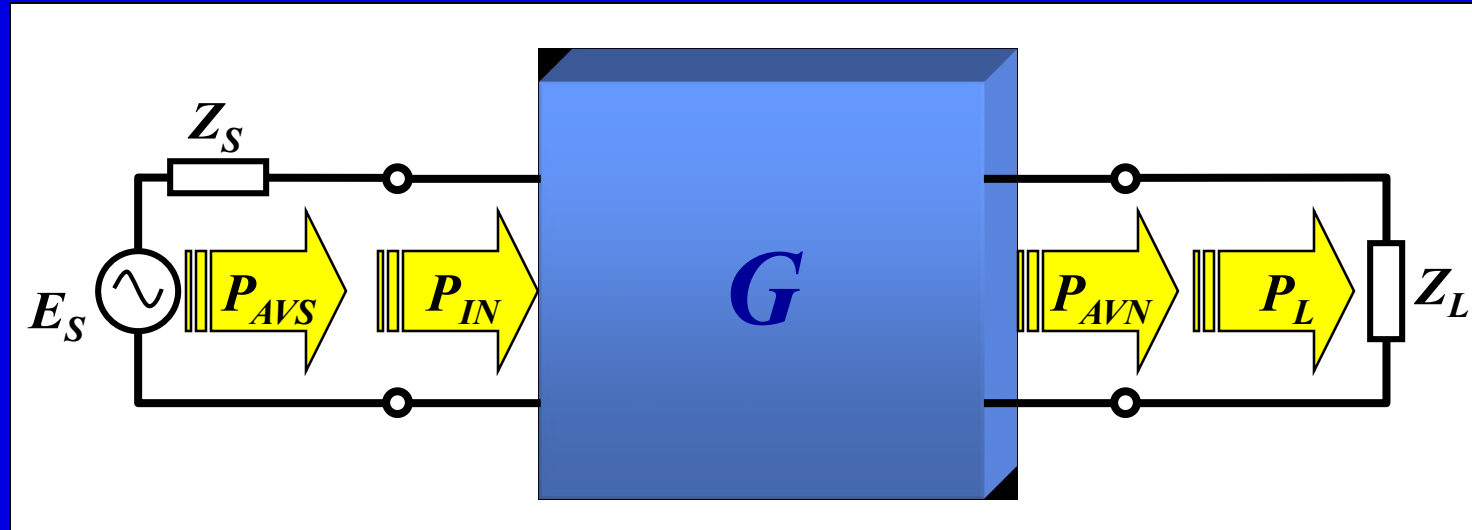

- P_{AVS} = Available power from Source
 - P_{IN} = power delivered to the Input of the two-port
 - P_{AVN} = Available power from Network (the output of the two-port)
 - P_L = power delivered to the Load
- How should we define the power gain?

Power Gain Definitions (cont.)

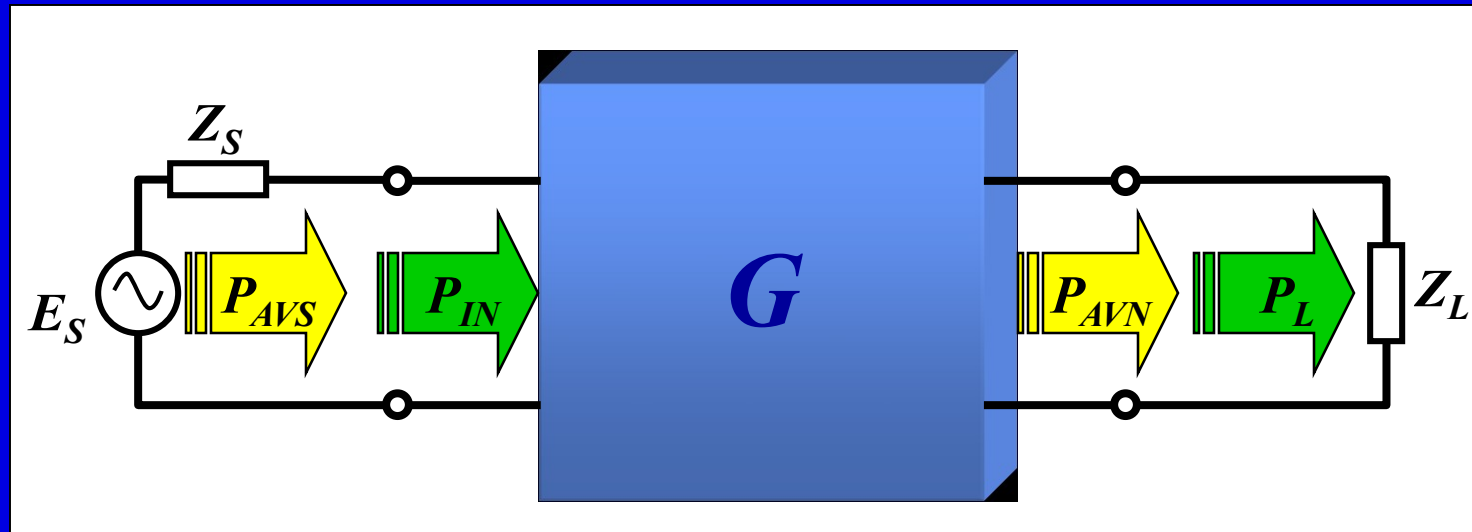


available gain $G_A = \frac{P_{AVN}}{P_{AVS}}$

Important definitions!

operating gain $G_P = \frac{P_L}{P_{IN}}$

transducer gain $G_T = \frac{P_L}{P_{AVS}}$

Power Gain from Several Stages

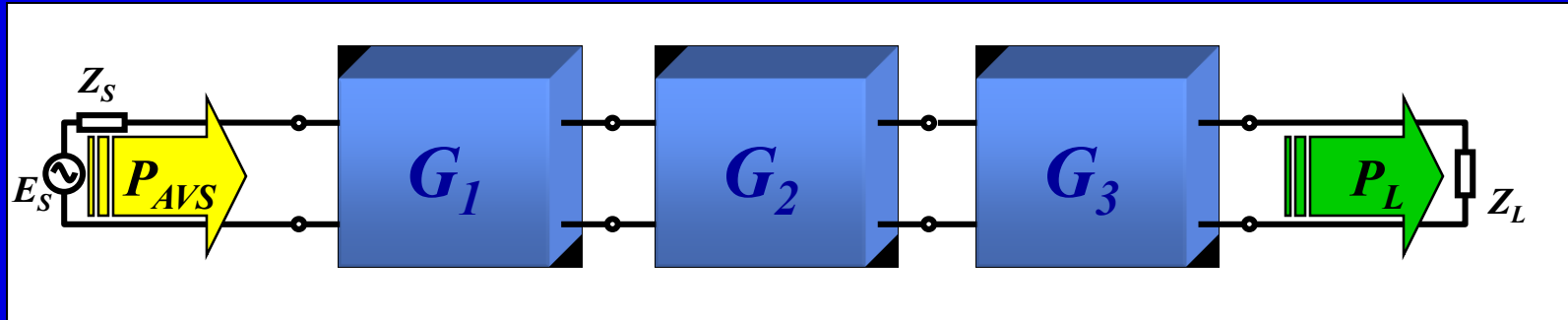

What is the total power gain?

total transducer gain $G_{Ttot} = \frac{P_L}{P_{AVS}}$


Extract the expression by using the gain definitions:

$$G_{Ttot} = \frac{P_L}{P_{AVS}} = \frac{P_{OUT1}}{P_{AVS}} \square \frac{P_{OUT2}}{P_{IN2}} \square \frac{P_L}{P_{IN3}} = G_{T1} \square G_{P2} \square G_{P3}$$

Can G_T be calculated in alternative ways?

How?

The Gain Expressed by y parameters

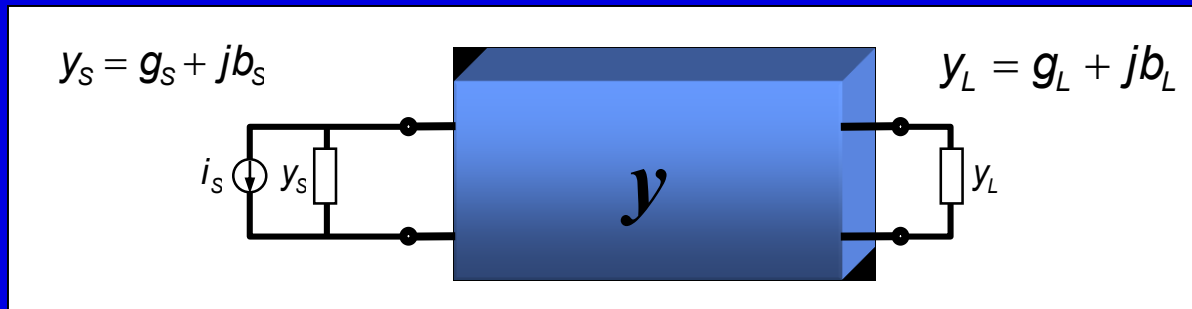


available gain $G_A = \frac{g_s |y_{21}|^2}{|y_s + y_{11}|^2 \operatorname{Re} \left[y_{22} - \frac{y_{12} y_{21}}{y_s + y_{11}} \right]}$

operating gain $G_P = \frac{g_L |y_{21}|^2}{|y_L + y_{22}|^2 \operatorname{Re} \left[y_{11} - \frac{y_{12} y_{21}}{y_L + y_{22}} \right]}$

transducer gain $G_T = \frac{4g_s g_L |y_{21}|^2}{|(y_s + y_{11})(y_L + y_{22}) - y_{12} y_{21}|^2}$

Port Admittances for a Two-Port

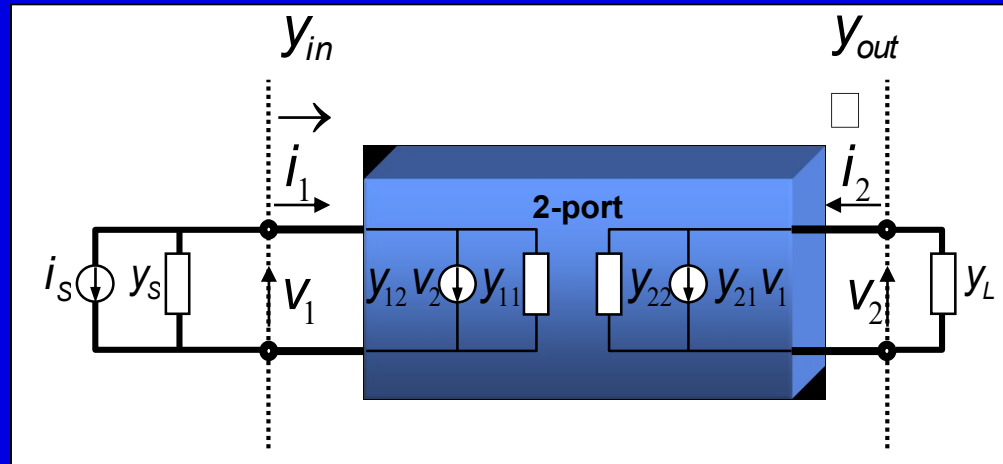

y_{12} connects output to input

input admittance

$$y_{in} = y_{11} - \frac{y_{12}y_{21}}{y_{22} + y_L}$$

y_{21} connects input to output


output admittance

$$y_{out} = y_{22} - \frac{y_{21}y_{12}}{y_{11} + y_s}$$

Stability

- If the circuit isn't able to self-oscillate it is considered to be stable (zero input signal, zero output signal).
- This is not an obvious quality at RF design because
 - several feedback paths (parasitic elements)
 - several reactive circuit elements (parasitic elements)
- Stability analysis based on poles is possible only if the complete circuit is completely known.
- It is not trivial (some may say impossible) to calculate poles and zeros if only the two-port parameters are available.
There is a need for alternative methods to study stability...

Stability - an Example

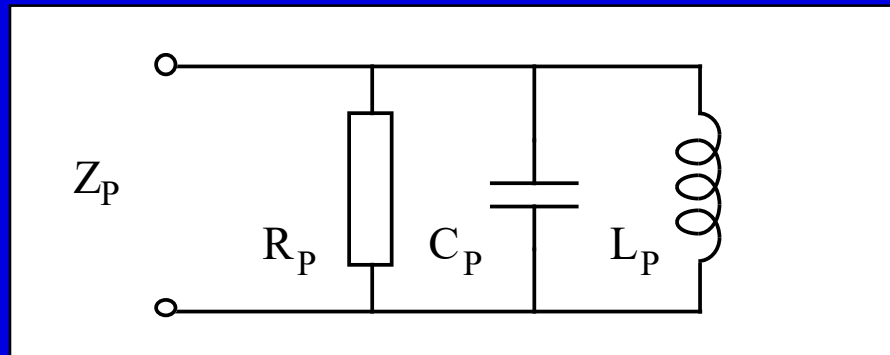

Stable when $R_P > 0$ - R_P denotes the circuit losses

Unstable when $R_P < 0$ - R_P supplies power to the circuit

Passive sign convention: positive power is dissipated

Unconditional Stability

$$y_{in} = y_{11} - \frac{y_{12} \square y_{21}}{y_{22} + y_L}$$

$$y_{out} = y_{22} - \frac{y_{12} \square y_{21}}{y_{11} + y_S}$$

A two-port is defined to be unconditionally stable if no y_S or y_L results in a negative port admittance

Linville's stability factor

$$C_L = \frac{|y_{12} \square y_{21}|}{2 \square g_{11} \square g_{22} - \text{Re}[y_{12} \square y_{21}]}$$

The two-port is unconditionally stable if

$$0 < C_L < 1$$


Note! The result is **only valid at the actual frequency** where the stability test is performed

Conditional Stability

- If it's not unconditionally stable the two-port **may be conditionally stable**:
 - some y_S or y_L causes a negative port admittance
 - **avoid these y_S and y_L if possible**
- If the port impedance still is negative
 - examine the loop impedance:

$$y_{in} = y_{11} - \frac{y_{12} \square y_{21}}{y_{22} + y_L}$$
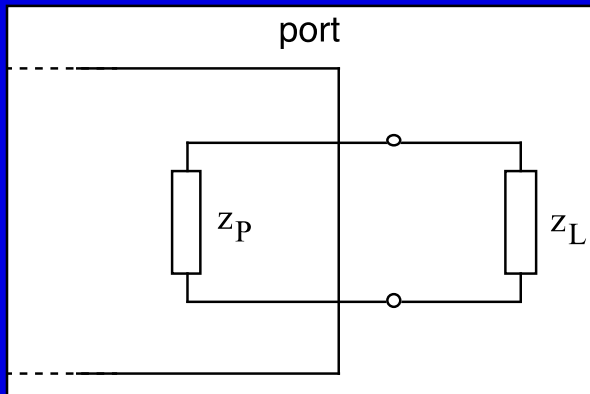
$$y_{out} = y_{22} - \frac{y_{12} \square y_{21}}{y_{11} + y_S}$$



$$r_{loop} = \text{Re} [z_P] + \text{Re} [z_L]$$

$$X_{loop} = \text{Im} [z_P] + \text{Im} [z_L]$$

- **The two-port is stable if the loop resistance $r_{loop} > 0$**
 - Note! The result is **only valid at the actual frequency** where the calculation is done.