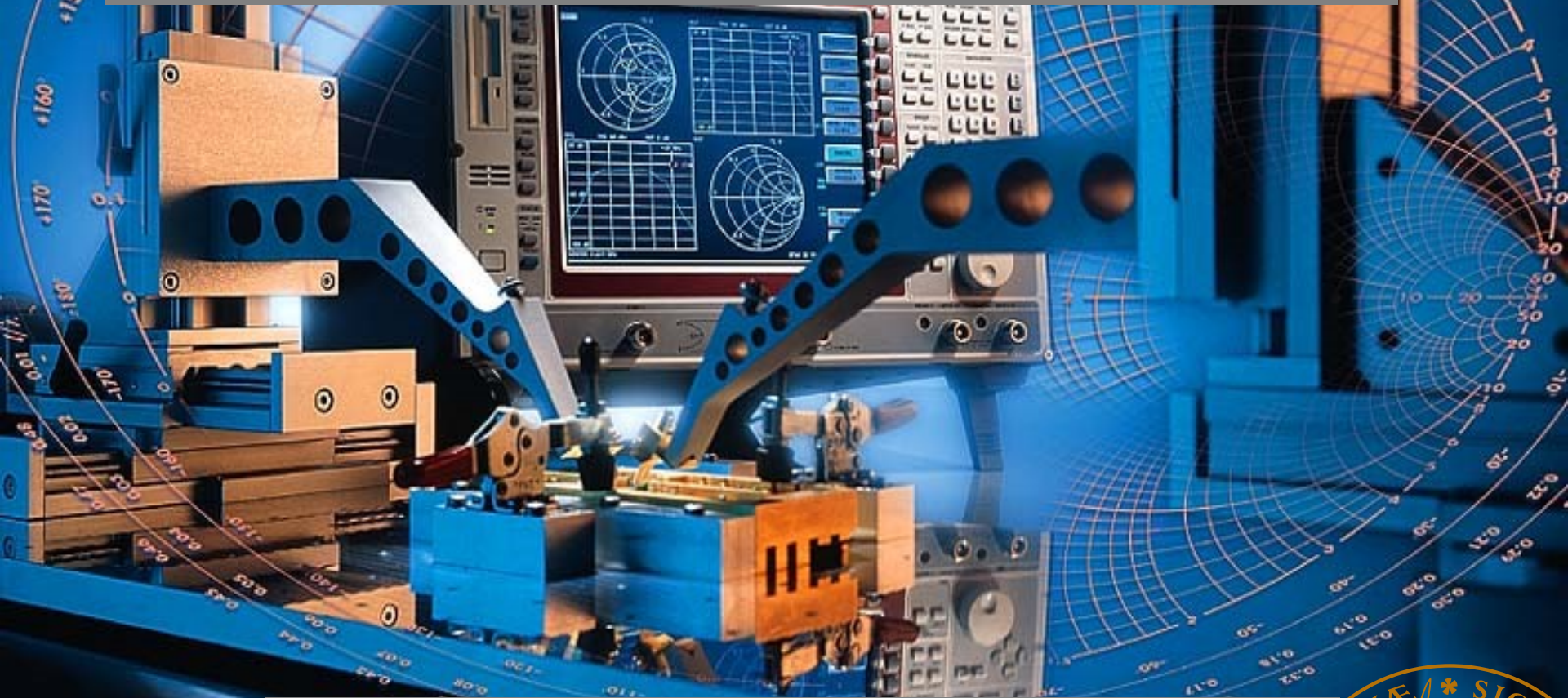


Lecture 7

2019-11-27

# RF Amplifier Design



Lars Ohlsson Fhager  
Electrical and Information Technology



# Schedule Reminder

- Lab 2: Thursday, Nov 28, 8:15-12:00
  - S-parameter measurement using a calibrated VNA
- Hand-in 2: Friday, Dec 6, 23:59
  - Matching and bias design for an LNA
  - ...to be validated in laboratory session 3
- Hand-in 1: with Hand-in 2
  - Revise according to feedback from supervisor
  - Re-submit corrected version

# Lecture 7

- Amplifier Design
  - Stability Analysis by S-parameters
  - Design Cases
    - unilateral two-port, maximum gain (Case 1)
    - unilateral two-port, specific gain (Case 2)
    - bilateral two-port, maximum gain (Case 3)
      - “simultaneous conjugate match”
    - bilateral two-port, specific gain (Case 4)
      - conjugate match at one port, mismatch the other port
      - design method using “operating gain”
      - design method using “available gain”
  - Noise in a Two-Port
  - Design of Low Noise Amplifiers (LNA)


# Stability Analysis by S-Parameters

$\text{Re}[z_{in}] > 0$  for any value of  $z_L$  ( $\text{Re}[z_L] > 0$ )

$\text{Re}[z_{out}] > 0$  for any value of  $z_S$  ( $\text{Re}[z_S] > 0$ )

$|\Gamma_{in}| < 1$  for all  $|\Gamma_L| < 1$

$|\Gamma_{out}| < 1$  for all  $|\Gamma_S| < 1$

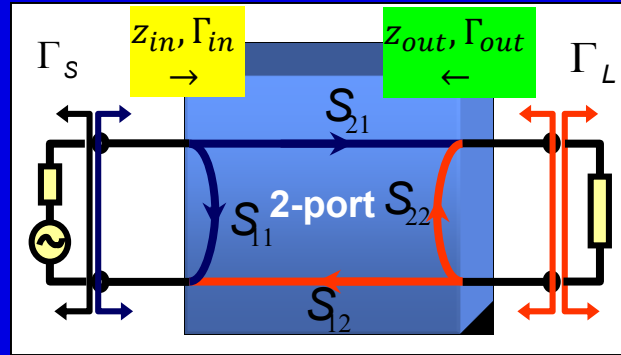

$$\Gamma_{in} = S_{11} + S_{12}S_{21} \frac{\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$\Gamma_{out} = S_{22} + S_{12}S_{21} \frac{\Gamma_S}{1 - S_{11}\Gamma_S}$$

A unilateral two-port ( $S_{12} = 0$ ) is unconditionally stable if

$$|\Gamma_{in}| = |S_{11}| < 1$$

and


$$|\Gamma_{out}| = |S_{22}| < 1$$

A bilateral two-port is  
1) unconditionally stable if


$$|\Delta| < 1 \text{ and } K > 1$$

where  $\Delta = S_{11}S_{22} - S_{12}S_{21}$  and  $K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$

2) conditionally stable if some  $\Gamma_S$  gives  $|\Gamma_{out}| < 1$

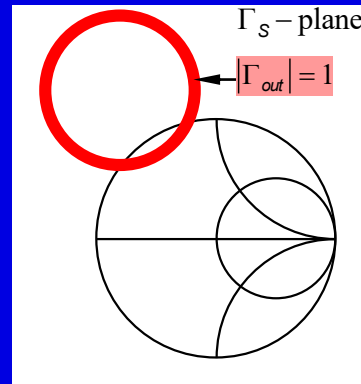


and some  $\Gamma_L$  gives  $|\Gamma_{in}| < 1$

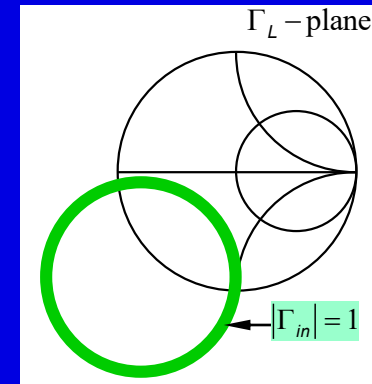


# Amplifier Design

## General design case

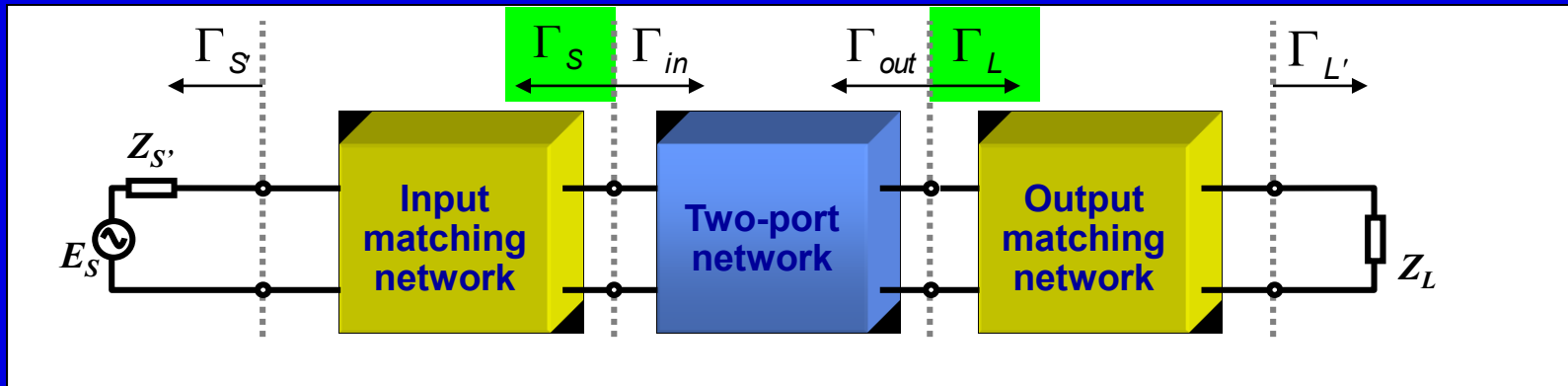

- Given this:
  - two-port (S-parameters) and
  - source  $\Gamma_S$  and load  $\Gamma_L$ ,
- The stability analysis gives allowed values of  $\Gamma_S$  and  $\Gamma_L$
- After a proper choice of  $\Gamma_S$  and  $\Gamma_L$  the matching networks may be designed

# Power Gain Definitions

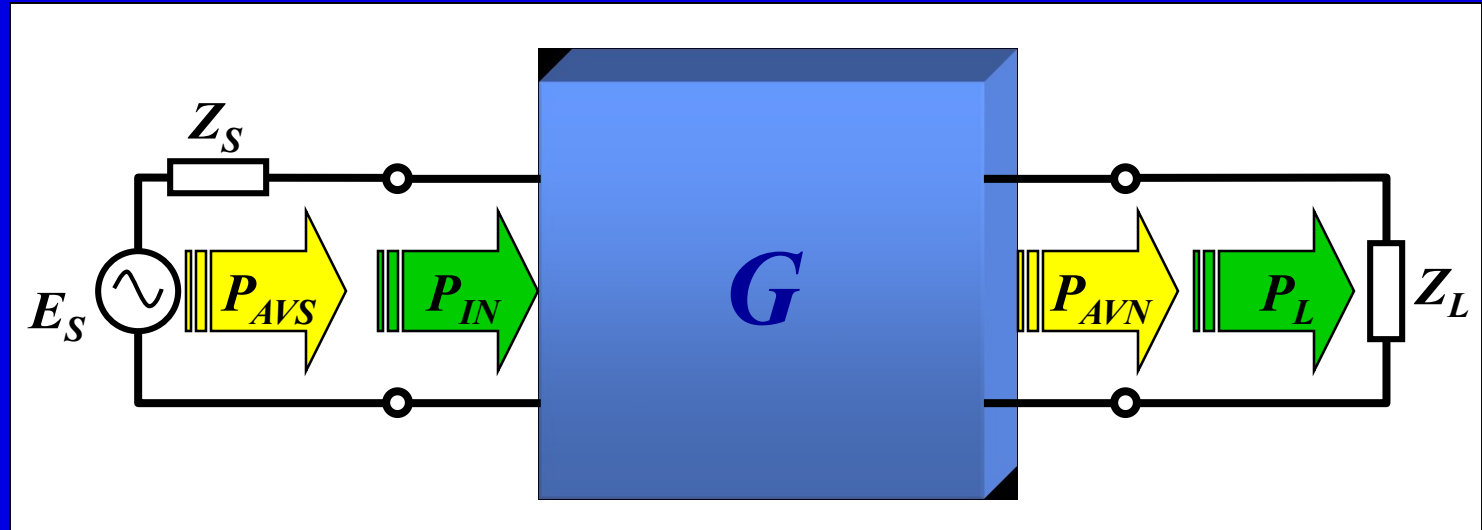


available gain  $G_A = \frac{P_{AVN}}{P_{AVS}}$

operating gain  $G_P = \frac{P_L}{P_{IN}}$

transducer gain  $G_T = \frac{P_L}{P_{AVS}}$

# Design Cases - Gain and Noise Figure

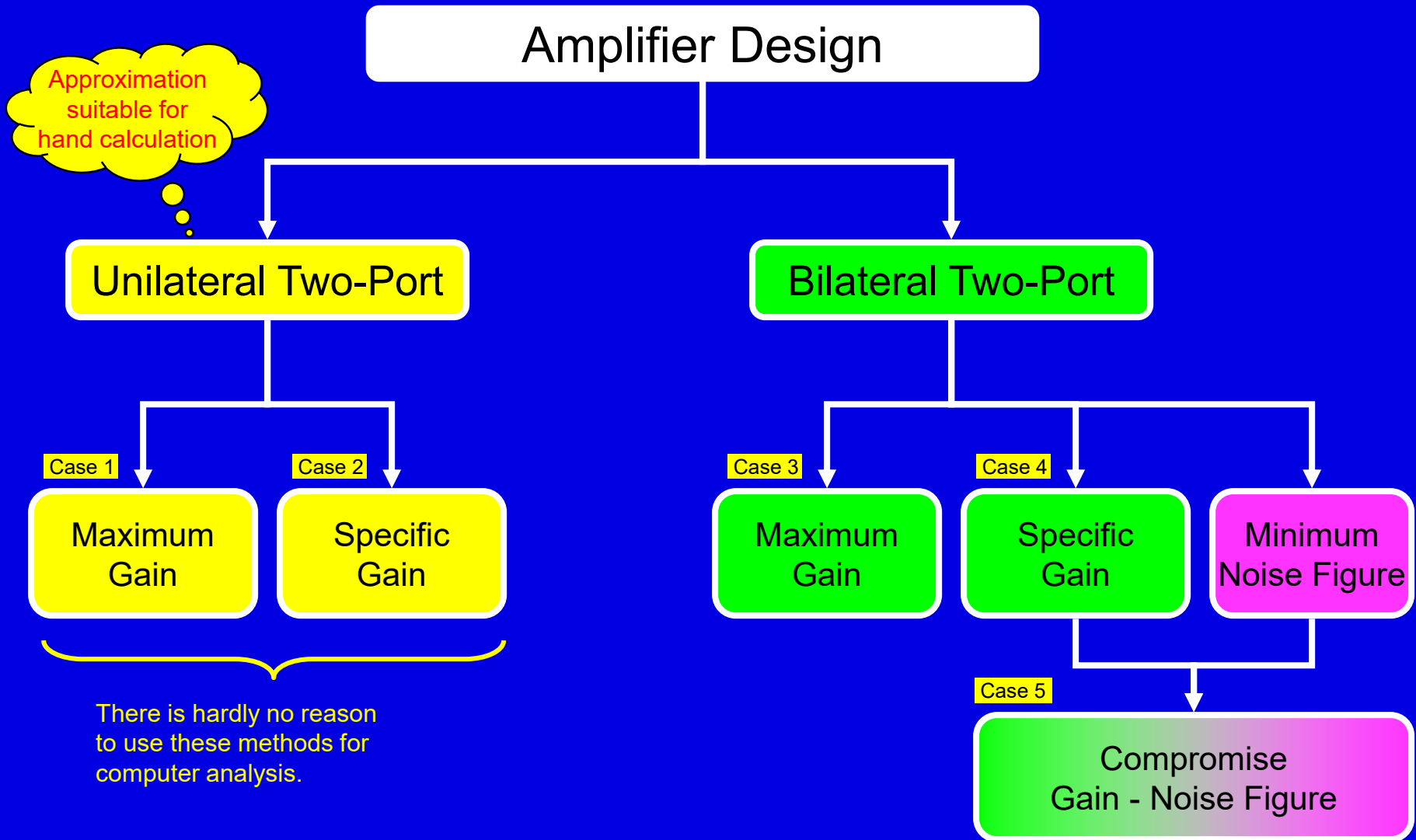

# Unilateral Two-Port, Maximum Gain

- Choose  $\Gamma_S = S_{11}^*$  and  $\Gamma_L = S_{22}^*$   
 i.e. apply conjugate match to both input and output
- The gain is then

$$G_T = \frac{P_L}{P_{AVS}} = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} =$$

$$= \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out}\Gamma_L|^2}$$


Maximum Unilateral Transducer Gain:

$$G_{TUM} = \frac{P_L}{P_{AVS}} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

Assumption:  $|\Gamma_{in}| = |S_{11}| < 1$  and  $|\Gamma_{out}| = |S_{22}| < 1$



# Design Cases - Gain and Noise Figure

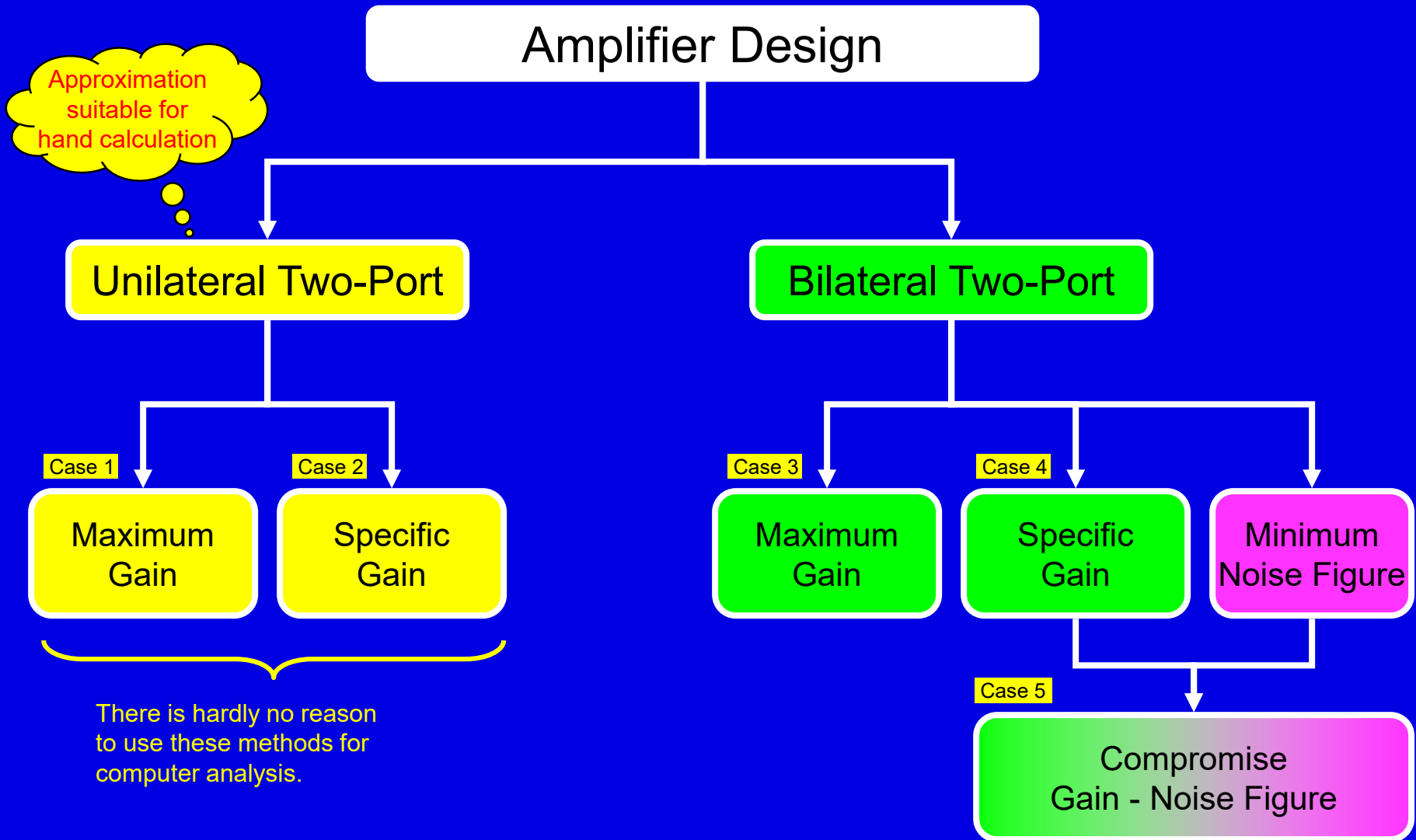

# Unilateral Two-Port, Specific Gain

- The gain is expressed by 
$$G_{TU} = \frac{P_L}{P_{AVS}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

(Unilateral Transducer Gain)

- Split up  $G_{TU} = \alpha_S |S_{21}|^2 \alpha_L$  note that 
$$\max(\alpha_S) = \frac{1}{1 - |S_{11}|^2}$$
 
$$\max(\alpha_L) = \frac{1}{1 - |S_{22}|^2}$$

- Result: 
$$G_{TU} = \frac{\alpha_S}{\max(\alpha_S)} \max(\alpha_S) |S_{21}|^2 \max(\alpha_L) \frac{\alpha_L}{\max(\alpha_L)}$$

$$G_{TU} = \frac{\alpha_S}{\max(\alpha_S)} G_{TUM} \frac{\alpha_L}{\max(\alpha_L)} = g_S G_{TUM} g_L \quad \text{where} \quad \begin{matrix} 0 \leq g_S \leq 1 \\ 0 \leq g_L \leq 1 \end{matrix}$$

- When  $g_S = g_L = 1$  only one solution exists:  $\Gamma_S = S_{11}^*$  and  $\Gamma_L = S_{22}^*$
- If  $g_S < 1$  and  $g_L < 1$  there are lot of solutions. Described by circles in the  $\Gamma_S$ -plane and the  $\Gamma_L$ -plane

# Unilateral Two-Port, Specific Gain

$$G_{TU} = g_S \square G_{TUM} \square g_L$$

For  $g_S < 1$  and  $g_L < 1$  there are lot of solutions. Described by circles in the  $\Gamma_S$ -plane and the  $\Gamma_L$ -plane

Input:

$$\text{radius: } r_S = \frac{\sqrt{1-g_S}(1-|S_{11}|^2)}{1-|S_{11}|^2(1-g_S)}$$


$$\text{centre: } \Gamma_{so} = \frac{g_S |S_{11}|}{1-|S_{11}|^2(1-g_S)} \square e^{j \arg(S_{11}^*)}$$

Output:


$$\text{radius: } r_L = \frac{\sqrt{1-g_L}(1-|S_{22}|^2)}{1-|S_{22}|^2(1-g_L)}$$

$$\text{centre: } \Gamma_{Lo} = \frac{g_L |S_{22}|}{1-|S_{22}|^2(1-g_L)} \square e^{j \arg(S_{22}^*)}$$

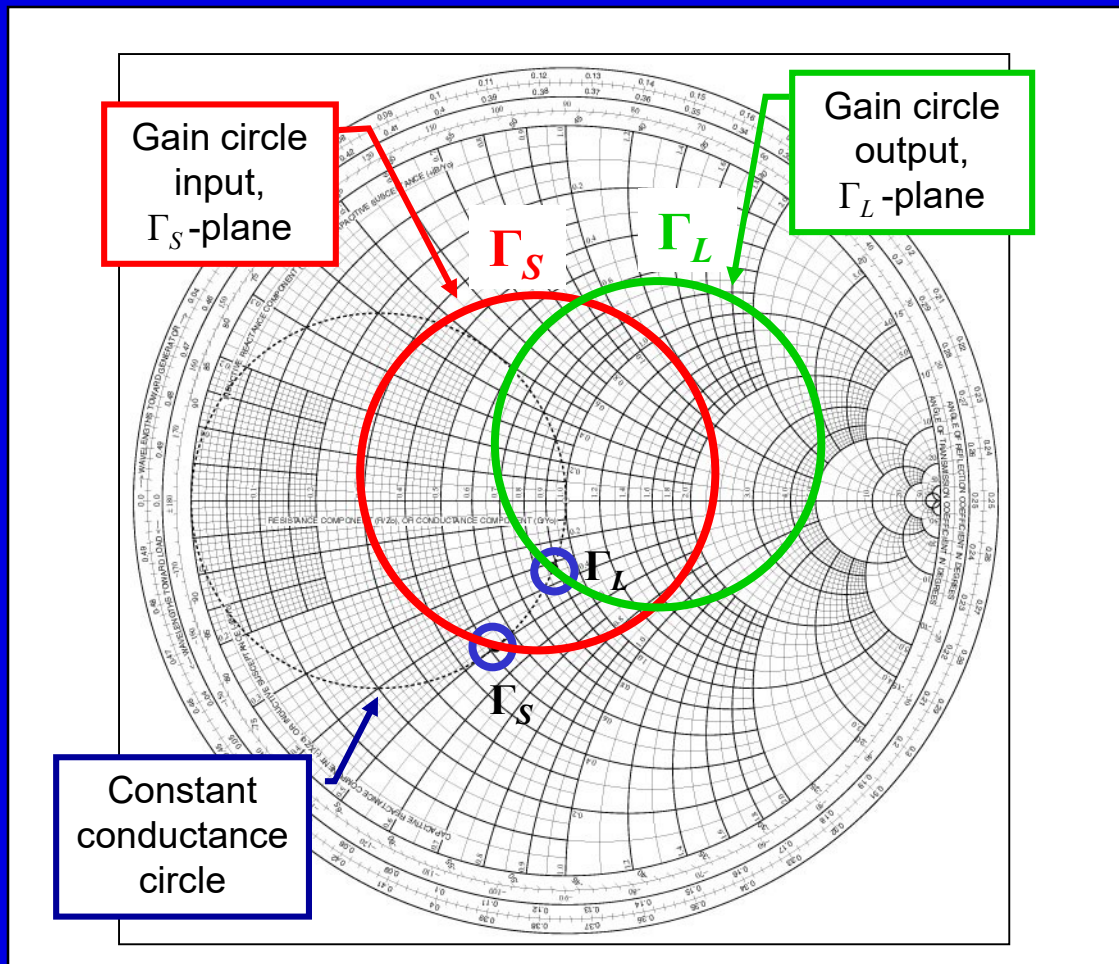How do you select "smart"  $\Gamma_S$  and  $\Gamma_L$ ?



# Design Cases - Gain and Noise Figure

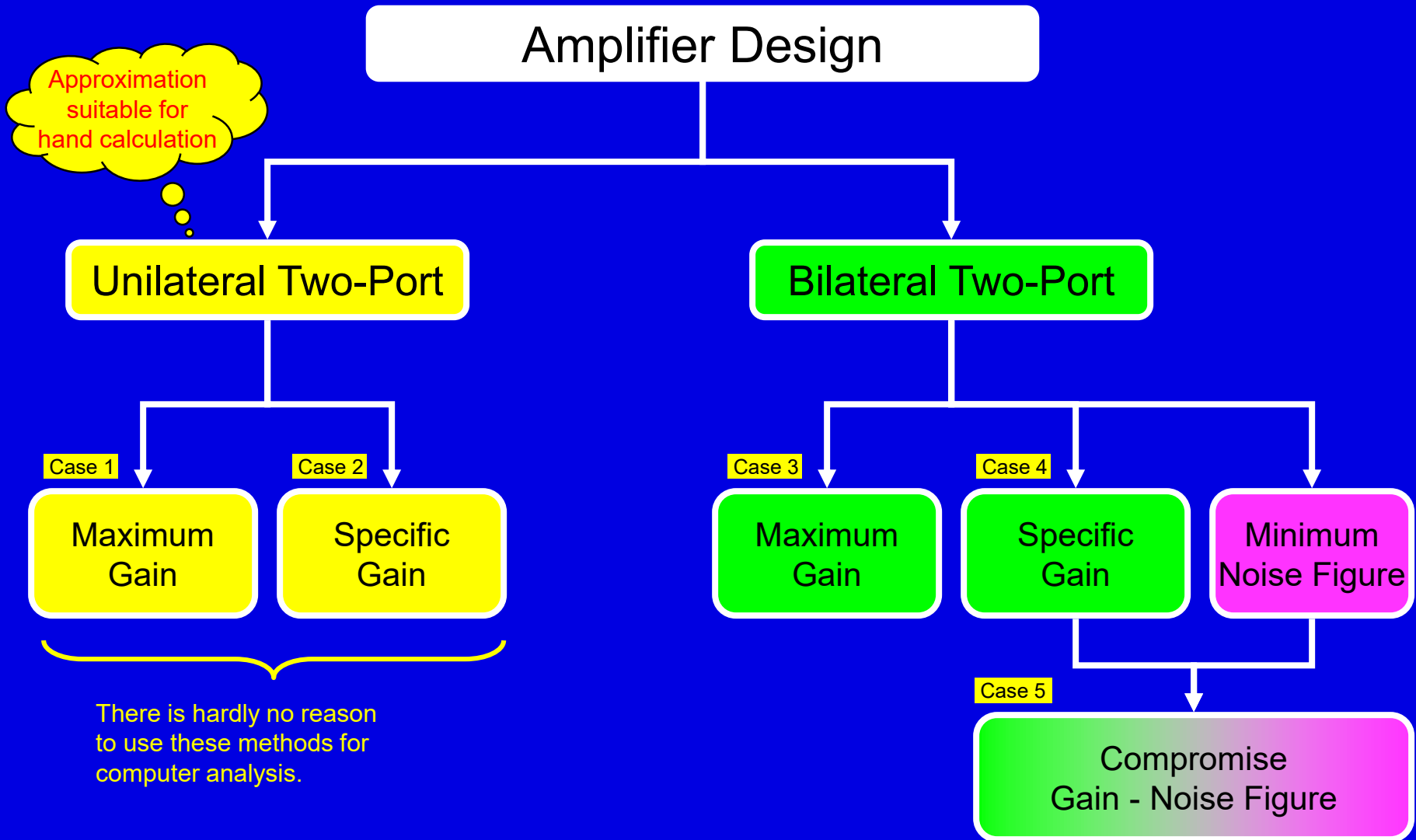

# Bilateral Two-Port, Maximum Gain

- Maximum gain is achieved when  $\Gamma_S = \Gamma_{IN}^*$  and  $\Gamma_L = \Gamma_{OUT}^*$   
 i.e. apply conjugate match to both input and output

$$\Gamma_S = \left( S_{11} + S_{12}S_{21} \frac{\Gamma_L}{1 - S_{22}\Gamma_L} \right)^* \quad \text{and} \quad \Gamma_L = \left( S_{22} + S_{21}S_{12} \frac{\Gamma_S}{1 - S_{11}\Gamma_S} \right)^*$$

- These equations need to be solved simultaneously, that's why it's called "simultaneous conjugate match"

- Explicit solution:

$$\Gamma_{SM} = \frac{B_1 - \sqrt{B_1^2 - 4|C_1|^2}}{2C_1} \quad \text{and} \quad \Gamma_{LM} = \frac{B_2 - \sqrt{B_2^2 - 4|C_2|^2}}{2C_2} \quad \text{where} \quad \begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta S_{22}^* \\ C_2 = S_{22} - \Delta S_{11}^* \end{cases}$$

**NOTE!** The solution only exists when the two-port is **unconditionally stable**, i.e.  $|\Delta| < 1$  and  $K > 1$ !

# Bilateral Two-Port

- At “simultaneous conjugate match” the maximum transducer gain is:

$$G_{TM} = \frac{|S_{21}|}{|S_{12}|} \left( K - \sqrt{K^2 - 1} \right)$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21} \text{ and } K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$$

- With  $K$  set to 1 the quantity **Maximum Stable Gain** is derived:

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|}$$

- For conditionally stable two-port, the stability factor  $K$  may be altered by resistive loading of the input or output without changing the ratio  $|S_{21}|/|S_{12}|$ .
- But for a conditionally stable two-port
  - it doesn't make any sense to the quantity “maximum transducer gain” and
  - the simultaneous conjugate match doesn't have any solution.
- Therefore, **the method changes to case 4** when there is conditional stability.

# Bilateral Two-Port

- The procedure will be like this:


1. Calculate the “maximum stable gain”:

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|}$$

2. Back off a few dB or so to set a safety margin.
3. Use the reduced gain as specific gain and design according to case 4.

- For conditionally stable two-port
  - may strictly any arbitrary gain be selected
  - but as the gain increases towards  $G_{MSG}$ , the risk for self-oscillation escalates
  - $G_{MSG}$  is in this sense the absolute maximum level.

# Design Cases - Gain and Noise Figure

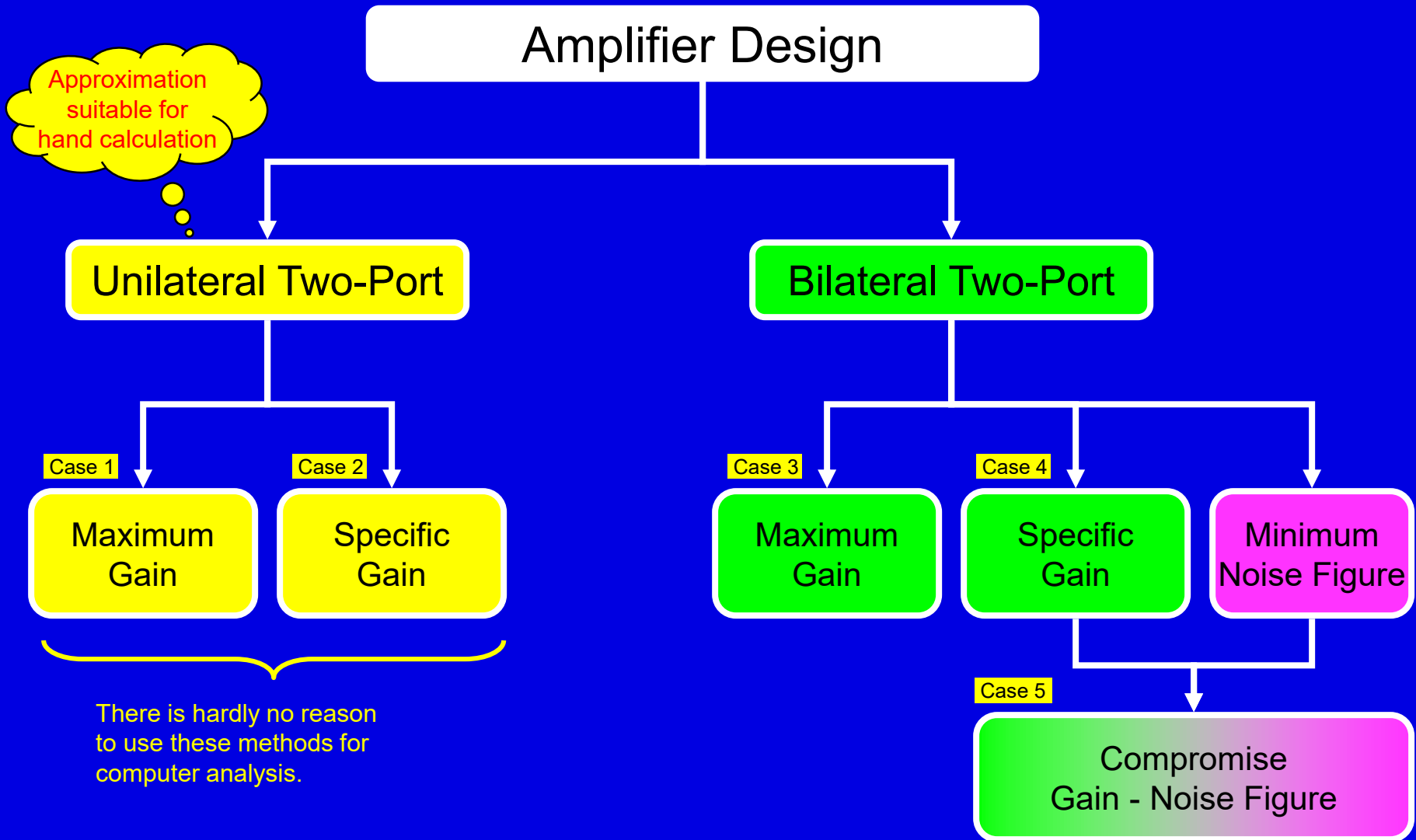



# Bilateral Two-Port, Specific Gain

- In the unilateral case it was possible to handle the input and output ports separately.
- BUT at the bilateral case the conditions at the input port depends on the load and vice versa.

$$\Gamma_{in} = S_{11} + S_{12} S_{21} \frac{\Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = S_{22} + S_{12} S_{21} \frac{\Gamma_S}{1 - S_{11} \Gamma_S}$$

Is it possible to disengage the ports from each other?

Yes it is:  
Assume conjugate match at one of the ports and the other is mismatched to obtain the specified gain ( $G_T$ )!

- Then

$$G_T = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2} = \{\Gamma_L = \Gamma_{out}^*\} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2} = G_A$$

# Bilateral Two-Port, Specific Gain

Assume conjugate match at one port and mismatch is applied to the other!

If a mismatch is wanted at the output:

1. use “operating gain”
2. apply mismatch at the output so that  $G_P = G_T$  and solve  $\Gamma_L$
3. conjugate match the input ( $\Gamma_{in}$  known) then  $G_P = P_L/P_{IN} = P_L/P_{AVS} = G_T$

$$G_P = \frac{P_L}{P_{IN}} = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$\Gamma_{in} = S_{11} + S_{12}S_{21} \frac{\Gamma_L}{1 - S_{22}\Gamma_L}$$

If a mismatch is wanted at the input:

1. use “available gain”
2. apply mismatch at the input so that  $G_A = G_T$  and solve  $\Gamma_S$
3. conjugate match the output ( $\Gamma_{out}$  known) then  $G_A = P_{AVN}/P_{AVS} = P_L/P_{AVS} = G_T$

$$G_A = \frac{P_{AVN}}{P_{AVS}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2}$$

$$\Gamma_{out} = S_{22} + S_{12}S_{21} \frac{\Gamma_S}{1 - S_{11}\Gamma_S}$$

# Bilateral Two-Port, Specific Gain

Design by “operating gain”

$$G_P = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

can be written as

$$G_P = |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{\left(1 - \left|\frac{S_{11} - \Delta\Gamma_L}{1 - S_{22}\Gamma_L}\right|^2\right) |1 - S_{22}\Gamma_L|^2} = |S_{21}|^2 g_P$$

Can we affect  $S_{21}$ ?


1.  $S_{21}$  is known, determine  $g_P$  to obtain the wanted gain
2. what  $\Gamma_L$  complies with the selected  $g_P$ ?
  - there are a number of solutions at a circle in the  $\Gamma_L$ -plane

$$\text{radius: } r_L = \frac{\sqrt{1 - 2K|S_{12}S_{21}|g_P + |S_{12}S_{21}|^2 g_P^2}}{|1 - g_P(|S_{22}|^2 - |\Delta|^2)|}$$

$$\text{centre: } \Gamma_{LO} = \frac{g_P C_L^*}{1 - g_P(|S_{22}|^2 - |\Delta|^2)}$$

$$\text{where } C_L = S_{22} - \Delta S_{11}^*$$

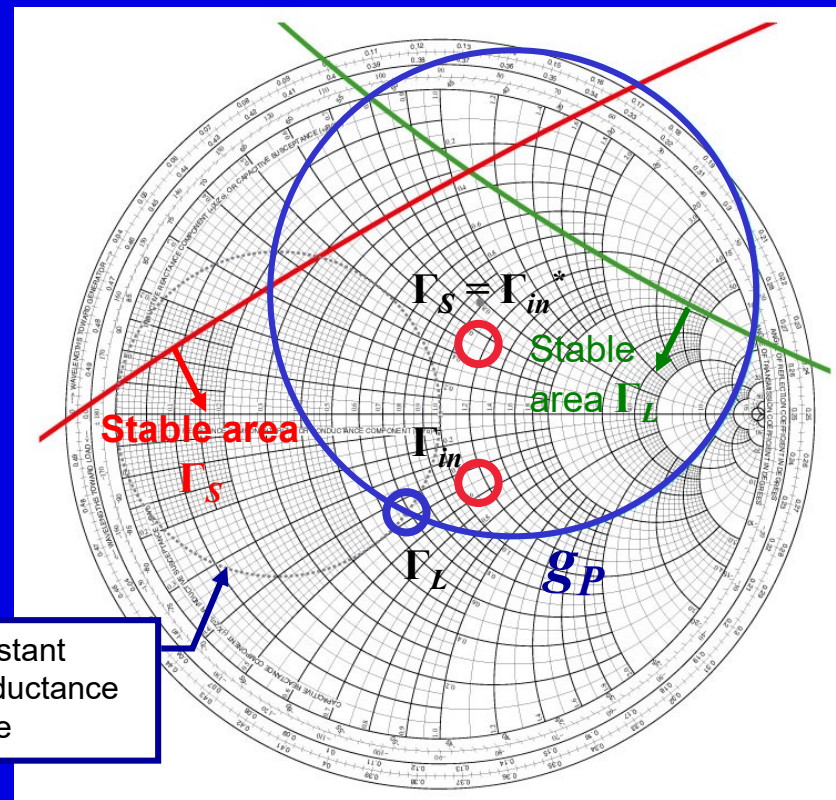3. select a “smart”  $\Gamma_L$ !
4. calculate  $\Gamma_{in}$  and conjugate match the input



# Bilateral Two-Port, Specific Gain

Design by “available gain”

$$G_A = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2}$$

can be written as

$$G_A = |S_{21}|^2 \cdot \frac{1 - |\Gamma_S|^2}{\left(1 - \left|\frac{S_{22} - \Delta\Gamma_S}{1 - S_{11}\Gamma_S}\right|\right) |1 - S_{11}\Gamma_S|^2} = |S_{21}|^2 g_A$$

1.  $S_{21}$  is known, determine  $g_A$  to obtain the wanted gain
  2. what  $\Gamma_S$  complies with the selected  $g_A$ ?
- there are a number of solutions at a **circle in the  $\Gamma_S$ -plane**

$$\text{radius: } r_S = \frac{\sqrt{1 - 2K|S_{12}S_{21}|g_A + |S_{12}S_{21}|^2 g_A^2}}{|1 - g_A(|S_{11}|^2 - |\Delta|^2)|}$$

$$\text{centre: } \Gamma_{so} = \frac{g_A C_S^*}{1 - g_A(|S_{11}|^2 - |\Delta|^2)}$$


$$\text{where } C_S = S_{11} - \Delta S_{22}^*$$

# Bilateral Two-Port, Specific Gain

## summary

- If a two-port is conditionally stable:
  1. Calculate stability circles
  2. Calculate a gain circle to obtain the wanted  $G_P, (G_A)$
  3. Select  $\Gamma_L, (\Gamma_S)$  at the gain circle in the stable area
  4. Calculate  $\Gamma_{IN}, (\Gamma_{OUT})$
  5. Check if conjugate match is possible
    - i.e. if  $\Gamma_S = \Gamma_{IN}^*$  ( $\Gamma_L = \Gamma_{OUT}^*$ ) is located in the stable area
    - if not, return to step 3 and make a new choice
    - alternatively lower the demand for gain

# Noise in a Two-Port

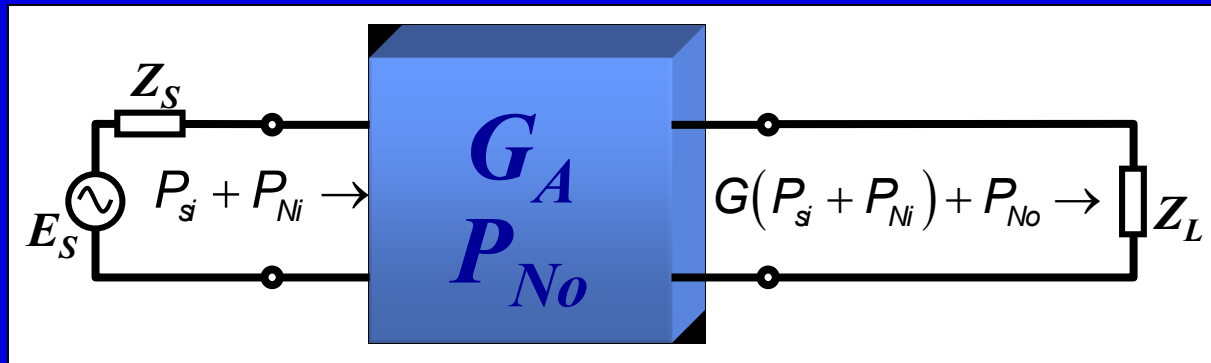

- The signal-to-noise ratio  $SNR = \frac{P_s}{P_N}$  is deteriorated due to **noise power** added by the two-port
- The **noise factor ( $F$ )**, linear, denotes the increase of noise by the two-port, assumed a source noise temperature of  $T_0 = 290$  K

$$F = \frac{P_{No} + P_{Ni} G_A}{P_{Ni} G_A}$$

but

$$G_A = \frac{P_{So}}{P_s}$$

leads to

$$F = \frac{\frac{P_s}{P_{Ni}}}{\frac{P_{So}}{P_{No} + P_{Ni} G_A}} = \frac{SNR_i}{SNR_o}$$

- Alternatively **noise figure ( $NF$ )**, decibel scale,  $NF = 10 \log_{10}(F)$ .

# Noise in Cascaded Two-Ports


- The total noise factor (remember: linear scale) is

$$F_{TOT} = \frac{\text{total available noise power at the output}}{\text{available noise at the output originating from the source}}$$

$$F_{TOT} = 1 + \frac{P_{No1}}{P_{Ni} G_{A1}} + \frac{P_{No2}}{P_{Ni} G_{A1} G_{A2}} + \dots$$

- Friis' formula:


$$F_{TOT} = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1} G_{A2}} + \dots$$



No decibels here!

- NOTE: all variables must be denoted in linear quantities!**

# Design Cases - Gain and Noise Figure

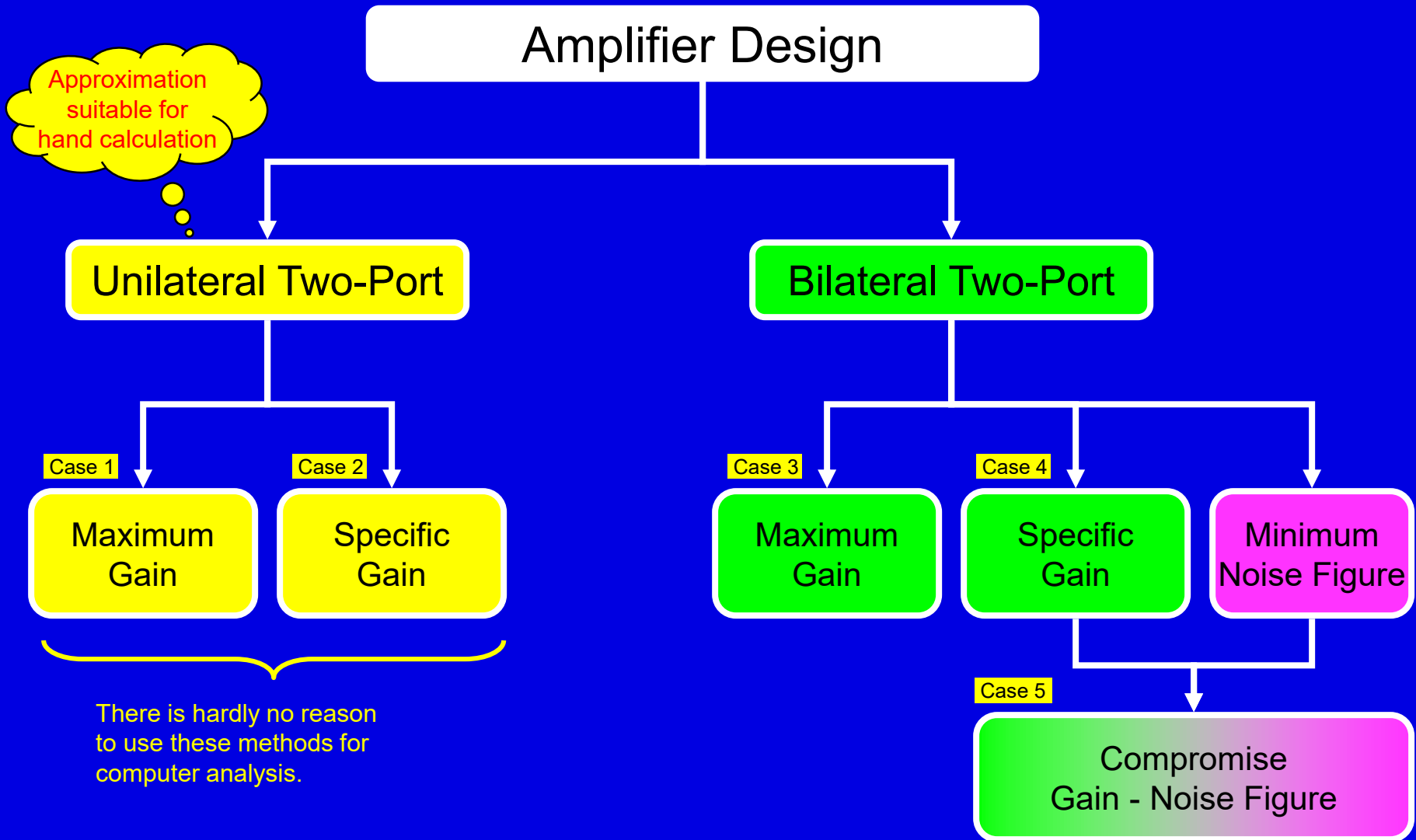



# Design of Low Noise Amplifiers (LNA)

- The noise power from a transistor depends on
  - the source impedance
  - the quiescent point ( $I_C$ ,  $V_{CE}$ )
- There is an **optimum source impedance** that gives the **minimum noise factor (or figure)** for a **specified quiescent point**
- The source impedance for minimum noise factor does unfortunately NOT coincide with the source impedance for maximum gain
  - **noise match**  $\Leftrightarrow$  **power mismatch at the input**

# Design of Low Noise Amplifiers (LNA)

- The noise factor:

$$F = F_{min} + \frac{R_N}{G_S} |Y_S - Y_{opt}|^2 \quad \text{where} \quad G_S = \text{Re}[Y_S]$$

$F_{min}$  - the minimum noise factor

$R_N$  - determines how much  $F$  increases when  $Y_S$  deviates from  $Y_{opt}$

$Y_{opt}$  - the source admittance providing  $F_{min}$

- The noise factor denoted by normalised parameters:

$$F = F_{min} + \frac{r_N}{g_S} |y_S - y_{opt}|^2 \quad \text{where} \quad g_S = \text{Re}[y_S]$$

- The noise factor denoted by reflection coefficients:

$$F = F_{min} + \frac{4r_N |\Gamma_S - \Gamma_{opt}|^2}{(1 - |\Gamma_S|^2) |1 + \Gamma_{opt}|^2}$$


# Design of Low Noise Amplifiers (LNA)

- There are a number of  $\Gamma_S$  that provides a specified noise factor
- These are found at **circles in the  $\Gamma_S$ -plane**


$$\text{radius: } r_s = \frac{\sqrt{N_i^2 + N_i(1 - |\Gamma_{opt}|^2)}}{1 - N_i}$$

$$\text{centre: } \Gamma_{so} = \frac{\Gamma_{opt}}{1 + N_i}$$

$$\text{where } N_i = (F - F_{min}) \frac{|1 + \Gamma_{opt}|^2}{4r_N}$$

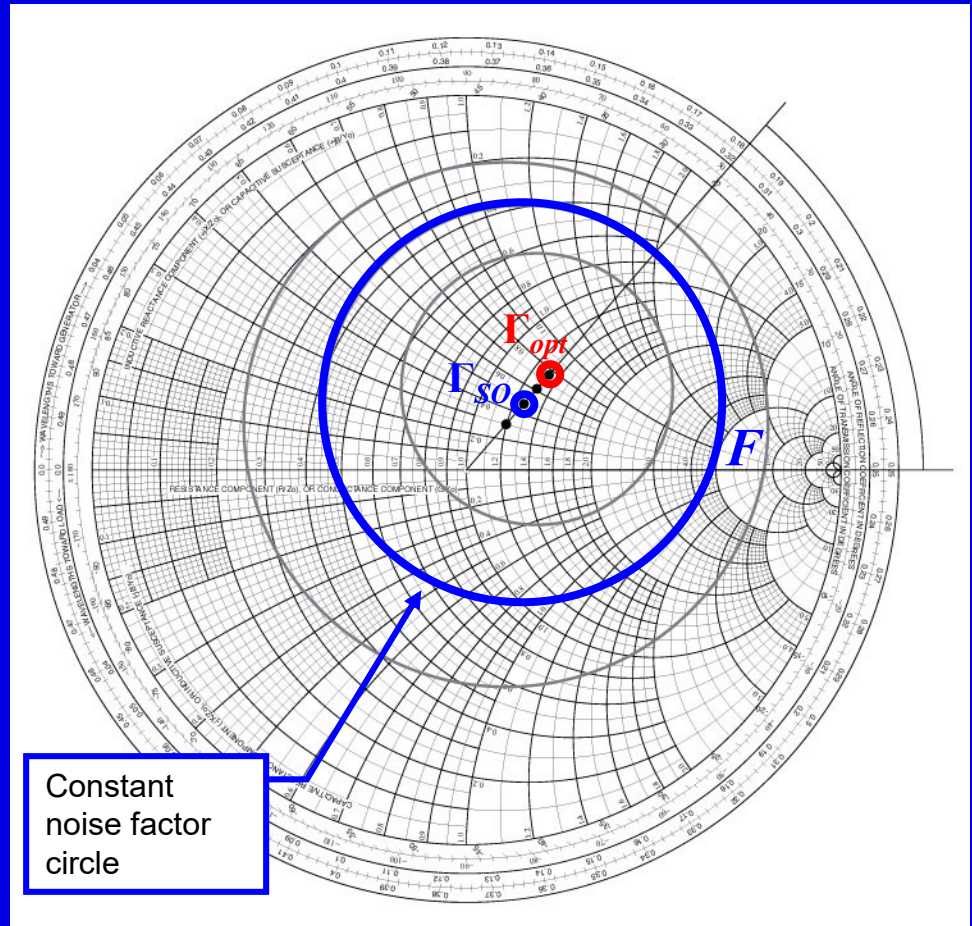

# Design Cases - Gain and Noise Figure

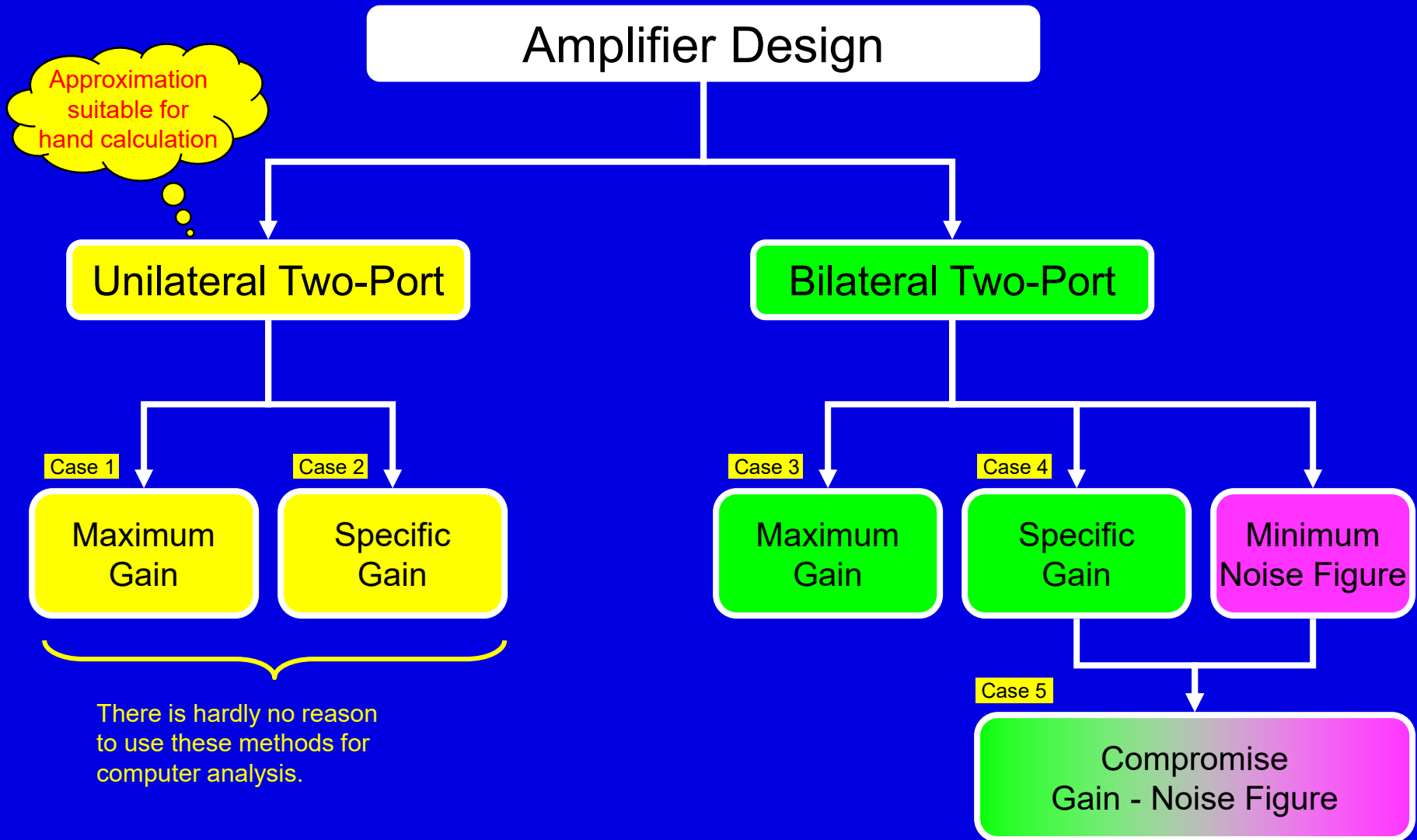

# Summary of Amplifier Design

1. Decide if the transistor is unconditionally stable
2. Calculate stability circles if necessary

$G_T$

3. Choose a method for specific or maximum gain
4. Assume conjugate match at the input (or the output)
5. Calculate a gain circle to obtain the wanted  $G_P$  (or  $G_A$ )
6. Select  $\Gamma_L$  (or  $\Gamma_S$ ) at the gain circle in the stable area
7. Calculate  $\Gamma_{IN}$  (or  $\Gamma_{OUT}$ )

$G_T, F$

3. Choose the method for specific gain using available gain
4. Assume conjugate match at the output
5. Draw noise and gain circles
6. Select  $\Gamma_S$  in the stable area that provides a suitable compromise of noise and gain
7. Calculate  $\Gamma_{OUT}$

8. Check if conjugate match is possible
  - i.e. if  $\Gamma_S = \Gamma_{IN}^*$  ( $\Gamma_L = \Gamma_{OUT}^*$ ) is located in the stable area
  - if not, return to step 6 and make a new choice
  - alternatively lower the demand for gain and return to step 5
9. Design the matching networks and verify stability at all frequencies of interest