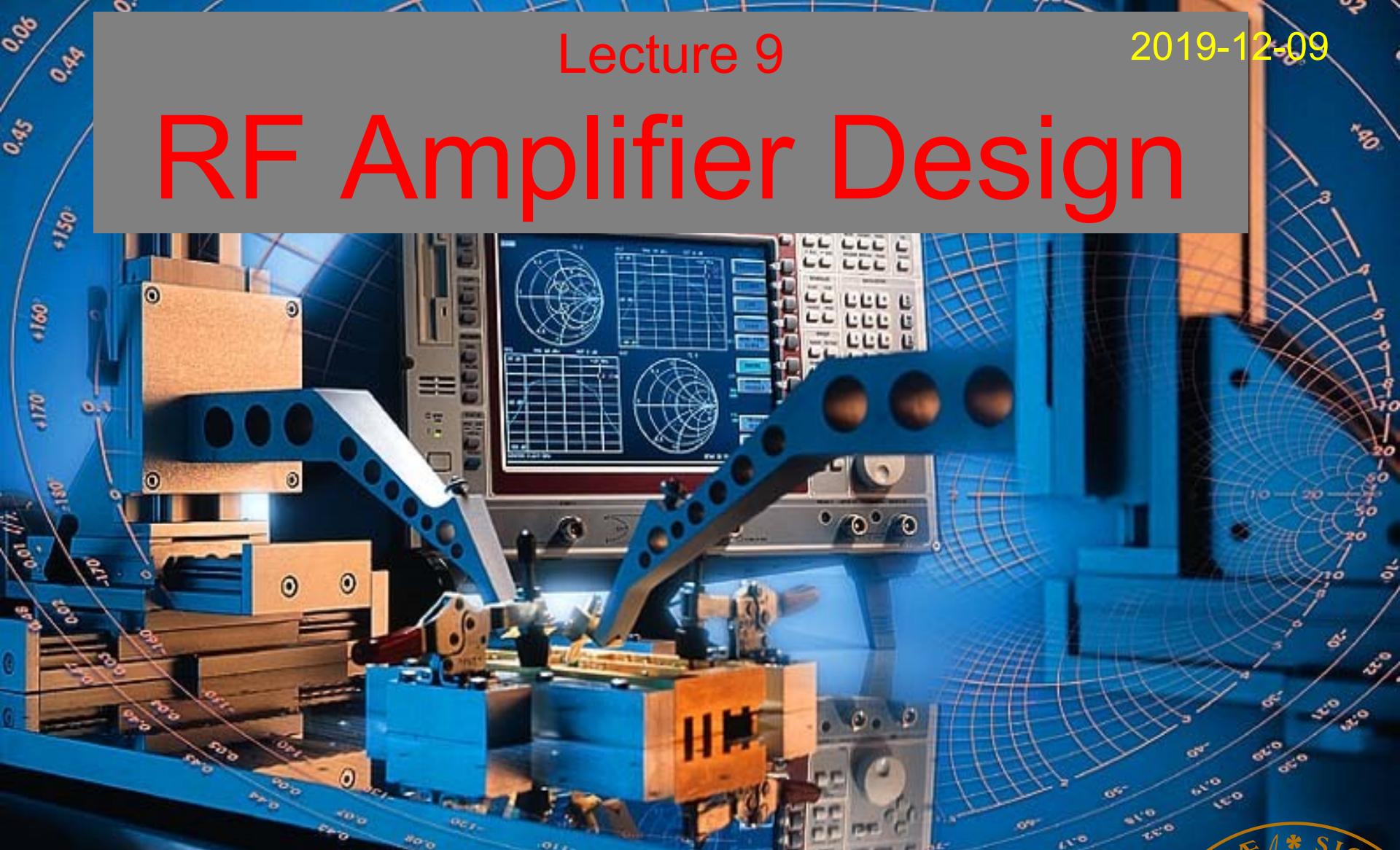


RF Amplifier Design



Lars Ohlsson Fhager
Electrical and Information Technology



Schedule Reminder

- Lab 3: Thursday, Dec 12, 8:15-12:00
 - Amplifier, IF and RF, characterisation
- Lab 4: Wednesday, Dec 18, 8:15-12:00
 - LC, negative resistance, and crystal oscillators
- Lab Catch-up: Friday, Dec 20, 8:15-12:00
 - Final laboratory session for those who for some reason were unable to attend another session

Schedule Reminder

- Also, make sure to correct and re-submit hand-in assignments
- Written Examination: Tuesday, Jan 14, 2020, 8:00-13:00 (5 h, starting at 8 sharp), E:2311
 - Allowed tools:
 - (1) Radio Electronics – Formulas and Tables
 - (2) Pocket calculator for complex numbers

Note: Laboratory sessions and hand-in assignments must be graded pass for admittance to examination.


Lecture 9

- Oscillators
 - Oscillators Based on Feedback
 - Requirements for Self-Oscillation
 - Output Power and Harmonic Distortion
- Tuned LC Oscillators
- Oscillator Noise
- Negative Resistance Oscillators
- Voltage Controlled Oscillators (VCO)
- Resonators
- Crystal Oscillators (XO)
- Some Good Practical Advice about Oscillator Design

Black's Feedback Model

$$V_{out} = A_v V_A$$

$$V_A = V_{in} + \beta V_{out}$$

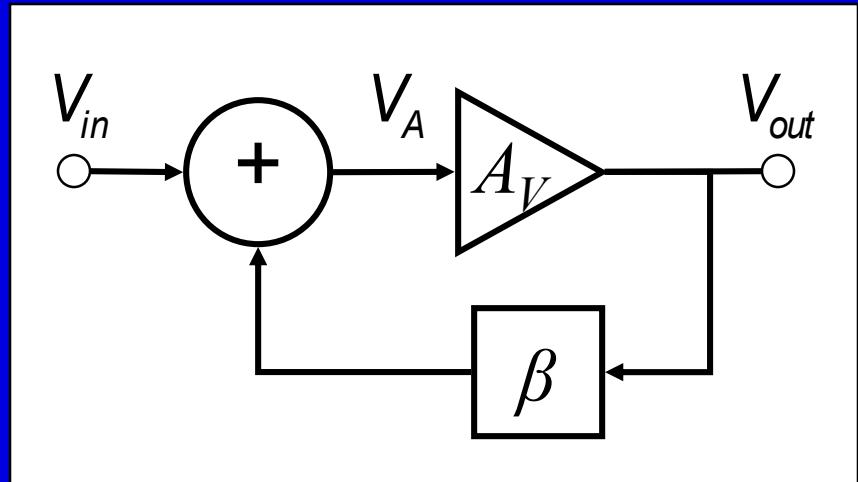

$$A_f = \frac{V_{out}}{V_{in}} = \frac{A_v}{1 - A_v \beta}$$

- Barkhaussen oscillation criteria:


$$A_v \beta = 1 \quad A_v \cdot \beta \text{ is called the loop gain}$$

Oscillators Based on Feedback

- If the oscillator runs at constant amplitude it complies with the Barkhaussen oscillation criteria:


$$A_v \beta = 1$$

- i.e. $|A_v \beta| = 1$
- and $\arg(A_v \beta) = 0$

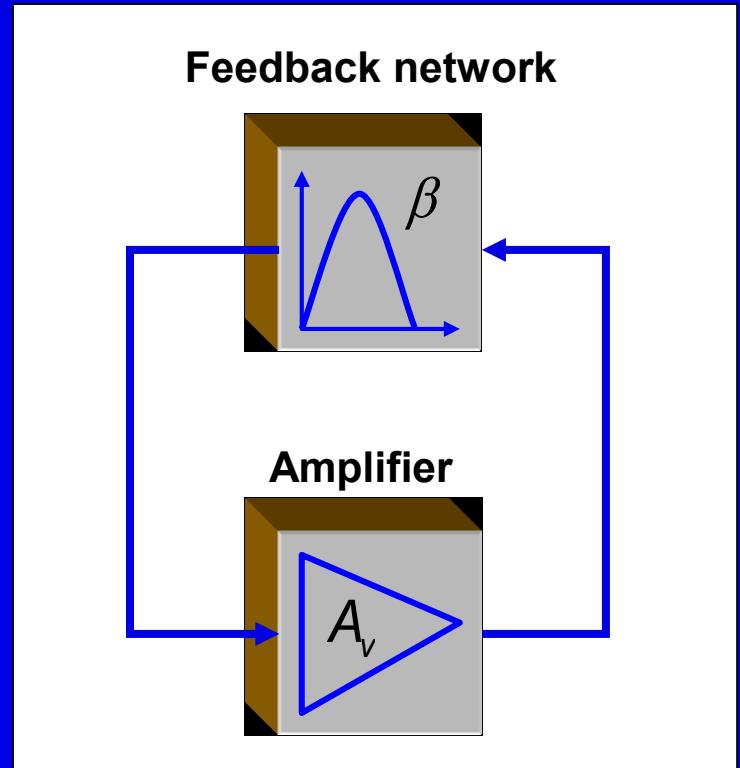

A_v = voltage gain
 β = feedback factor

Output Power and Harmonic Distortion

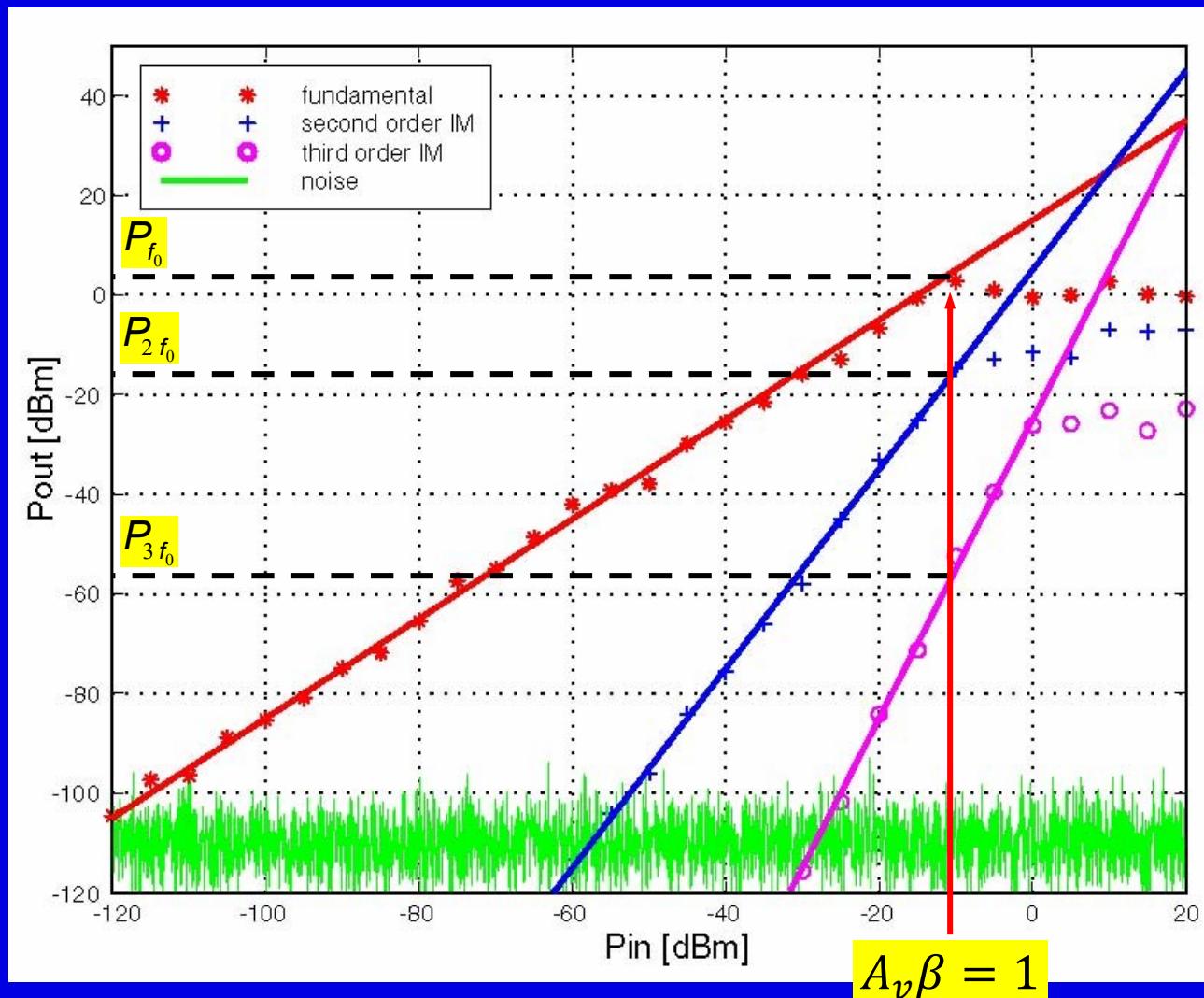

$A_v\beta = 1$ when the oscillator runs at constant amplitude, ↑
which must occur in the vicinity of gain compression

The Generalized Oscillator Model for LC Oscillators


- The phase criteria in Barkhaussen is fulfilled when

$$X_1 + X_2 + X_3 = 0$$

i.e. the circuit is at resonance

- The amplitude criteria in Barkhaussen is fulfilled when



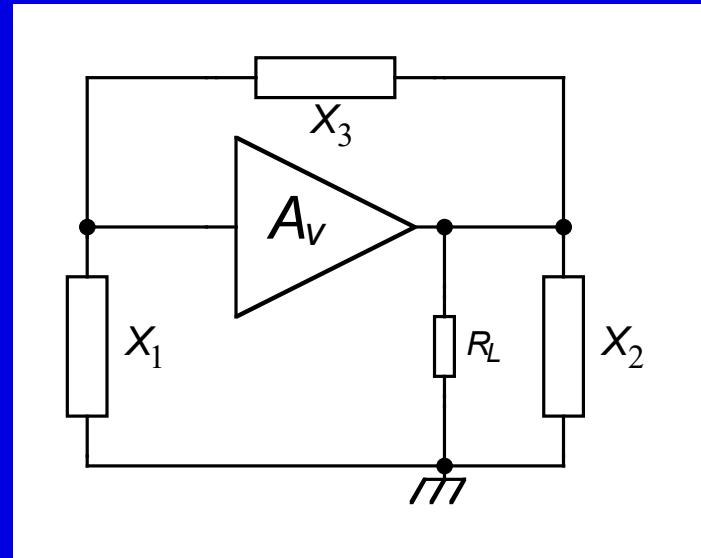
$$\beta = \frac{1}{A_v} = \frac{X_1}{X_1 + X_3} = \frac{X_1}{-X_2} = \frac{X_2 + X_3}{X_2}$$



Tip: choose an expression for β where both reactance's are inductive or capacitive

Oscillator Circuits

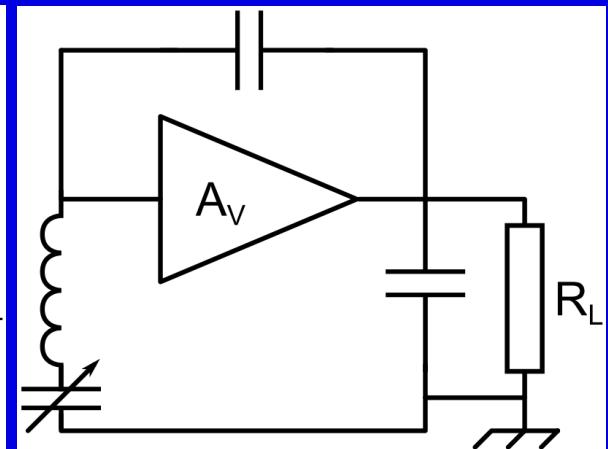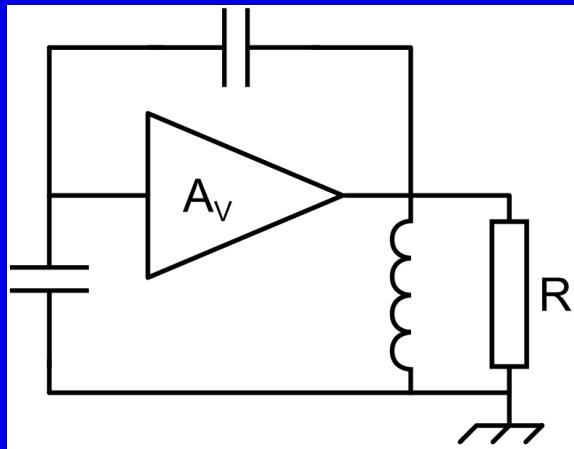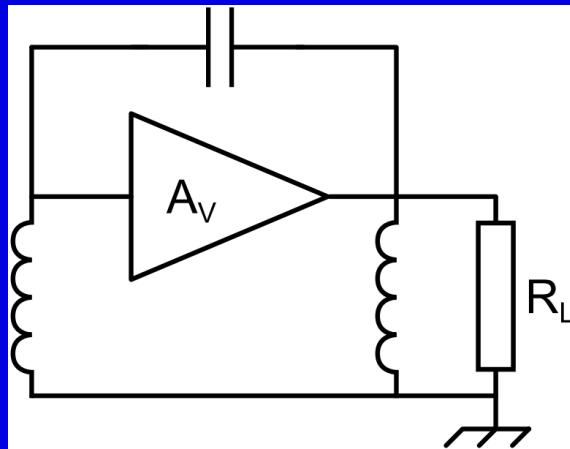
- The feedback network in LC oscillators may be configured in different ways:
 - Hartley
 - Colpitts
 - Clapp




- ❖ one capacitive branch
- ❖ two inductive branches
- ❖ two capacitive branches
- ❖ one inductive branch
- ❖ a variation of the Colpitts oscillator

Depending on the selected transistor configuration (CE, CB or CC) there are a lot more variations.

Example 1

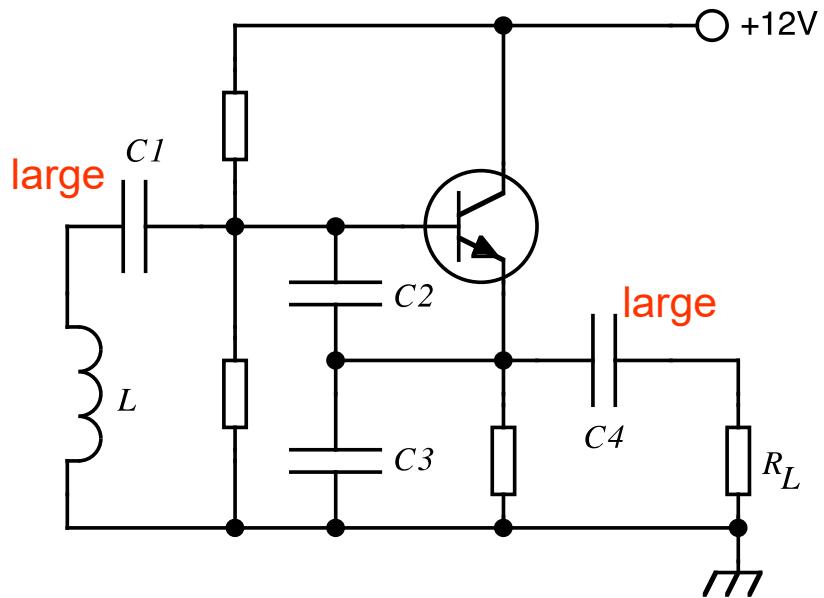


Example 2

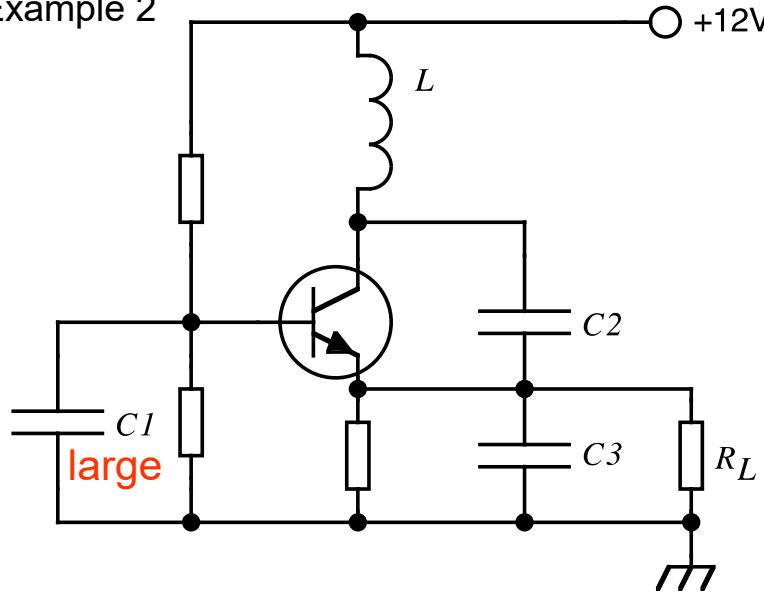

Oscillator Analysis

1. determine the amplifier configuration (CE, CB or CC)?
2. identify components that determines the frequency and feedback?
3. draw the generalized oscillator model
4. calculate the voltage gain A_V
5. calculate the resonant frequency f_0
6. calculate the feedback factor β
7. check if the Barkhaussen criteria is fulfilled

Calculation of A_V and β

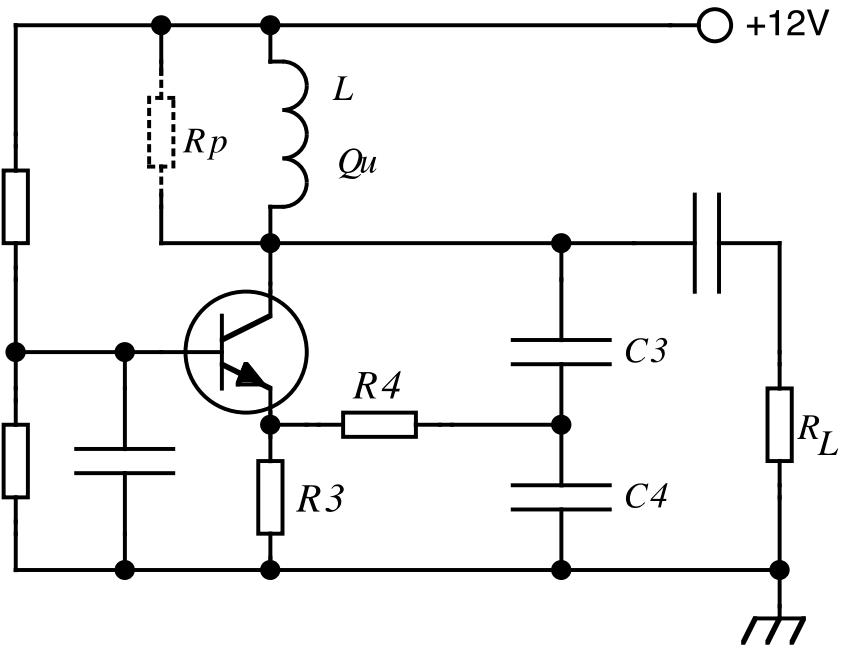

$$A_v \beta = 1$$

$$g_m = \frac{I_c}{V_T}$$

$$A_v = g_m R_{ctot}$$

$$R_{ctot} = R_p || R_L || R'_{in} || r_o$$


$$R_p = Q_u \omega_0 L$$

$$R'_{in} = [(r_e || R_3) + R_4] \left(\frac{C_3 + C_4}{C_3} \right)^2$$

$$\beta = \frac{(r_e || R_3)}{(r_e || R_3) + R_4} \frac{C_3}{C_3 + C_4}$$

compare with lab 4!


Oscillator Noise

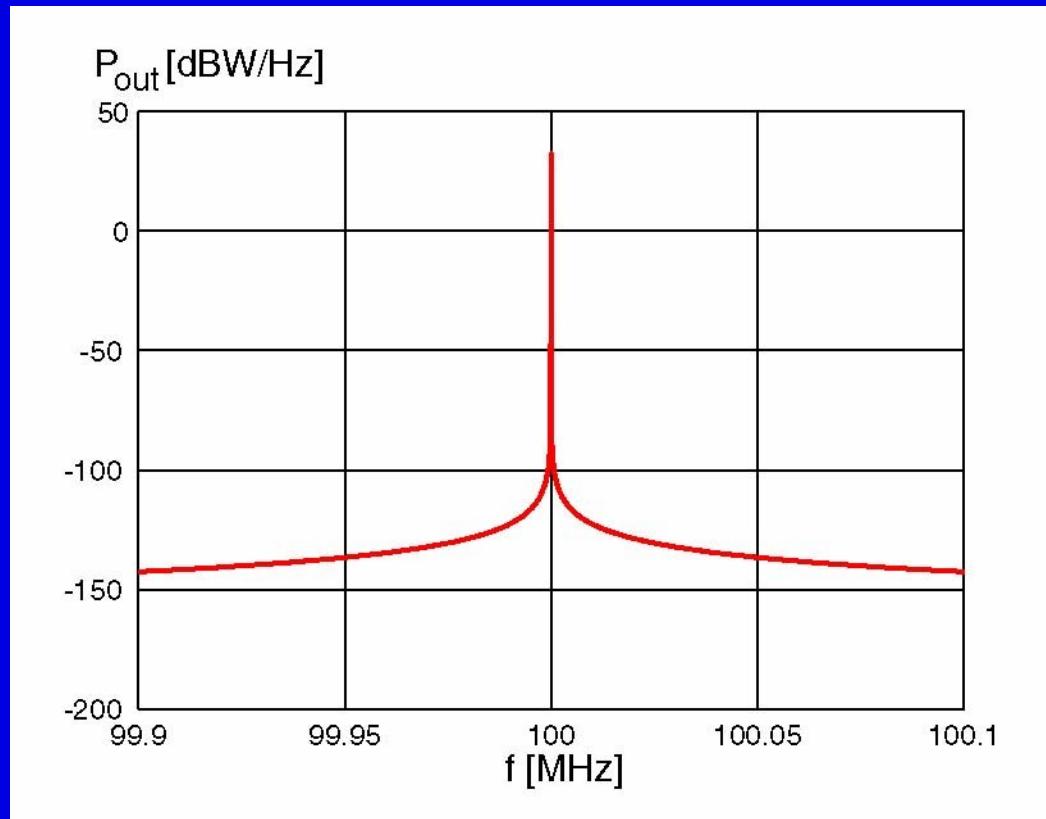

- The noise level increases close to the resonant frequency as

$$A_f = \frac{A}{1 - \beta A} \quad A_f \rightarrow \infty \text{ when } f \rightarrow f_0$$

Noise Model of the Oscillator

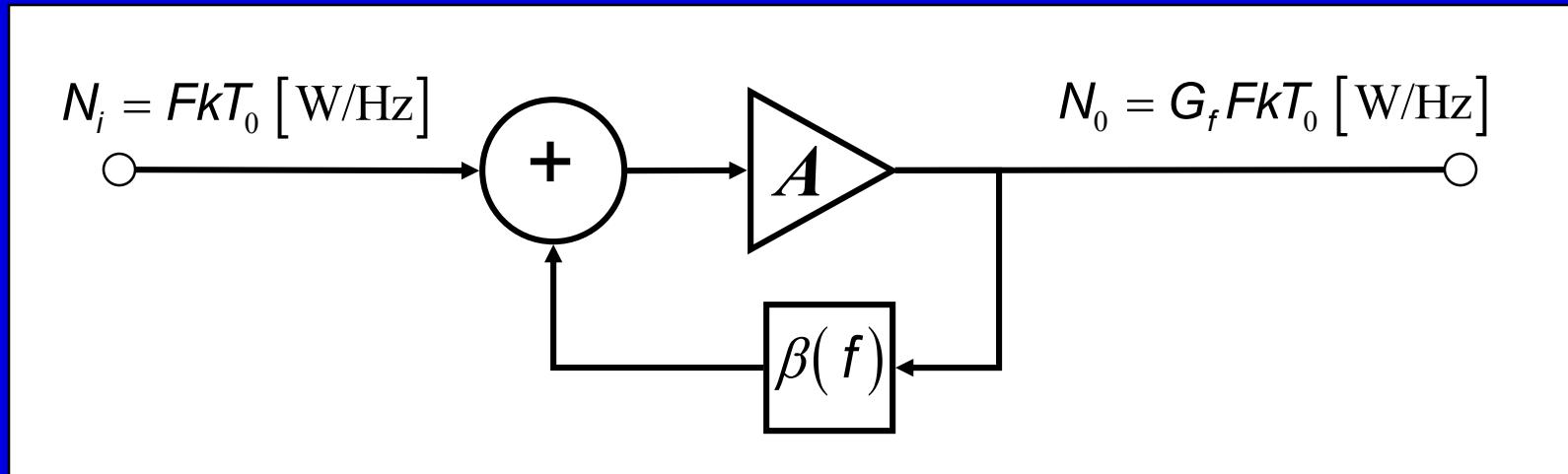


$$A_f(f) = \frac{A}{1 - \beta(f)A}$$

$$G_f = A_f^2$$

$$\beta(f) = \frac{\beta_0}{1 + jQ} \frac{2|f - f_0|}{f_0}$$

Noise Spectrum

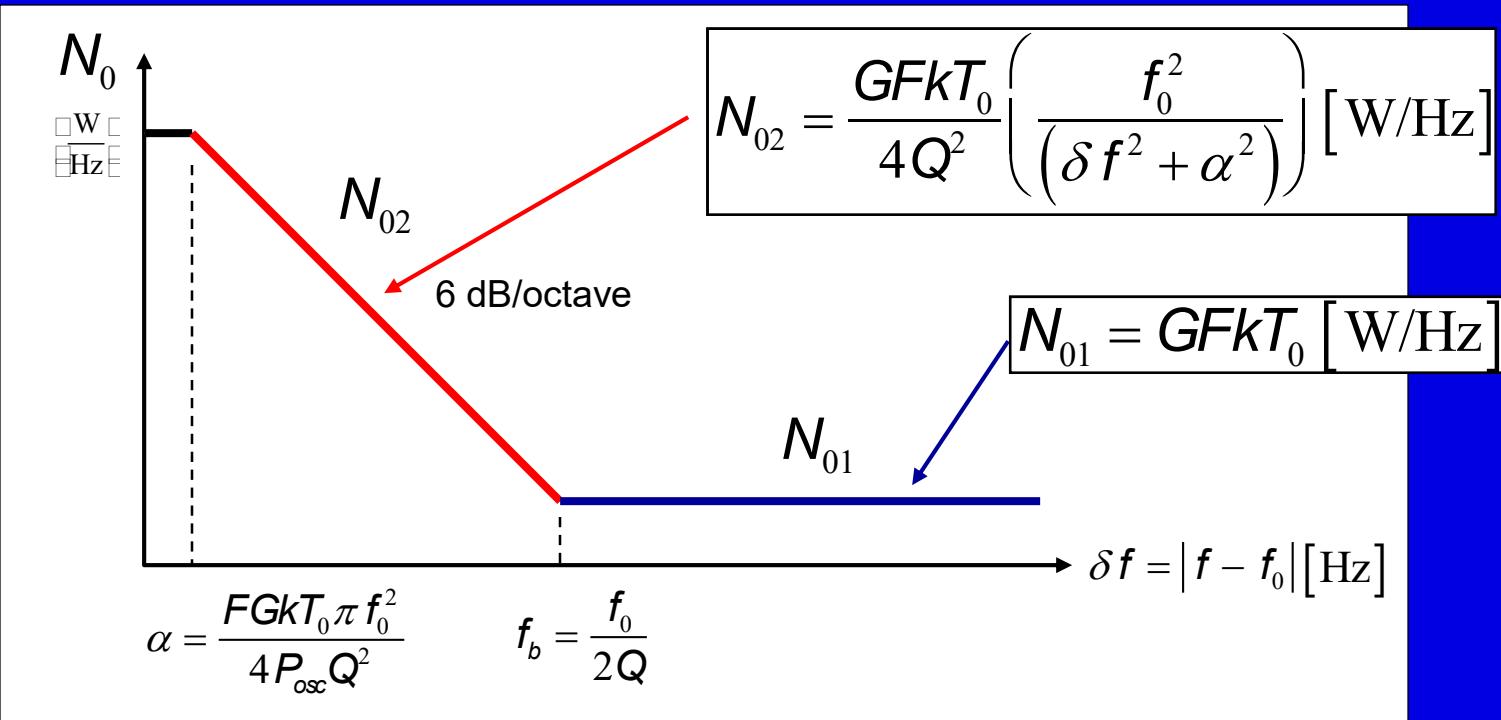


- To achieve low phase noise choose:
 - a high-Q resonant circuit
 - a low noise amplifier
 - as low gain as possible
 - high power level in the oscillator
- The noise consists of both amplitude and phase noise
 - if a limiter is used the amplitude noise will be suppressed and the total noise level is reduced by 3 dB

Negative Resistance Oscillators

Lab 4

Which transistor configuration is used?



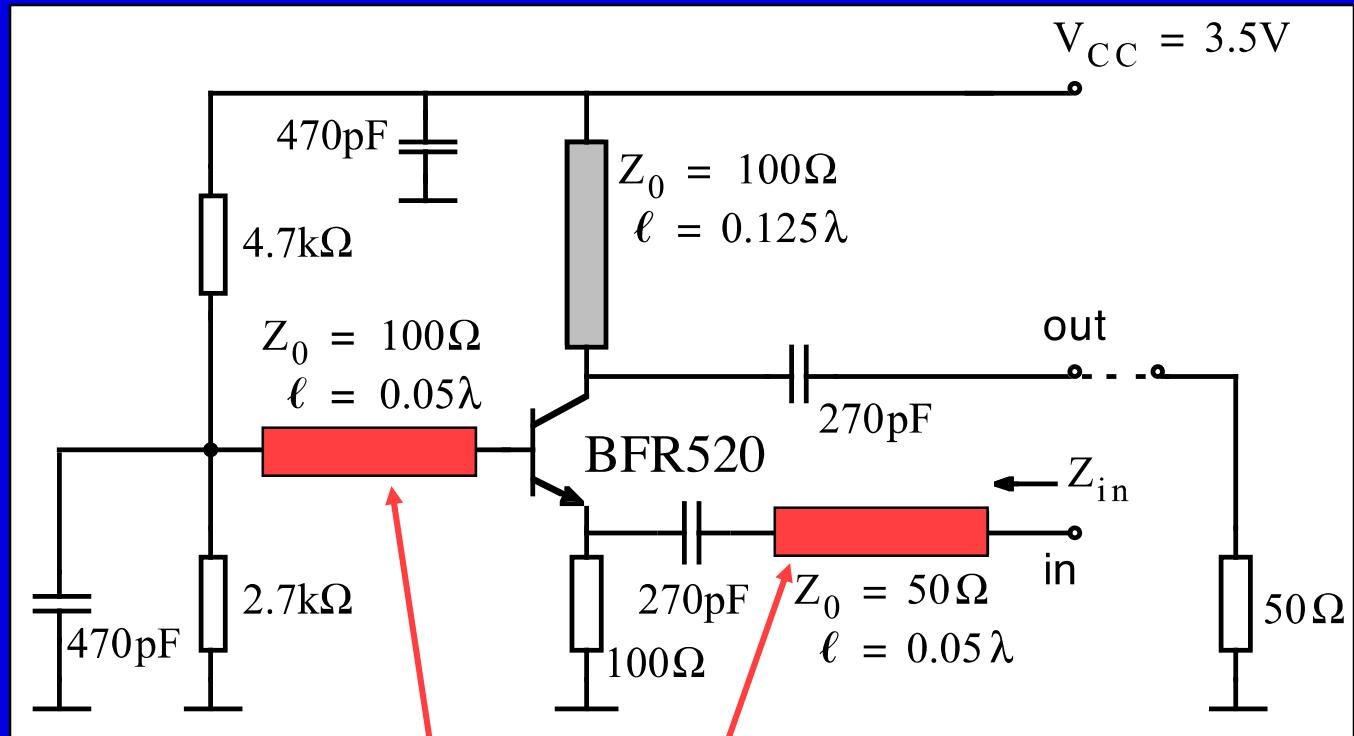


A serial inductor (a short-circuited stub) is inserted to the base to intentionally make the transistor unstable

A resonator (an open stub) is connected to the input to set the resonant frequency

Negative Resistance Oscillator

Lab 4

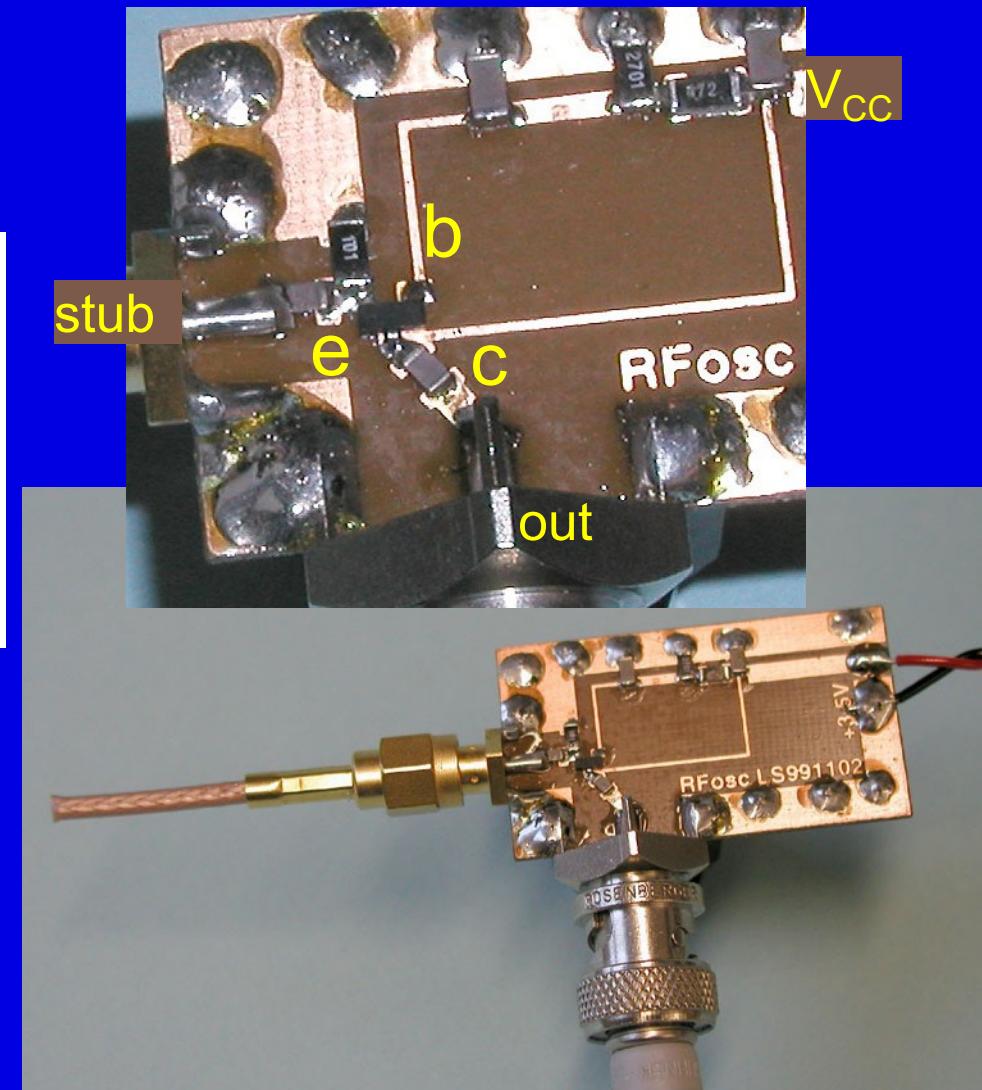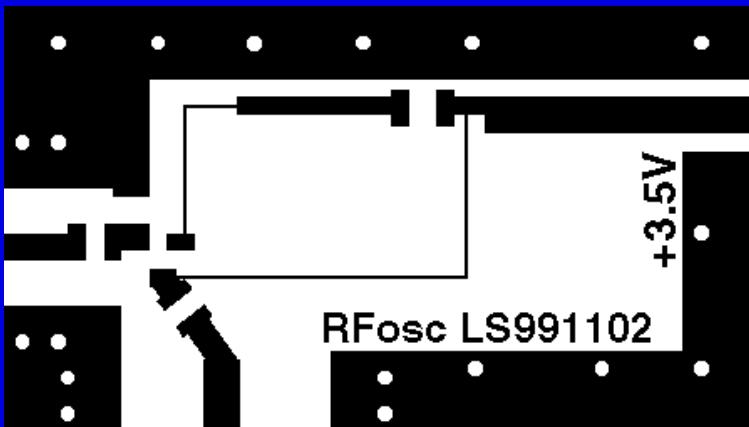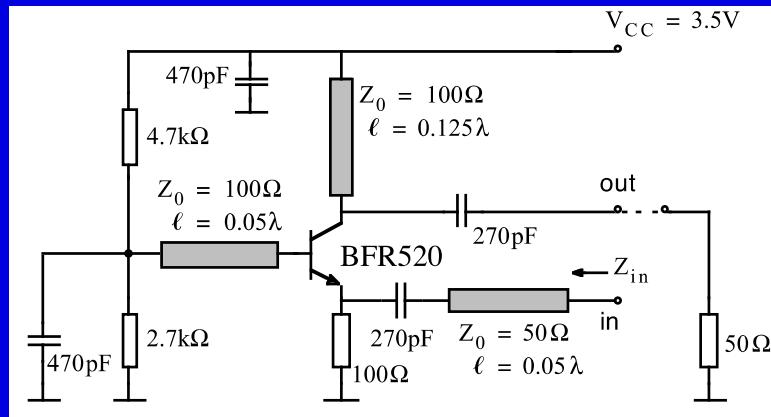

Conditions for Oscillation in a Two-Port

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12}S_{21}|} < 1$$

$$\Delta = S_{11}S_{22} - S_{21}S_{12}$$



$$\left. \begin{array}{l} \Gamma_{IN}\Gamma_S = 1 \\ \Gamma_{UT}\Gamma_L = 1 \end{array} \right\} \text{Express this in impedance!}$$

$$\Gamma_{IN}\Gamma_S = \frac{R_{IN} + jX_{IN} - Z_0}{R_{IN} + jX_{IN} + Z_0} \frac{R_S + jX_S - Z_0}{R_S + jX_S + Z_0} = 1$$



$$\begin{aligned} R_{IN} + R_S &= 0 \\ X_{IN} + X_S &= 0 \end{aligned}$$

Voltage Controlled Oscillator (VCO)


Clapp oscillator

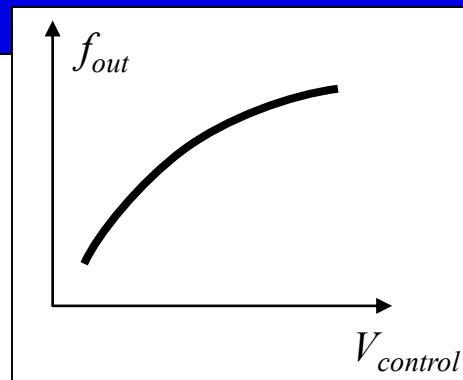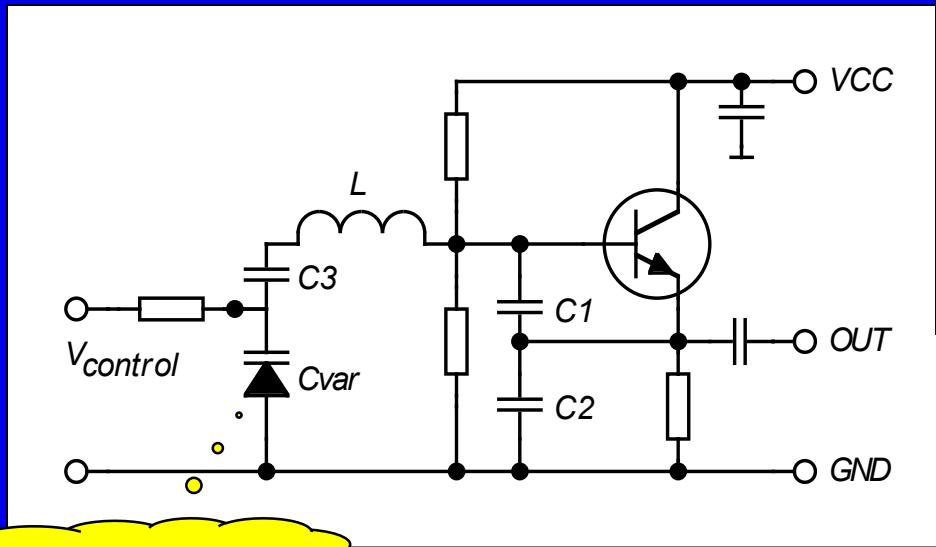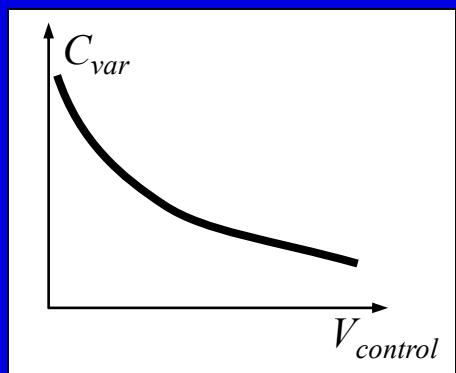

Varicap diode





Negative resistance oscillator


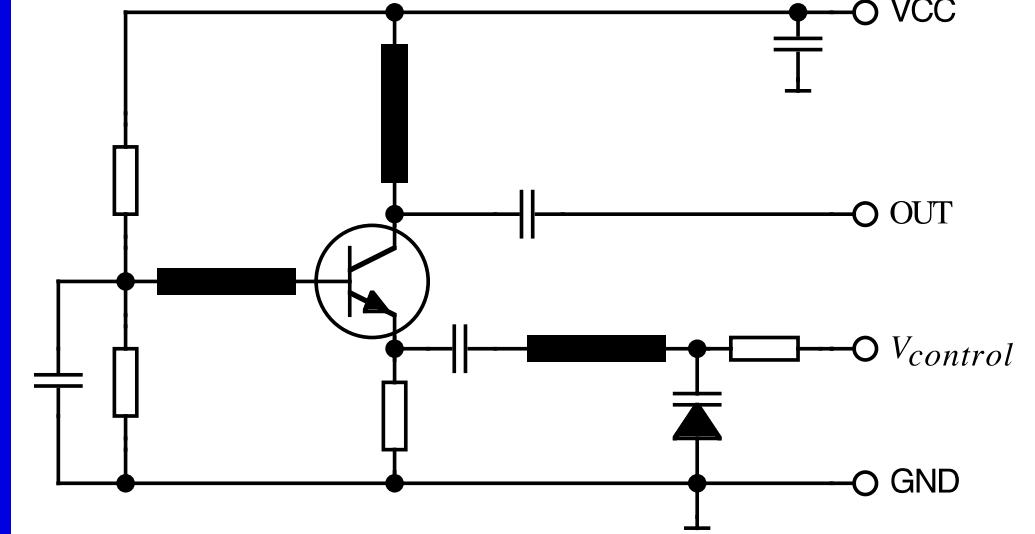


Varicap Diode

Forward bias

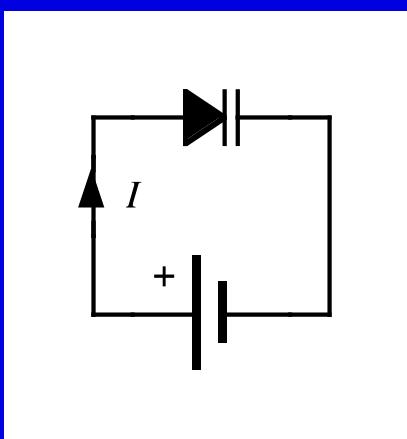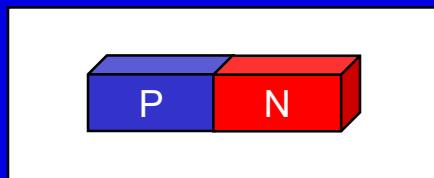


Reversed bias

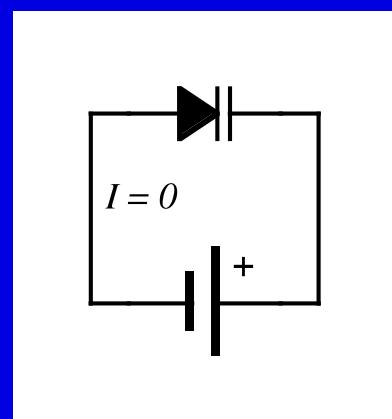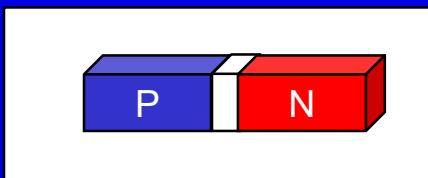

$$C_d(V_R) = \frac{C_j(0)}{1 + \frac{|V_R|}{V_j}^M}$$

Ex.: BB811

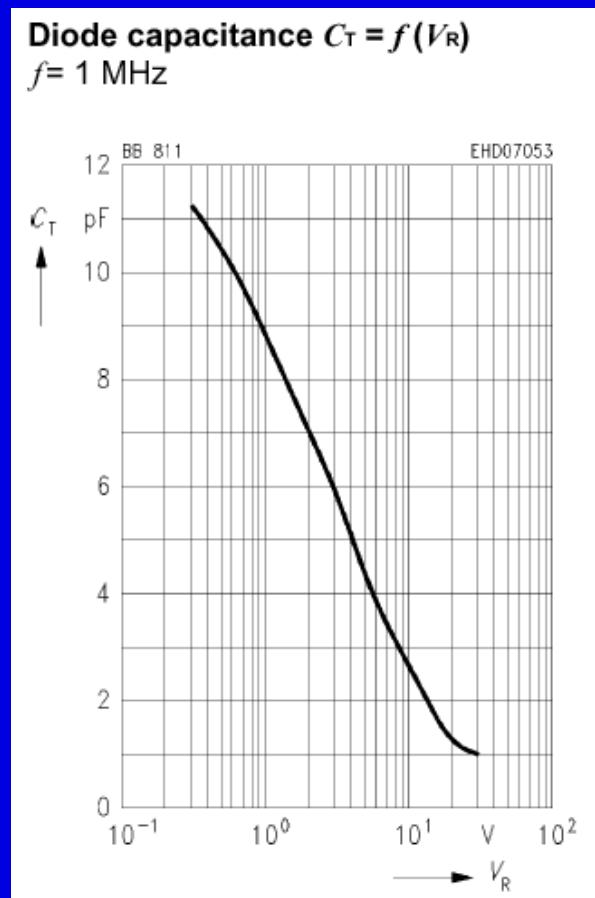


V_R = reverse voltage


Resonators

- In order to improve the Q-factor, instead of or as a compliment to the LC circuit, you may use:
 - Transmission line
 - microstrip resonator
 - coaxial resonator
 - Ceramic resonator
 - Quartz crystal


The Quartz Crystal (Xtal)

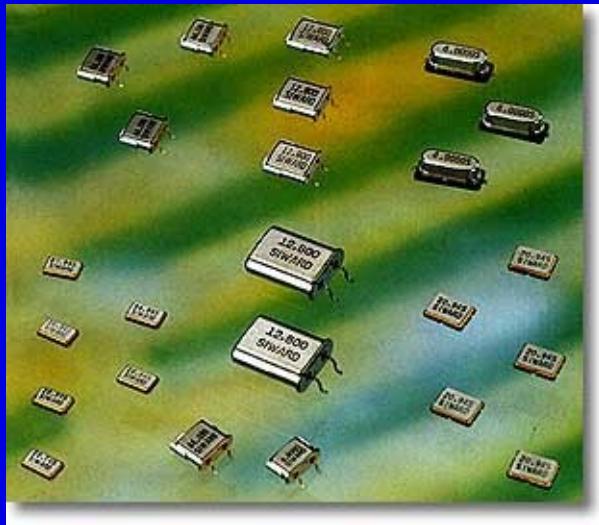

Symbol

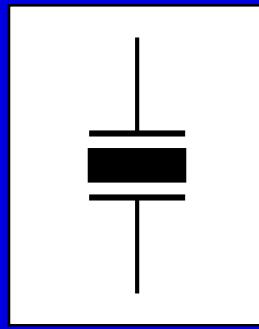

equivalent circuit
diagram

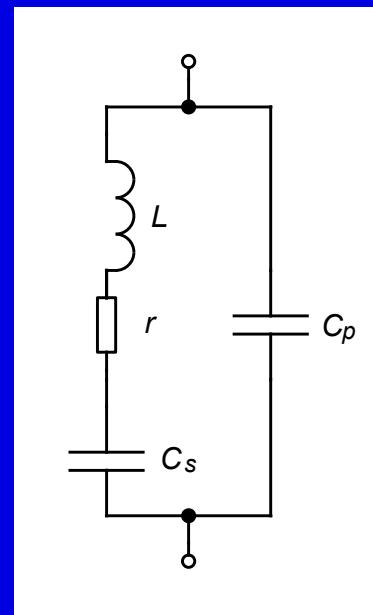



$$\begin{aligned}L &= 5 \text{ mH} \\C_p &\approx 10 \text{ pF} \\C_s &\approx 50 \text{ fF} \\r &< 3 \Omega\end{aligned}$$

Q □ 10^5




The Impedance of a Crystal

$$Z_{\text{Xtal}} [\Omega] = R + jX$$

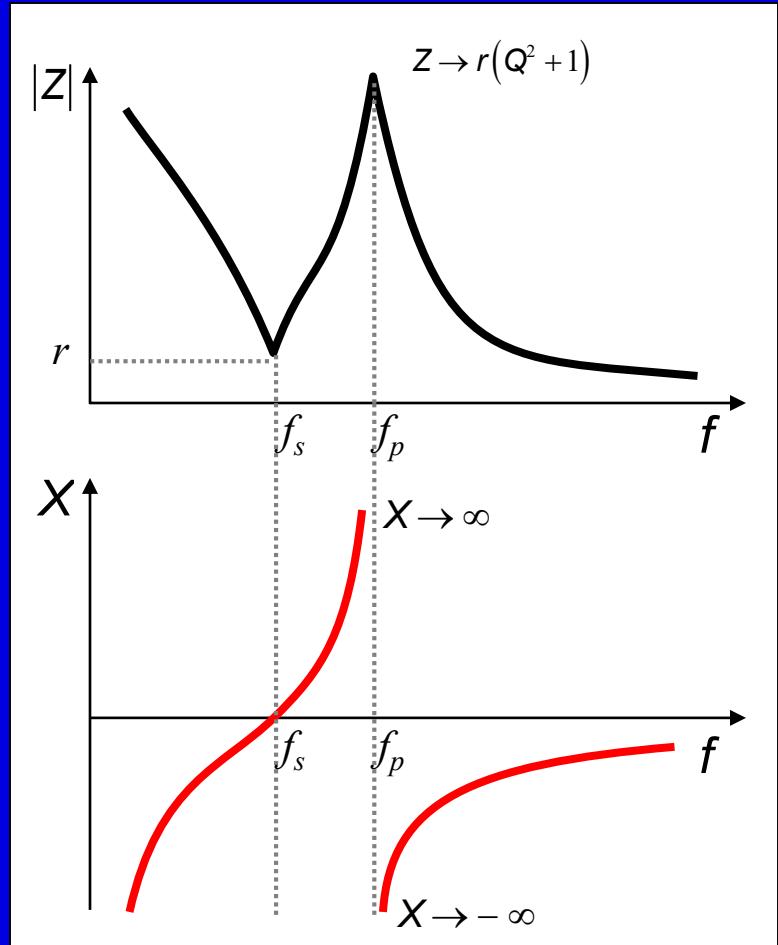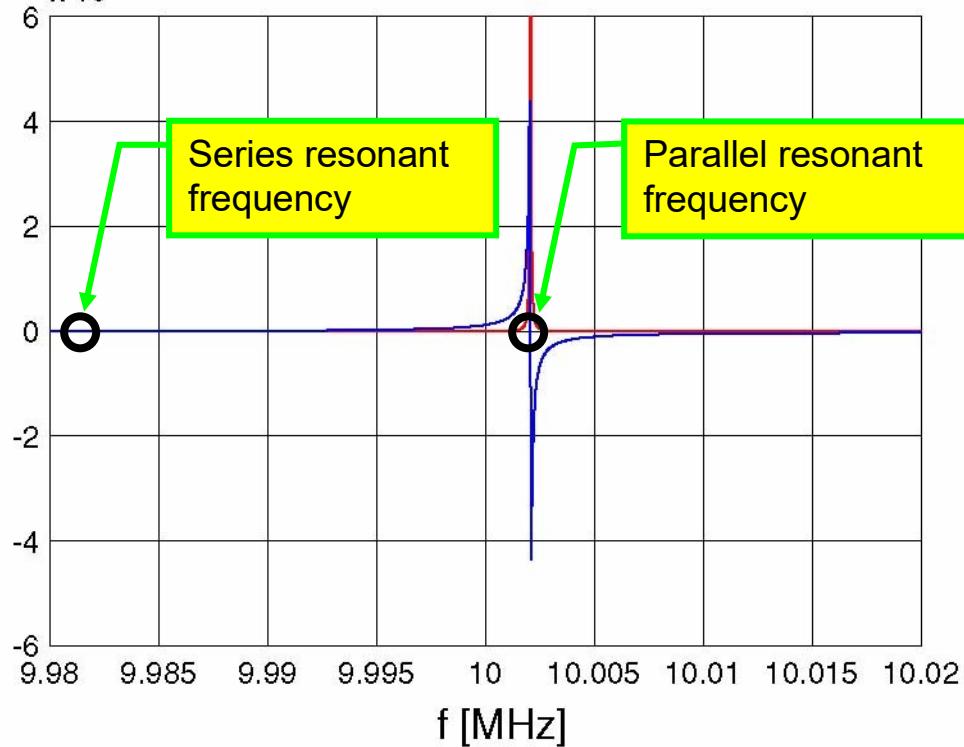


Crystal Oscillators


- circuit examples

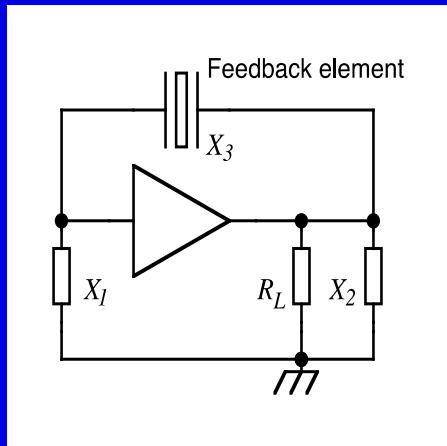


series resonance

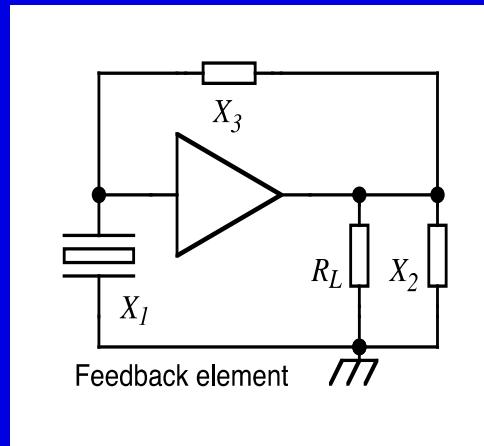


parallel resonance

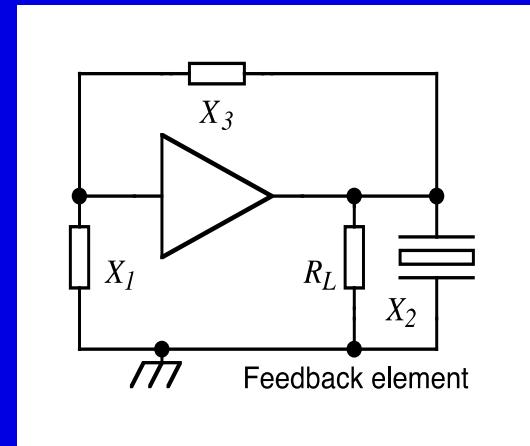

parallel resonance

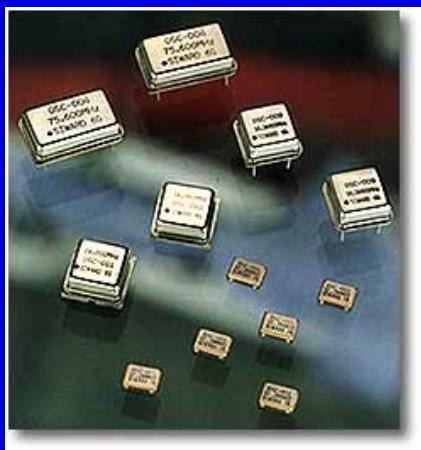

Pierce Crystal Oscillator

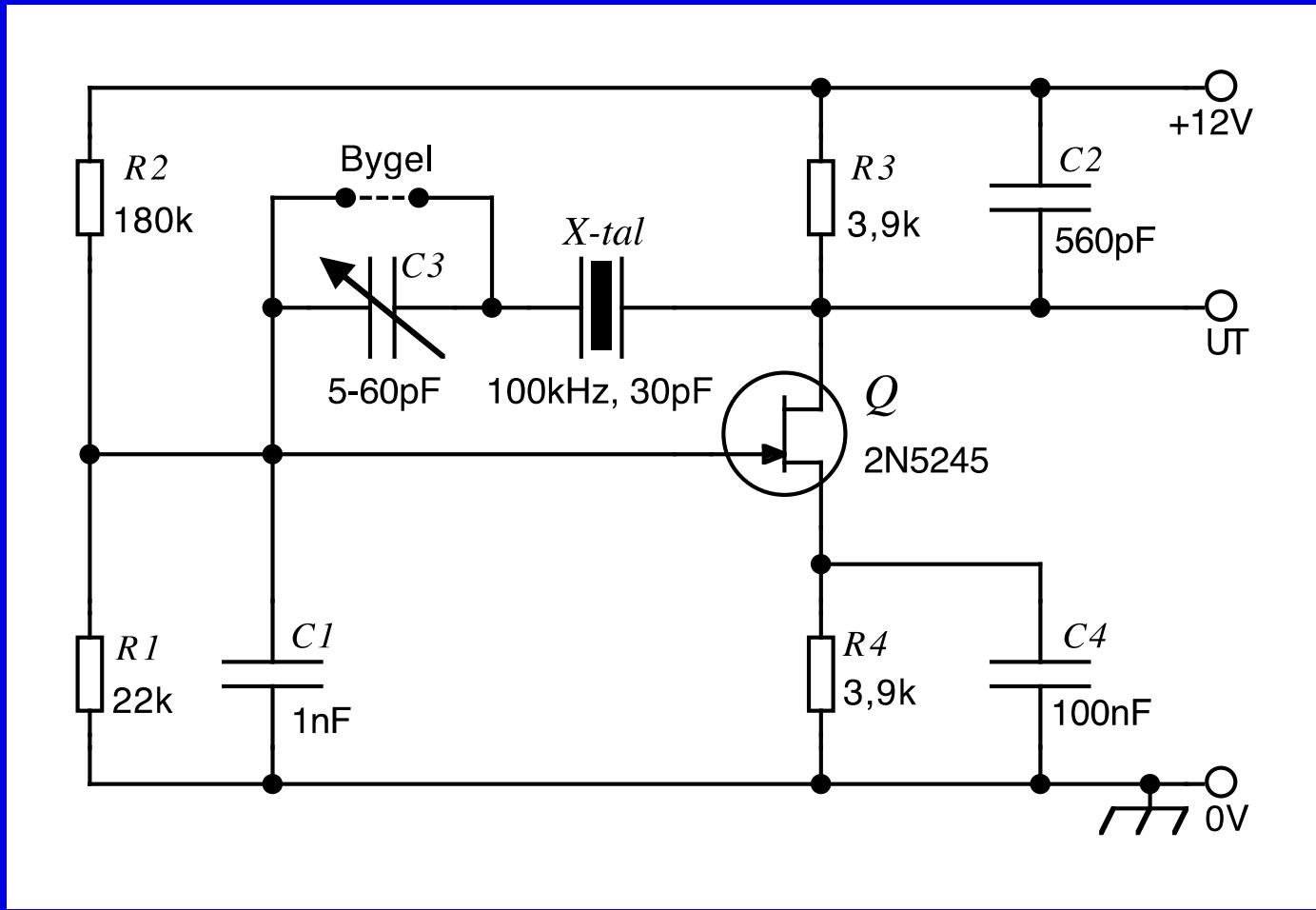

Compare with lab 4!

Some Good Practical Advice about Oscillator Design

- Generally:
 - select components of high quality
 - use buffer amplifier
 - use filtered and well stabilized supply voltage
 - apply good shielding
- For high frequency stability:
 - design the resonant circuit for high Q
 - use a ceramic resonator alternatively a quartz crystal
 - "pre-aging" of crystals
 - the oscillator may be enclosed in a temperature controlled oven
 - frequency control by temperature sensor and varicap diode
- Low phase noise:
 - design the resonant circuit for high Q
 - use low noise amplifier
 - use as low gain as possible
 - let the oscillator operate at a high power level