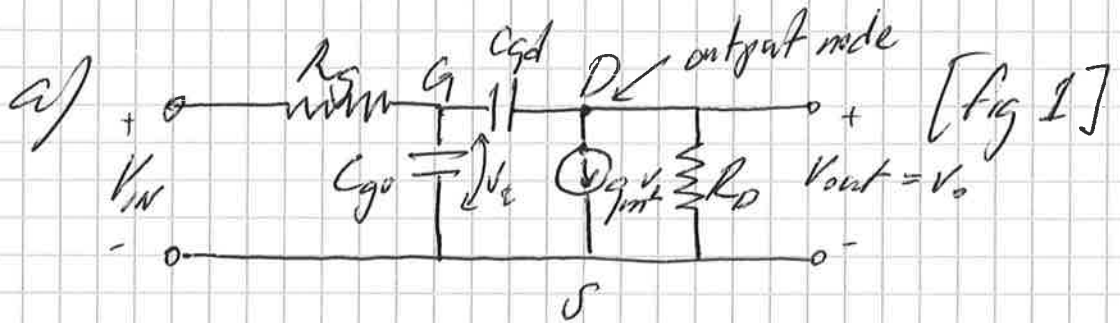


4.




$$b) A_v = \frac{v_o}{v_i} \text{ at low-} f \Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m R_D$$

$$C_M = C_{gd} (1 - A_v) = C_{gd} (1 + g_m R_D)$$

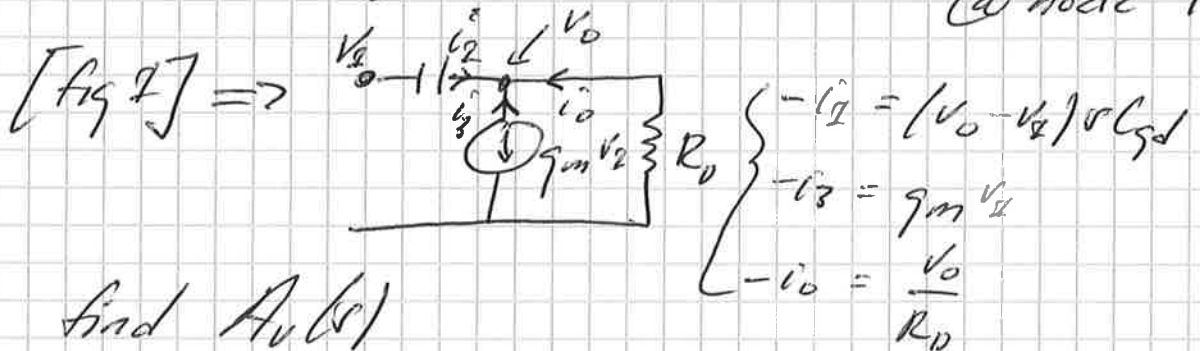c) see page 492 in book (analysis and design...)

$$\begin{cases} i_2 = (v_i - v_o) s C_{gd} & \text{(i)} \\ g_m v_i + \frac{v_o}{R_D} + (v_o - v_i) s C_{gd} = 0 & \text{(KCL @ output node) (ii)} \end{cases}$$



find $A_v(s)$

$$\text{from (ii)} \Rightarrow A_v(s) = -g_m R_D \left(\frac{1 - s \frac{C_{gd}}{g_m}}{1 + s R_D C_{gd}} \right)$$

$$\text{insert in (i)} \Rightarrow i_2 = (1 - A_v(s)) s C_{gd} v_i$$

$$= s C_M v_i \Rightarrow C_M = (1 - A_v(s)) C_{gd}$$


when approximating the parasitic the low freq. volt. amp. is used

$$A_v(s) = A_{v0} \Rightarrow C_M = (1 - A_{v0}) C_{gd}$$

Decoupling output from input by approximating current through C_{gd} .

(2016 exam)


4.

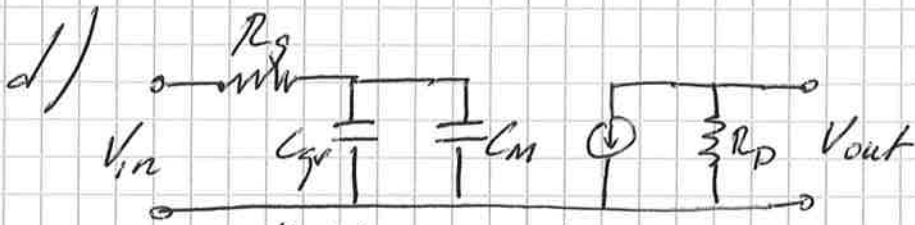

parallel capacitances are added

$$\Rightarrow C_{tot} = C_{gv} + C_m = C_{gv} + C_{gd}(1 + g_m R_p)$$

looking at the input;

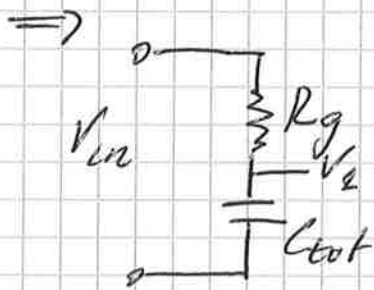

voltage div. $(s = j\omega)$

$$\Rightarrow V_x = \frac{1}{R_g + \frac{1}{sC_{tot}}} V_{in} = \frac{1}{1 + sR_g C_{tot}} V_{in}$$


$$H(s) = \frac{V_{out}}{V_{in}} = -g_m R_p = \frac{1}{1 + sR_g C_{tot}}$$

5.

$$g_m = \sqrt{2k' \frac{W}{L} I_D} = \sqrt{2 \cdot 60 \cdot 10^{-6} \cdot \frac{100}{2} \cdot 10^{-3}}$$

$$= 7,7 \cdot 10^{-3} \text{ A/V} \quad (\text{note } R_L = R_D)$$
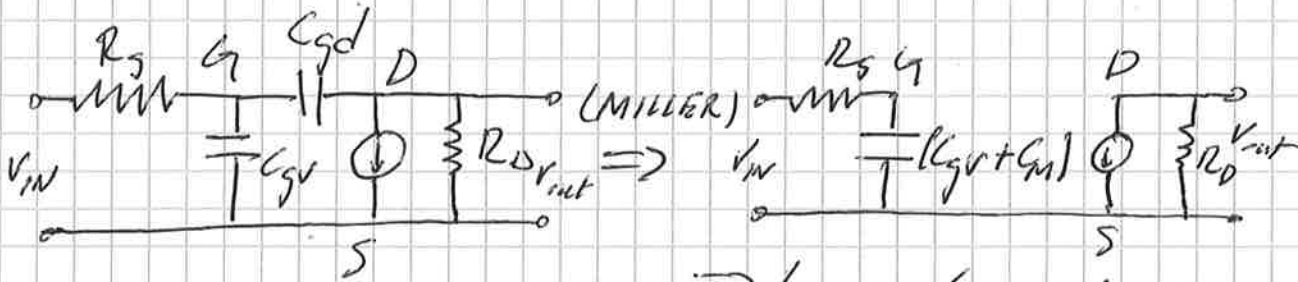
$$A_v = -g_m R_D = -7,7 \cdot 10^{-3} \cdot 5 \cdot 10^3 = -38,5$$



\Rightarrow decoupling of gate and drain with miller approximation

$$C_m = C_{gd}(2 - A_v)$$

$$|P_{\omega}| = \frac{1}{R_g(C_{gs} + C_{gd}(1 - A_v))}$$

$$= \frac{1}{10 \cdot 10^3 (30 \cdot 10^{-12} + 20 \cdot 10^{-12} \cdot 39,5)} = 1,2 \text{ Mrad/s}$$


$$f_{-3dB} = \frac{|P_{\omega}|}{2\pi} = 0,2 \text{ MHz}$$

2016 EXAM

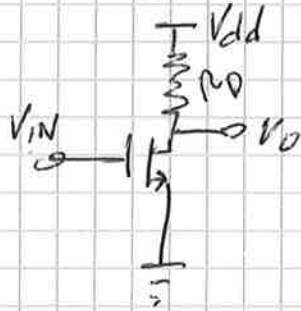6.

Common source


- gives rise to gain
- large input resistance
- load @ drain determines gain



- unilateral
→ output disconnected from input

Common gate

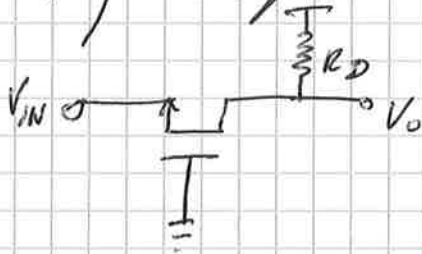
- "current buffer" $i_o = i_i$ (input = output)
- low input resistance
- high output resistance



- bilateral
output influences input


Common drain

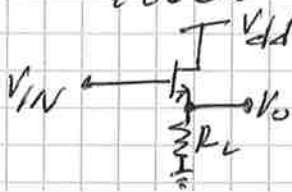- "voltage buffer" $A_V \leq 1$
- source follower
- low output resistance
⇒ works well for an output stage
- level shifter ⇒ offsets the voltage



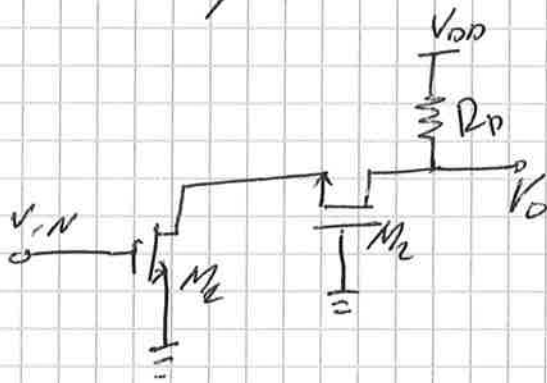b. Cascode (CS-CG) p. 207

- two stage amplifier
- increased output resistance
⇒ common gate at output
- gain set by a first stage CS transistor
- good high frequency properties
- high input resistance and
output resistance ⇒ increased



by a factor
gain of
the second
stage