

F8 – Building Blocks of Integrated Circuit Amplifiers

Outline

- Integrated circuit (IC) design
- Current mirrors, steering circuits, sources, sinks
- Intrinsic gain cell
- Common source (CS) amplifier w/ output resistance
- CS amplifier w/ active load
- Common gate (GS) amplifier w/ output resistance
- CS-CG Compound Device: Cascode amplifier
- Common drain (CD) amplifier w/ output resistance

Reading Guide

Sedra/Smith 7ed int

- Chapter 7.1-7.5


Problems

Sedra/Smith 7ed int

- P7.7, 7.20(a), 7.26, 7.51, 7.64

Integrated Circuits (ICs) and Components

- Area = \$\$\$
 - Performance vs. integration density tradeoff
 - Avoid large components if possible
- Complementary MOS (CMOS) technology
 - Best cost per transistor if mass produced in very-large-scale ICs (VLSI) technology
 - Low-power digital logic ($V_{DD} < 1\text{ V}$ in scaled CMOS) + decent analogue circuits = very versatile!
- BJT technology
 - Very useful, but mainly for special applications
- Historically, IC size scaling improved performance

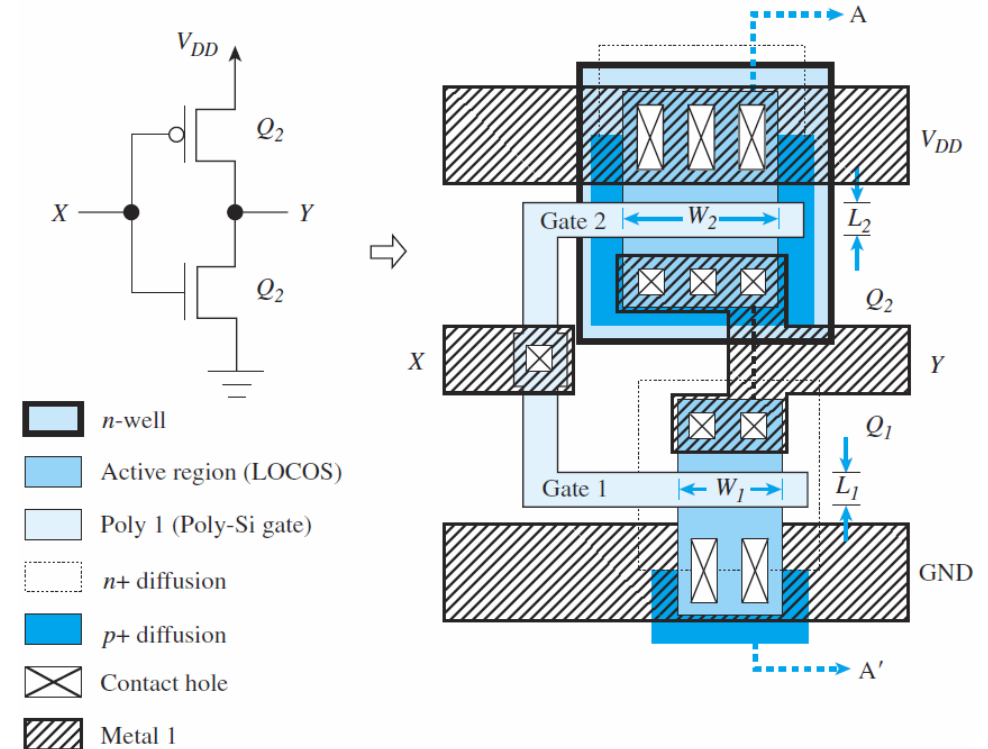

IC design provides good device uniformity, as compared to discrete devices.


MOSFET Current Mirror

- Resistance to supply provides reference current
- Reference (input) branch
 - Diode connected (G bound to D) CS device Q1, $V_{DS1} = V_{GS1} > V_{OV1}$, enforces saturation

$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_1 (V_{GS} - V_{tn})^2 = I_{REF} - 0 = \frac{V_{DD} - V_{GS}}{R}$$

- Source (output) branch
 - CS device Q2 shares S and G with Q1, in saturation if $V_{DS2} > V_{OV1}$

 
$$I_{D2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_2 (V_{GS} - V_{tn})^2 = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$



Current mirrors only make sense in IC technology, where variability is low.

MOSFET Current Mirror w/ Output Resistance

 - Work on board, also available in lecture notes...




MOSFET Current Mirror w/ Output Resistance

- Output resistance yields dependence on output voltage

$$R_O = \frac{\partial V_O}{\partial I_O} = r_{o2} = \frac{1}{\lambda_2 I_{D2}}$$


- Exact transfer requires equivalent voltages on all terminals of Q1 and Q2
 
$$I_O = \frac{(W/L)_2}{(W/L)_1} I_{REF} (1 + \lambda_2 [V_O - V_{GS}])$$





Current Steering Circuit

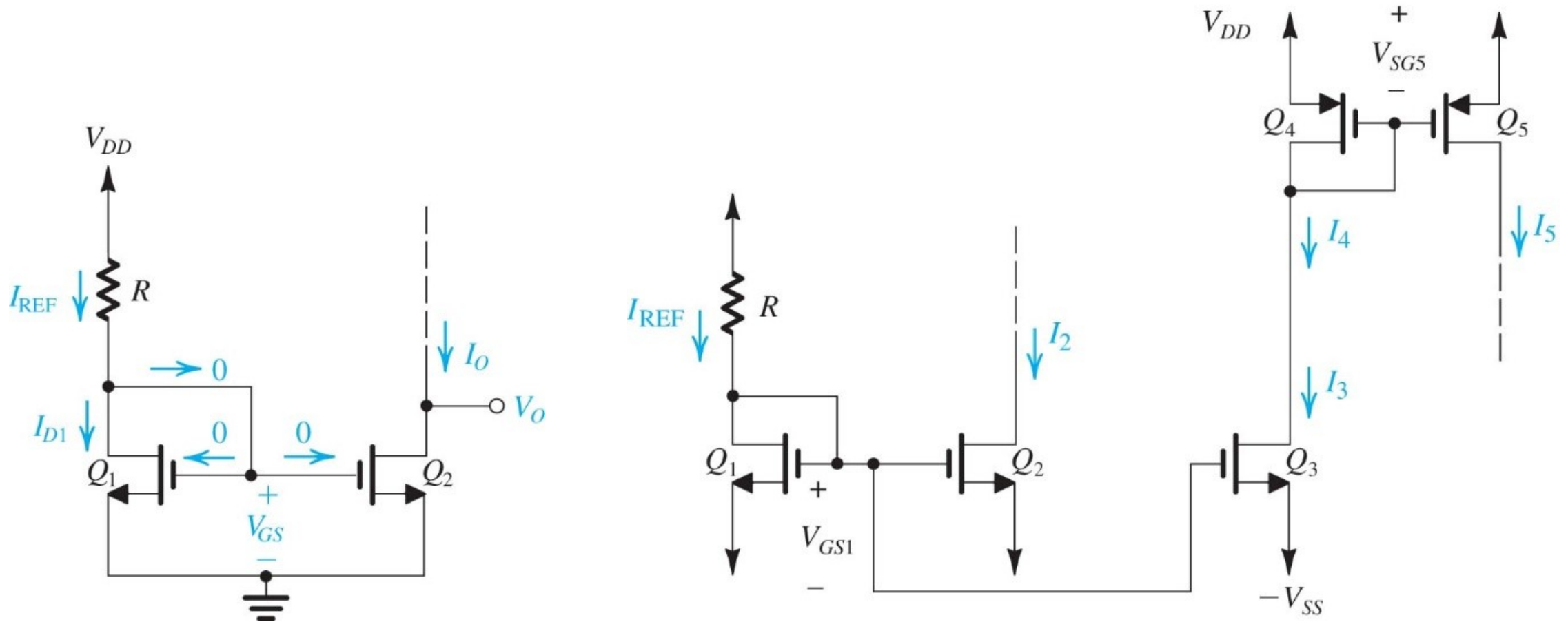- One reference path can control several current sources/ sinks



(Current Source vs Current Sink)

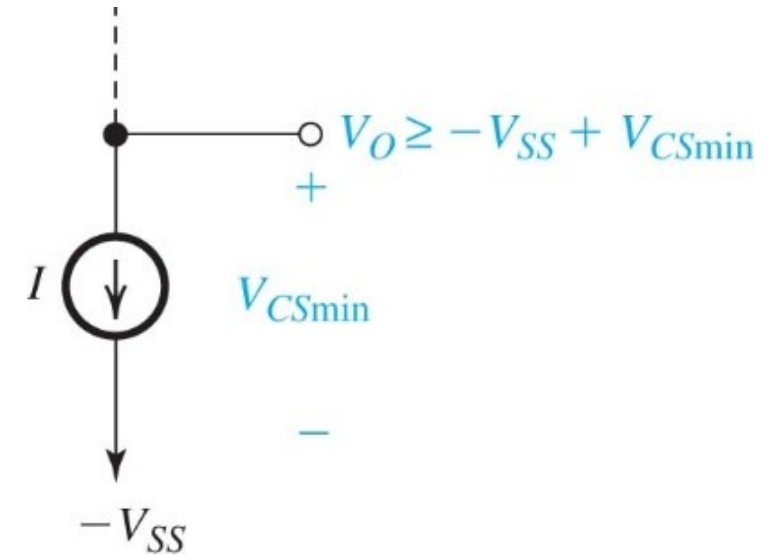
 
- Current source
 - Extracts current from supply
- Current sink
 - Injects current into ground



This is a matter of definition.

BJT Current Mirror

  
- BJT current mirror similar to MOSFET, but scaling w.r.t. BE junction area
- Base current loss may be compensated by additional BJT



Advanced current mirror circuits can suppress the BJT base current error.

MOSFET Current Mirror: Small Signal Operation

 - Work on board, also available in lecture notes...




MOSFET Current Mirror: Small Signal Operation

- Excellent linearity
 - Small signal current gain and bias current ratio virtually equal


- $R_i = \frac{v_i}{i_i} = r_{o1} \parallel \frac{1}{g_{m1}} \approx \frac{1}{g_{m1}}$

- $R_o = \left. \frac{v_o}{i_o} \right|_{i_{sig}=0} = r_{o2}$

- $A_{is} = \left. \frac{i_o}{i_i} \right|_{R_L=0} = g_{m2} \left(r_{o1} \parallel \frac{1}{g_{m1}} \right) \approx \frac{g_{m2}}{g_{m1}} = \frac{(W/L)_2}{(W/L)_1} = \frac{I_O}{I_{REF}}$

 
 
$$g_m = k'_n \left(\frac{W}{L} \right) V_{OV}$$





The Basic Gain Cell: CS Amplifier w/ Active Load

- CS amplifier with current source load
 - Load is an active component
 - Small signal analysis, $I = 0$, i.e. open circuit
 - Intrinsic SC stage gain, $A_0 = g_m r_o$

$$A_0 \gg 1 \Leftrightarrow \frac{1}{g_m} \ll r_o$$

- $R_i = \frac{v_i}{i_i} = \infty$
- $R_o = \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} = r_o$
- $A_{vo} = A_v|_{R_L=\infty} = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -g_m r_o = -A_0$
- $A_v = -g_m r_o = A_{vo} = A_0$

  

Intrinsic Gain

- MOSFET

- Intrinsic can be designed to vary among different devices
 - Tradeoff: gain vs. BW

$$A_0 = g_m r_o \approx \frac{2}{\lambda V_{OV}} = \frac{2L}{\lambda' V_{OV}} = \frac{1}{\lambda'} \sqrt{2k'_n WL/I_D}$$

$$g_m = k'_n \left(\frac{W}{L}\right) V_{OV} = \sqrt{2k'_n \left(\frac{W}{L}\right) I_D} = \frac{2I_D}{V_{OV}}$$
$$r_o = \frac{1}{\lambda I'_D} = \frac{L}{\lambda' I'_D} = \frac{V'_A L}{I'_D} = \frac{V_A}{I'_D}$$

- BJT

- Intrinsic gain is a technology constant


$$A_0 = g_m r_o \approx \frac{V_A}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$
$$r_o = \frac{V_A}{I'_C}$$
$$A_0 \gg 1 \Leftrightarrow \frac{1}{g_m} \ll r_o$$

Intrinsic gain is magnitude of open circuit voltage gain of the basic CS(/ CE) amplifier.

Active Load w/ Output Resistance

 - Work on board, also available in lecture notes...







Active Load w/ Output Resistance

- CS amplifier with active load w/ output conductance
 - Small signal analysis, $I = 0$, i.e. open circuit
 - CG presents load similar to CS output conductance

- $R_i = \frac{v_i}{i_i} = \infty$


- $R_o = \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} = r_{o1} || r_{o2} \approx \frac{r_o}{2}$

    - $A_{vo} = \frac{-g_m r_o}{2} = -\frac{A_0}{2}$




Output resistance of active load reduces the gain.

BREAK

 

Increasing the Gain of the Basic Cell

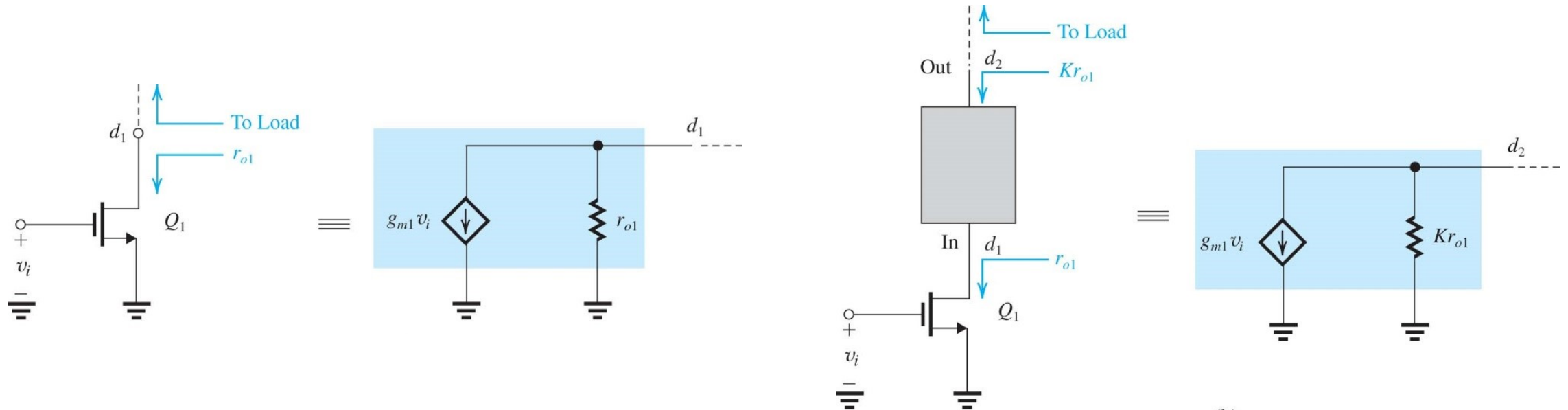
- Need to insert a circuit, between output and load, that...
 - Transfers current unchanged
 - Increases output resistance



What transfers current unchanged and increases output conductance?



Think, think, think.

 

Common Gate (CG) Amplifier as a Current Buffer (recap)

- Low input resistance, moderate output resistance


- $R_i = \frac{v_i}{i_i} = \frac{1}{g_m}$

- $R_o = \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} = R_D$

- $A_{vo} = A_v |_{R_L=\infty} = g_m R_D$

- $A_v = A_{vo} \frac{R_L}{R_L + R_o} = g_m (R_D || R_L)$

- $G_v = \frac{R_i}{R_i + R_{sig}} A_v = \frac{R_D || R_L}{R_{sig} + 1/g_m} < A_v$

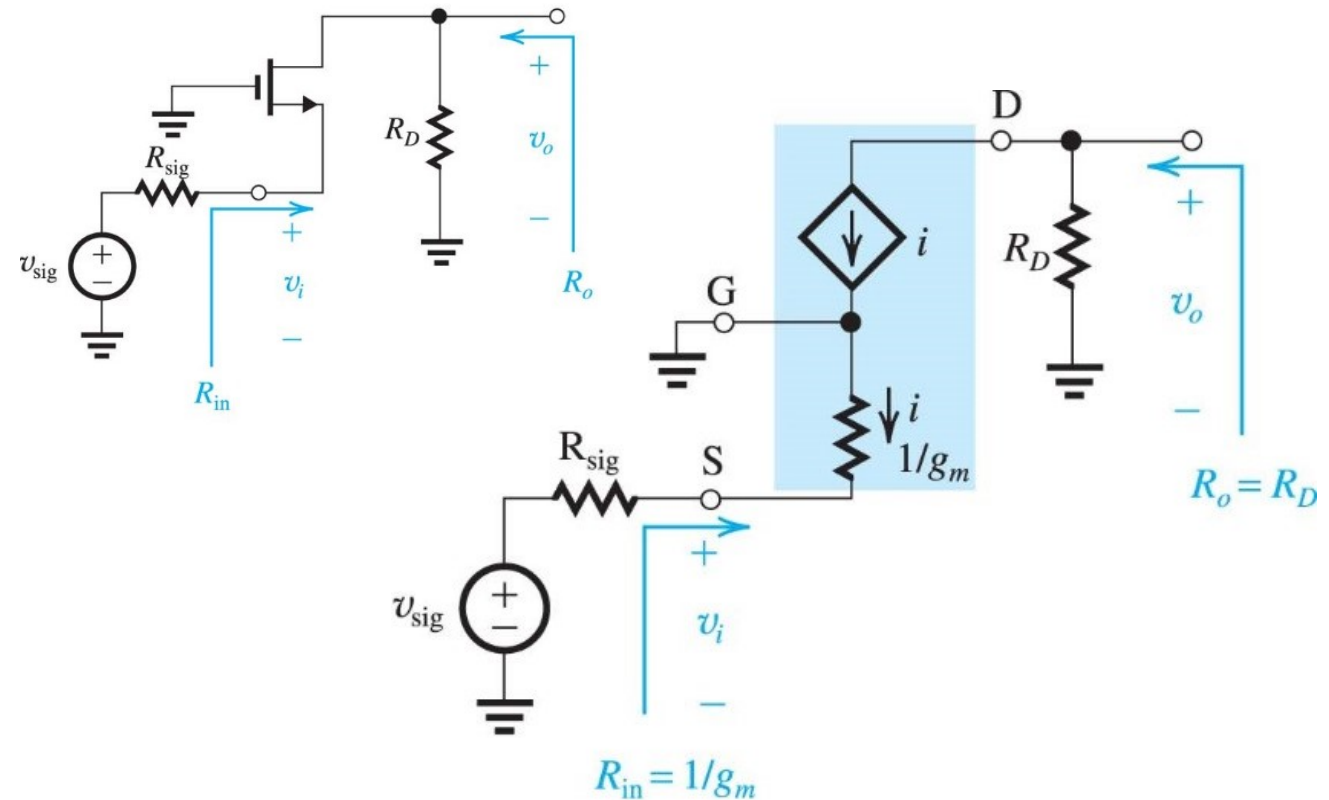

Transistor output resistance would somewhat complicate analysis.

CG Amplifier w/ Output Resistance

- Low input resistance, moderate output resistance
 - Buffers current even w/ output resistance (of device), but output/ input resistance depend on source/ load

$$R_i = \frac{v_i}{i_i} = \frac{r_o + R_L}{1 + g_m r_o} \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$


$$R_o = \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} = r_o + R_s + g_m r_o R_s \approx r_o + g_m r_o R_s$$

$$A_{vo} = A_v |_{R_L=\infty} = g_m R_o \approx g_m^2 r_o R_s$$

$$A_v = g_m (R_o || R_L)$$


$$g_{mb} = \chi g_m$$

$$\frac{1}{g_m} \ll r_o$$

 


CG Amplifier w/ Output Resistance: Output Resistance

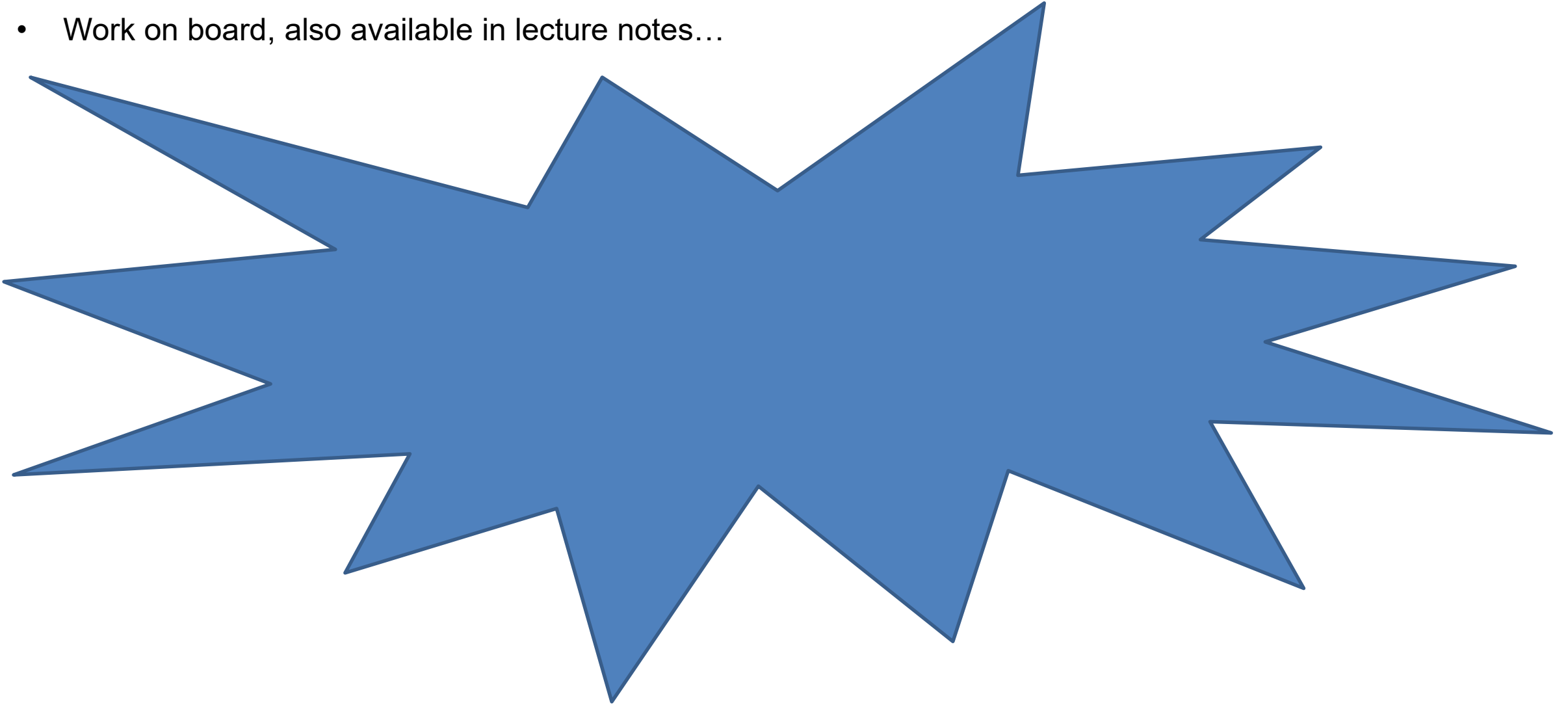- Work on board, also available in lecture notes...




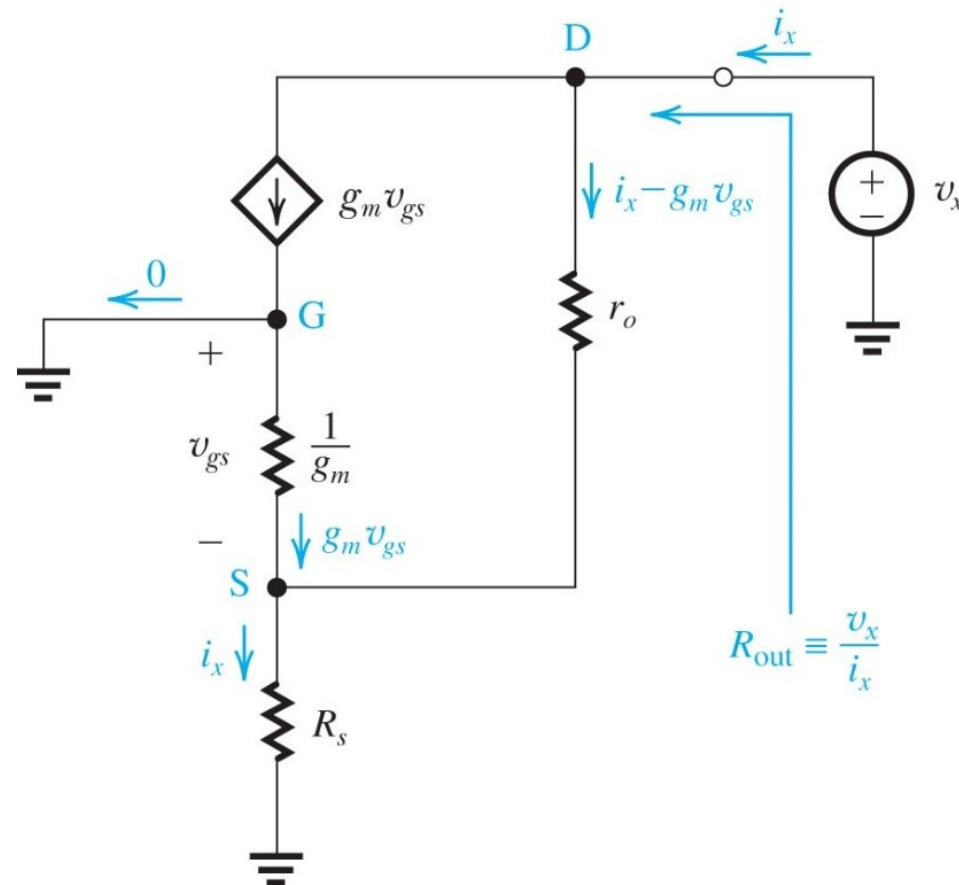CG Amplifier w/ Output Resistance: Output Resistance




CG Amplifier w/ Output Resistance: Input Resistance

 - Work on board, also available in lecture notes...



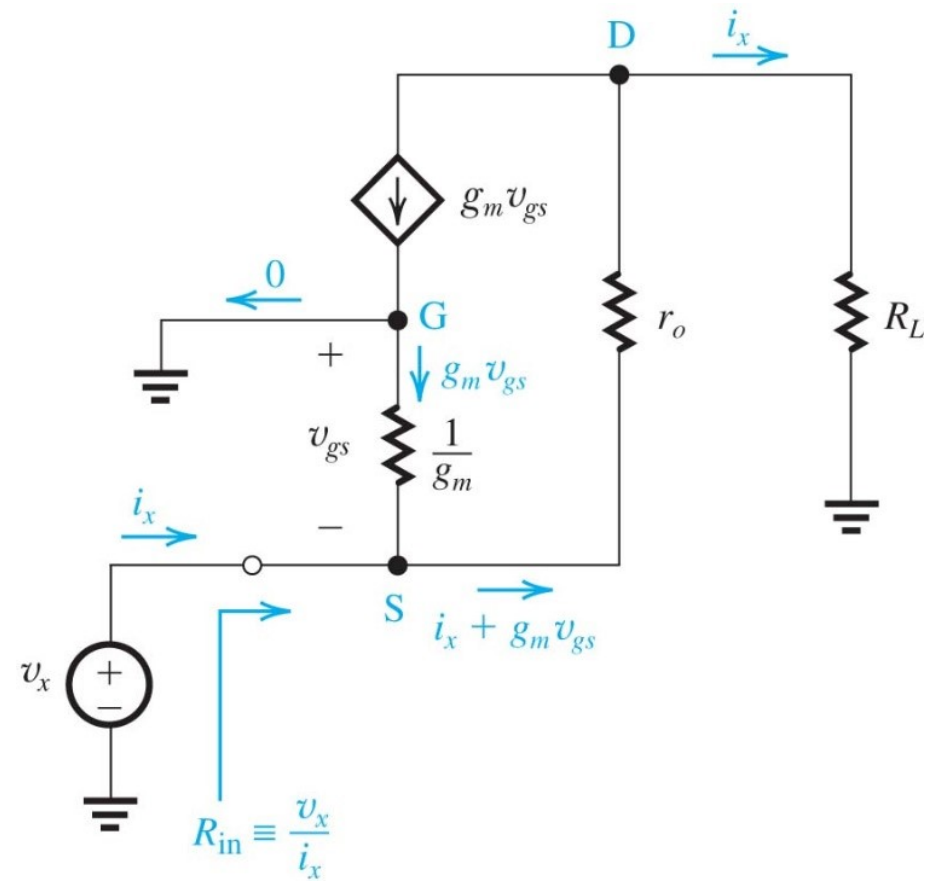CG Amplifier w/ Output Resistance: Input Resistance



CG Output/ Input Resistance: Source/ Load Transformations

- CG w/ vs w/o output resistance

- Input

- Value w/o plus reduced load


$$R_i = \frac{r_o + R_L}{1 + g_m r_o} \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o} = \frac{1}{g_m} + \frac{R_L}{A_0}$$

- Output

- Value w/o plus increased source

$$R_o = r_o + R_s + g_m r_o R_s \approx r_o + g_m r_o R_s = r_o + A_0 R_s$$
 
$$g_{mb} = \chi g_m$$
$$\frac{1}{g_m} \ll r_o$$



Output/ input resistance w/o r_o plus scaled up/ down source/ load resistance.


(CG Body Effect)

- Body transconductance g_{mb}
 - An additional gate

$$g_{mb} = \chi g_m$$
$$0.1 < \chi < 0.2$$

- Buffer CG stage
 - Source not on ground potential, but gate is
 - Body also on ground
 - Body effect acts in parallel to main gate

$$g'_m = (1 + \chi)g_m \approx g_m$$

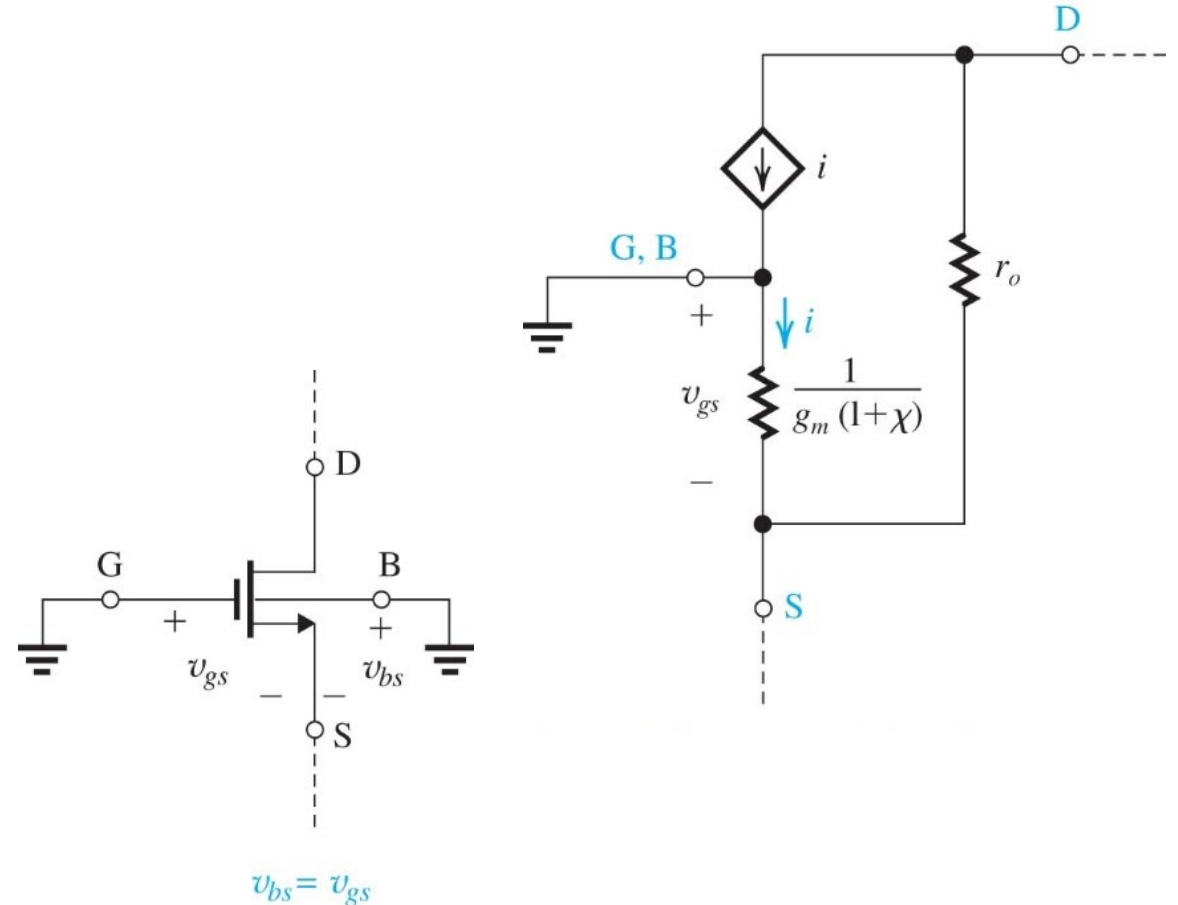


We neglect the body effect, once again, as it has small (positive) impact.

CS-CG Compound Device: Cascode Amplifier

- CS gain input stage
 - Loaded by buffer
- CG current buffer output stage
 - Increases output resistance


- $R_i = \frac{v_i}{i_i} \approx \frac{R_L}{g_{m1}r_{o2}}$
- $R_o = \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} = Kr_{o1} \approx (g_{m2}r_{o2})r_{o1}$
- $A_{vo} = A_v|_{R_L=\infty} = g_{m1}R_o \approx g_{m1}(g_{m2}r_{o2})r_{o1}$
- $A_v = g_{m1}(R_o || R_L)$

 

Cascaded cathode, cf. vacuum tube technology.

Cascode w/ Active Load

 - Work on board, also available in lecture notes...






Cascode w/ Active Load

- Ideal active load
 - Cascode output resistance preserved

$$A_v \approx g_{m1}(g_{m2}r_{o2})r_{o1}$$

- Real active load
 - Implemented with a PMOS w/ output resistance
 - Gain lowered approximately to intrinsic gain

$$A_v = g_{m1}(R_o || R_L) \approx g_{m1}r_{o3}$$

  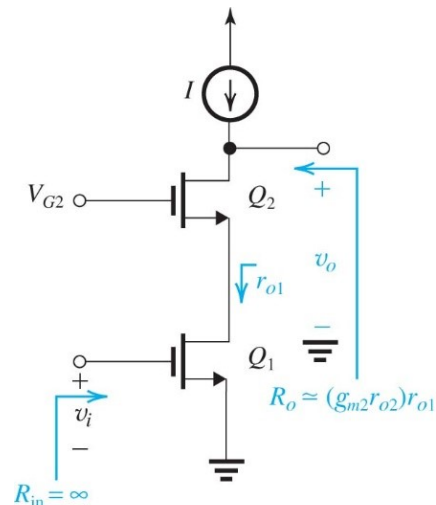


Output resistance ruins the gain boost, but active load improves BW.

Cascode w/ Cascode Active Load

 
- Problem
 - Output resistance of active load reduces cascode gain

- Solution
 - Cascode the active load to increase its output resistance

$$A_v \approx \frac{g_{m1}(g_{m2}r_{o2})r_{o1}}{2}$$




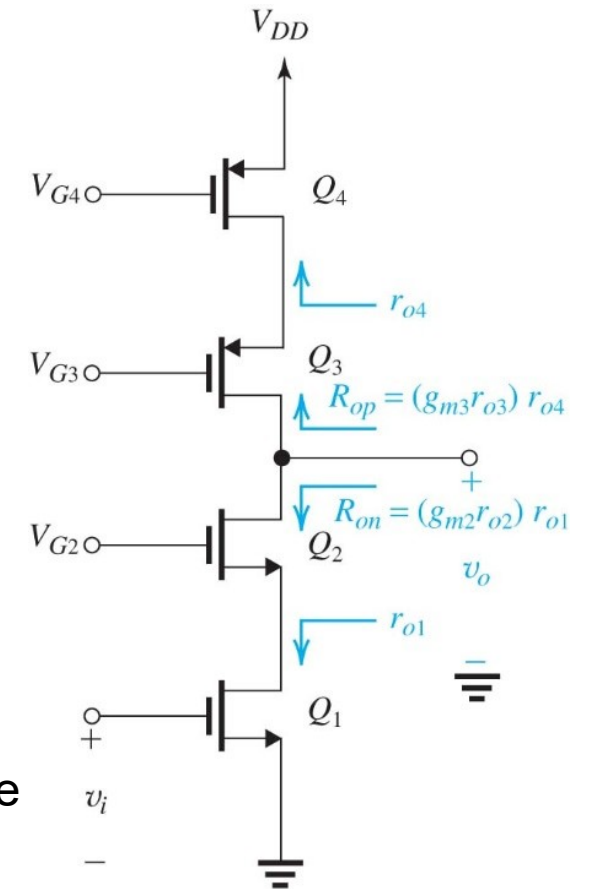- Problems remain
 - Current source resistance higher, but still similar to cascode output resistance
 - Very high supply voltage required (four stacked saturation conditions)



Folded, Instead of Telescopic, Cascode

 - CS gain NMOS input stage
- CG current buffer PMOS output stage



Popular CMOS stage that limits the required drive voltage.

CD w/ Output Resistance



- CD is useful as input stage
 - High input impedance
 - Output resistance and body effect shunt to ground

$$R_i = \frac{v_i}{i_i} = \infty$$

$$R_o = \left. \frac{v_o}{i_o} \right|_{v_{sig}=0} = \frac{1}{g_m} \parallel r_{o1} \parallel \frac{1}{g_{mb}} \parallel r_{o3} \approx \frac{1}{g_m(1+\chi)}$$

$$A_{vo} = \frac{r'_o}{r'_o + \frac{1}{g_m}} \approx \frac{1}{1+\chi}$$
  
$$A_v = \frac{r'_o \parallel R_L}{r'_o \parallel R_L + \frac{1}{g_m}}$$



$$g_{mb} = \chi g_m$$

$$r'_o = r_{o1} \parallel \frac{1}{g_{mb}} \parallel r_{o3}$$

$$\frac{1}{g_m} \ll r_{o1}, r_{o3}$$

Body effect limits the gain, in proportion relative to gate strength.