

# F10 – Frequency Response

## Outline

- Amplifier gain function
- Low frequency coupling/ bypass of a discrete CS amplifier
- High frequency transistor internal capacitive effects
- High frequency MOS and BJT model
- Current gain transition frequency
- Miller's voltage theorem
- Frequency response analysis
  - Gain, dominant pole, short/ open circuit time constants
  - CS amplifier
  - CG amplifier and Cascode amplifier

## Reading Guide

*Sedra/Smith 7ed int*

- Chapter 9.1-9.5, (9.6-9.8)
- Appendix F (Bode plot rules)

## Problems


*Sedra/Smith 7ed int*

- P9.14, 9.15, 9.24, 9.30, 9.67

# Frequency Response of Amplifiers

- Low frequency band,  $f < f_L$   
(not in dc coupled IC amplifiers)
  - Low corner frequency,  $f_L$
  - Coupling and bypass capacitances
- Midband,  $f_L < f < f_H$ 
  - Bandwidth,  $BW = f_H - f_L$
  - Midband gain,  $A_M$
  - Neglect capacitances
- High frequency band,  $f > f_H$ 
  - High corner frequency,  $f_H$
  - Intrinsic capacitances

$$GB = |A_M|BW = |A_M|(f_H - f_L)$$

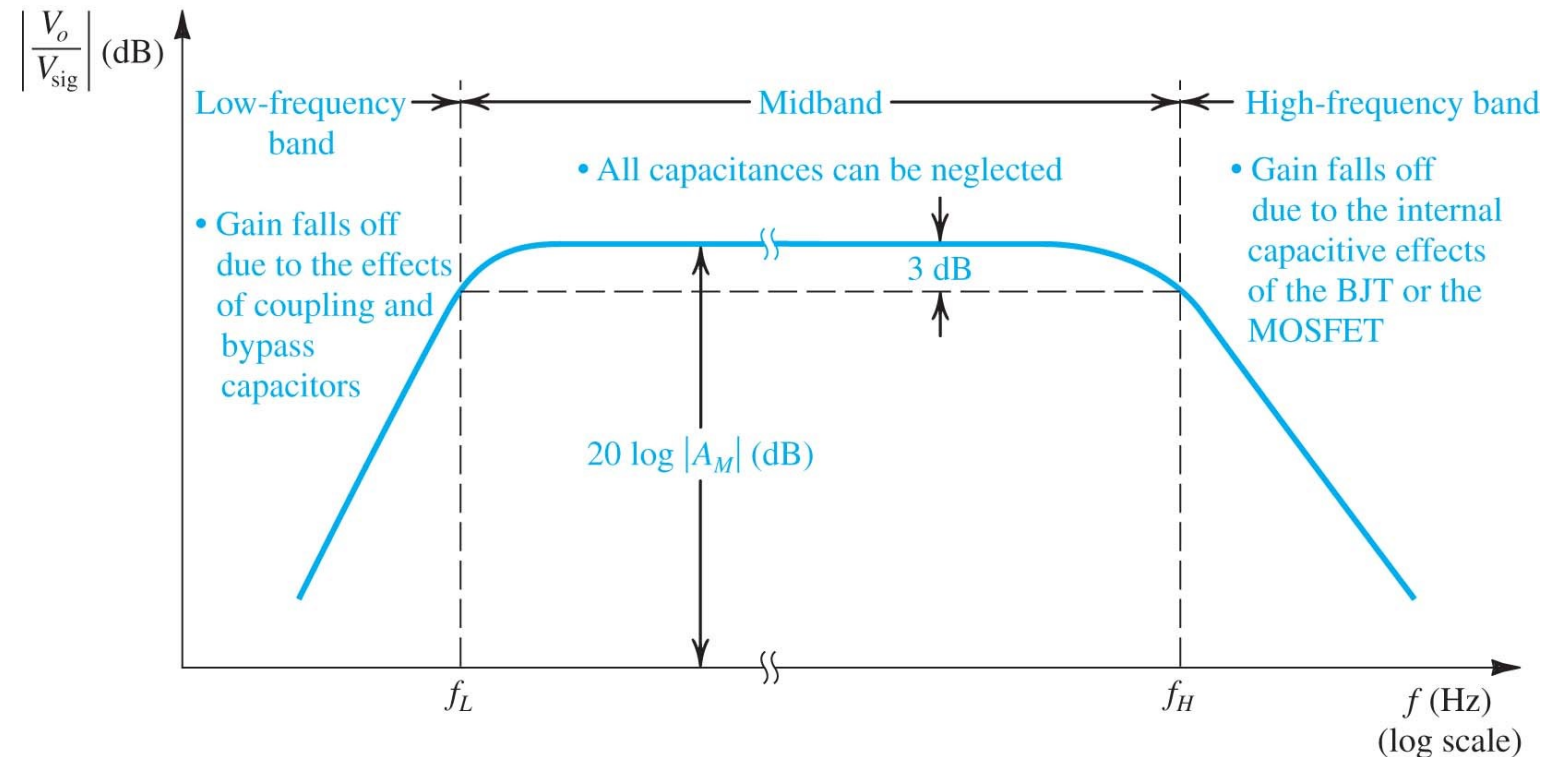

**Gain bandwidth product, GB, is a key figure of merit.**

# Amplifier Gain Function



- Amplifier gain function,  $A(s)$ , where  $s = j\omega = j2\pi f$  is the complex angular frequency
  - Low frequency transfer function,  $F_L(s)$
  - Midband gain (no frequency dependence),  $A_M$
  - High frequency transfer function,  $F_H(s)$

$$A(s) = F_L(s)A_M F_H(s)$$

- Transfer functions,  $F(s)$ , can be found from circuit analysis in the  $s$ -plane (using immittances)
  - Rational polynomial in  $s$ , with  $m$  numerator coefficients  $a_i$  and  $n \geq m$  denominator coefficients  $b_j$
  - Physical ( $R, G, C, L$ ) networks produce real coefficients, which yield real or conjugate paired roots
  - Numerator roots,  $Z_i = -\omega_{Zi}$ , a.k.a. transmission zeros (+20 dB/dec and +90° about  $|s| \approx \omega_{Zi}$ )
  - Denominator roots,  $P_j = -\omega_{Pj}$ , a.k.a. poles, natural modes (−20 dB/dec and −90° about  $|s| \approx \omega_{Pj}$ )


$$F(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{j=0}^n b_j s^j} = a_m \frac{\prod_{i=1}^m (s - Z_i)}{\prod_{j=1}^n (s - P_j)} = A \frac{\prod_{i=1}^m \left(1 + \frac{s}{\omega_{Zi}}\right)}{\prod_{j=1}^n \left(1 + \frac{s}{\omega_{Pj}}\right)}$$

**Poles may come with up to an equal number of zeros.**
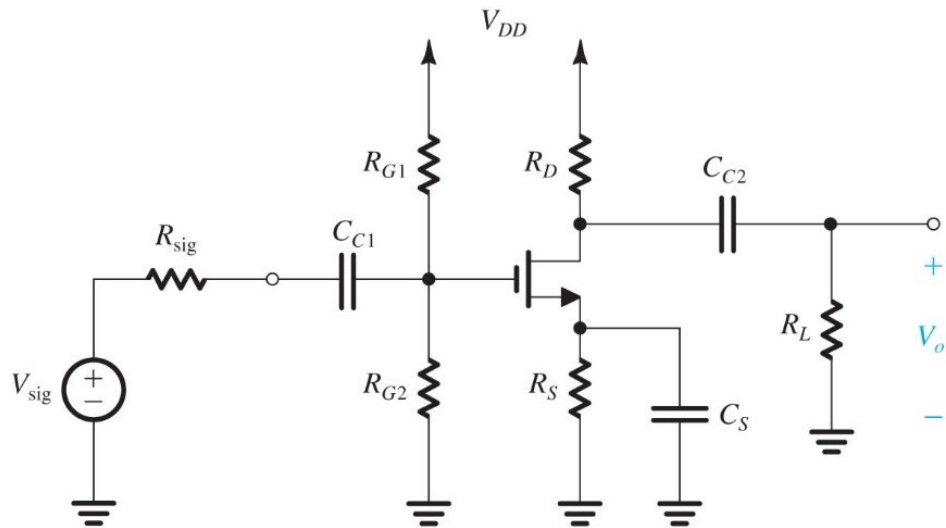
# Low Frequency Coupling/ Bypass of Discrete CS Amplifier




- Signal coupling capacitances, isolates bias and pass signals to/ from input/ output
  - Gate input
  - Drain output
- Bypass capacitance, cancels parallel component
  - Source bias network resistance



$$Z_C = \frac{1}{Y_C} = \frac{1}{j\omega C}$$

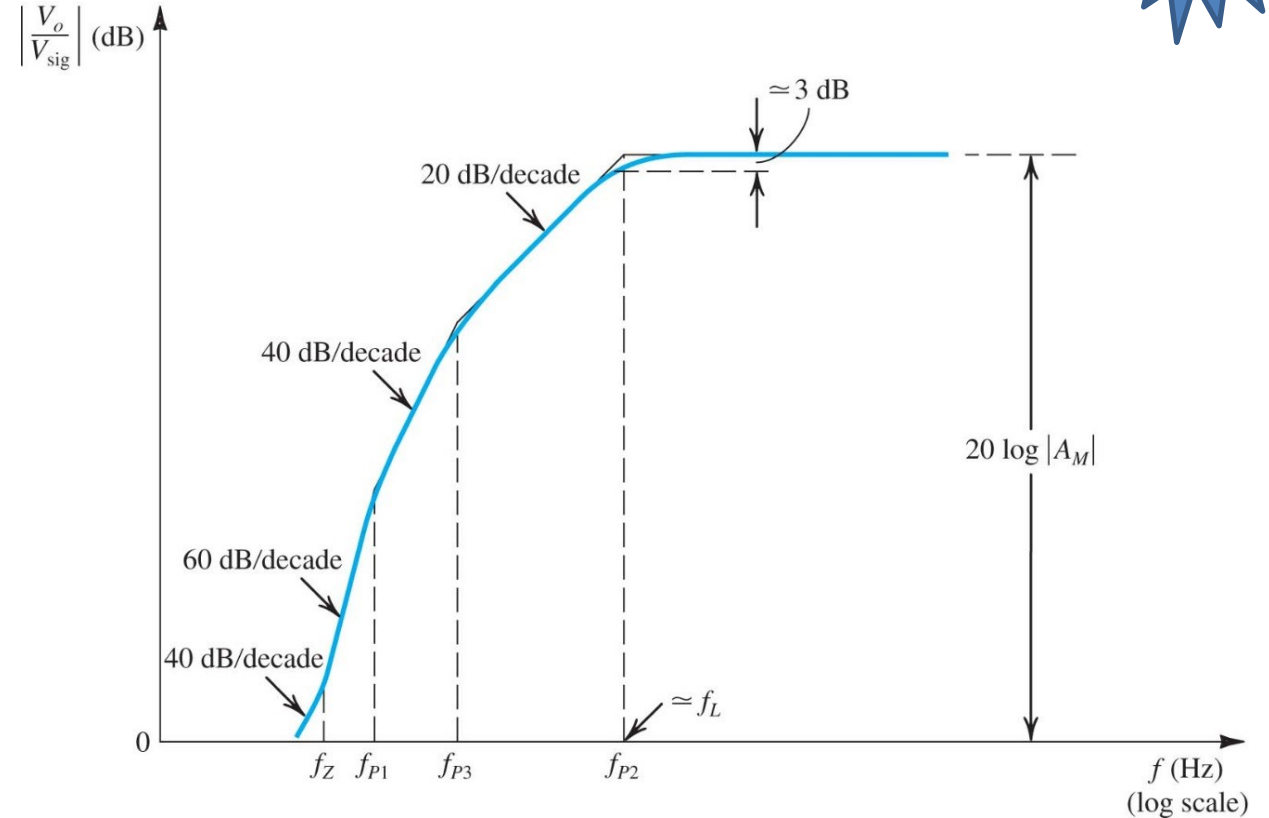**Coupling and bypass impedances “disappear” at high frequency.**



# MOSFET Internal Capacitive Effects

- Channel capacitance

- Gate-source

$$C_{ch} = \frac{2}{3} W L C_{ox}$$


- Overlap capacitances

- Gate-source
- Drain-source

$$C_{ov} = W L_{ov} C_{ox}$$

- Junction capacitances

- Source-body
- Drain-body

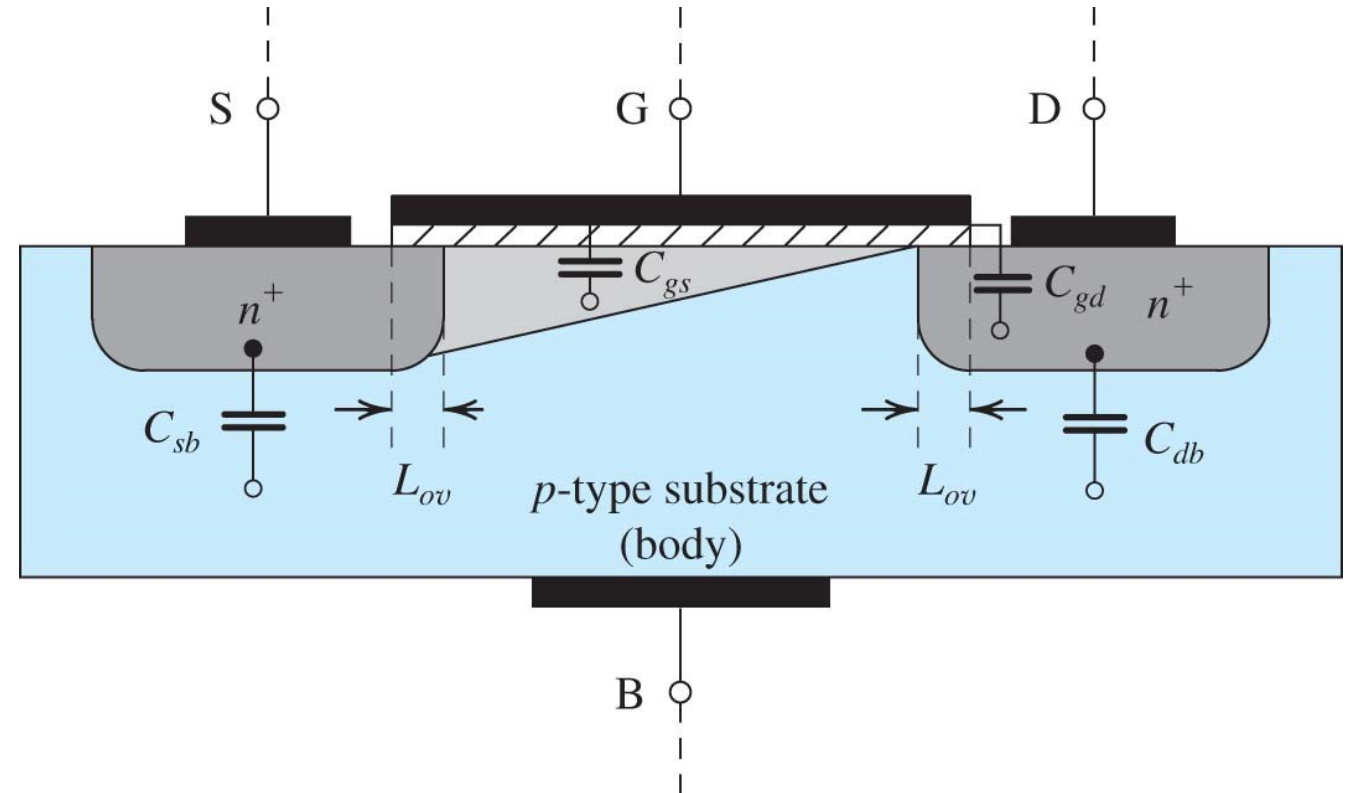

# High Frequency MOSFET Model (recap)

- Transconductance

$$g_m = k'_n \left(\frac{W}{L}\right) V_{OV} = \sqrt{2k'_n \left(\frac{W}{L}\right) I_D} = \frac{2I_D}{V_{OV}}$$

- Output resistance

$$r_o = \frac{1}{\lambda I'_D} = \frac{L}{\lambda' I'_D} = \frac{LV'_A}{\lambda' I'_D} = \frac{V_A}{I'_D}$$

- Channel and overlap capacitance

$$C_{gs} = C_{ch} + C_{ov} = \frac{2}{3}WL C_{ox} + WL_{ov} C_{ox}$$




$$C_{ds} = C_{ov} = WL_{ov} C_{ox} < C_{gs}$$

- (Body)

- Transconductance  $g_{mb} = \chi g_m, 0.1 < \chi < 0.2$

- Junction capacitance
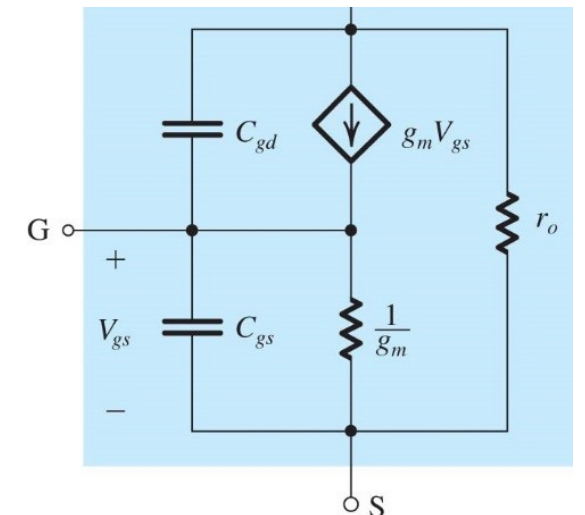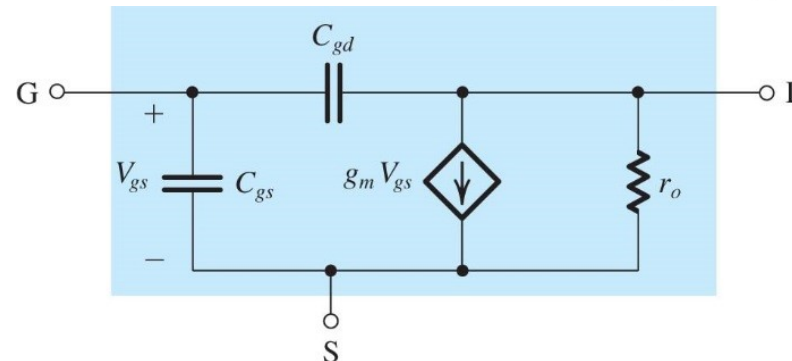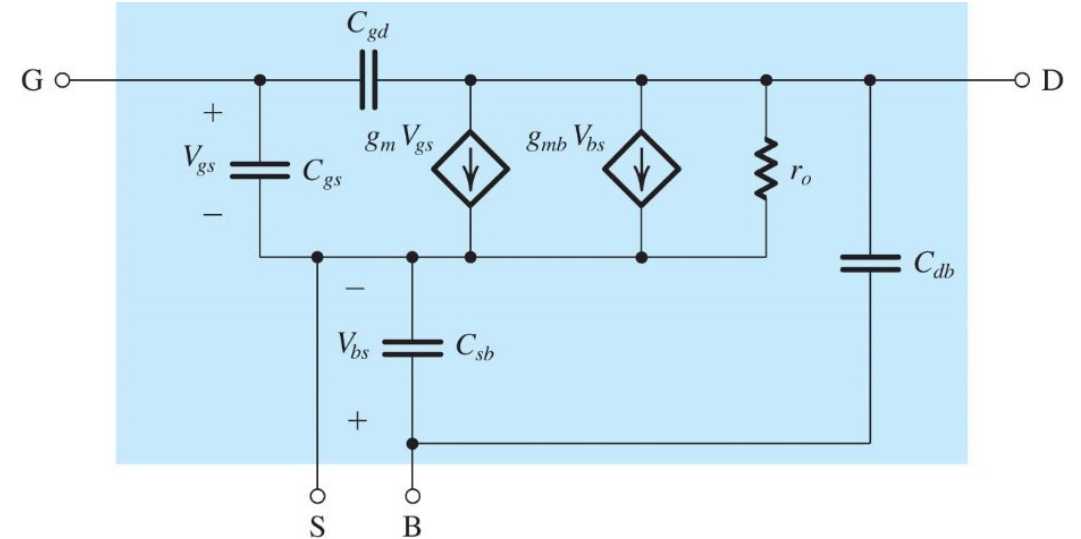
$$C_{xb} = C_{xb0} / \sqrt{1 + \frac{V_{XB}}{V_0}}$$



# High Frequency BJT Model (recap)

- Transconductance

$$g_m = \frac{I_C}{V_T}$$

- Output resistance

$$r_o = \frac{V_A}{I'_C}$$

- Base/ emitter resistance




$$r_\pi = \frac{\beta}{g_m} \quad r_e = \frac{r_\pi}{(1 + \beta)}$$

- Base access resistance


$$r_x$$

- Base transit and junction capacitances
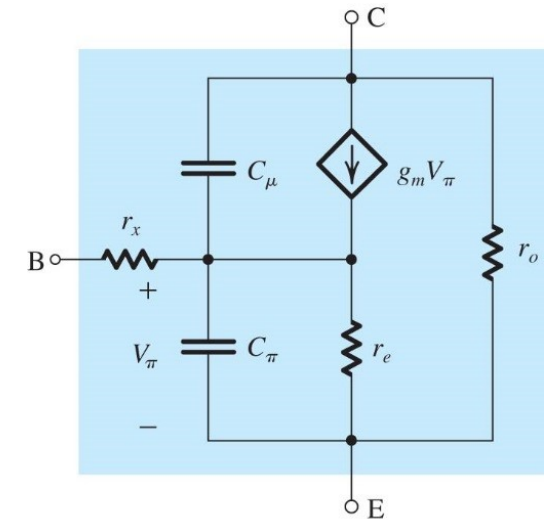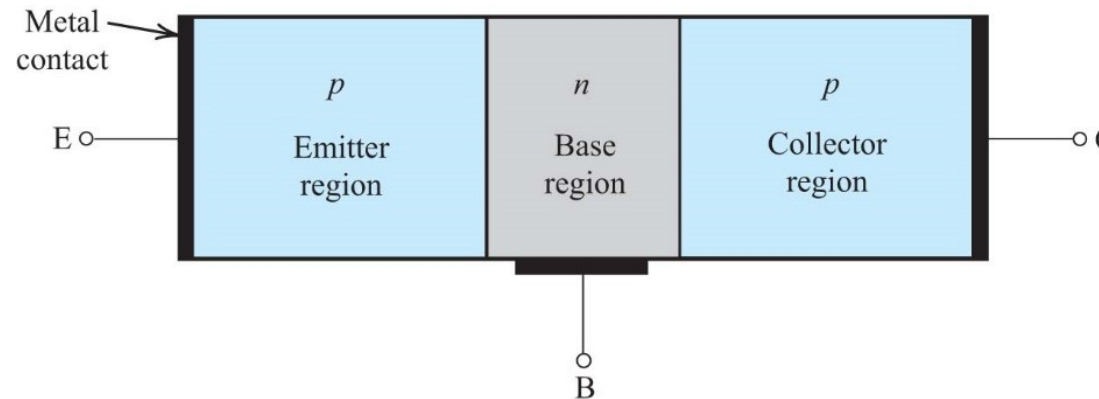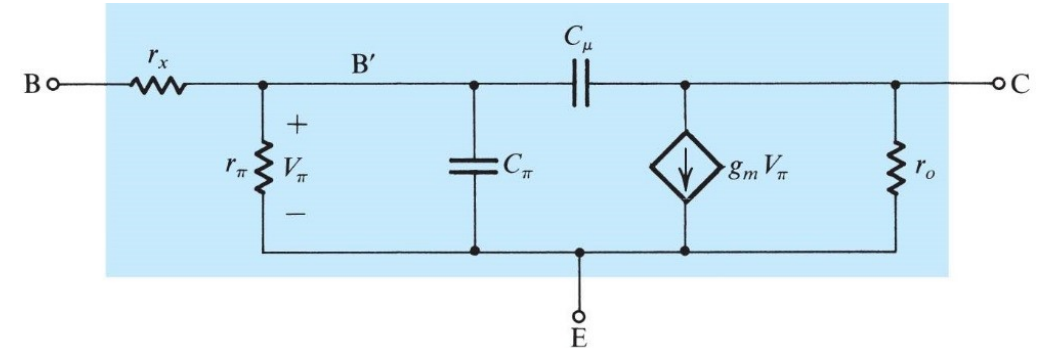
$$C_\pi = C_{de} + C_{je} \approx \tau_F g_m + 2C_{je0} \quad C_\mu = C_{jc} = C_{jc0} / \left( 1 + \frac{V_{CB}}{V_{0c}} \right)^m, \quad 0.3 < m < 0.5$$



# CS(/ CE) Amplifier Cutoff Frequency

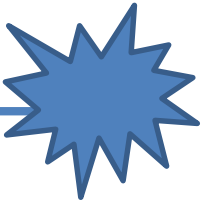

- The frequency where the transistor current gain transitions from above unity to below unity, i.e. where the gain cuts off
  - Current gain transition frequency,  $f_T$


$$A_i(f_T) = \frac{I_o}{I_i} = 1$$

- MOSFET

$$f_T \approx \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- BJT
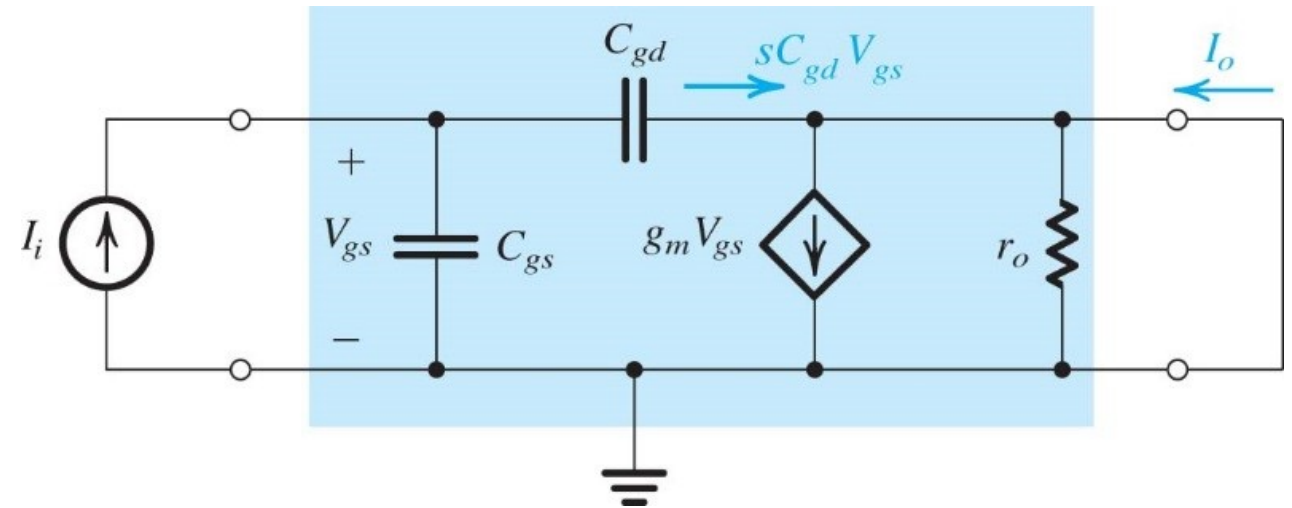
$$f_T \approx \frac{g_m}{2\pi(C_\pi + C_\mu)}$$






**Current gain transition frequency, cutoff frequency, unity gain frequency...  
An important metric for MOSFETs and BJTs.**


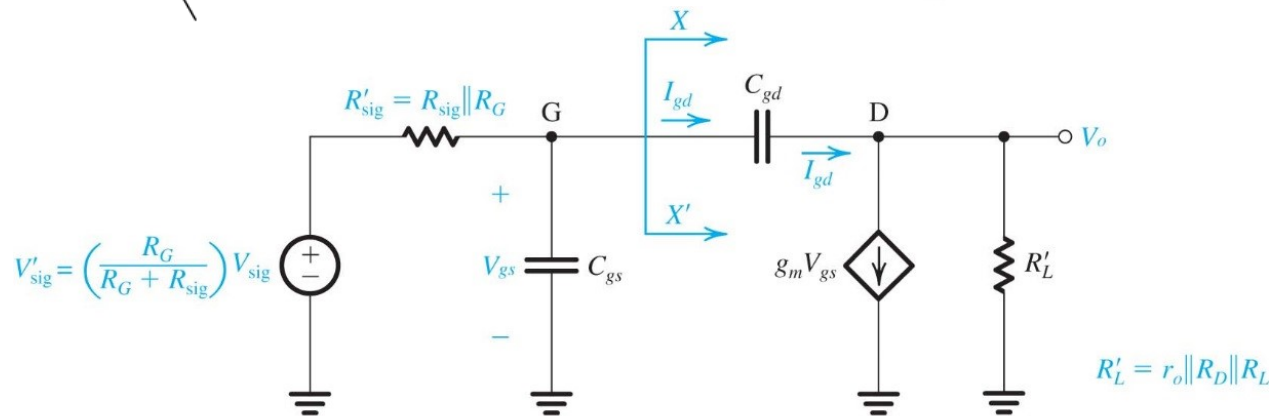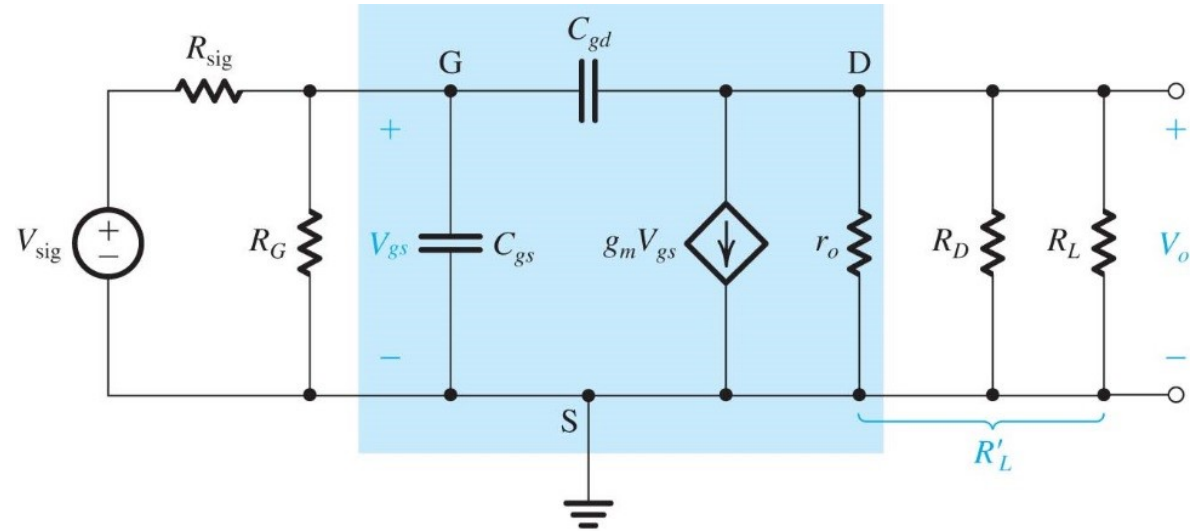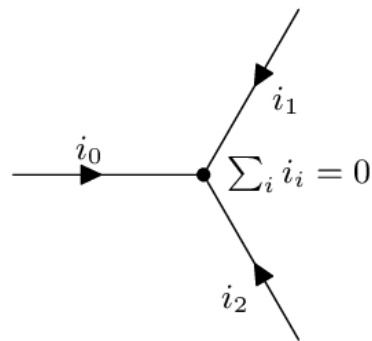
# Gain Function by Nodal Analysis: CS Amplifier

- Simplify with source theorems
- Formulate KCL node equations
  - Equations system with immittances
- Gauss elimination of internal node voltages
  - Large rational expressions in complex numbers

$$F(s) = A \frac{\prod_{i=1}^m \left(1 + \frac{s}{\omega_{Zi}}\right)}{\prod_{j=1}^n \left(1 + \frac{s}{\omega_{Pj}}\right)}$$




**Nodal analysis works, but it is tedious and gives a “complex” result.**

- Is there not a simpler way???


# BREAK

---

# Miller's Voltage Theorem

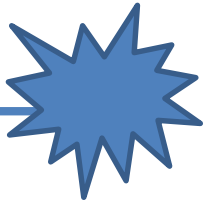

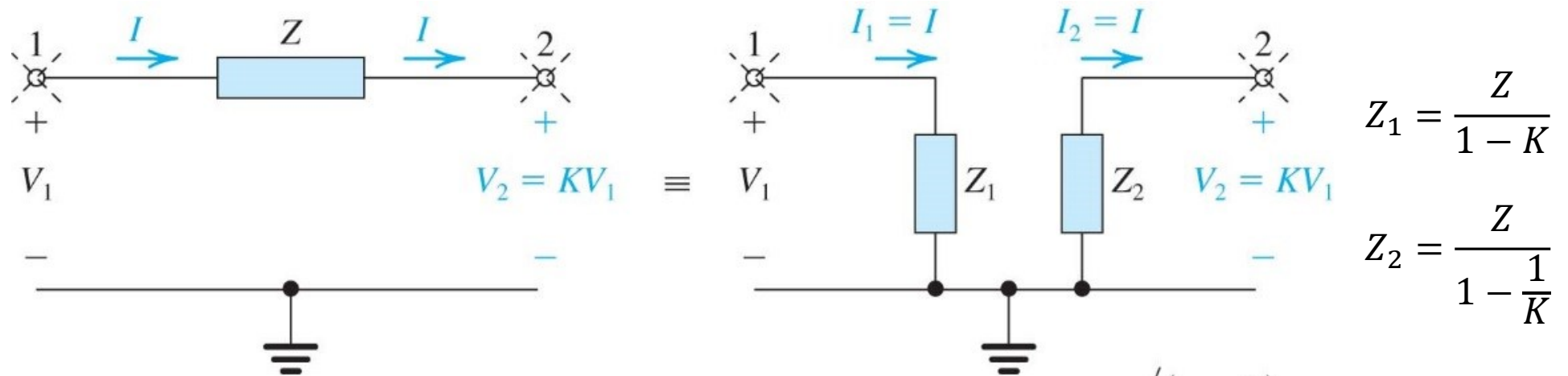
- Impedance,  $Z$ , connected between dependent nodes 1 and 2, where voltages are  $V_2 = KV_1$  related to a common node
- Equivalent to impedances,  $Z_1$  and  $Z_2$ , to common terminal




**Only valid for finding input impedance, since external circuit must remain invariant.**

# How can Miller's theorem be adapted to transistor analysis?


- Z?
- K?

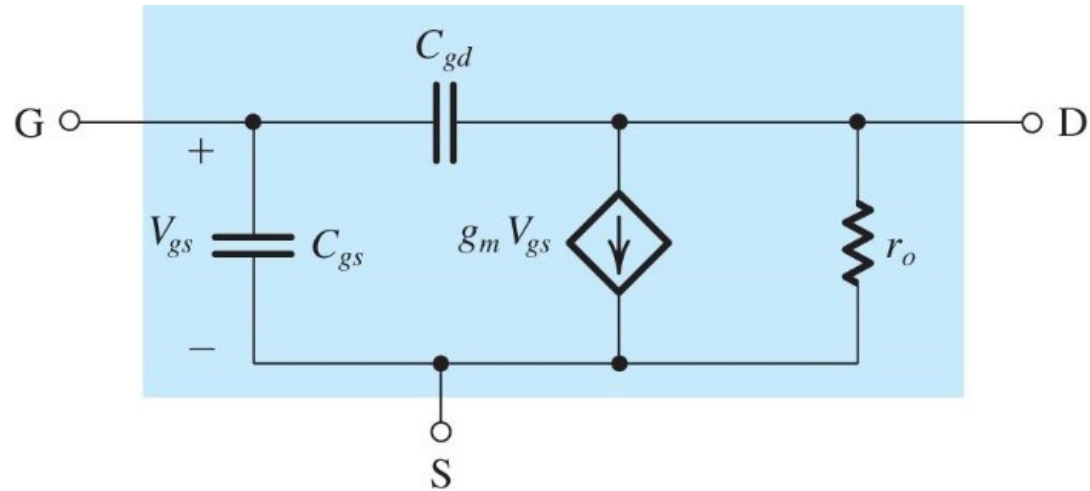

Think, think, think.

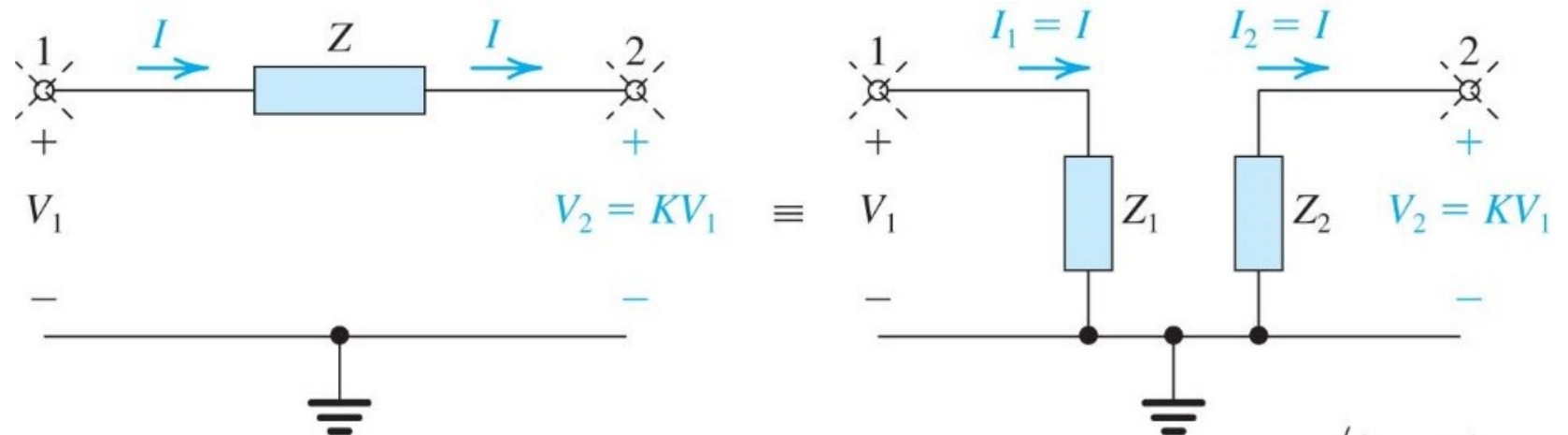
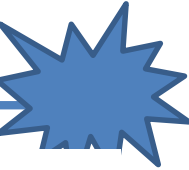
# Gain Function by Miller Approximation: CS Amplifier






- Midband gain (same as before)

$$A_M = -g_m R'_L$$

- High corner frequency


- Miller multiplier,  $(1 + g_m R'_L)$
- Input time constant
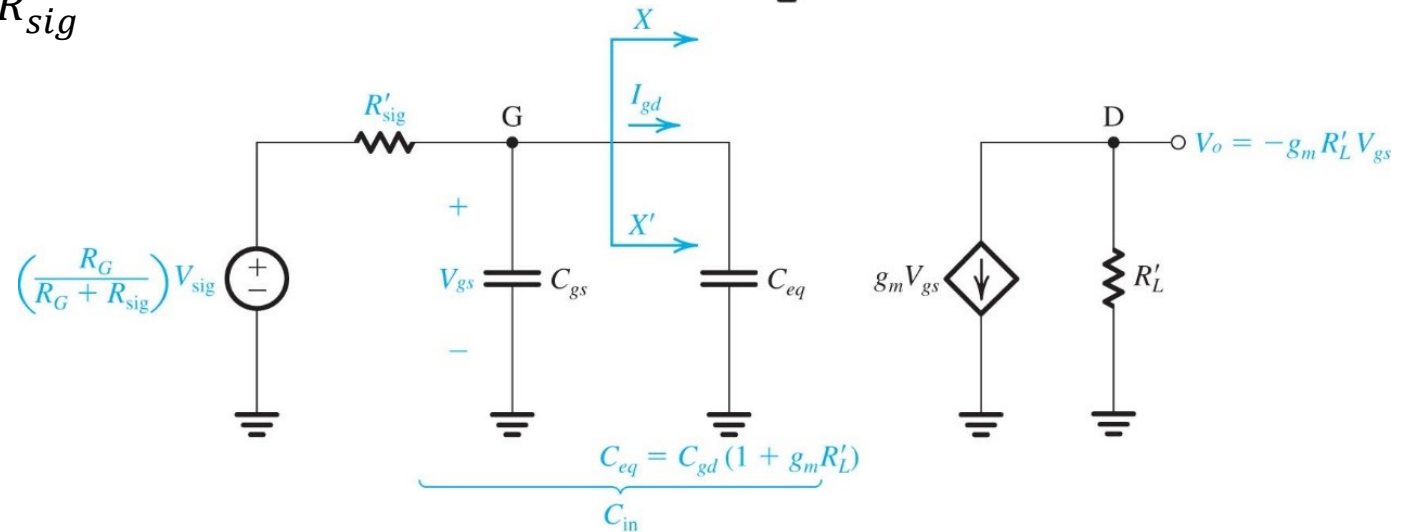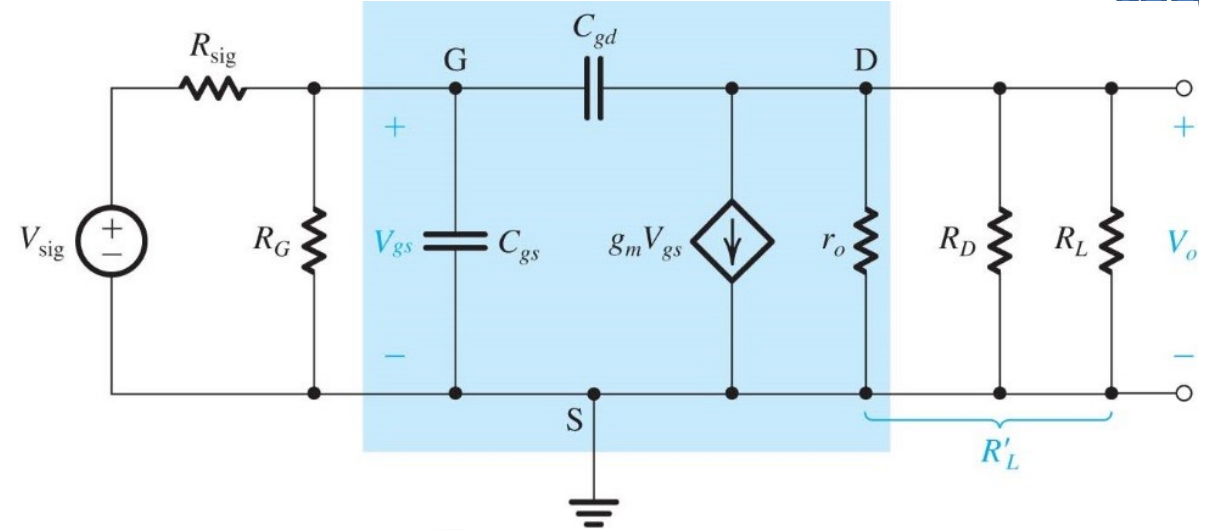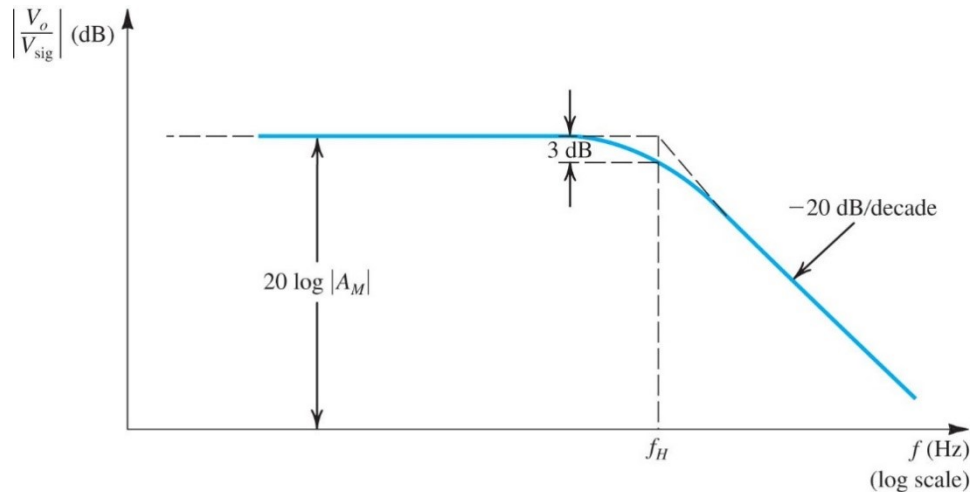
$$f_H = \frac{1}{2\pi\tau_H} \approx \frac{1}{2\pi [C_{gs} + (1 + g_m R'_L)C_{gd}] R'_{sig}}$$


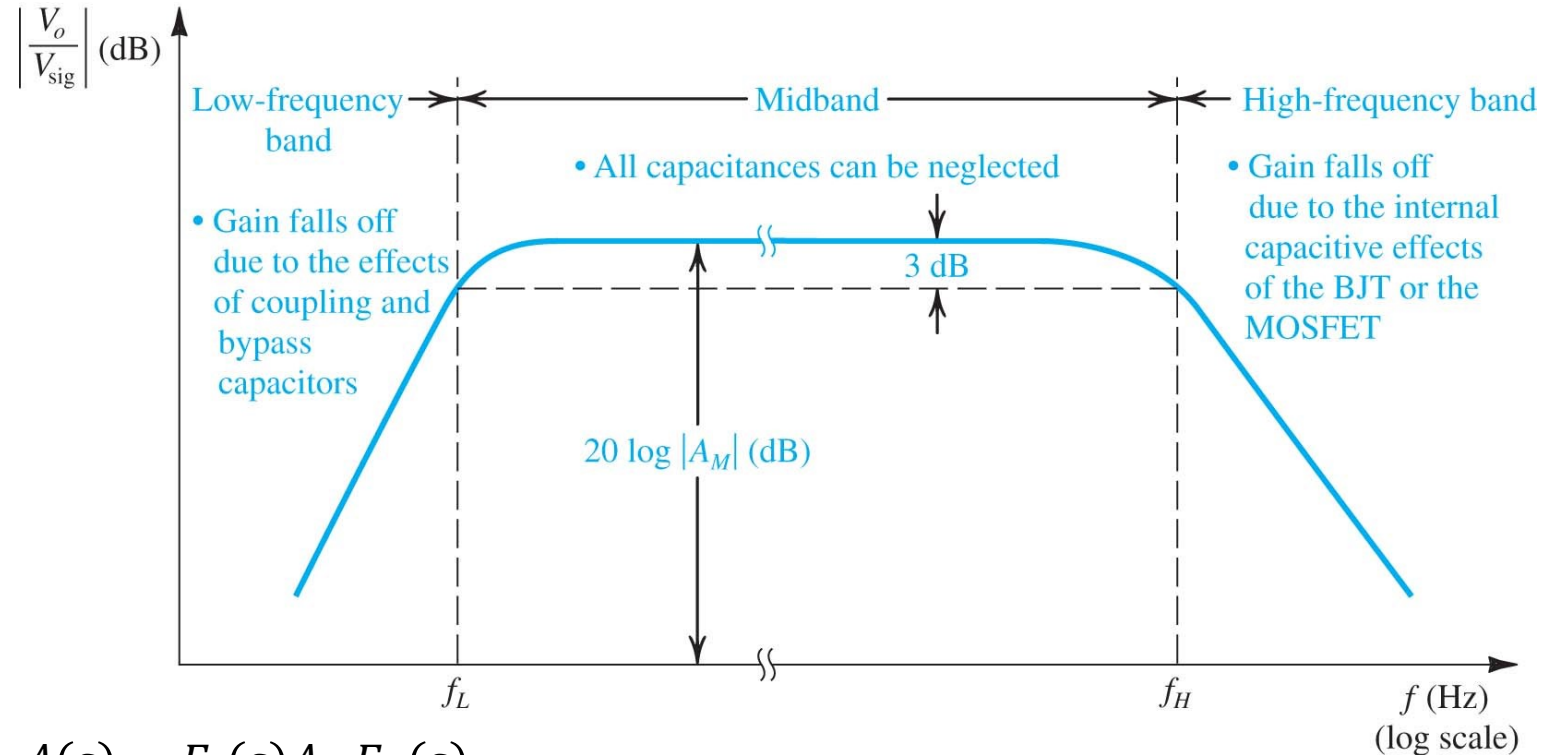
# Frequency Response – Gain Function Zeros and Poles



- Low frequency band,  $f < f_L$  (not in dc coupled IC amplifiers)
  - Low corner frequency,  $f_L$
  - Coupling and bypass capacitances
- Midband,  $f_L < f < f_H$ 
  - Bandwidth,  $BW = f_H - f_L$
  - Midband gain,  $A_M$
  - Neglect capacitances
- High frequency band,  $f > f_H$ 
  - High corner frequency,  $f_H$
  - Intrinsic capacitances



$$A(s) = F_L(s)A_M F_H(s)$$

$$F(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{j=0}^n b_j s^j} = a_m \frac{\prod_{i=1}^m (s - Z_i)}{\prod_{j=1}^n (s - P_j)} = A \frac{\prod_{i=1}^m \left(1 + \frac{s}{\omega_{Zi}}\right)}{\prod_{j=1}^n \left(1 + \frac{s}{\omega_{Pj}}\right)}$$
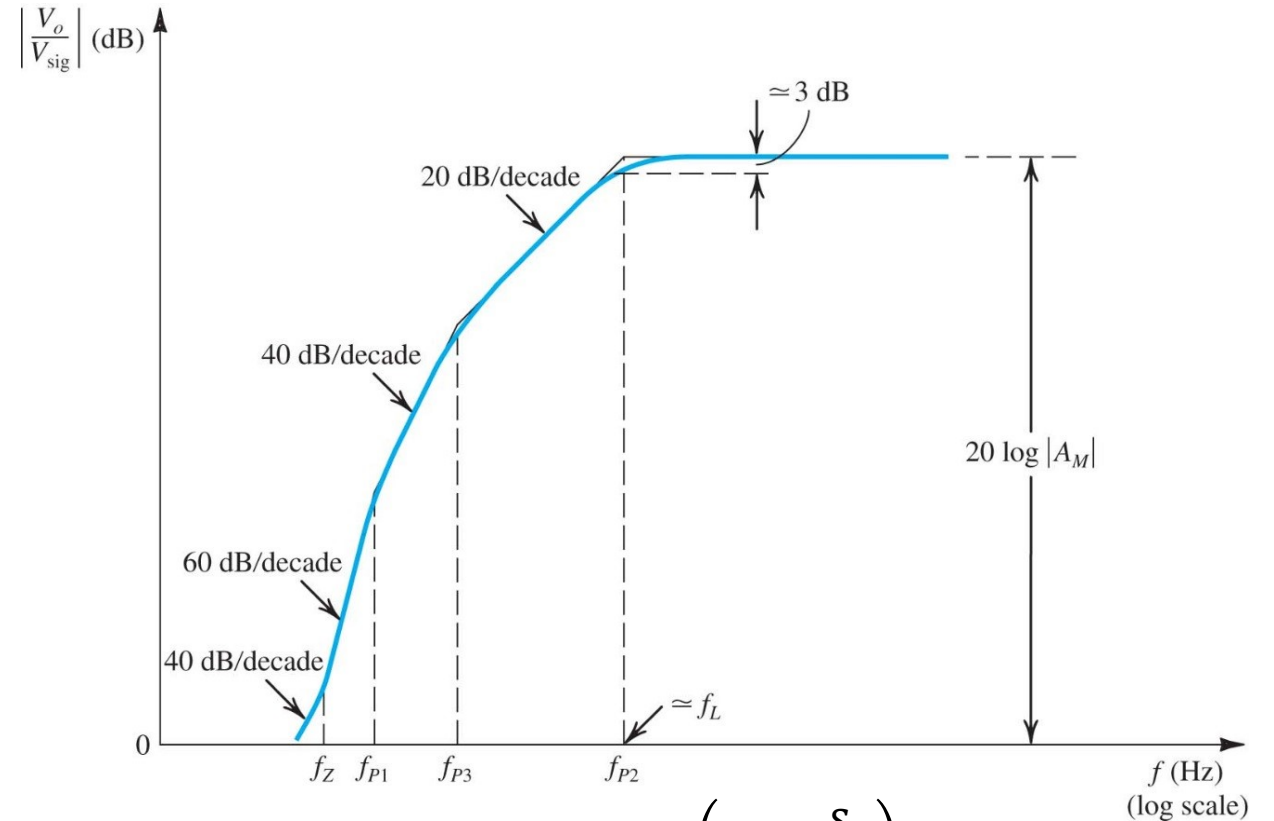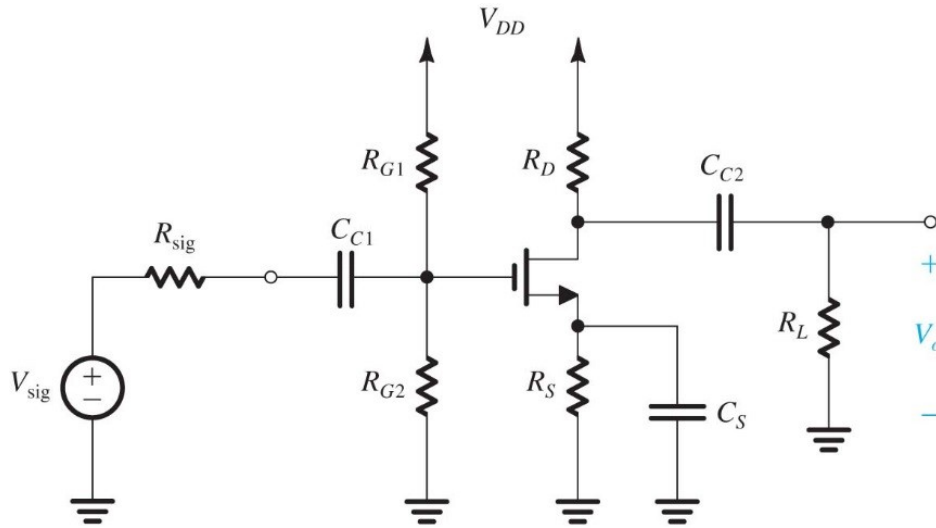
# Of all the zero and pole frequencies, which is important?



$$F(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{j=0}^n b_j s^j} = a_m \frac{\prod_{i=1}^m (s - Z_i)}{\prod_{j=1}^n (s - P_j)} = A \frac{\prod_{i=1}^m \left(1 + \frac{s}{\omega_{Zi}}\right)}{\prod_{j=1}^n \left(1 + \frac{s}{\omega_{Pj}}\right)}$$



Think, think, think.

# Dominant Poles

- Estimate low and high corner frequencies of midband from highest and lowest respective pole frequency
- Low corner dominant pole,  $P_L$ 
  - Defines the “turn” towards midband
  - Pole related to coupling and bypass capacitors, disconnects the input/output at low frequency
  - Higher frequency than all else by some margin...
- High corner dominant pole,  $P_H$ 
  - Defines the “turn” towards cutoff
  - A pole related to intrinsic input and output capacitors, short circuits the input/output at high frequency
  - Lower frequency than all else by some margin...

$$F_L(s) \approx \frac{\frac{s}{\omega_L}}{1 + \frac{s}{\omega_L}} \text{ where } Z_L = 0 \text{ and } P_L = -\omega_L$$

$$\omega_L = \frac{1}{\tau_L} \approx \sqrt{\sum_{j=1}^n \omega_{Pj} - 2 \sum_{i=1}^m \omega_{Zi}} \approx \omega_{P,max}$$

$$F_H(s) \approx \frac{1}{1 + \frac{s}{\omega_H}} \text{ where } P_H = -\omega_H$$

$$\omega_H = \frac{1}{\tau_H} \approx 1 / \sqrt{\sum_{j=1}^n \frac{1}{\omega_{Pj}} - 2 \sum_{i=1}^m \frac{1}{\omega_{Zi}}} \approx \omega_{P,min}$$

**Two octaves (x4) of separation is the rule of thumb for the dominant approximation.**



# Low Corner: Method of Short Circuit Time Constants (SCTCs)


- Assume that one capacitor generates a dominant pole in the low frequency transfer function

- Implies other capacitors are short circuited at the low corner frequency

- Method of SCTCs  $F_L(j\omega) \approx \frac{j\omega}{\omega_L} = \frac{j\omega\tau_L}{1 + j\omega\tau_L}$

- Turn off external sources
- For each capacitor,  $C_i$ 
  - Short circuit all other capacitors
  - Analyse resistance seen by capacitor
  - Calculate individual time constant,  $\tau_i$
- Sum up the inverse time constants
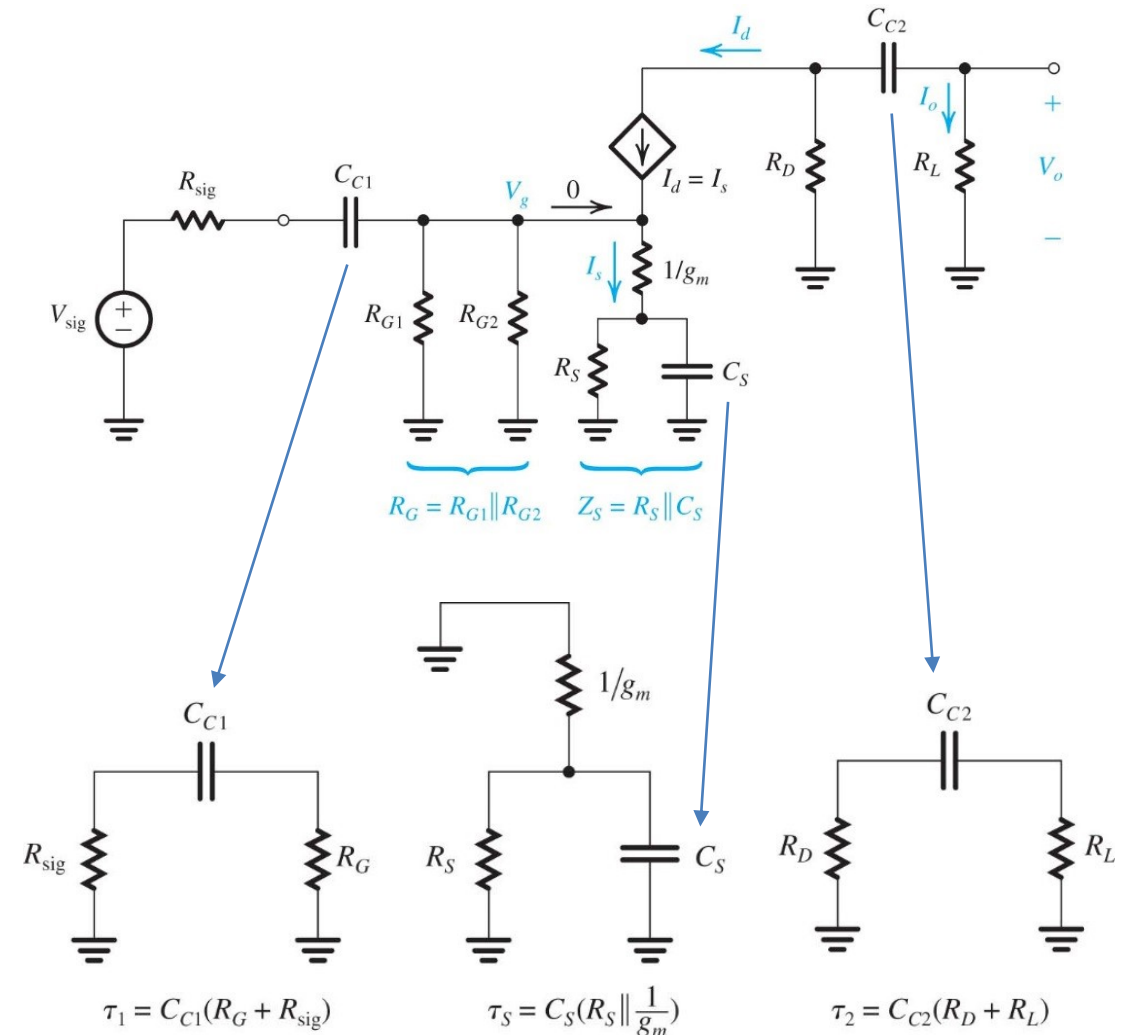
$$f_L = \frac{1}{2\pi\tau_L} \approx \frac{1}{2\pi} \sum_i \frac{1}{\tau_i} = \frac{1}{2\pi} \sum_i \frac{1}{C_i R_i}$$




# High Corner: Method of Open Circuit Time Constants (OCTCs)

- Assume that one capacitor generates a dominant pole in the high frequency transfer function
  - Implies other capacitors are open circuited at the high corner frequency

- Method of OCTCs  $F_H(j\omega) \approx \frac{1}{1 + \frac{j\omega}{\omega_H}} = \frac{1}{1 + j\omega\tau_H}$

- Turn off external sources
- For each capacitor,  $C_i$ 
  - Open circuit all other capacitors
  - Analyse resistance seen by capacitor
  - Calculate individual time constant,  $\tau_i$
- Sum up the time constants
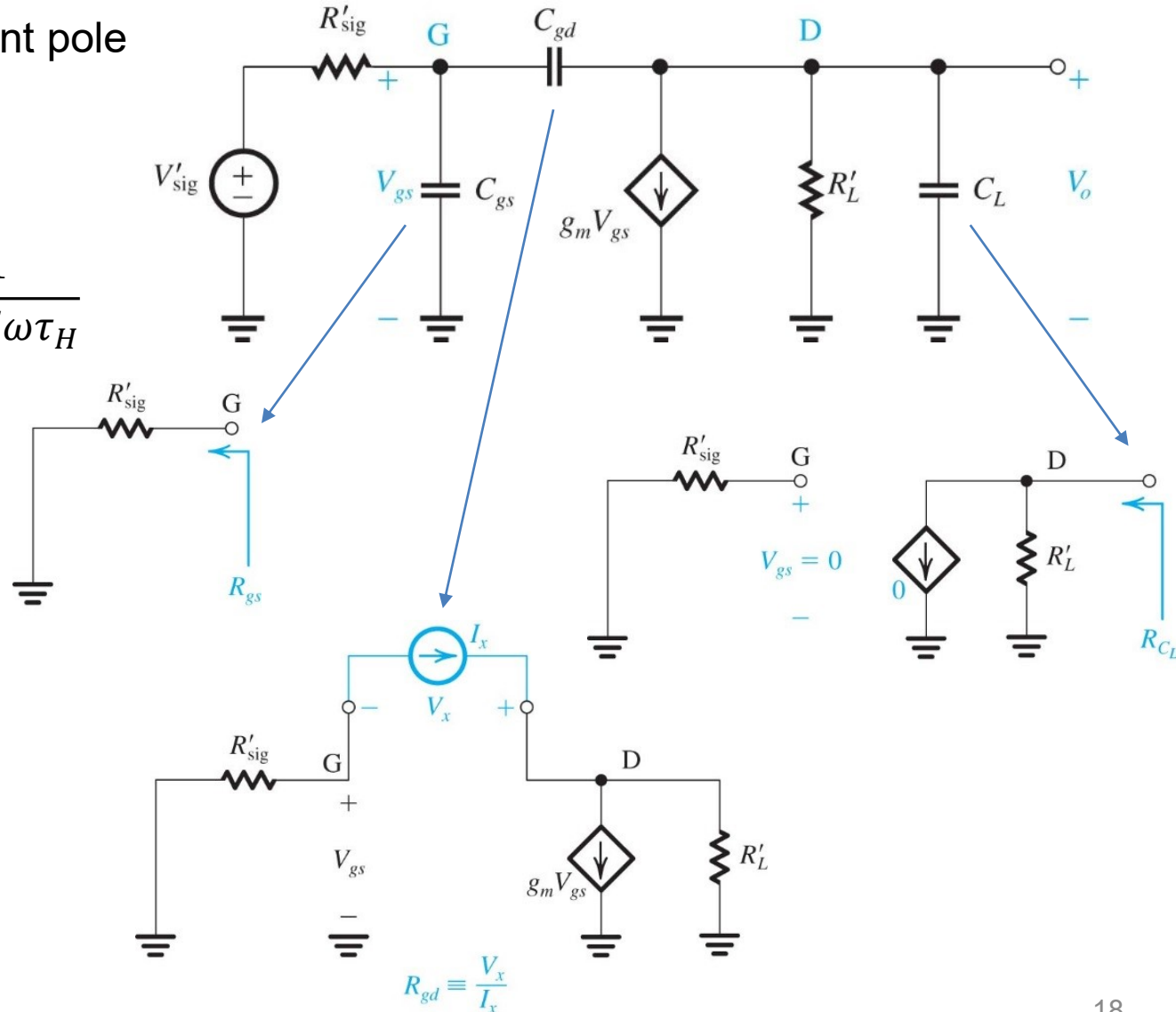
$$f_H = \frac{1}{2\pi\tau_H} \approx \frac{1}{2\pi} / \sum_{i=1}^n \tau_i = \frac{1}{2\pi} / \sum_{i=1}^n C_i R_i$$



# OCTC: CS Amplifier


- Method of OCTCs
  - Turn off external sources
  - For each capacitor,  $C_i$ 
    - Open circuit all other capacitors
    - Analyse resistance seen by capacitor
    - Calculate individual time constant,  $\tau_i$
  - Sum up the time constants

$$\tau_{gs} = C_{gs}R_{gs} = C_{gs}R'_{sig}$$

$$\tau_{gd} = C_{gd}R_{gd} = C_{gd}([1 + g_m R'_L]R'_{sig} + R'_L)$$

$$\tau_L = C_L R_{CL} = C_L R'_L$$

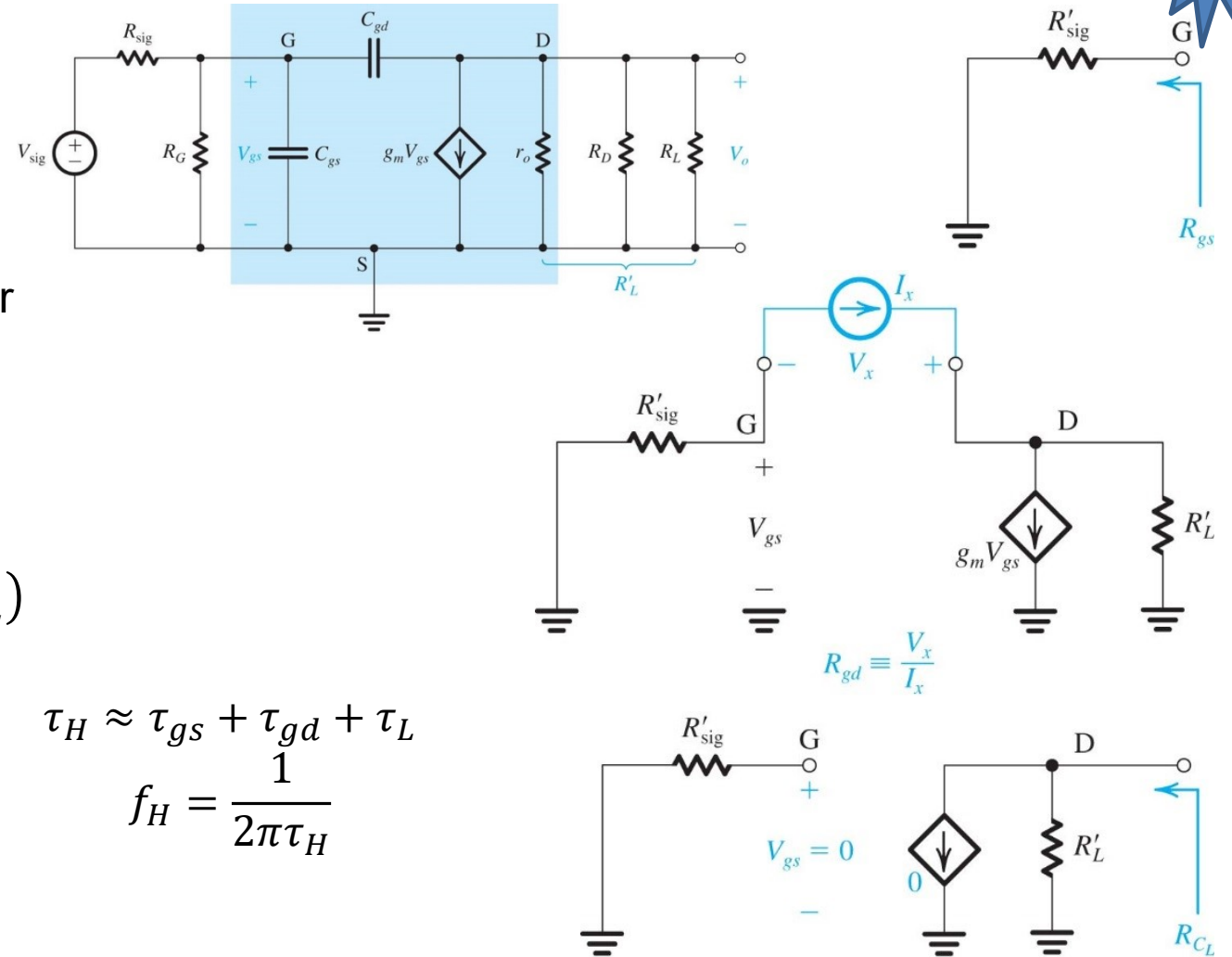- If signal source resistance high
  - Miller effect dominates corner frequency



$$\tau_H \approx \tau_{gs} + \tau_{gd} + \tau_L$$

$$f_H = \frac{1}{2\pi\tau_H}$$

# OCTC: CG Amplifier

- Method of OCTCs

- Turn off external sources
- For each capacitor,  $C_i$ 
  - Open circuit all other capacitors
  - Analyse resistance seen by capacitor
  - Calculate individual time constant,  $\tau_i$
- Sum up the time constants

$$\tau_{gs} = C_{gs}(R_{sig} || R_i)$$

$$\tau_{gd} = (C_{gd} + C_L)(R_L || R_o)$$

- Capacitances to grounded gate


- Effectively “moved” to ground
- Analysis simplified

$$R_o = r_o + (1 + g_m r_o) R_{sig}$$

$$R_i = \frac{r_o + R_L}{1 + g_m r_o}$$

$$\tau_H \approx \tau_{gs} + \tau_{gd}$$

$$f_H = \frac{1}{2\pi\tau_H}$$

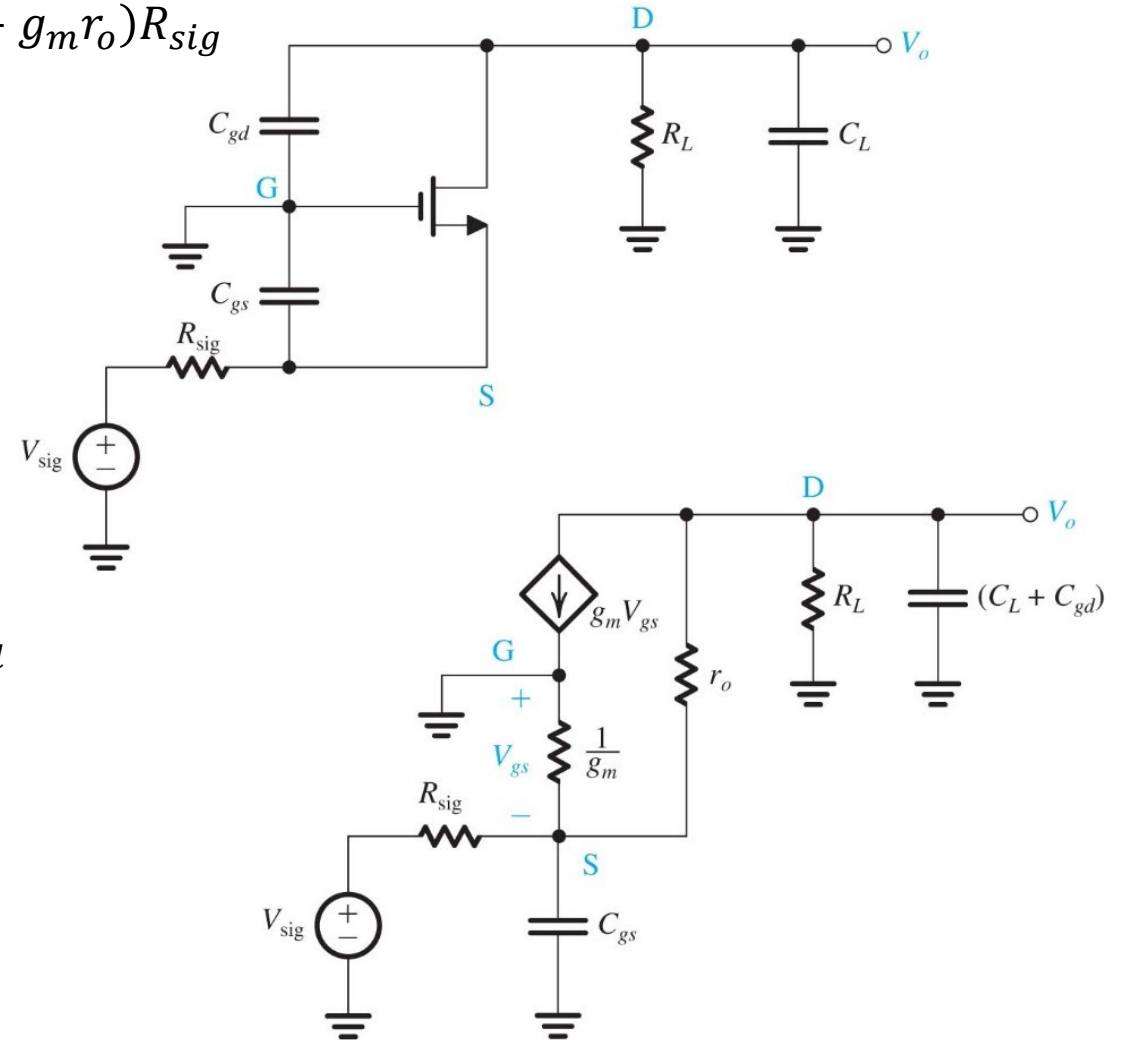

# OCTC: Cascode Amplifier

- Method of OCTCs

- Turn off external sources
- For each capacitor,  $C_i$ 
  - Open circuit all other capacitors
  - Analyse resistance seen by capacitor
  - Calculate individual time constant,  $\tau_i$

- Sum up the time constants

$$\tau_{gs1} = C_{gs1}R_{sig}$$

$$\tau_{gd1} = C_{gd1}[(1 + g_{m1}R_{d1})R_{sig} + R_{d1}]$$

$$\tau_{gs2} = (C_{gs2} + C_{db1})R_{d1}$$


$$\tau_{gd2} = (C_{gd2} + C_L)(R_o || R_L)$$

$$\tau_H \approx \tau_{gs1} + \tau_{gd1} + \tau_{gs2} + \tau_{gd2}$$

$$f_H = \frac{1}{2\pi\tau_H}$$

- If signal source resistance negligible

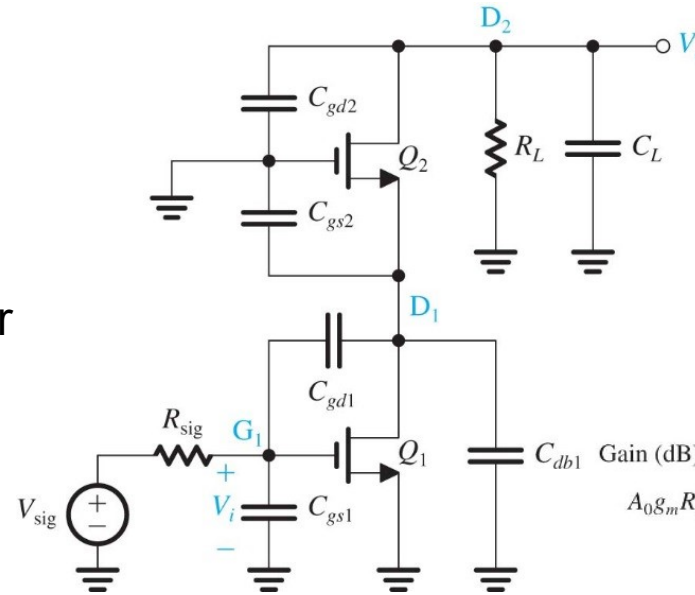
- Increased dc gain, reduced BW, same cutoff w.r.t. CS



$$R_o = r_{o2} + (1 + g_{m2}r_{o2})r_{o1}$$

$$R_{in2} = \frac{r_{o2} + R_L}{1 + g_{m2}r_{o2}}$$



$$R_{d1} = r_{o1} || R_{in2}$$

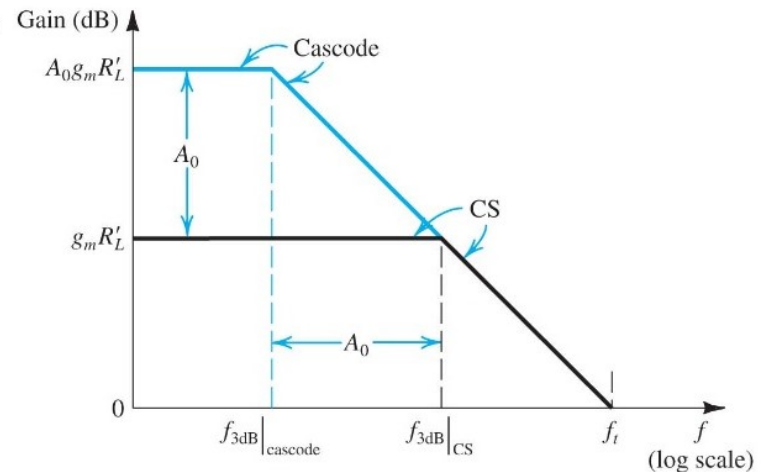

**Cascode input, middle node (D1,S2), or output may dominate...**
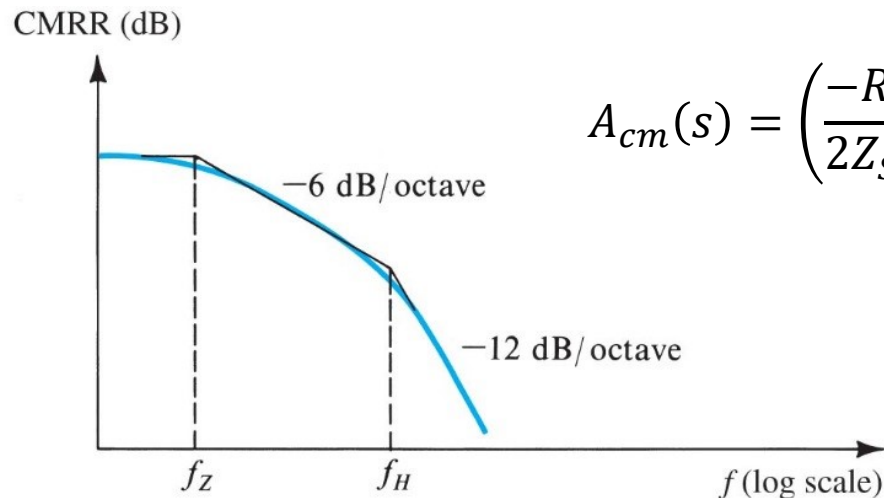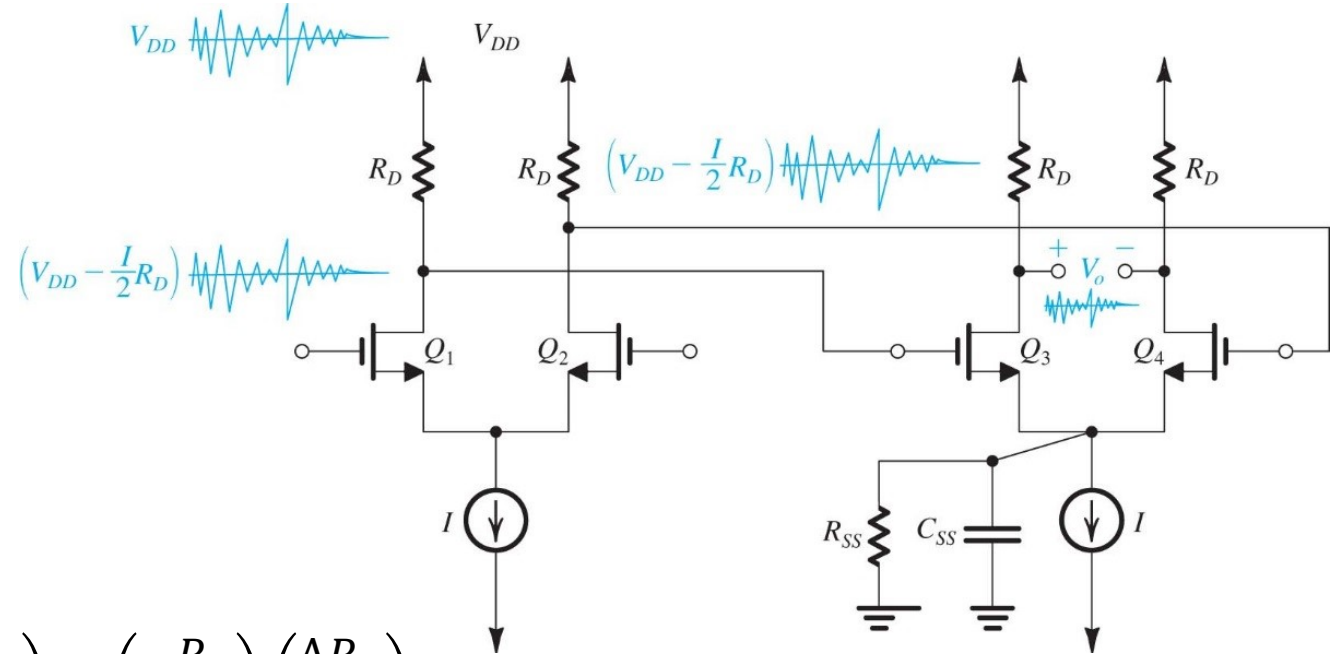
# (Differential Amplifier: Common Mode Gain and CMRR)

- Noise injected from supply in first stage
  - Common mode signal
- Second stage relied on to suppress CM noise
  - CMRR proportional to sink resistance
  - Capacitance in parallel to sink resistance



$$A_{cm}(s) = \left( \frac{-R_D}{2Z_{SS}} \right) \left( \frac{\Delta R_D}{R_D} \right) = \left( \frac{-R_D}{2R_{SS}} \right) \left( \frac{\Delta R_D}{R_D} \right) (1 + sC_{SS}R_{SS})$$

$$Z = \frac{-1}{C_{SS}R_{SS}}$$

**Already at low frequency (large RC time constant), CMRR degraded by sink bypass.**