

F13 – Digital Logic

Outline

- Digital logic
- CMOS complementary switches
- CMOS logic gate circuits
- CMOS inverter
 - Static operation
 - Dynamic operation
 - Power dissipation
 - Power-delay product
 - Energy-delay product

Reading Guide

Sedra/Smith 7ed int

- Chapter 15.1-4, 15.6
- (Chapter 15.5 (transistor sizing))
- (Chapter 16 (logic families))


Problems

Sedra/Smith 7ed int

- P15.3, 15.4, 15.33, 15.34, 15.57, 15.60

Digital Logic Families

- Complementary MOS (CMOS) digital logic
 - Complementary common source devices
 - Low static power dissipation but high dynamic
- Current-steering logic (CSL)/ emitter coupled logic (ECL)
 - Differential pair + followers for level shift
 - Naturally produces complementary output variables
 - Fast operation and approximately constant supply current
- Pass transistor logic (PTL) and complementary pass transistor logic (CPL)
 - PTL: CMOS transmission gates, typically requiring some complementary input variables
 - CPL: Zero threshold NMOS (or PMOS) only, demanding complementary input variables
 - Slow operation, susceptible to noise, and poor 1 logic level, but can be area efficient
- ... and many other digital logic families

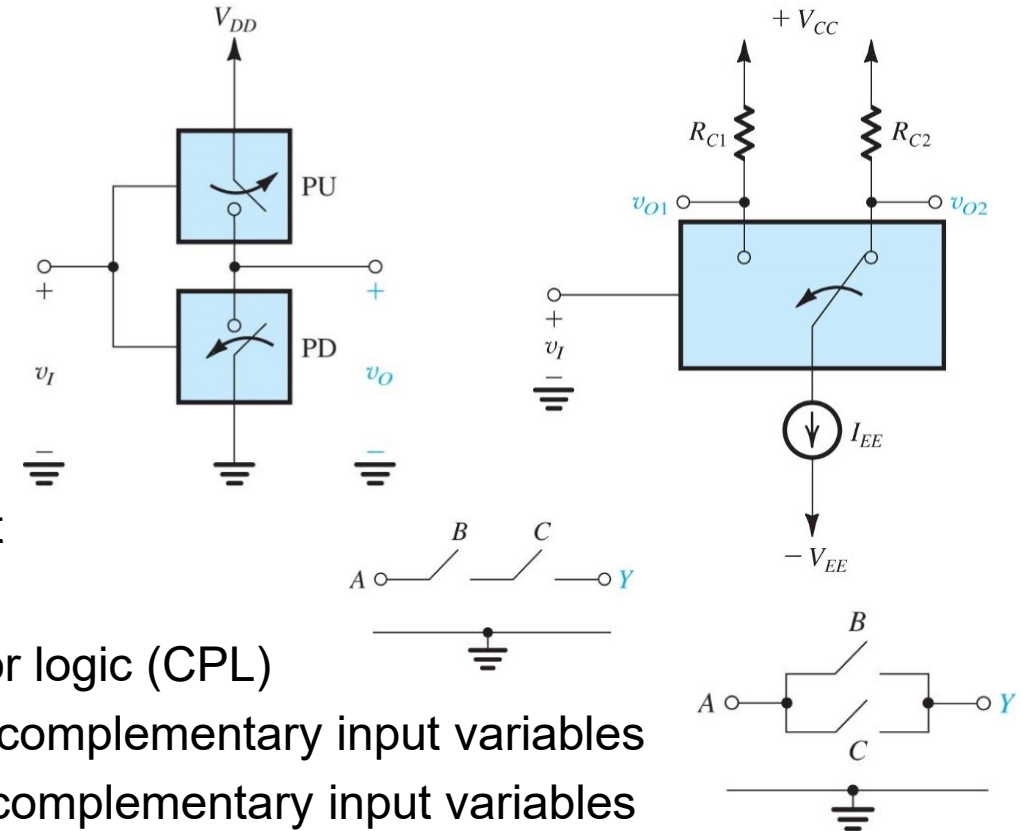


Every logic family has its pros and cons, but CMOS logic is economic, versatile, and low static power.

CMOS: Complementary MOS Devices Operated as Switches



- Switch level transistor models utilised in function design
- CMOS logic levels
 - Logic 0: Ground level (low), i.e. $0 \leftrightarrow V_{"0"} = 0\text{ V}$
 - Logic 1: Positive supply (high), i.e. $1 \leftrightarrow V_{"1"} = V_{DD}$
- PMOS w/ source connected towards supply: active low
 - Gate high: cut off, i.e. open switch
 - Gate low: saturation, i.e. closed switch, with a small resistance
- NMOS w/ source connected towards ground: active high
 - Gate high: saturation, i.e. closed switch, with a small resistance
 - Gate low: cut off, i.e. open switch

 



NOT Gate a.k.a. Inverter


- Logic (boolean) NOT function

- Input, X

$$X \in \{0, 1\}$$

- Output, Y

 
$$Y = \bar{X} = \begin{cases} 1, & X = 0 \\ 0, & X = 1 \end{cases}$$



X	$Y = \bar{X}$
0	1
1	0

- CMOS inverter (i.e. NOT gate)

 
- Pull up transistor Q_P , $Y = \bar{X}$
 - Connects output towards supply if input is low, otherwise isolates
- Pull down transistor Q_N , $\bar{Y} = X$
 - Connects output towards ground if input is high, otherwise isolates



Digital logic gate circuits perform logic (boolean) functions.

CMOS Logic Gates

- Input nodes
 - Gate nodes of various NMOS and PMOS transistors
- Output node
 - Routed either to supply or ground, depending on input levels
- Pull up network (PUN), $Y = f_{PUN}(\bar{A}, \bar{B}, \bar{C}, \dots)$
 - PMOS connects output node towards supply for low input
- Pull down network (PDN), $\bar{Y} = f_{PDN}(A, B, C, \dots)$
 - NMOS connects output node towards ground for high input
- Complementary PUN and PDN device operation
 - Input variables (A, B, C, \dots) connect to both PUN and PDN
 - Per input variable, PUN PMOS does opposite of PDN NMOS

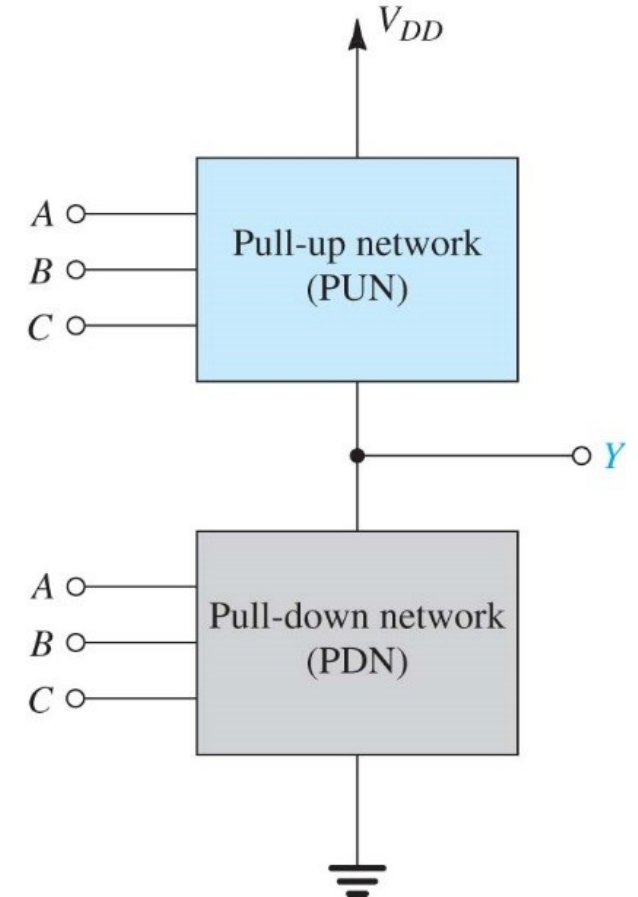

Boolean logic requires three basic operations: NOT, IF and AND.

Two Input NOR Gate

- Logic (boolean) NOT-OR compound function

- Inputs, $\{A, B\}$

$$A, B \in \{0, 1\}$$

- Output, Y

$$Y = \overline{A + B} = \overline{A} \overline{B} = \begin{cases} 1, & (A = 0, B = 0) \\ 0, & \text{otherwise} \end{cases}$$


- CMOS NOR gate

- PUN, $Y = \overline{A} \overline{B}$


- One series branch with all inputs

- PDN, $\overline{Y} = A + B$

- One parallel branch for each input

 

A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

 

Inclusive OR function, dissimilar from exclusive XOR function.

Two Input NAND Gate

- Logic (boolean) NOT-AND compound function

- Inputs, $\{A, B\}$

$$A, B \in \{0, 1\}$$

- Output, Y

$$Y = \overline{AB} = \bar{A} + \bar{B} = \begin{cases} 0, & (A = 1, B = 1) \\ 1, & \text{otherwise} \end{cases}$$


- CMOS NAND gate

- PUN, $Y = \bar{A} + \bar{B}$


- One parallel branch for each input

- PDN, $\bar{Y} = AB$




- One series branch with all inputs

 



A	B	$Y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

 

How can OR and AND gates be implemented?

 
 
 


Think, think, think.

  


CMOS Pull Up Networks (PUNs)

- PUNs consist of active low PMOS transistors only
- PMOS w/ source towards supply
 - Active when gate input is low (0)
 - Not active if gate input is high (1)
- Parallel connection: NAND
 - At least one low yields conductive path towards supply
- Series connection: NOR
 - All, and only all, low yields conductive path towards supply
- Scalable to arbitrary number of devices in series/ parallel branches

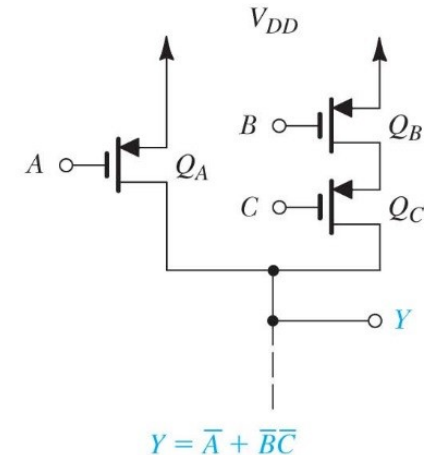  

CMOS Pull Down Networks (PDNs)

- PDNs consist of active high NMOS transistors only
- NMOS w/ source towards ground
 - Not active if gate input is low (0)
 - Active when gate input is high (1)
- Parallel connection: NOR
 - At least one high yields conductive path towards ground
- Series connection: NAND
 - All, and only all, high yields conductive path towards ground
- Scalable to arbitrary number of devices in series/ parallel branches

 

Complex Gates: Duality, Boolean Algebra, and De Morgan's Law



- PUN-PDN duality between series and parallel connections
- Basic operators in boolean algebra/ set theory/ digital logic

- Disjunction/ union/ OR

$$A \vee B \Leftrightarrow A \cup B \Leftrightarrow \text{OR}(A, B) \sim \max(A, B) = A + B - AB$$

- Conjunction/ intersection/ AND

$$A \wedge B \Leftrightarrow A \cap B \Leftrightarrow \text{AND}(A, B) \sim \min(A, B) = AB$$

- Negation/ complement/ NOT


$$\neg \Leftrightarrow \bar{} \Leftrightarrow \text{NOT}(X) \sim 1 - X$$

- De Morgan's law

- Negation of disjunction is equivalent to conjunction of negations, and vice versa


$$\neg(A \vee B) = (\neg A) \wedge (\neg B) \Leftrightarrow \overline{A \cup B} = \bar{A} \cap \bar{B} \Leftrightarrow \overline{A + B} = \bar{A} \bar{B}$$
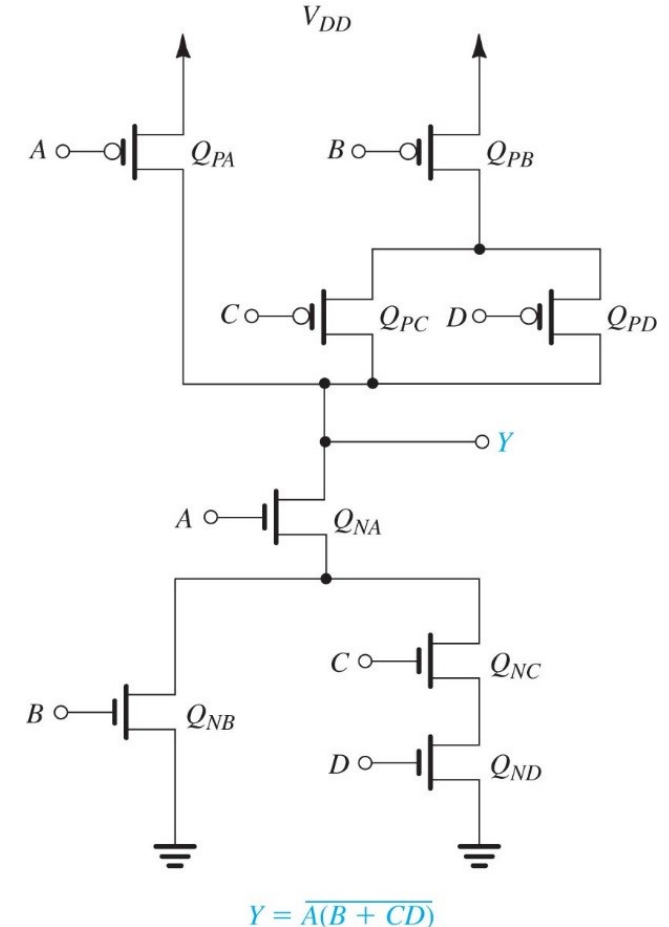
$$\neg(A \wedge B) = (\neg A) \vee (\neg B) \Leftrightarrow \overline{A \cap B} = \bar{A} \cup \bar{B} \Leftrightarrow \overline{AB} = \bar{A} + \bar{B}$$



De Morgan's law: "break the line, change the sign".

Synthesis by Duality: Two Input XOR Gate

 

- Logic (boolean) XOR function

- Inputs, $\{A, B\}$

$$A, B \in \{0, 1\}$$

- Output, Y

$$Y = A\bar{B} + \bar{A}B = \begin{cases} 1, & (A \neq B) \\ 0, & \text{otherwise} \end{cases}$$

- CMOS XOR gate

- PUN, $Y = A\bar{B} + \bar{A}B$


- Parallel branches with series devices

- PDN


- Series branch with parallel devices

- Auxiliary logic

- Inverters for complemented variables

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

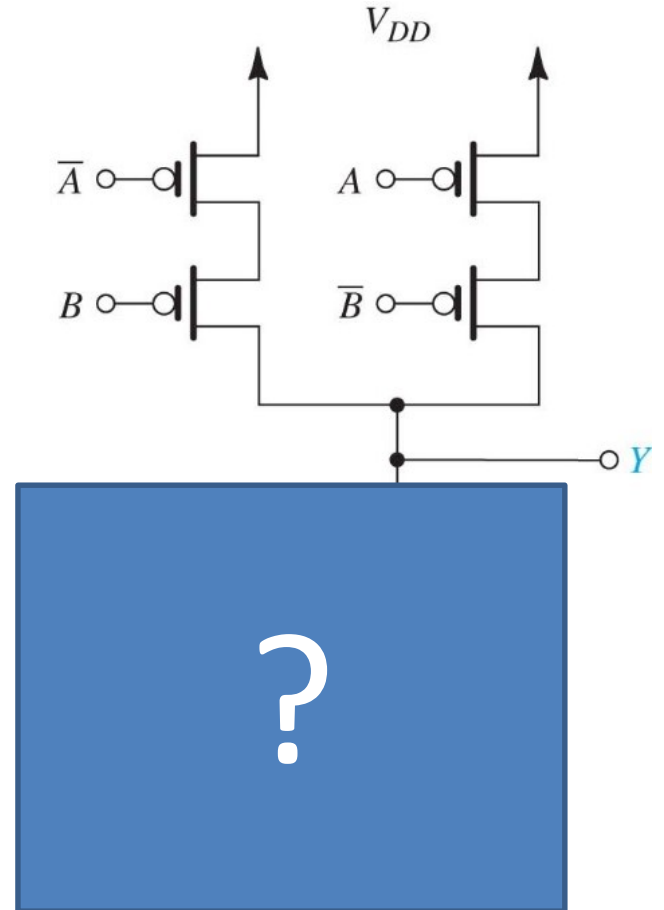

Two-input inclusive OR(A, B) $\sim \max(A, B)$, whereas exclusive XOR(A, B) $\sim \text{mod}(A + B, 2)$.

Synthesis by Complementary Expressions: Two Input XOR Gate



- Logic (boolean) XOR function

- Inputs, $\{A, B\}$

$$A, B \in \{0, 1\}$$

- Output, Y

$$Y = A\bar{B} + \bar{A}B = AB + \bar{A}\bar{B} = \begin{cases} 1, & (A \neq B) \\ 0, & \text{otherwise} \end{cases}$$

- CMOS XOR gate

- PUN, $Y = A\bar{B} + \bar{A}B$


- Parallel branches with series devices

- PDN, $\bar{Y} = AB + \bar{A}\bar{B}$


- Parallel branches with series devices

- Auxiliary logic

- Inverters for complemented variables

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

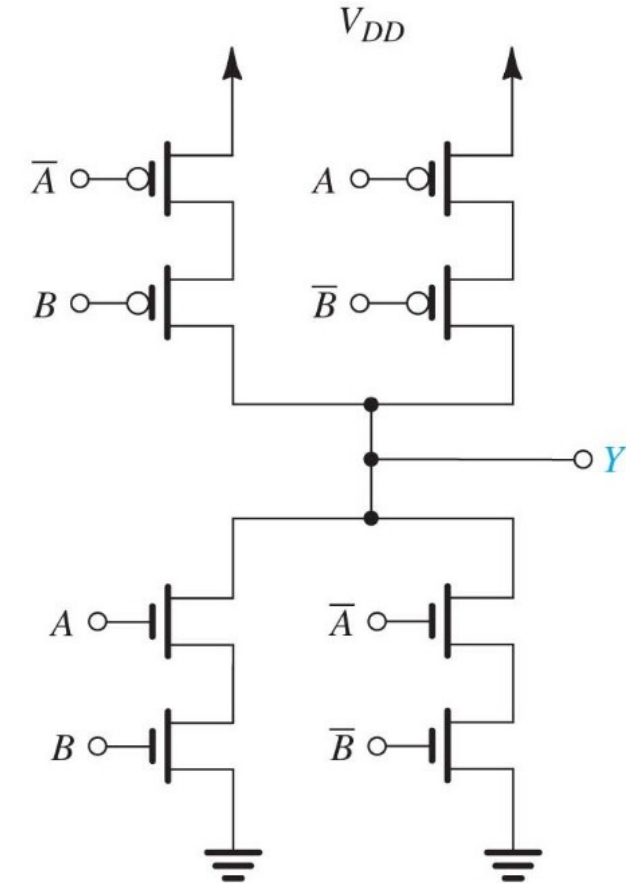


**PDN is not the dual of the PUN;
gate design is not unique.**

BREAK

 

CMOS Inverter

- Two complementary MOS switches between ground and supply
 - High off resistance (open switch)
 - Small on resistance (closed switch)
- Ideal characteristics
 - Full range output swing
 - $0 = V_{OL} < v_O < V_{OH} = V_{DD}$
 - Discrete switch at midpoint
 - $V_{IL} = V_{IH} = V_M = \frac{V_{DD}}{2}$
 - High output for low input level
 - $v_I < V_{IL} \Rightarrow v_O = V_{OH} = V_{DD}$
 - Low output for high input level
 - $v_I > V_{IH} \Rightarrow v_O = V_{OL} = 0$

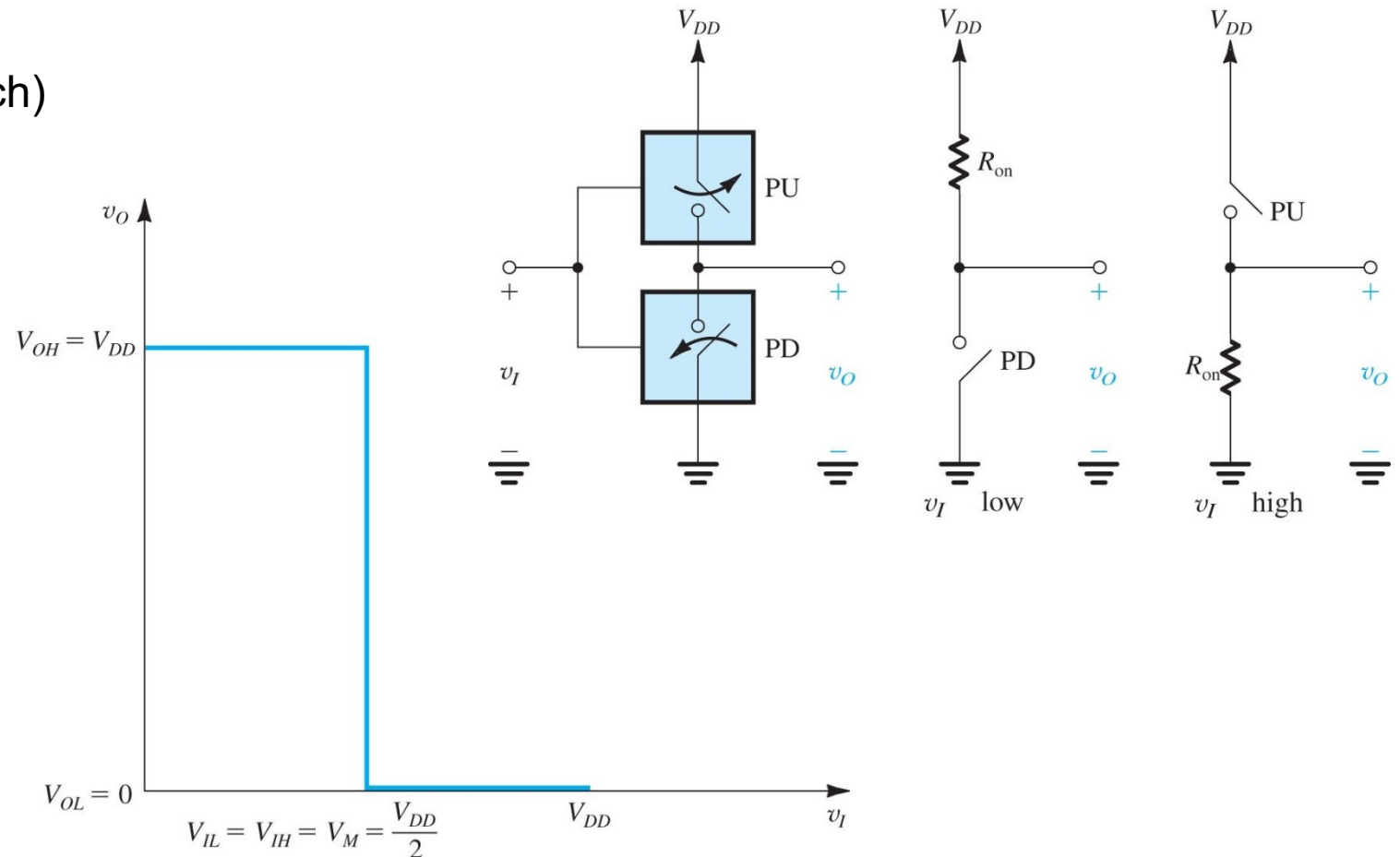


Inverter VTC

- Simplified characteristics
 - Reduced output range
 - Off state leakage
 - Midpoint smeared
 - Output resistance due to MOSFET channel length modulation
 - PUN triode operation just below output midpoint
 - PDN triode operation just above output midpoint
- Noise margins (to intrinsic switching region)
 - High output state

$$NM_H = V_{OH} - V_{IH}$$

- Low output state

$$NM_L = V_{IL} - V_{OL}$$

 




CMOS Inverter: High Input

- Inverter with high input voltage, investigated through “load line”
 - QN triode, QP cutoff
 - Low output voltage
- QP resistance, $R_P = r_{OP} \approx \infty$
- QN resistance, $R_N = r_{DSN}$

$$i_{DN} = k'_n \left(\frac{W}{L}\right)_n \left(v_{OV} - \frac{1}{2}v_{DSN}\right)v_{DSN}(1 + \lambda v_{DSN})$$

$$\approx \{v_{DSN} \ll 2v_{OV}\} \approx k'_n \left(\frac{W}{L}\right)_n v_{OV}v_{DSN}$$
   
$$\Rightarrow r_{DSN} = \frac{\partial v_{DSN}}{\partial i_{DN}} \approx 1/k'_n \left(\frac{W}{L}\right)_n v_{OV}$$





CMOS Inverter: Low Input

- Inverter with low input voltage, investigated through “load line”
 - QN cutoff, QP triode
 - High output voltage
- QN resistance, $R_N = r_{ON} \approx \infty$
- QP resistance, $R_P = r_{DSP}$

$$i_{DP} = k'_p \left(\frac{W}{L}\right)_p \left(v_{OV} - \frac{1}{2}v_{DSP}\right)v_{DSP}(1 + \lambda v_{DSP})$$



$$\approx \{v_{DSP} \ll 2v_{OV}\} \approx k'_p \left(\frac{W}{L}\right)_p v_{OV}v_{DSP}$$
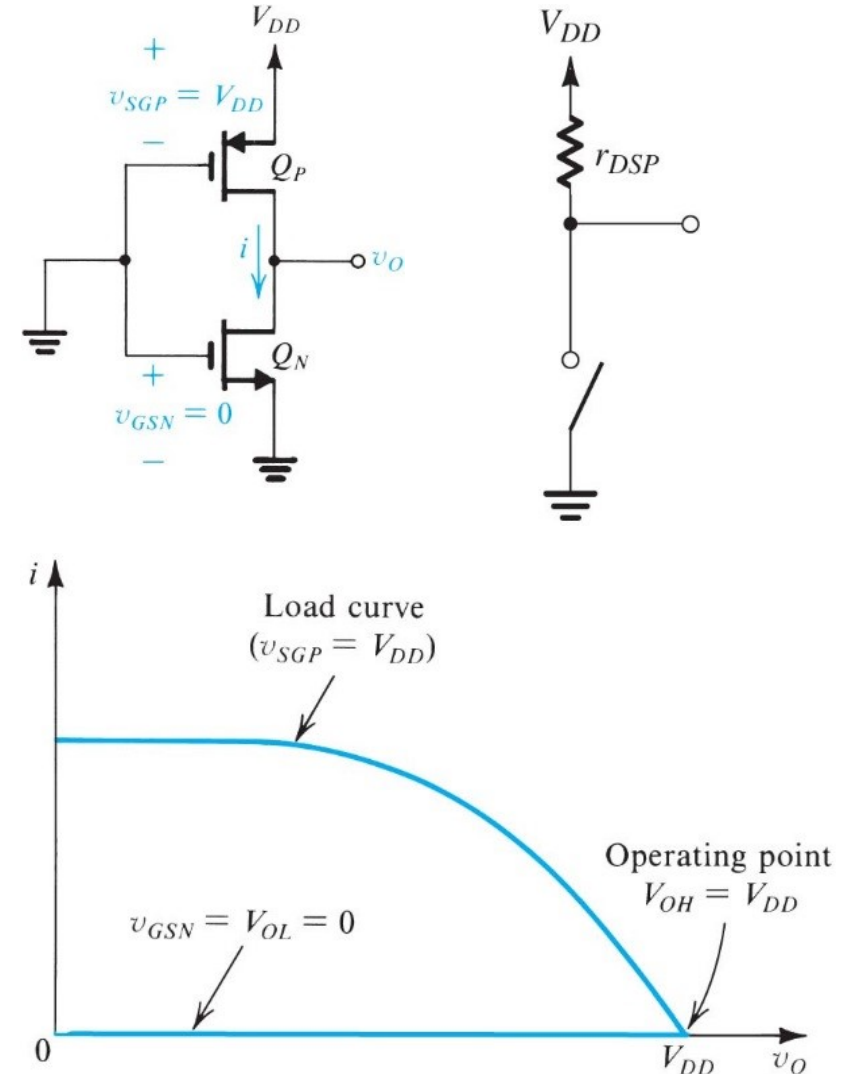 
$$\Rightarrow r_{DSP} = \frac{\partial v_{DSP}}{\partial i_{DP}} \approx 1/k'_p \left(\frac{W}{L}\right)_p v_{OV}$$



Detailed CMOS Inverter VTC for Matched Devices

  - Voltage transfer characteristics for input starting low, going high
 - Low input/ high output
 - QN cutoff, QP zero bias
 - Passing threshold for QN
 - QN saturation, QP triode
 - Steep drop at midpoint
 - QN and QP saturation, (neglecting channel length modulation)
 - Passing midpoint
 - QN triode, QP saturation
 - Passing threshold for QP
 - QN zero bias, QP cutoff
 - High input/ low output




Matched devices assumed, i.e. equivalent NMOS and PMOS characteristics.

What is the effect of circuit capacitance on the inverter step response?




Think, think, think.

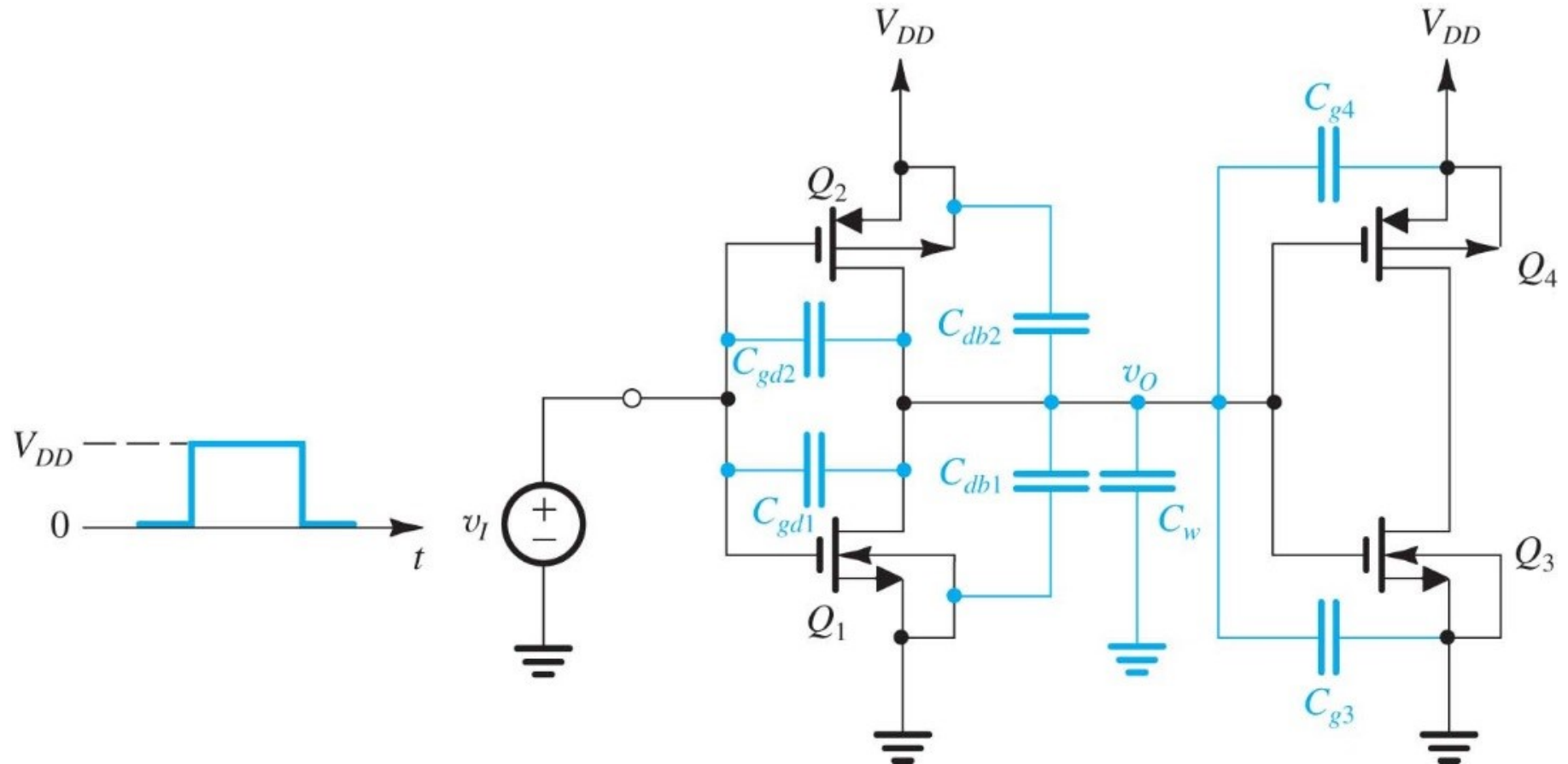

Propagation Delay: Equivalent Circuits

 - Effective capacitance at output node, C , and equivalent MOSFET resistance, R , sourcing/ sinking current I




- Input low, going high
 - Output capacitance discharges from high to low through QN

$$I\Delta t = \Delta Q = C\Delta V$$

$$y(t) = Y_{\infty} - (Y_{\infty} - Y_{0+}) \exp\left(-\frac{t}{\tau}\right), \quad \tau = RC$$

 - Input high, going low
 - Output capacitance charges from low to high through QP



- Generalised step response of single time constant (STC) network

Propagation Delay and Maximum Switching Frequency



- Effective inverter transition time constant, τ

$$\tau = RC$$

- Propagation delay, t_p

$$t_p = \frac{1}{2}(t_{PLH} + t_{PHL}) = \frac{\ln 2}{2}(\tau_{PLH} + \tau_{PLH})$$




$$t_{PHL} \approx \frac{CV_{DD}}{2i_{DN}}, \quad t_{PLH} \approx \frac{CV_{DD}}{2i_{DP}}$$

- Minimum switching period, T_{min}

$$T_{min} = t_{PLH} + t_{PHL} = 2t_p$$

- Maximum switching frequency, f_{max}
   
$$f_{max} = \frac{1}{T_{min}} = \frac{1}{2t_p}$$



Propagation delay defined from start to output midpoint.

Equivalent Capacitance at Inverter Output

- Large signal equivalent capacitance at output, C
 - Contributions from input and load inverter

$$C \approx 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_w$$


- Gate-drain capacitance of input stage, C_{gdx}
 - Miller feedback

$$\Delta v_O = K \Delta v_I = -1 \Delta v_I \Rightarrow (1 - K) = 2$$

- Drain-body capacitance of input stage, C_{dbx}

- Wiring capacitance between stages, C_w

- Gate capacitance of load stage, C_{gx}

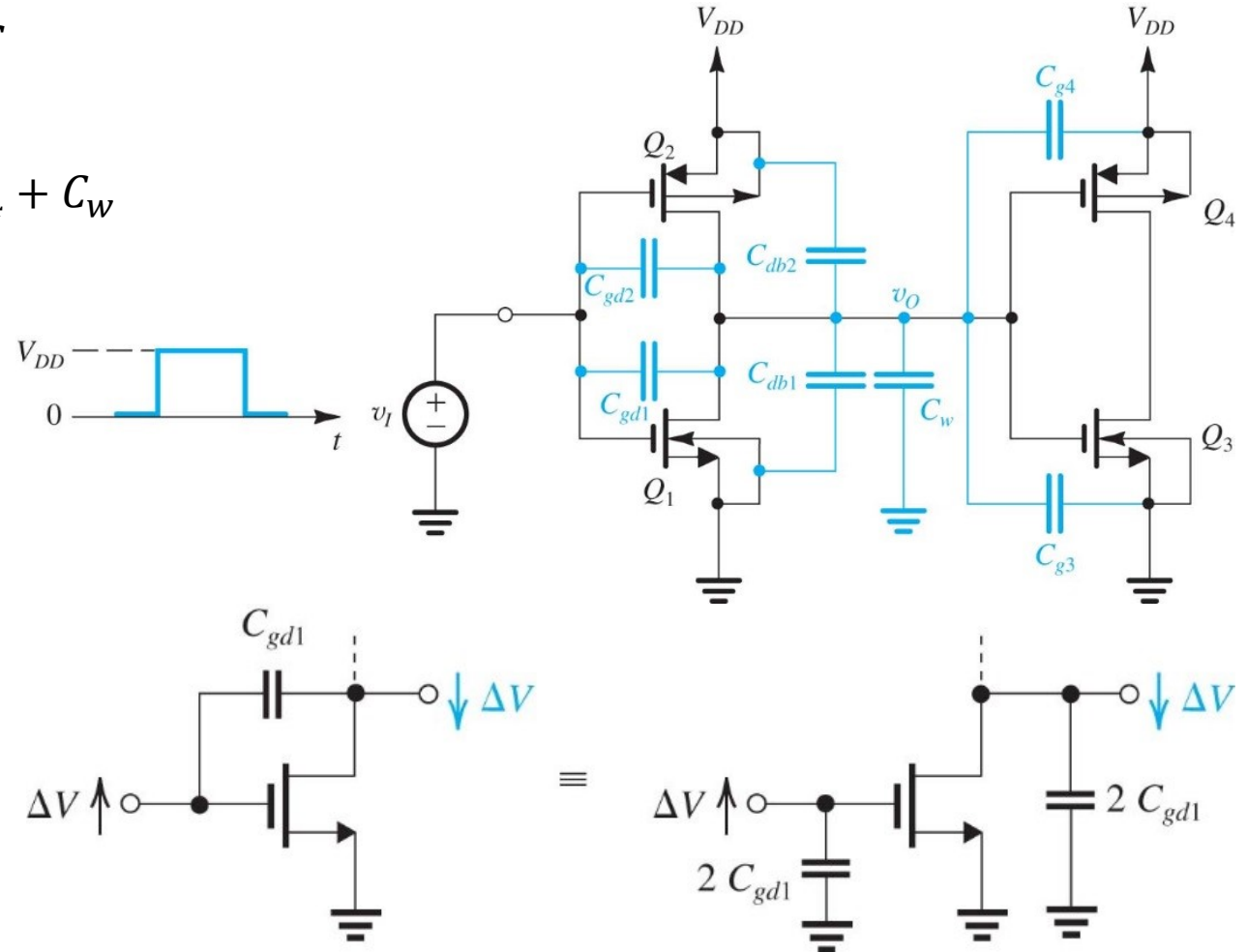

Static and Dynamic Power Dissipation



- Static power dissipation, P_{static}
 - No connection between supply and ground
 - No (or quite small) static power dissipation





$$P_{static} = V_{DD}i_{static} \approx 0$$

- Dynamic power dissipation, $P_D = P_{dynamic} + P_{leakage}$
 - Repeated output node charge/ discharge cycles through PUN/ PDN equivalent resistances

$$P_{dynamic} = f(E_{PLH} + E_{PHL}) = fCV_{DD}^2 = f\left(\frac{1}{2}CV_{DD}^2 + \frac{1}{2}CV_{DD}^2\right)$$

- Small direct leakage current from supply to ground through PUN and PDN, peaking at midpoint (often negligible)
    
$$P_{leakage} = f \int_0^T V_{DD}i_{leakage}(t) \partial t \ll P_{dyn}, \quad T = \frac{1}{f}$$



Power Delay Product and Energy Delay Product

- Dynamic power, P_D , of inverter operated at frequency, f

$$P_D \approx fCV_{DD}^2$$

- Propagation delay, t_P , at frequency, f



$$t_P \approx \frac{1}{2f}$$

- Power delay product, PDP, is a logic technology figure of merit (should be small)

$$PDP = R_D t_P \approx \frac{1}{2} CV_{DD}^2$$

- Energy delay product, EDP, is a logic design figure of merit (should be small)
  
$$EDP = \{\text{energy} \times \text{time per transition}\} = PDP \times t_P$$



Power delay product can be physically interpreted as average energy dissipation per inverter transition.