

# F14 – Memory Circuits

## Outline

- Combinatorial vs. sequential logic circuits
- Analogue multivibrator circuits
- Noise in digital circuits
- CMOS latch
- CMOS SR flip flop
- 6T SRAM cell
- 1T DRAM cell
- Memory column-row-block organisation
- Memory peripheral circuits
  - Sense amplifiers, (address decoders, clocks, etc.)

## Reading Guide

*Sedra/Smith 7ed int*

- Chapter 14.4 (bistable multivibrators)
- Chapter 17.1-17.4.1 memory cells
- (Chapter 17.4.2-17.6 (address decoders, ROM, image sensor))

## Problems




*Sedra/Smith 7ed int*

- P17.2, 17.4, 17.15, 17.19
   
# Combinatorial vs. Sequential Logic Circuits


- Digital systems require logic gates and memory circuits

- Perform logic operations and save the result
- Store input data until needed in an operation
- ...




- Combinatorial logic circuits (logic gates)

 - Given a specific input, output is always the same





- Sequential logic circuits (memory circuits)

 - Given a specific input, output may depend on history


  
# Analogue Multivibrator Circuits

- Bistable, a.k.a. latch
  - Retains its state until change is triggered
  - A circuit with two stable operating points, e.g. an op amp with positive feedback
- (Astable, a.k.a. function generator)
  - Switches states periodically
  - Self-triggered bistable multivibrator utilising an additional feedback circuit with delay
- (Monostable, a.k.a. pulse generator)
  - Switches state momentarily when triggered
  - A circuit with one stable state and one quasi-stable state that initiates self-triggering at predefined delay



**Bistable circuits exhibit memory functionality, but analogue versions are large and power hungry.**

# Bistable Multivibrator Operation



- Trigger input applied to either of “grounds” in bistable multivibrator circuit

- Toggling output from high to low, using trigger at inverting input

$$v_+ = \beta v_O, \quad v_O = A(v_+ - v_-) \rightarrow L_{\pm}$$

$$v_- = v_I < v_+, \quad v_+ = \beta v_O = \beta A(v_+ - v_-) \rightarrow \beta L_+$$
  
$$v_I > \beta L_+ \Rightarrow v_+ - v_- < 0 \Rightarrow v_O = L_- \Rightarrow v_+ = \beta L_-$$



**Trigger input point determines if characteristic is inverting or non-inverting.**

# Noise Sources

- Power supply noise due to switching logic gates, output stages, etc.

- Thermal noise(/ hot electron noise)

- Carrier energy fluctuations due to temperature(/ apparent temperature)

$$S_{v,Thermal}(\omega) = \frac{\overline{v^2}}{\Delta f} = 4kTR \Leftrightarrow S_{v,Thermal}(\omega) = \frac{\overline{i^2}}{\Delta f} = 4kTG$$

- Shot noise

- Carrier fluctuations due to MOSFET gate tunnelling

$$S_{i,Shot}(\omega) = \frac{\overline{i^2}}{\Delta f} = 2qI_G$$

- Burst noise




- Carrier fluctuations due to MOSFET channel interaction with a trap with a time constant

$$S_{i,Burst}(\omega) = \frac{\overline{i^2}}{\Delta f} = k_{Burst} \frac{I_D}{1 + (\omega\tau)^2}$$

- Flicker noise


- Carrier fluctuations due to MOSFET channel interaction with multiple traps with evenly distributed time constants
   
$$S_{i,Flicker}(\omega) = \frac{\overline{i^2}}{\Delta f} = k_{Flicker} \frac{I_D}{f}$$




 
# Basic CMOS Latch

- Latch (bistable multivibrator) circuit
  - Retains its own output signal by means of positive feedback
- Basic CMOS latch
  - Two inverters in positive feedback loop
  - Inverted output fed back to input of the same inverter
  - Three possible operating points
    - Low/ high
    - Midpoint
    - High/ low



$W$	$X = Y$	$Z$
0	1	0
1	0	1

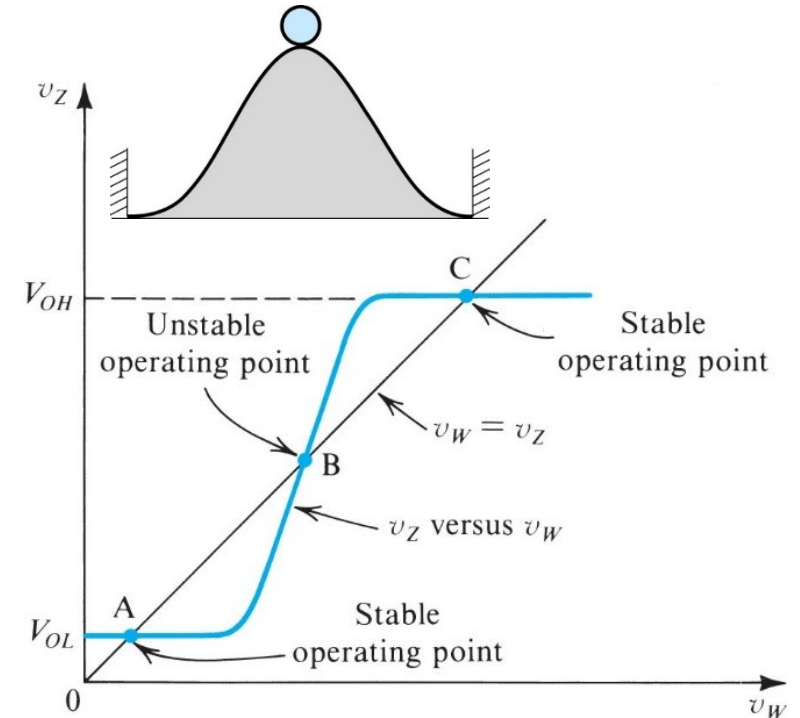
 


**Latch provides volatile memory, requiring power supply for data storage, at minimal static power.**



  
# Basic Latch Operation

- Three possible operating points
  - A: Low/ high
  - B: Midpoint (unstable)
  - C: High/ low
- Operation at slight offset above(/ below) B will initiate regenerative latch process towards A(/ C)
- Inverter butterfly diagram can be used to illustrate operation points and noise margins



# Two inverters in a loop yields latched output, but what about three inverters?

---

 

Think, think, think.



## Two Input NOR Gate (recap)

- Logic (boolean) NOT-OR compound function

- Inputs,  $\{A, B\}$

$$A, B \in \{0, 1\}$$

- Output,  $Y$

$$Y = \overline{A + B} = \overline{A} \overline{B} = \begin{cases} 1, & (A = 0, B = 0) \\ 0, & \text{otherwise} \end{cases}$$


- CMOS NOR gate

- PUN,  $Y = \overline{A} \overline{B}$


- One series branch with all inputs

- PDN,  $\overline{Y} = A + B$

- One parallel branch for each input

 

A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

 

**Inclusive OR function, dissimilar from exclusive XOR function.**



# Set/ Reset (SR) Flip Flop

- SR flip flop: latch with trigger inputs
  - Two NOR gates in latch configuration allow set/ reset trigger operations

- Storage mode
  - $R$  and  $S$  low, i.e.  $\bar{R}\bar{S}$ , preserves latched output


$$Q_{n+1} = \text{NOR}(\bar{R}, \bar{Q}_n) = Q_n, \quad \bar{Q}_{n+1} = \text{NOR}(\bar{S}, Q_n) = \bar{Q}_n$$

- Set operation
  - $R$  low,  $S$  high yields  $Q$  forced high

$$\bar{Q}_{n+1} = \text{NOR}(S, Q_n) = 0 \Rightarrow Q_{n+1} = 1$$

- Reset operation
  - $R$  high,  $S$  low yields  $Q$  forced low
 
$$Q_{n+1} = \text{NOR}(R, \bar{Q}_n) = 0$$




$R$	$S$	$Q_{n+1}$	$\bar{Q}_{n+1}$
0	0	$Q_n$	$\bar{Q}_n$
0	1	1	0
1	0	0	1
1	1	Not used	Not used

**Complementary SR flip flop using NAND gates is also possible, etc.**


 
# Clocked SR Flip Flop

- Inverter latch with clocked set/ reset inputs
  - Clock,  $\phi$ , form AND functions with respective trigger inputs,  $S$  and  $R$ 
    - Trigger inputs ignored when clock is low,  $\bar{\phi}$
  - Clock and trigger inputs use NMOS transistors only
- Requirements for set operation
  - Q5-Q6 sink enough current to pull  $\bar{Q}$  below threshold of Q3-Q4 inverter
  - Set signal remains high long enough to cause regeneration to take over the switching process
- Requirements for reset (parallels set due to symmetry)
  - Q7-Q8 sink ...  $Q$  below threshold... Q1-Q2 inverter
  - Reset signal remains high...



**Superior functionality at same transistor count as SR flip flop: clock low enforces storage mode.**

# Set Operation on Clocked SR Flip Flop: Part I

- Set operation on clocked SR flip flop in reset storage mode

$$v_\phi = V_{DD}, \quad v_S = V_{DD}, \quad v_R = 0 \text{ V}$$

$$Q_n = 0, \quad \overline{Q}_n = 1, \quad \phi S \overline{R} = 1$$

$$\Rightarrow Q_{n+1} = 1, \quad \overline{Q}_{n+1} = 0$$

- Part I: Q5-Q6 must pull  $\overline{Q}_{n+1}$  down past midpoint...



$$v_Q = 0, \quad v_{\overline{Q}} < \frac{V_{DD}}{2} \Rightarrow I_{D2} < I_{D5} = I_{D6} \approx I_{Deq} \Big|_{\frac{1}{2} \left( \frac{W}{L} \right)_{5,6}}$$

$$I_{D2} = I_{Deq} = i_{Dx} \left( |V_{GS}| = V_{DD}, |V_{DS}| = \frac{V_{DD}}{2} \right)$$

$$i_{Dx} = k'_x \left( \frac{W}{L} \right)_x \left[ V_{DD} - V_{tx} - \frac{1}{2} \left( \frac{V_{DD}}{2} \right) \right] \left( \frac{V_{DD}}{2} \right)$$

$$\Rightarrow \left( \frac{W}{L} \right)_{5,6} > 2 \frac{k'_p}{k'_n} \left( \frac{W}{L} \right)_2$$

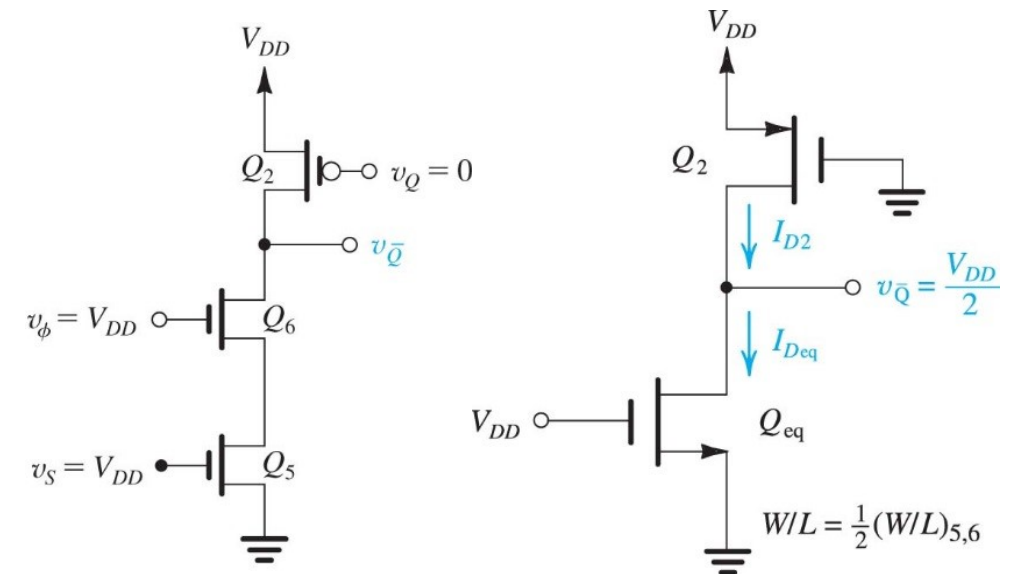 - Part II: ... and hold at least until latch responds



**Reset operation parallels that of set operation.**

## Set Operation on Clocked SR Flip Flop: Part II

- Set operation on clocked SR flip flop in reset storage mode

$$v_\phi = V_{DD}, \quad v_S = V_{DD}, \quad v_R = 0 \text{ V}$$

$$Q_n = 0, \quad \overline{Q}_n = 1, \quad \phi S \overline{R} = 1 \\ \Rightarrow Q_{n+1} = 1, \quad \overline{Q}_{n+1} = 0$$

- Part I: Q5-Q6 must pull  $\overline{Q}_{n+1}$  down past midpoint...


- Part II: ... and hold at least until latch responds

- Flip...

$$v_Q = 0, \quad v_{\overline{Q}} = V_{DD} \rightarrow \frac{V_{DD}}{2} \Rightarrow t_{PHL}(Q_{eq}-Q_2) = \frac{CV_{DD}}{2I_{PHL}}$$

- ... flop
 
$$v_{\overline{Q}} \approx 0, \quad v_Q = V_{DD} \rightarrow \frac{V_{DD}}{2} \Rightarrow t_{PLH}(Q_3-Q_4) = \frac{CV_{DD}}{2I_{PLH}}$$



$$T_{min} = t_{PHL}(Q_{eq}-Q_2) + t_{PLH}(Q_3-Q_4)$$


$$I_{PHL} \approx i_{Deq} \Big|_{t=0} = \frac{1}{2} k'_n \left( \frac{W}{L} \right)_{eq} (V_{DD} - V_{tn})^2$$

$$I_{PLH} \approx i_{D4} \Big|_{t=t_{PHL}} = \frac{1}{2} k'_p \left( \frac{W}{L} \right)_4 (V_{DD} - |V_{tp}|)^2$$

**Reset operation parallels that of set operation.**


# BREAK

---

 
 
# 6T Static Random Access Memory (SRAM) Cell

- Simplified implementation of the CMOS clocked SR flip flop
  - CMOS inverter latch
    - Q1-Q2 and Q3-Q4
  - Set/ reset and output are all provided through clocked access transistors (cf. pass transistor logic)
    - Q5 and Q6
- Storage mode,  $\bar{\phi}$
- Reset operation,  $\phi\bar{S}\bar{R}$
- Set operation,  $\phi S\bar{R}$
- Read operation,  $\phi$ 
  - Must be controlled to not accidentally set or reset the 6T cell




**This is the industry standard volatile static memory cell.**
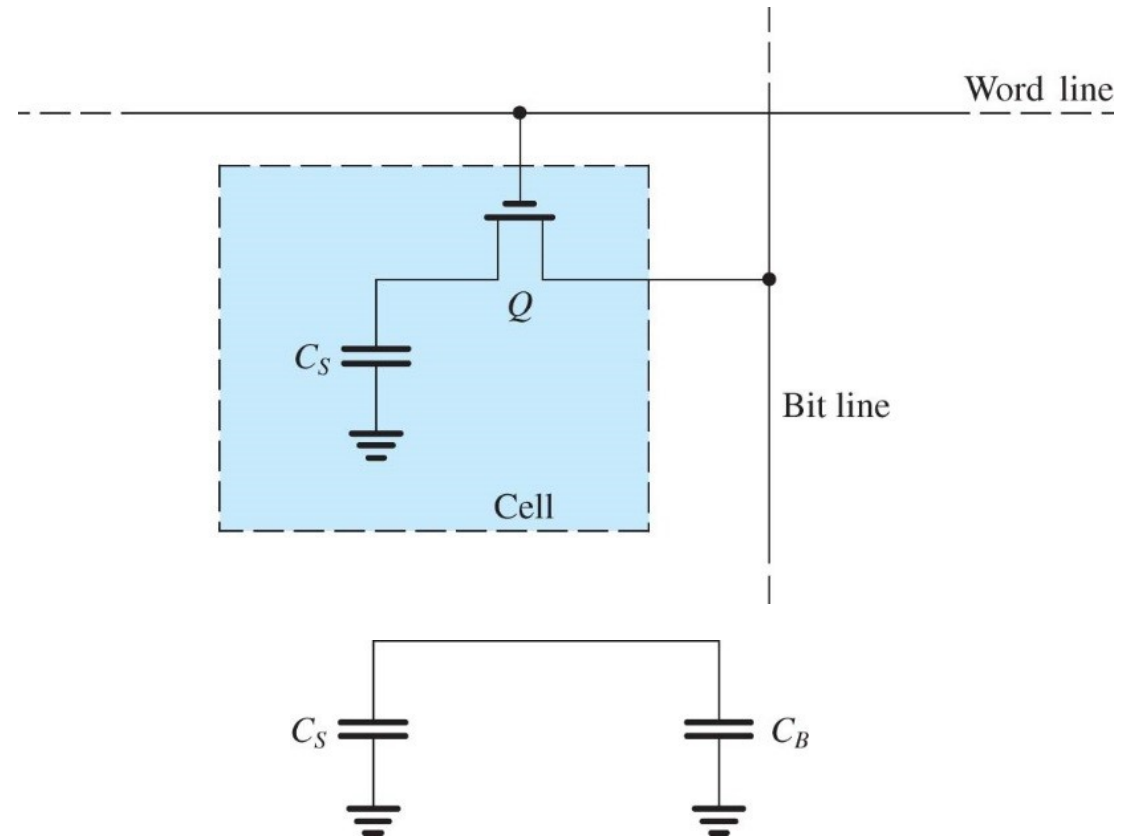
# 1T Dynamic RAM (DRAM) Cell

- One single access transistor
- Storage capacitor
  - Logic 0: not charged
  - Logic 1: charged
- Read operation exchanges charges with bit line
- Leakage demands periodic refresh
- Word line boost required to charge storage capacitor to full supply voltage

$$v_{OV} = v_W - v_{C_S} - V_{tn} \Rightarrow v_W = V_{DD} + V_{tn}$$




**1T is dynamic, requiring periodic refresh on millisecond time scale.**




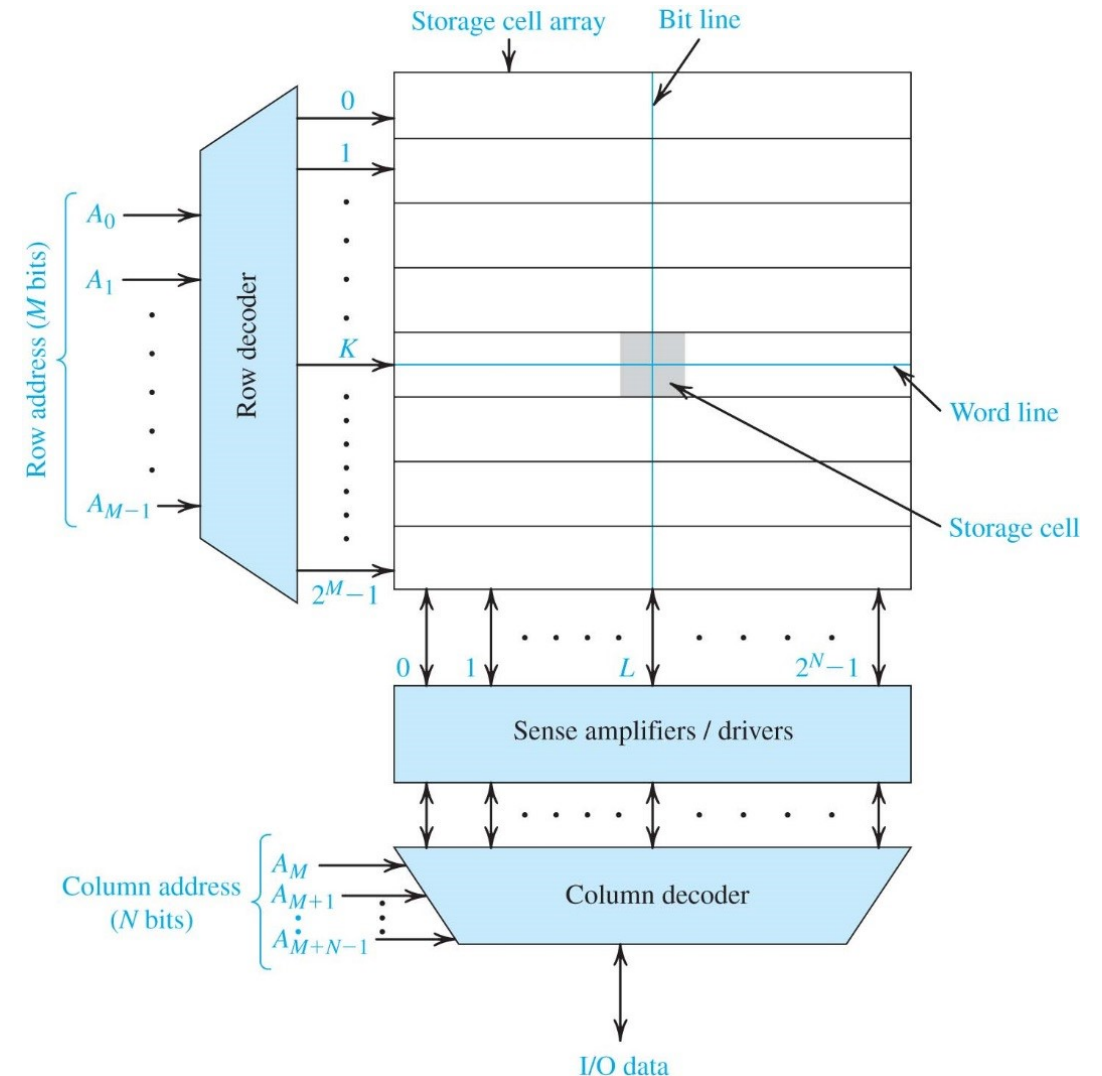
# Memory Chip Column-Row-Block Organisation

- Memory organisation needed to (time/ energy) efficiently read or write data in a controlled fashion
  - Matrix minimizes bit and word line RC time constant
    - Bits stored in columns
    - Words in rows (across columns)
  - Several blocks required for large memories
- Memory peripheral circuits
  - Row and column address decoders, built from combinatorial logic circuits
  - Precharge and equalisation for differential bit line preconditioning
  - Sense amplifiers read data from memory cells
  - Drivers write data into memory cells


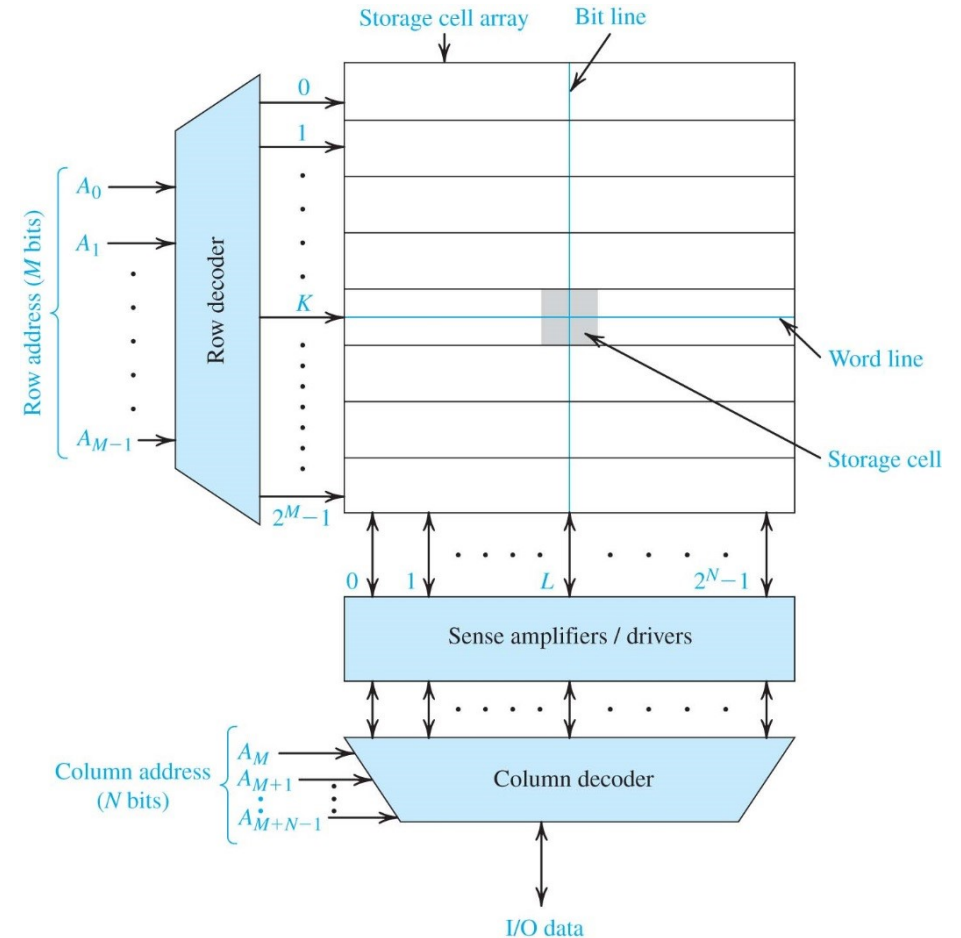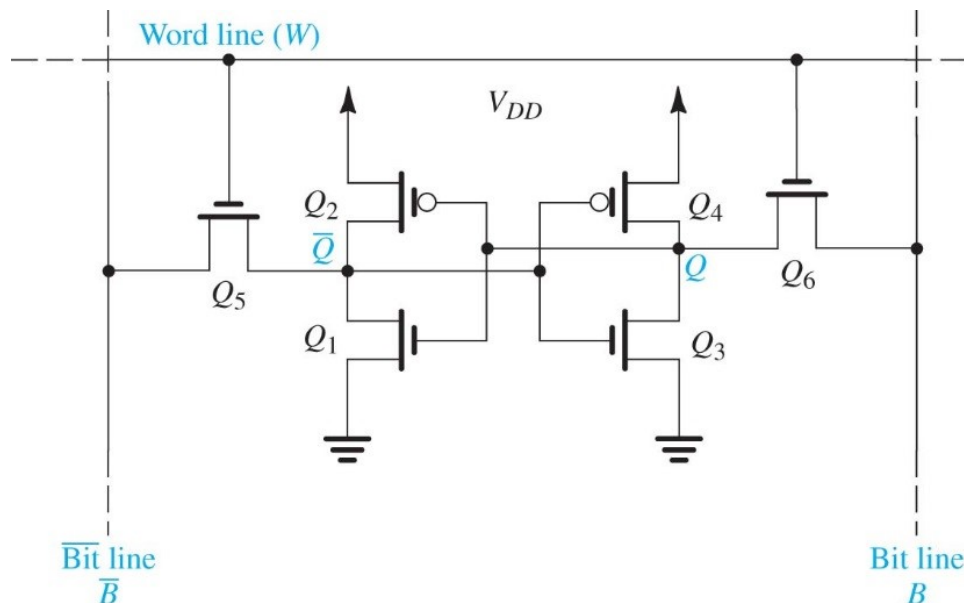
# 6T SRAM Cells in a Memory Block



- Row address lets row decoder activate all access transistors in a specific row
- Column address lets column decoder operate on a pair of complementary bit lines
  - Read to or write from I/O data bus



**Memory cycle time is on nanosecond time scale, limited by word line RC and sense response.**
 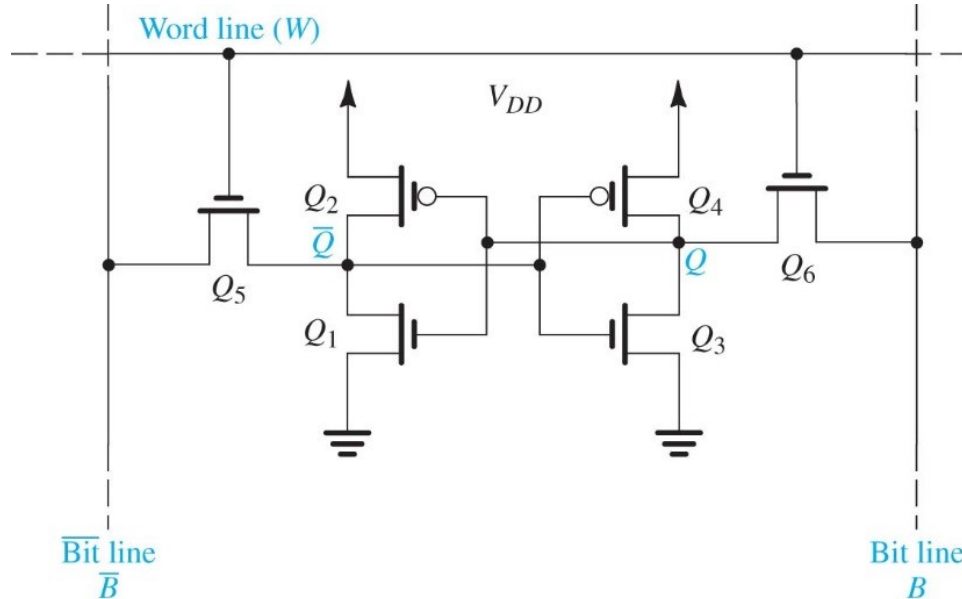
# 6T SRAM Cell Operation Conditions

- Read and write functionality through access transistors
- Read operation must not shift the logic level more than a threshold voltage from stored value
- Write operation must toggle the logic level to within a threshold voltage of new value





# 6T SRAM Cell: Reading a Stored Logic 1

- Initial data and bit lines precharged to supply voltage

$$V_{\bar{Q}_n} = 0 \text{ V}, \quad V_{Q_n} = V_{DD}, \quad v_{\bar{B}}|_{t=0} = V_{DD}, \quad v_B|_{t=0} = V_{DD}$$

- Non-destructive read 1 operation

$$v_{\bar{Q}} < V_{\bar{Q}_n} + V_{tn} = V_{tn}$$

$$\frac{V_{\bar{Q}}}{V_{DD} - V_{tn}} = 1 - 1 / \sqrt{1 + \frac{(W/L)_5}{(W/L)_1}}$$

$$\frac{(W/L)_{a:5}}{(W/L)_{n:1}} < 1 / \left( \frac{V_{tn}}{V_{DD} - V_{tn}} \right)^2 - 1$$



$$\Delta Q = I_5 \Delta t = C_{\bar{B}} \Delta V \quad C_{\bar{B}} \gg C_{\bar{Q}}$$

$$\Rightarrow v_{\bar{B}} = V_{DD} - \Delta V$$

$$\Delta V = \frac{I_5 \Delta t}{C_{\bar{B}}} \Leftrightarrow \Delta t = \frac{C_{\bar{B}} \Delta V}{I_5}$$

$$I_5 = \frac{1}{2} k'_n \left( \frac{W}{L} \right)_5 (V_{DD} - V_{\bar{Q}} - V_{tn})^2$$
  
$$I_1 = k'_n \left( \frac{W}{L} \right)_1 \left( V_{DD} - V_{tn} - \frac{1}{2} V_{\bar{Q}} \right) V_{\bar{Q}}$$



**Read must not shift data more than a threshold voltage.**

# 6T SRAM Cell: Writing a Logic 0 Over a Logic 1

- Initial data and bit lines precharged to new data

$$V_{\overline{Q_n}} = 0 \text{ V}, \quad V_{Q_n} = V_{DD}, \quad v_{\overline{B}} \Big|_{t=0} = V_{DD}, \quad v_B \Big|_{t=0} = 0 \text{ V}$$

- Successful 1 through 0 toggling

$$v_Q < V_{Q_{n+1}} + V_{tn} = V_{tn}$$

$$\frac{V_Q}{V_{DD} - V_{tn}} = 1 - \sqrt{1 + \frac{k'_p(W/L)_4}{k'_n(W/L)_6}}$$

$$\frac{(W/L)_{p:4}}{(W/L)_{a:6}} < \frac{k'_n}{k'_p} \left[ 1 - \left( 1 - \frac{V_{tx}}{V_{DD} - V_{tx}} \right)^2 \right]$$



$$\Delta Q = I_6 \Delta t = C_Q \Delta V \quad C_B \gg C_Q$$

$$\Rightarrow v_Q = V_{DD} - \Delta V$$

$$\Delta V = \frac{I_6 \Delta t}{C_Q} \Leftrightarrow \Delta t = \frac{C_Q \Delta V}{I_6}$$


$$I_4 = \frac{1}{2} k'_p \left( \frac{W}{L} \right)_4 (V_{DD} - |V_{tp}|)^2$$
  
$$I_6 = k'_n \left( \frac{W}{L} \right)_6 \left( V_{DD} - V_{tn} - \frac{1}{2} V_Q \right) V_Q$$





**Write must toggle data to within a threshold voltage.**
 
# How to boost small differential signal from memory cell to logic levels?





Think, think, think.

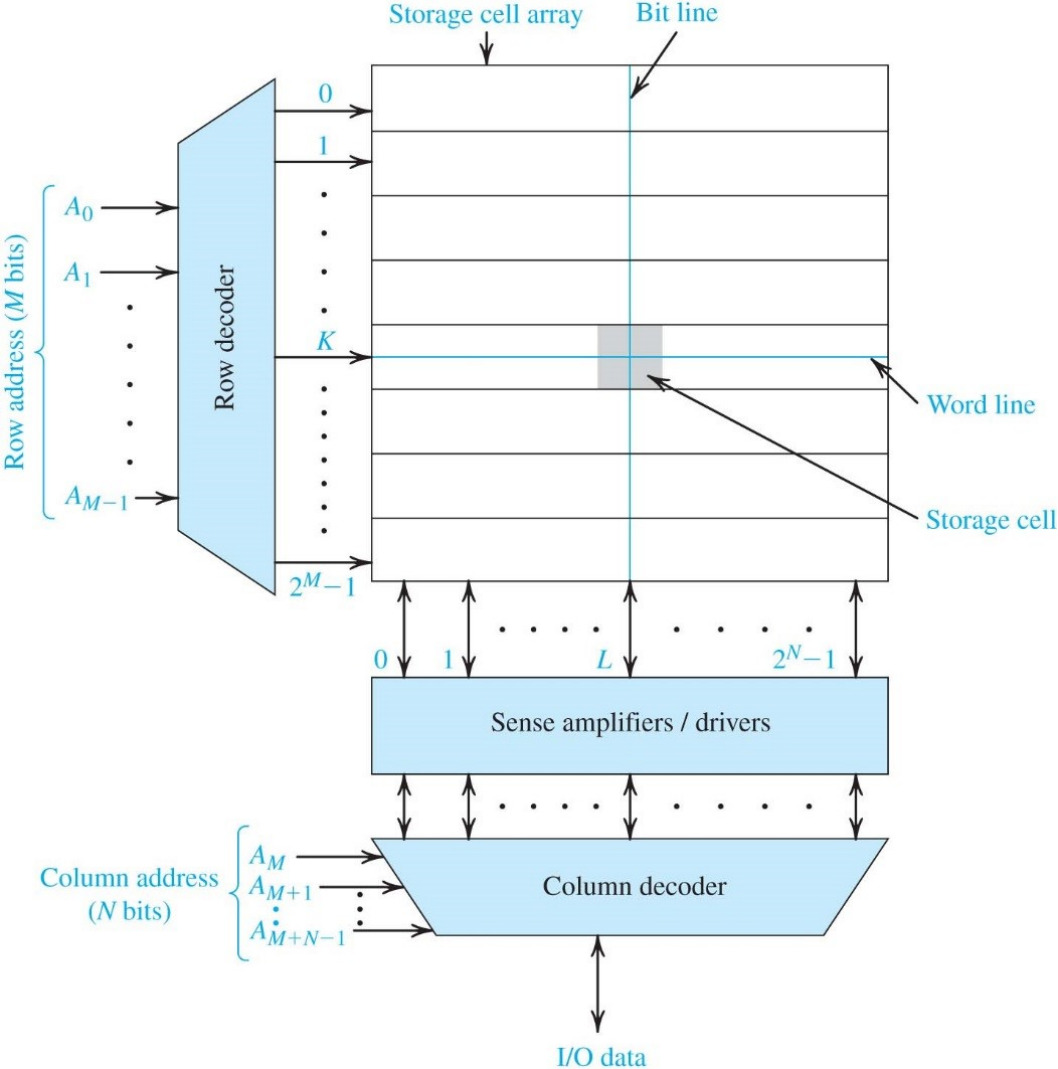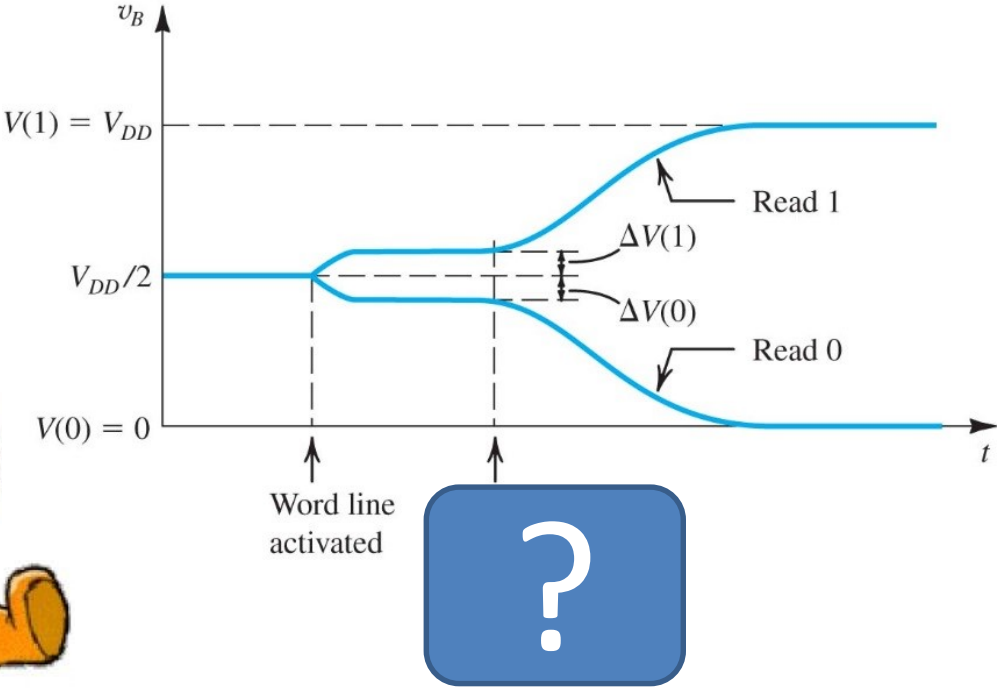

# Clocked Latch as a Differential Sense Amplifier

- Latch with clocked bias between bit lines
  - First, bit lines are precharged/ equalised
  - Then, word line with addressed memory cell is activated
  - Finally, sense amplifier is activated, latching the detected difference towards full logic levels


$$v_B \Big|_{0 < v_B < V_{DD}} \approx \frac{V_{DD}}{2} \pm \Delta V \exp\left(\frac{G_m}{C_B} t\right) = \frac{V_{DD}}{2} \pm \Delta V \exp\left(\frac{g_{mn} + g_{mp}}{C_B} t\right)$$

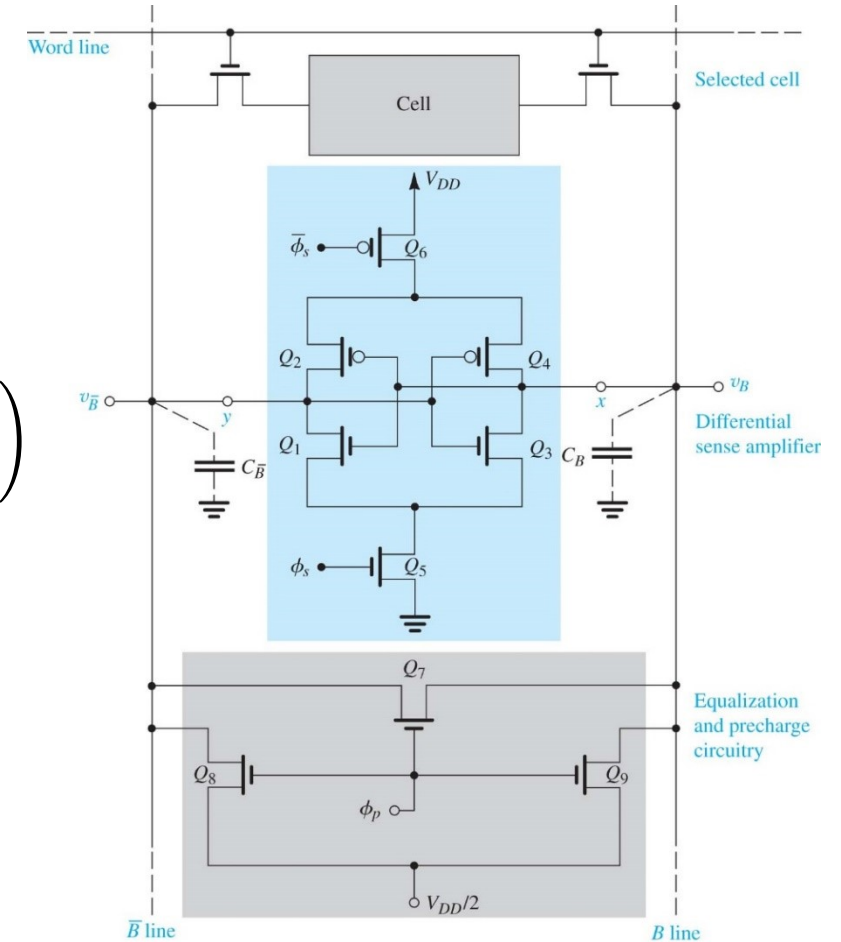 

**Exponential time response, set by latch transistors and bit line parasitics.**
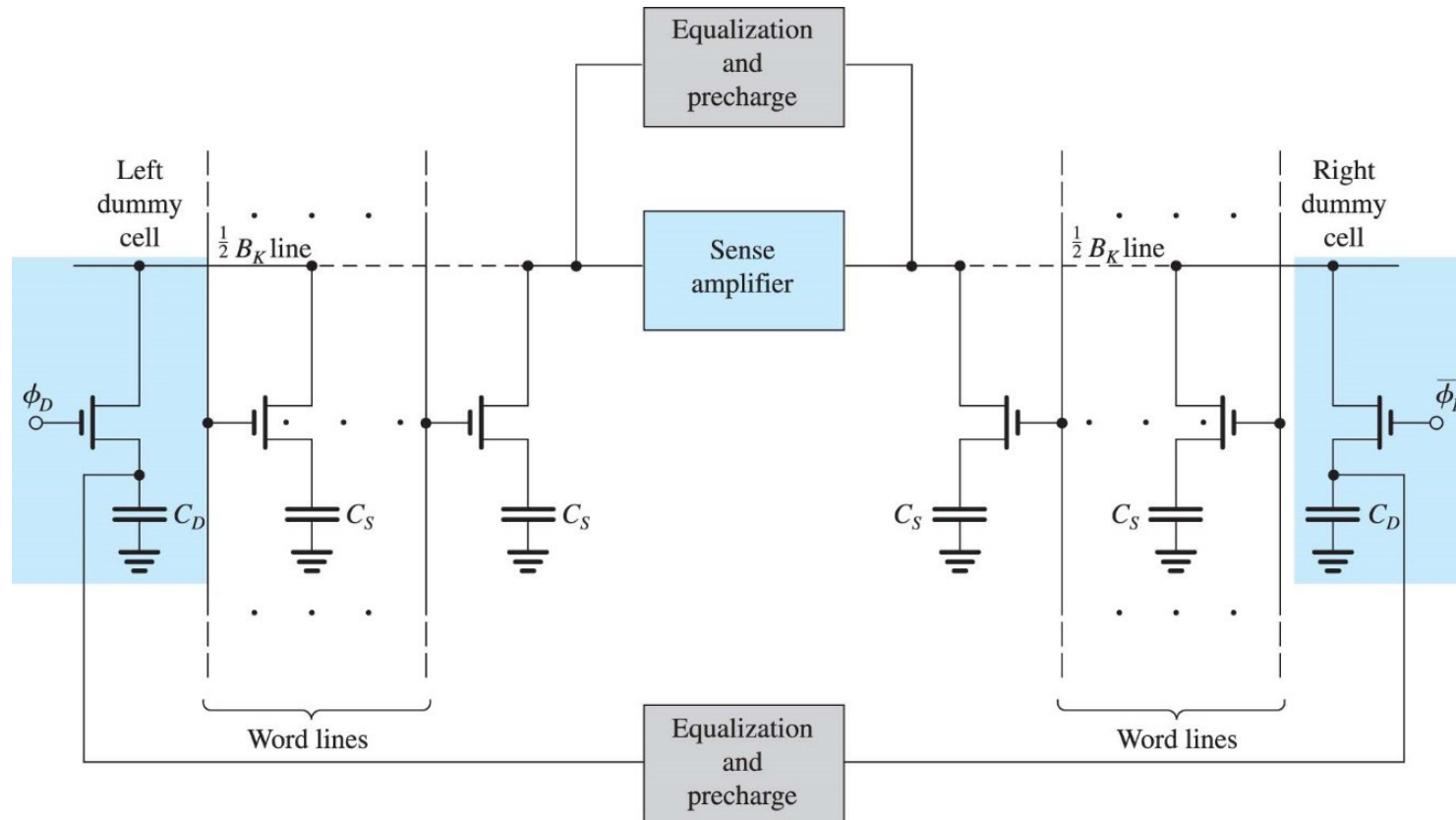
# Dummy Cells for Differential DRAM Operation

- DRAM cells yield single ended output, not compatible with differential sense amplifier/ driver
- Dummy cells at memory block edge used to simulate differential characteristics





# MOS Differential Amplifier as a Sense Amplifier

- MOS differential pair w/ current mirror load
  - Sufficient differential input switches bias current,  $I$ , to one branch

$$\Delta V > \sqrt{2}V_{OV} = \sqrt{\frac{2I}{k'_n \left(\frac{W}{L}\right)_{1,2}}}$$

- Current mirror forces current to/ from output, charging/ discharging its voltage to either logic level within  $\Delta t$

$$\Delta t = \frac{CV_{DD}}{I}$$

- Increased speed costs static power dissipation

$$P = V_{DD}I$$

