

# Bipolar Junction Transistors (BJT)

---

**Ideal Transistor**

**Bipolar Transistor - Terminals**

**NPN Bipolar Transistor Physics**


**Large Signal Model**

**Early Effect**

**Small Signal Model**

Reading: (Sedra, Smith, 7<sup>th</sup> edition)  
4.1 - 4.2  
6.2.2 (small signal model)  
9.2.2 small signal model with capacitances

# Ideal Transistor - characteristics

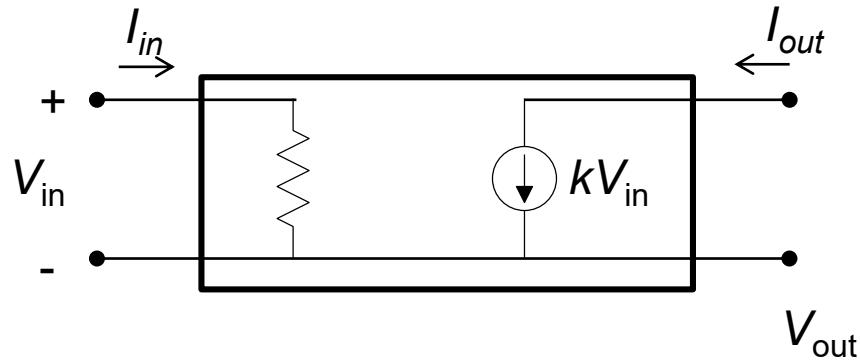

Two main transistor types:


**Bipolar Transistors (Power Amplifiers, High Speed AD/DA converters)**

Field Effect Transistors (99.999% - mainly integrated circuits / digital)

current source controlled by a voltage ( $V_{in}$ )


$I_{out}$

Increasing  $V_{in}$

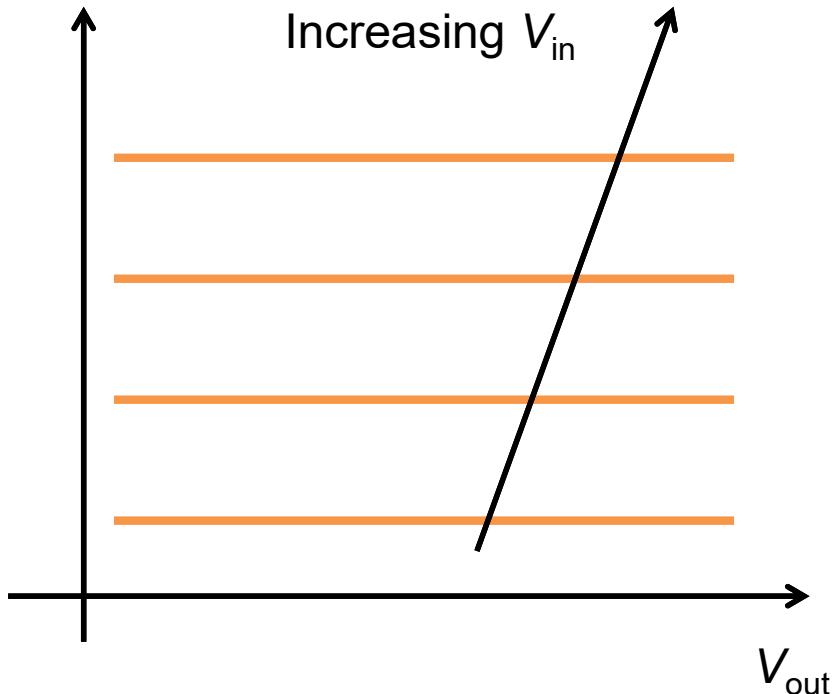

$I_{out}$  independent of  $V_{out}$ !  
 $I_{in}$  independent of  $V_{out}$ !

# Bipolar Transistor - npn

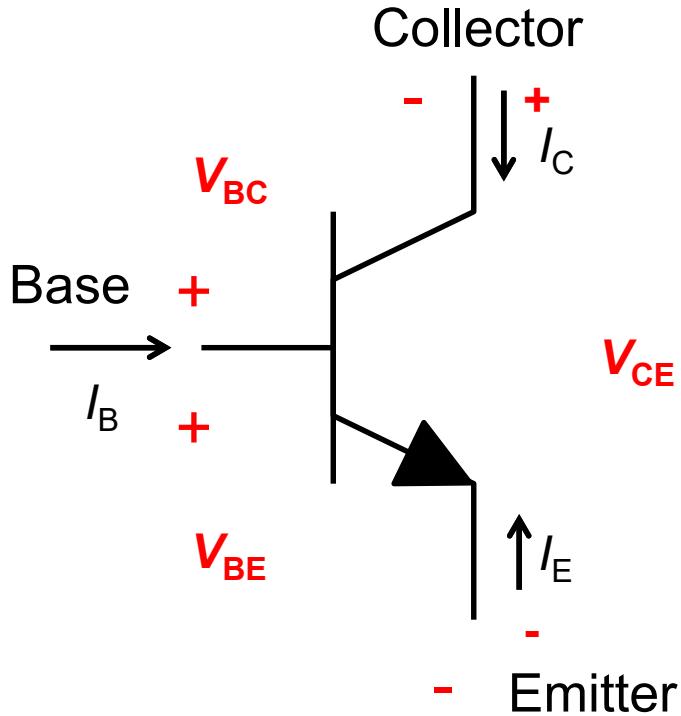


Sign convention:  $V_{xy} = V_x - V_y$

$I_B$  – base current

$I_C$  – collector current

$I_E$  – emitter Current =  $-(I_C + I_B)$
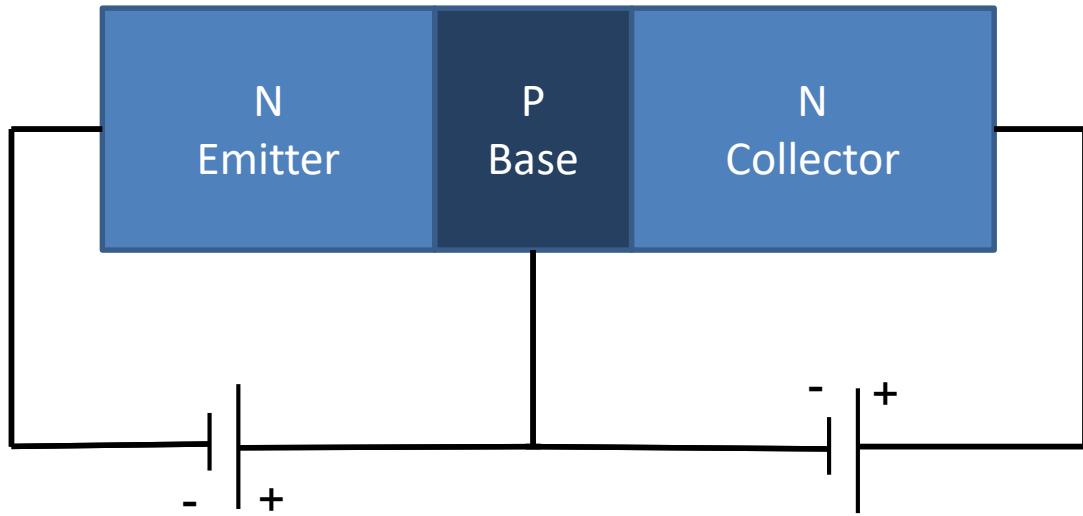
# Bipolar Transistor - npn in active mode




Forward biased PN junction


$$V_{BE} > 0$$

Reverse biased PN junction


$$V_{BC} < 0$$

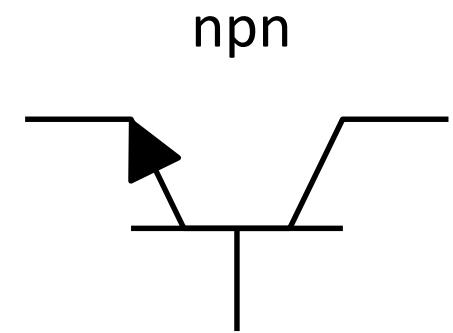


# Bipolar transistor: band structure

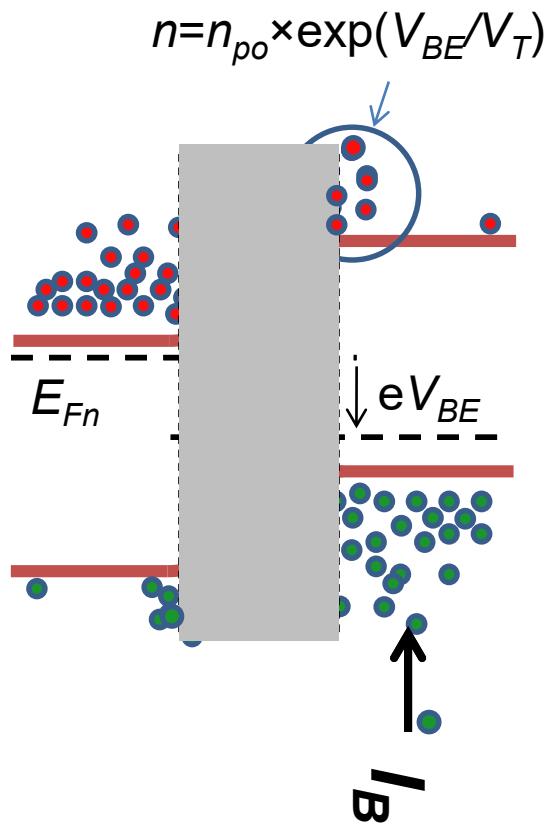

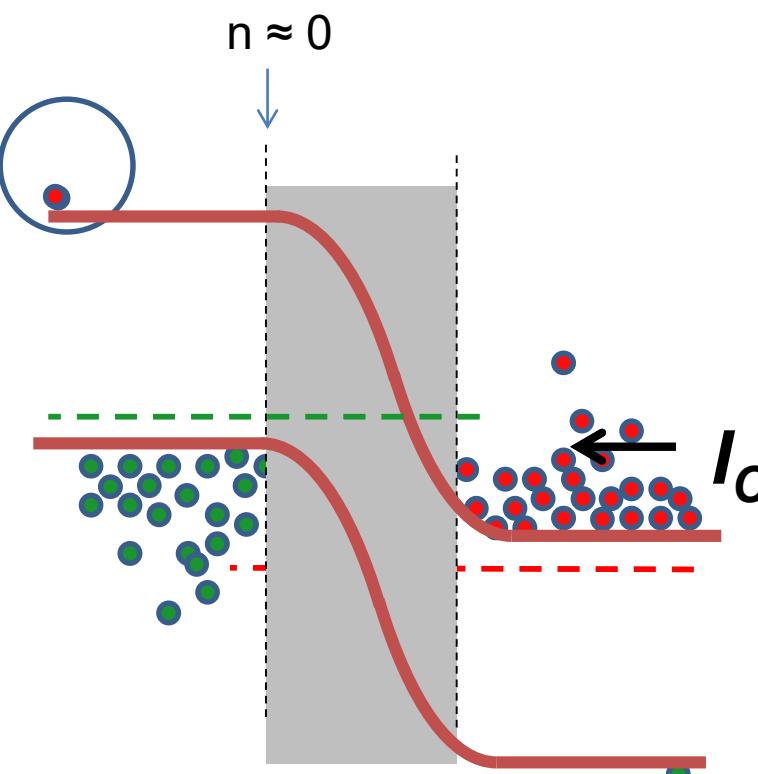Forward biased emitter-base junction injects electrons




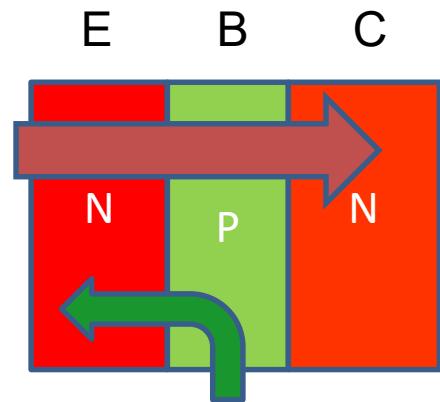Reverse biased base-collector junction sweeps away electrons (independent of  $V_{BC}$ )





# Operating modes

Active  
EBJ: forward / CBJ: reverse

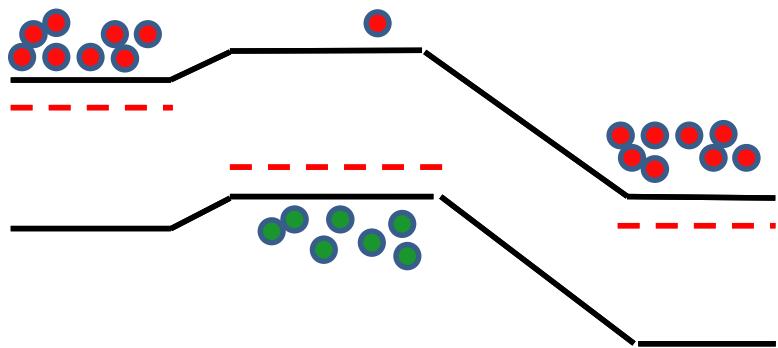

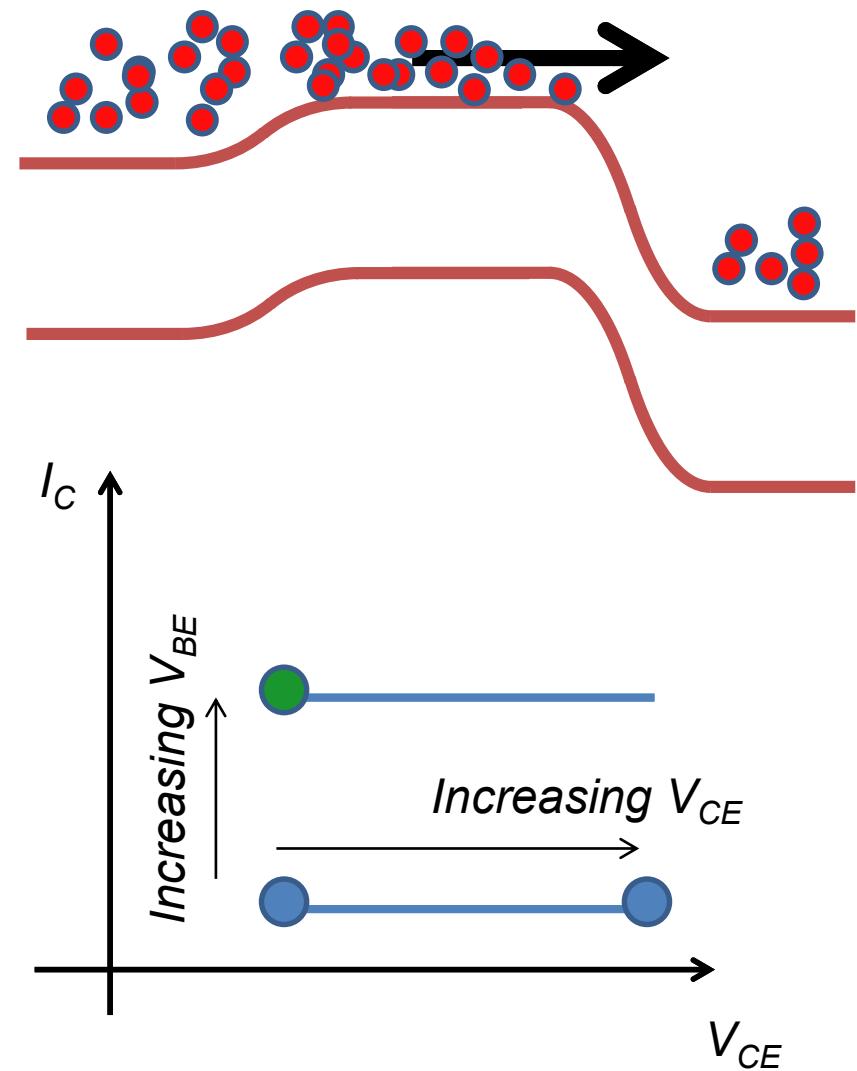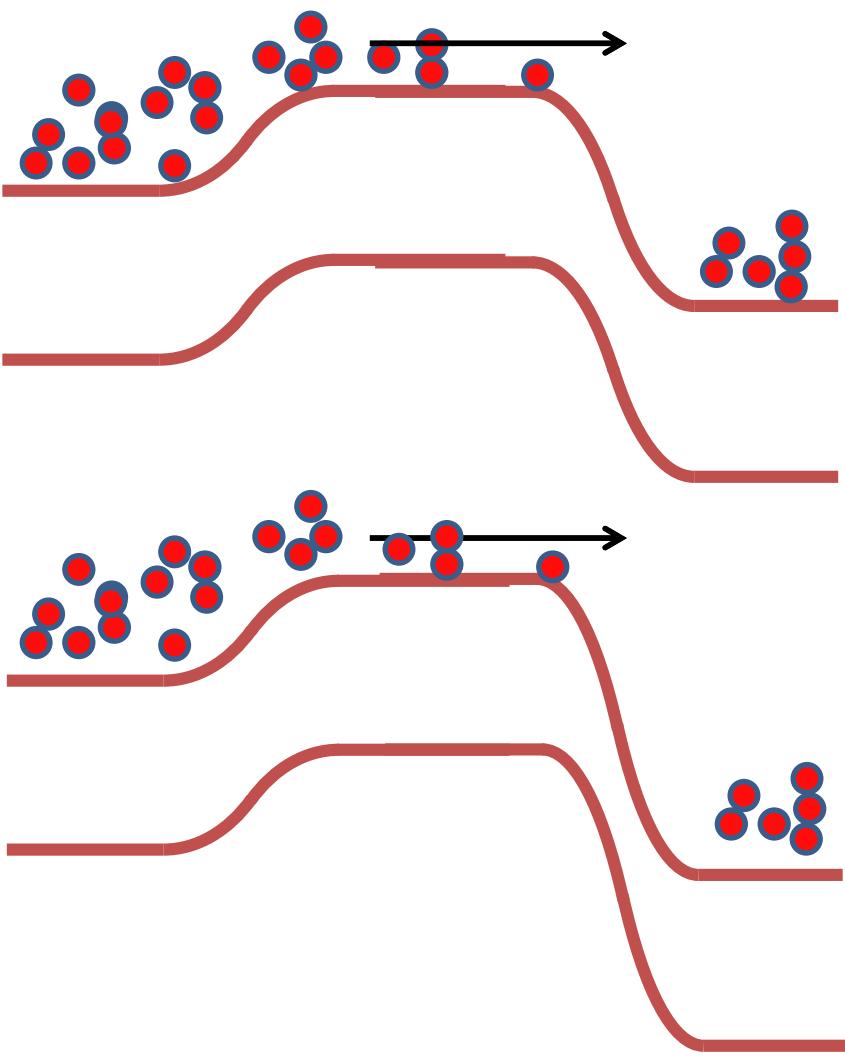
## Electron diffusion currents – active mode



# Currents in active mode

$$I_E + I_{B1} + I_{B2} + I_C = 0$$

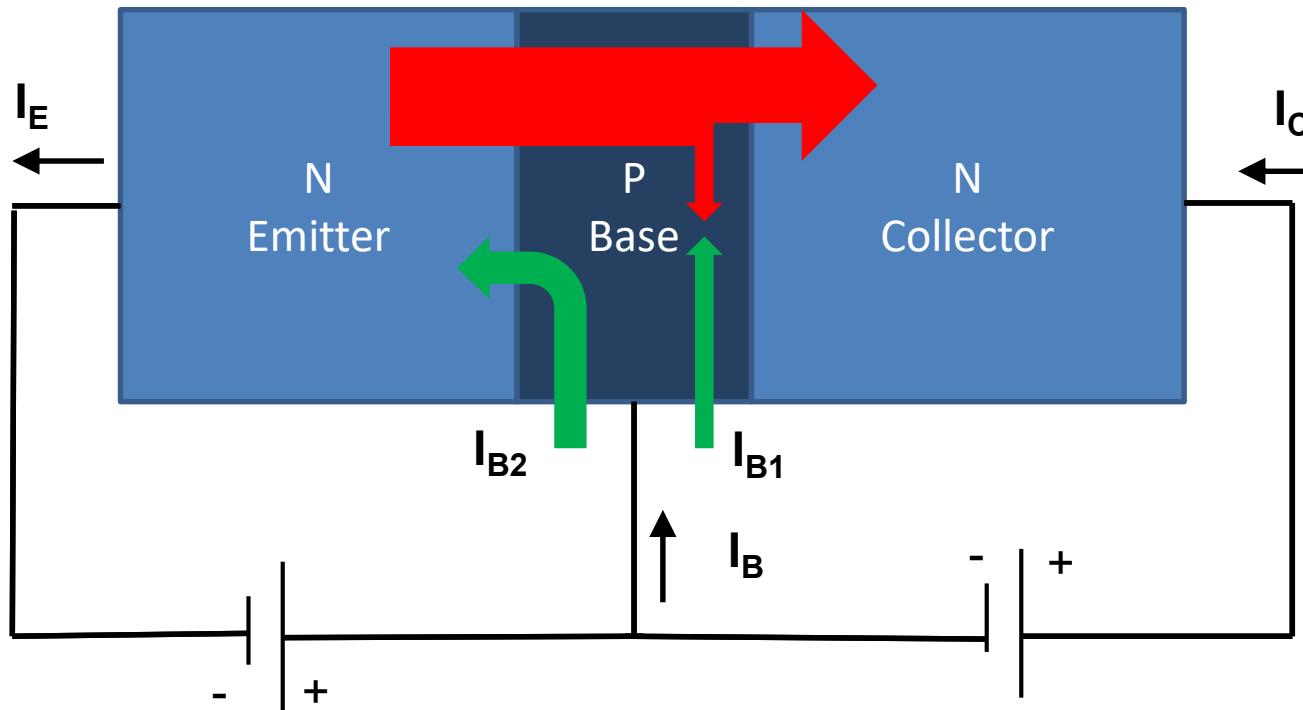


$$V_{BE} > 0$$

$$V_{BC} < 0$$

**On whiteboard:** calculate  $I_C$ ,  $I_{B1}$ ,  $I_{B2}$  and the gain  $\beta$

# Large Signal Model – active mode

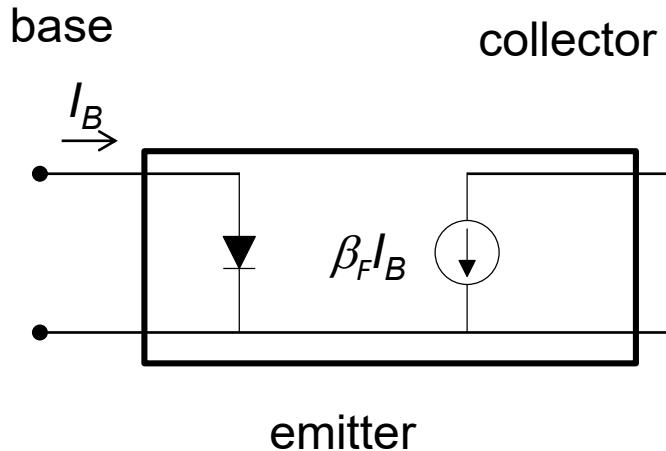


$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$


$$I_B = \frac{I_C}{\beta}$$

$$\begin{aligned} V_{BE} &> 0.6V \\ V_{BC} &< 0.4V \\ V_{CE} &< V_{BR} \end{aligned}$$

$\beta$  : current gain

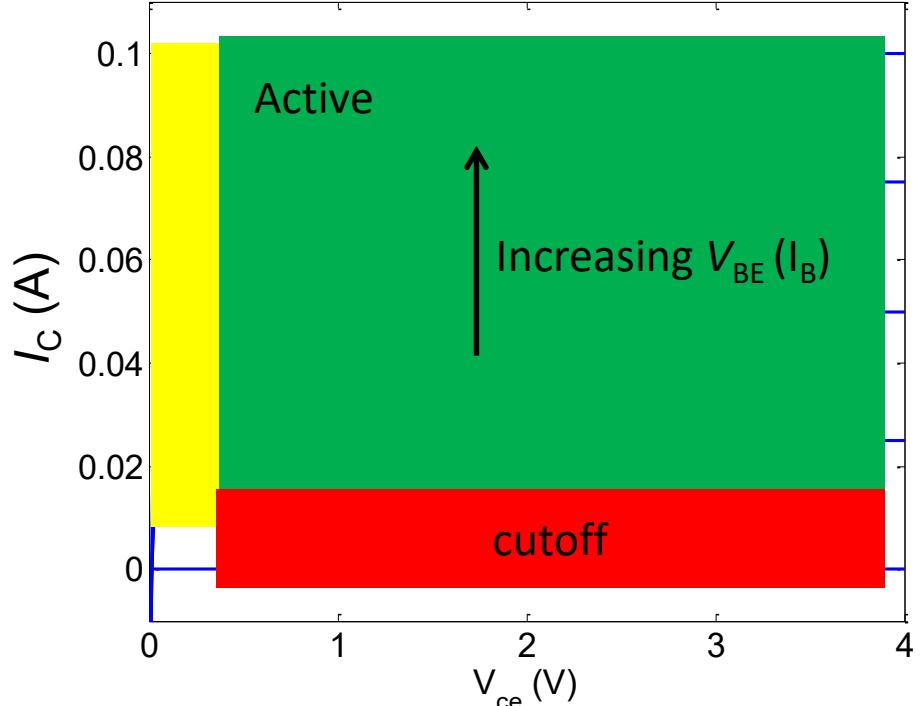

## Example – typical Si NPN Transistor

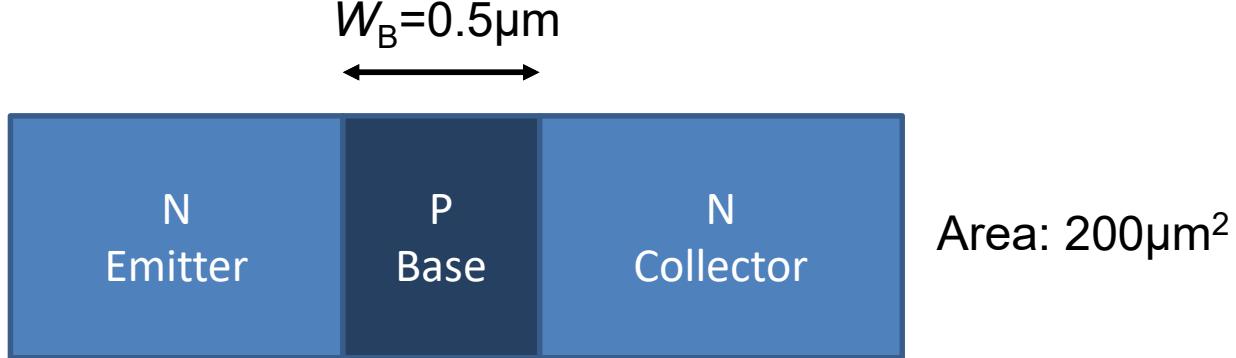

$N_D = 1 \times 10^{19} \text{ cm}^{-3}$  (emitter doping)  
 $D_p = 1 \text{ cm}^2/\text{s}$  (hole diffusion constant)  
 $L_p = 0.5\mu\text{m}$  (diffusion length)


$N_A = 2 \times 10^{17} \text{ cm}^{-3}$  (base doping)  
 $D_n = 15 \text{ cm}^2/\text{s}$  (electron diffusion constant)  
 $\tau_b = 1 \mu\text{s}$  (minority carrier lifetime)

Calculate  $\beta$  and  $I_S$


## 2 min excersise – Early effect (4.2.3)

Ideally  $I_C$  should not increase with  $V_{CE}$ , however the width of a pn-junction depends on applied voltage!

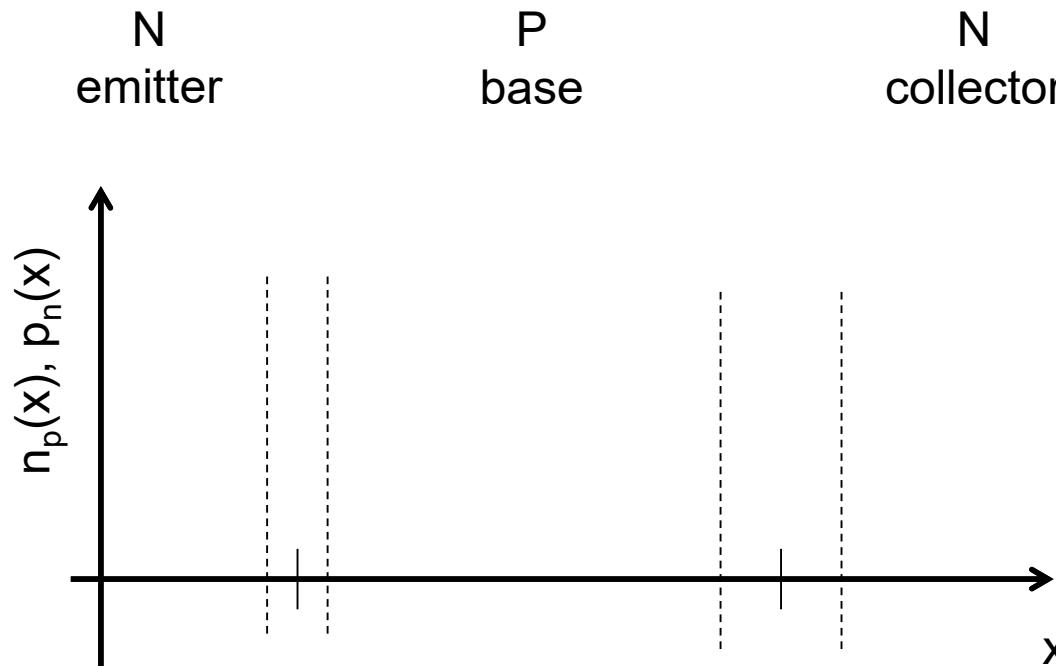1. How does the base-collector depletion region change for increasing  $V_{CE}$ ?
2. Sketch the minority carrier distribution in the base with  $V_{CE}$  applied?
3. How does  $I_C$  change with  $V_{CE}$  in this case?



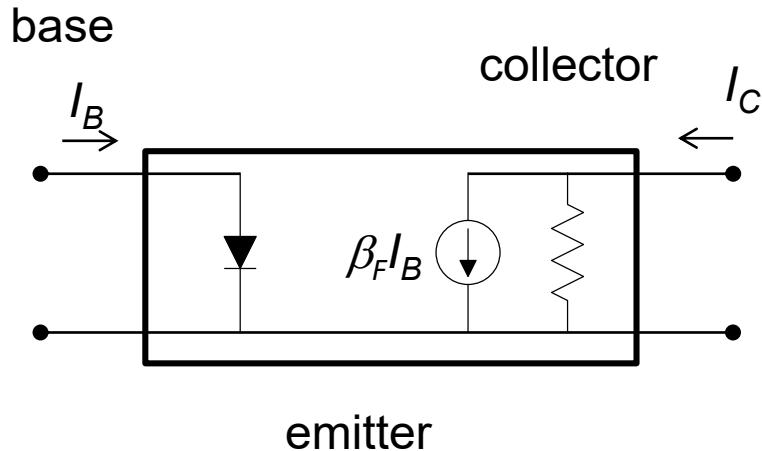
## Large Signal Model – Early Effect (4.2.3)







$$I_C = I_S \left( 1 + \frac{V_{CE}}{V_A} \right) e^{\frac{V_{BE}}{V_T}}$$
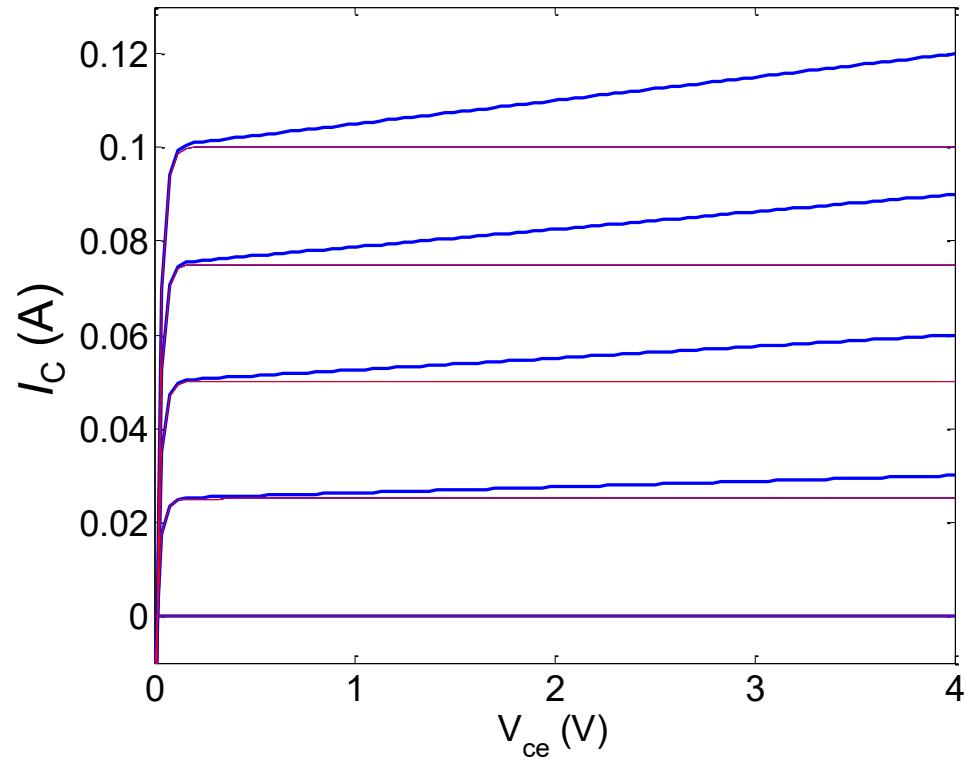
$$I_B = \frac{I_C}{\beta_F} = \frac{I_S \left( 1 + \frac{V_{CE}}{V_A} \right) e^{\frac{V_{BE}}{V_T}}}{\beta_F}$$



$V_A$  – Early voltage  
15-100V

# Small Signals– Taylor Expansion

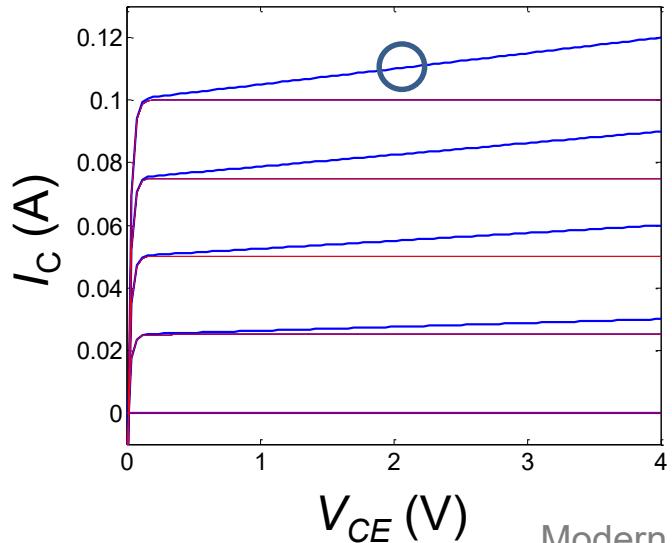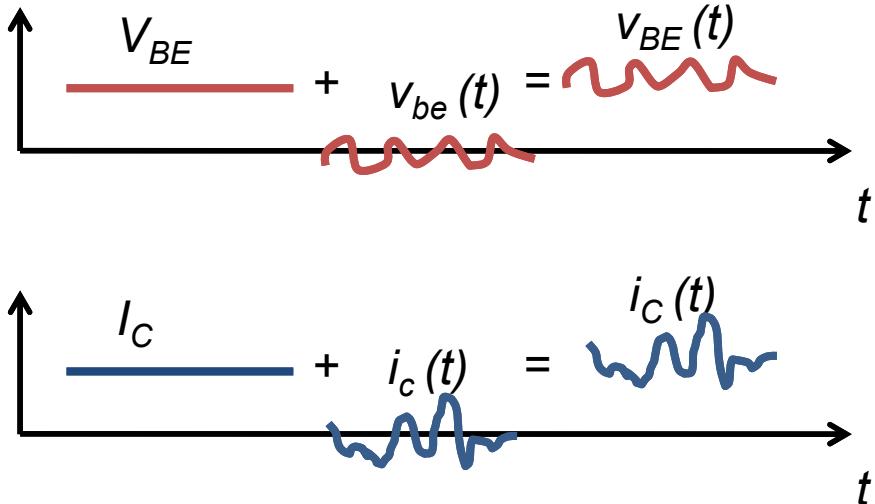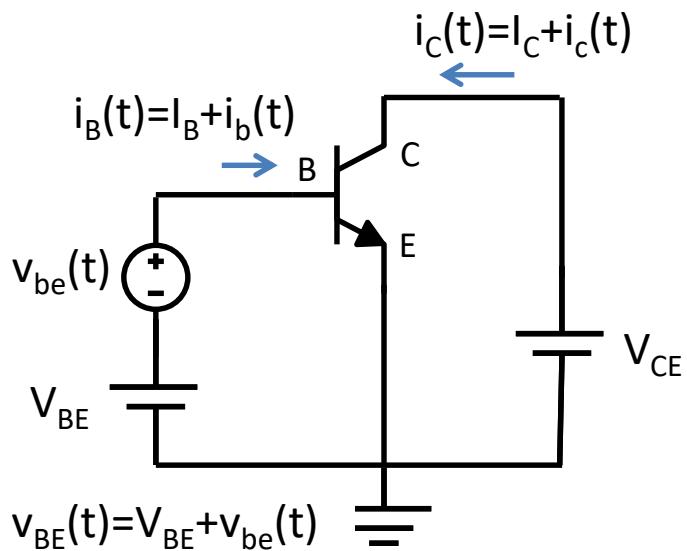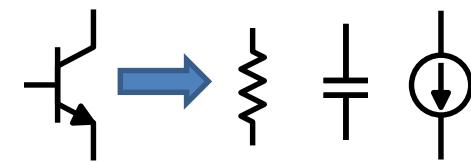



1<sup>st</sup> order Taylor expansion - linearization

$$f(x_0 + \delta x) \approx f(x_0) + \frac{df(x)}{dx} \Big|_{x=x_0} \delta x + \dots$$

$$i_C(V_{BE} + v_{be}) \approx i_C(V_{BE}) + g_m \cdot v_{be}$$

$$i_C(V_{CE} + v_{ce}) \approx i_C(V_{CE}) + \frac{1}{r_0} \cdot v_{ce}$$
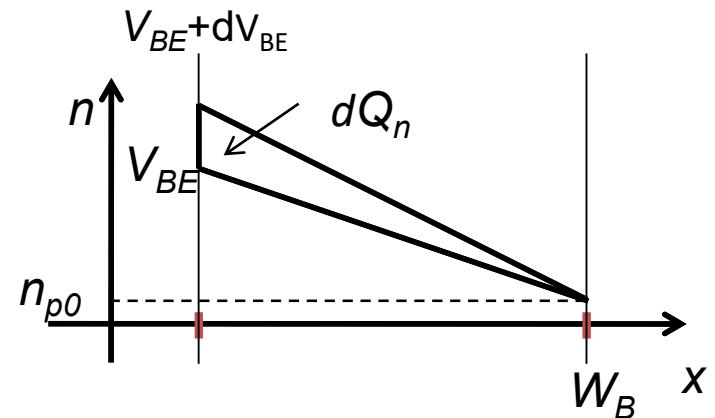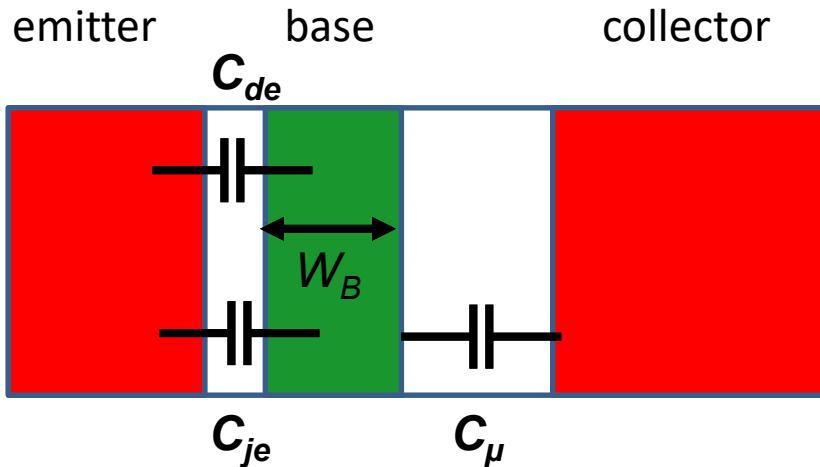
## capacitances: $C_\mu$ , $C_{je}$ , $C_{de}$ (9.2.2 (partially))



$C_{je}$ ,  $C_\mu$  : junction capacitances (small).

$C_{de}$  : diffusion (base charging) capacitance (only forward biased pn-junction). Change in  $V_{BE}$  give change in charge in base ( $Q_n$ ) -> capacitance


Capacitances become important for high-frequencies

$$C_{de} = \frac{dQ_n}{dv_{BE}} = \tau_F \frac{di_C}{dv_{BE}} = \tau_F g_m$$

$\tau_F$ : base transit time, average time for a carrier to cross base

$$\tau_F = W_B^2 / 2D_n$$
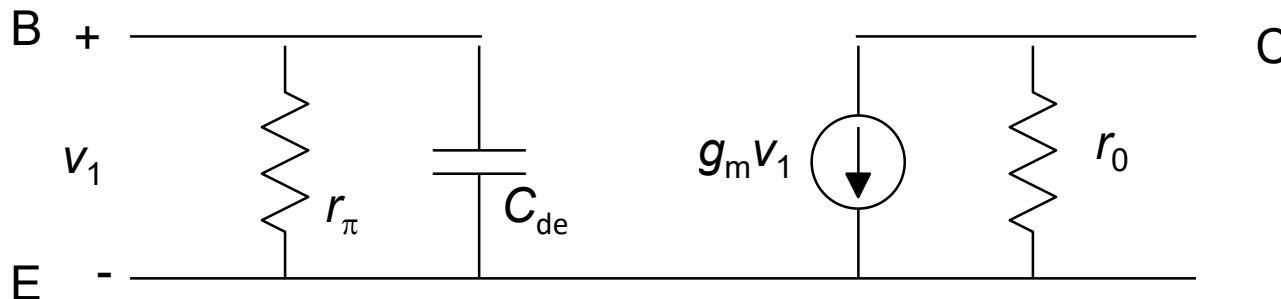
## (simple) small Signal Model – Active Mode



Transconductance – controls  
the current source

$$g_m = \frac{I_C}{V_T}$$

Remember:  
 $V_T = kT/q$

Input resistance –  $I_B$  change with  $V_{BE}$

$$r_\pi = \frac{\beta_F}{g_m}$$

Output resistance – Early effect

$$r_0 = \frac{V_A}{I_C} = \frac{V_A}{g_m V_T}$$

Diffusion (base charging) capacitance –  
forward biased BE junction

$$C_{de} = \tau_F g_m$$

## Example – low f model

A BJT is biased so that  $I_C=5\text{mA}$ .

Low frequency  $\rightarrow$  capacitances are “open circuit”



Parameters:

$$\beta = 500$$

$$V_A = 100 \text{ V}$$


$$V_T = 25.9 \text{ mV}$$

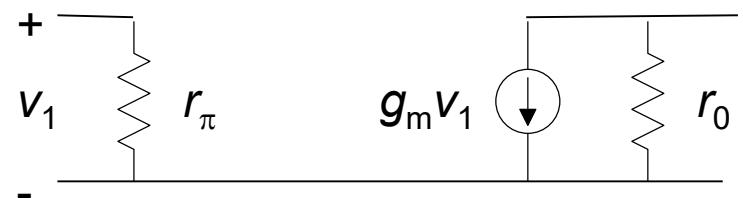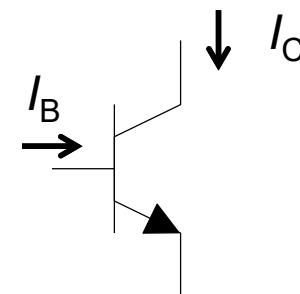Calculate  $I_B$  and the corresponding small signal model.


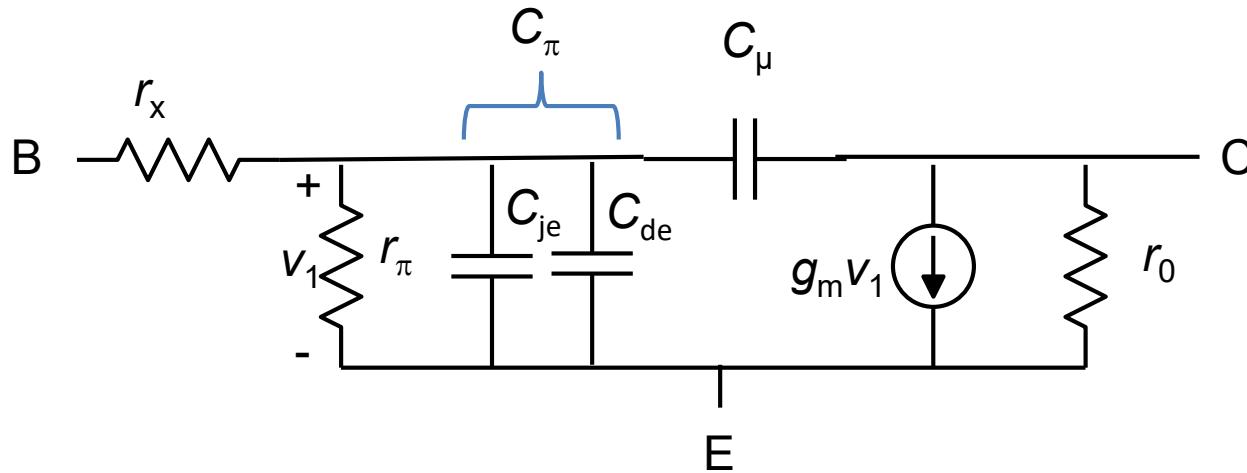
## Small Signal Model – more advanced

- Add junction capacitances  $C_\mu$  (BC junction) and  $C_{je}$  (BE junction).
- Sum capacitances  $C_\pi = C_{je} + C_{de}$ .
- Add series resistances in base ( $r_x$ ).



$r_x$ ,  $C_{je}$  and  $C_\mu$ : Depends on exact transistor geometry.

## Summary - BJTs

---

- NPN or PNP. NPN is faster due to higher electron mobility
- Active mode (used for amplifiers):
  - Emitter-base junction is forward biased (injects minority carriers into base)
  - Collector-base junction is reverse biased (removes minority carriers from base)
- Early effect: increasing  $V_{CE}$  extends the collector-base depletion region narrowing the base resulting in a higher diffusion current  $I_C$ .
- Small signal model:
  - Input resistance ( $r_\pi$ ) due change in base current ( $I_B$ ) when changing  $V_{BE}$ .
  - Output resistance ( $r_0$ ) due to Early effect.
  - Base charging capacitance ( $C_{de}$ ) due to change in charge in base region when changing  $V_{BE}$ .
  - Can add more capacitances and resistances to get more accurate (and complicated) model.

# State-of-the Art: SiGe Bipolar Transistor

- Vertical device
- Not symmetric – high emitter doping, lower in collector
- Heterostructure with graded  $E_g$  to enable high doping in base (low resistance) without backinjection into emitter.

