



# EITN90 Radar and Remote Sensing

## Lecture 9: Radar transmitters and receivers


Daniel Sjöberg

Department of Electrical and Information Technology
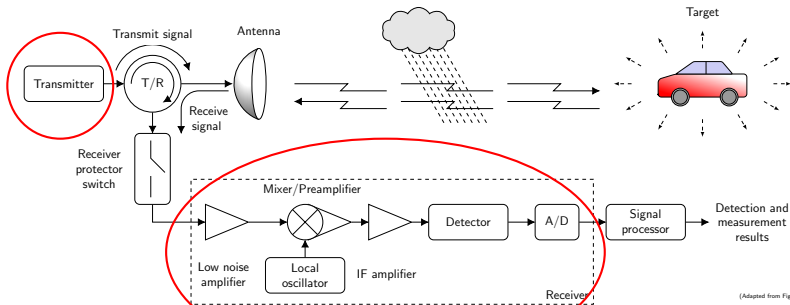
# Learning outcomes of this lecture

In this lecture we will

- ▶ Learn about the basic parameters of transmitters and receivers.
- ▶ See typical transmitter and receiver configurations.
- ▶ Understand different frequency stages in the receiver chain.
- ▶ See influence of receiver and ADC dynamic range.



(Adapted from Fig. 1-1)

## 1 Transmitters

- Transmitter configurations and parameters

- Power sources and amplifiers

- Modulators and power supplies

- EM transmitter impacts and operational considerations

## 2 Receivers

- Receiver types

- Major receiver functions

- Demodulation

- Receiver noise power

- Receiver dynamic range

- Analog-to-digital data conversion

## 3 Conclusions

# Outline

---

## 1 Transmitters

- Transmitter configurations and parameters

- Power sources and amplifiers

- Modulators and power supplies

- EM transmitter impacts and operational considerations

## 2 Receivers

- Receiver types

- Major receiver functions

- Demodulation

- Receiver noise power

- Receiver dynamic range

- Analog-to-digital data conversion

## 3 Conclusions

# Outline

---

## 1 Transmitters

- Transmitter configurations and parameters

- Power sources and amplifiers

- Modulators and power supplies

- EM transmitter impacts and operational considerations

## 2 Receivers

- Receiver types

- Major receiver functions

- Demodulation

- Receiver noise power

- Receiver dynamic range

- Analog-to-digital data conversion

## 3 Conclusions

# The transmitter in a pulsed radar


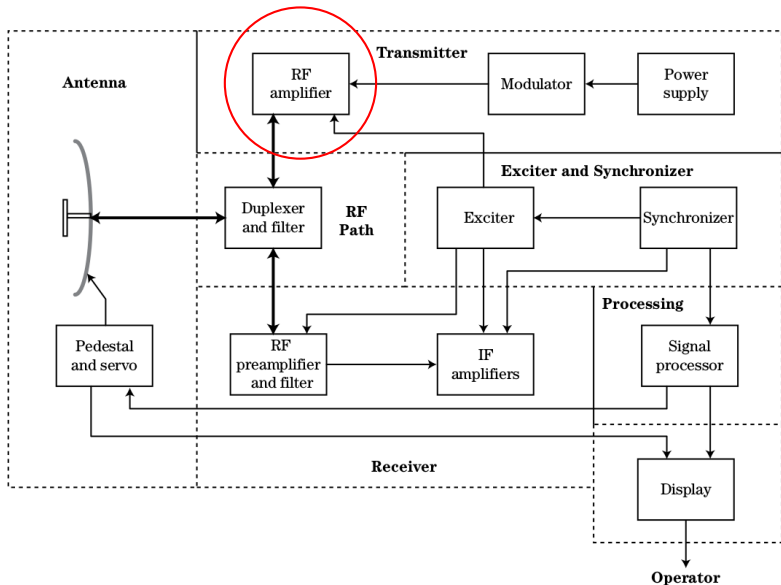


FIGURE 10-1 ■ Block diagram of typical pulsed radar. (From [1]. With permission.)

# The transmitter in a phased array

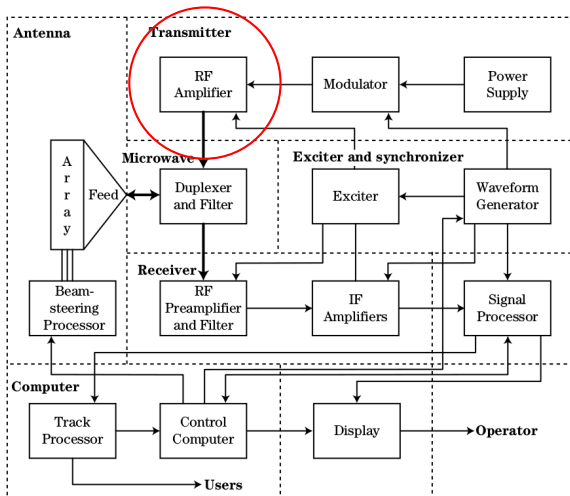

**FIGURE 10-2 ■**  
Block diagram of a  
typical phased array  
radar. (From [1]. With  
permission.)

Above is a passive array. In an active array, lower-power T/R-modules are placed at each array antenna element.

## Radar transmitter parameters

---

Average RF output power  $P_{\text{ave}}$  in terms of peak power  $P_p$ , pulse time  $\tau$ , and pulse repetition frequency PRF:

$$P_{\text{ave}} = P_p \underbrace{\tau \cdot \text{PRF}}_{=\text{duty cycle}}$$

Transmitter efficiency (typically in the order of 15% to 35%)

$$\eta_t = \frac{P_{\text{ave}}}{P_{\text{DC}}}$$

Overall radar efficiency (around 5% to 25% or more)

$$\eta_r = \frac{P_{\text{ave}}}{P_{\text{DC}} L_m L_\Omega}$$

$L_m$  = transmitter to antenna loss factor.


$L_\Omega$  = antenna ohmic loss factor.




# Transmitter configurations

Free running oscillator (direct use of the RF power, often noncoherent):

**FIGURE 10-3** ■  
Free-running  
oscillator-based  
transmitter.

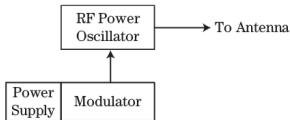


Master oscillator / power amplifier (amplification of RF power, often coherent):

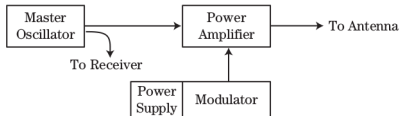


**FIGURE 10-4** ■  
Master oscillator/  
power amplifier  
transmitter.

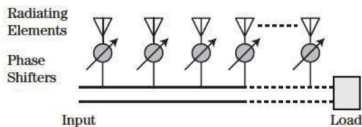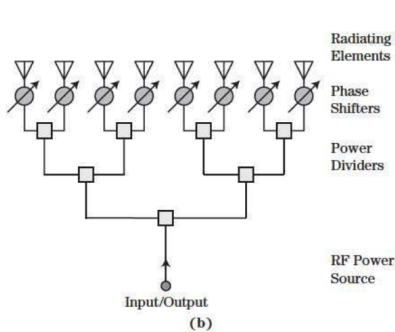
# Feeding of array antenna



(a)




(b)

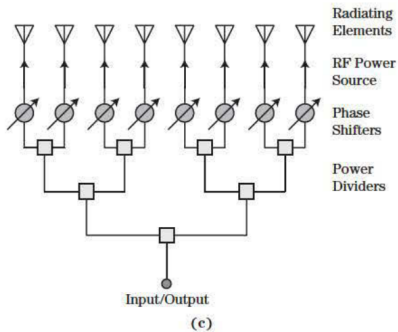

(c)

Distributing the feed using transmission lines.

## Feeding of array antenna, continued

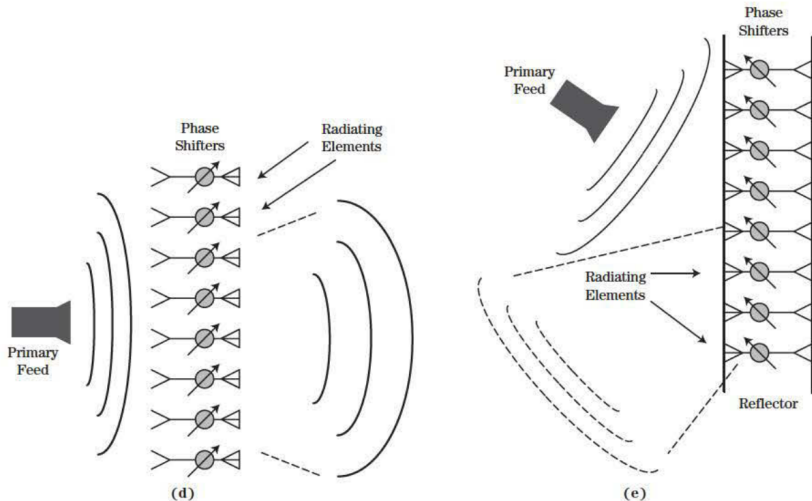

**FIGURE 10-5** ■ Examples of phased array feed types. (a) Constrained series feed. (b) Constrained corporate feed. (c) Constrained distributed feed. (d) In-line space-fed array. (e) Reflect space-fed array.

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation

Receiver noise power

Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions

## Different power sources


---

Two major variants of power sources can be identified, both as oscillators and amplifiers:

- ▶ Vacuum electron devices (VED, high power, relatively narrow bandwidth, bulky)
- ▶ Solid state devices (GaAs, GaN, SiC, lower power, wide bandwidth, flexible and integrable)

# The magnetron

**FIGURE 10-8** ■  
Cross section of a  
magnetron tube.

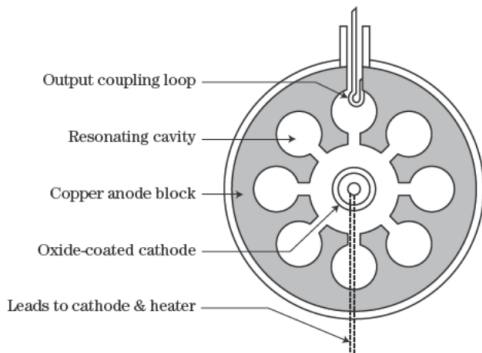


Electrons are emitted from the cathode, and moves in circular orbits inside the cavity. The startup process is random, hence the pulses are incoherent. See for instance <http://www.radartutorial.eu/08.transmitters/Magnetron.en.html> for more in-depth explanation. You can also follow the course EITN80 Electrodynamics, starting next study period.

# The magnetron, physical appearance


---

**FIGURE 10-9** ■  
Cutaway drawing of  
a typical magnetron.

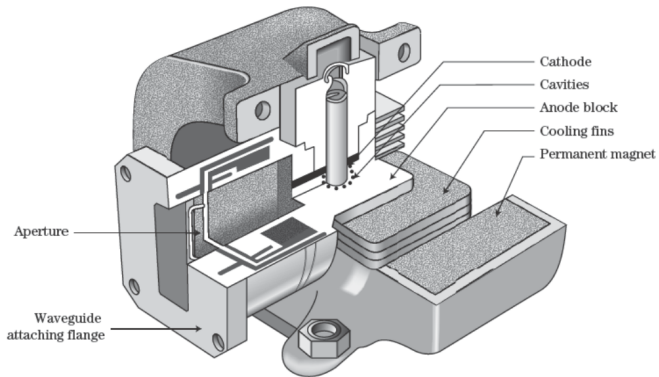

# Klystron

**FIGURE 10-12** ■  
Schematic view of a  
two-cavity klystron  
tube.

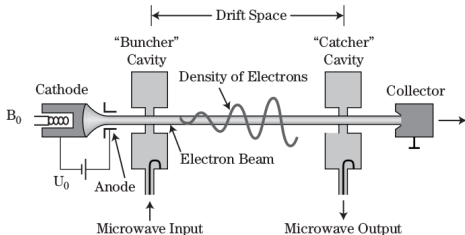

**FIGURE 10-13** ■  
A variety of klystron  
tubes. (Photo  
courtesy of CPI.  
With permission.)




<http://www.radartutorial.eu/08.transmitters/Klystron.en.html>



# Travelling wave tube (TWT)

---

1. Electron Gun
2. RF Input
3. Magnets
4. Attenuator
5. Helix Coil
6. RF Output
7. Vacuum Tube
8. Collector

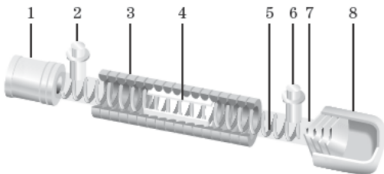

**FIGURE 10-14** ■  
Functional diagram  
of a traveling wave  
tube.

Careful design makes the electromagnetic wave on the helix coil to propagate at the same speed as the electron beam, coupling power from the electron beam to the RF port.

[http://www.radartutorial.eu/08.transmitters/Traveling Wave Tube.en.html](http://www.radartutorial.eu/08.transmitters/Traveling%20Wave%20Tube.en.html)

# Some common vacuum devices

**TABLE 10-1** ■ Compilation of Characteristics of Common Vacuum Devices


Tube Type	Frequency	Power Out (Typical)	Attributes	Applications
	Bandwidth		Drawbacks	
Klystron	0.1–300 GHz 5–10%	10 kW CW ** 10 MW Pulse	High Power 40–60% Efficient Low Noise Narrow Bandwidth	Radar Television Industrial Heating Satellite Uplinks Medical Therapy Science
Traveling Wave Tube (Helix)	1–90 GHz Wide Bandwidth 2–3 Octaves*	20 W CW 20 kW Pulse	Broad Bandwidth Power Handling Limitations Efficiency	Electronic Warfare Communications Commercial Broadcasting Industrial Applications
Coupled-Cavity TWT	1–200 GHz 10–20%	300 W CW 250 kW Pulse	Average Power Capability Complex & Expensive Slow Wave Structure	Airborne Radar Satellite Communications AEGIS FC Illuminator
Magnetron	1–90 GHz N/A	100 W CW 10 MW Pulse	Simple–Inexpensive Rugged Noisy	Radar/Medical Industrial Heating
Crossed-Field Amplifier	1–30 GHz 10–20%	1000 W CW 5 MW Pulse	Compact Size 30–40% Efficient Complex and Expensive Slow Wave Structure	Transportable Radars Shipboard Radar Seeker Radar Industrial Heating
Gyrotron	30–200 GHz 10% Max	0.2–3 MW Pulse	High Power at High Frequencies High Voltage Required	High-Frequency Radar Fusion Accelerators Industrial Heating

\*One octave is the range defined where the highest frequency is twice the lowest (e.g., 2–4, 4–8).

\*\*DOE's APT klystrons will run at 1 MW CW.

Source: From [15] (with permission).

# Solid state T/R modules

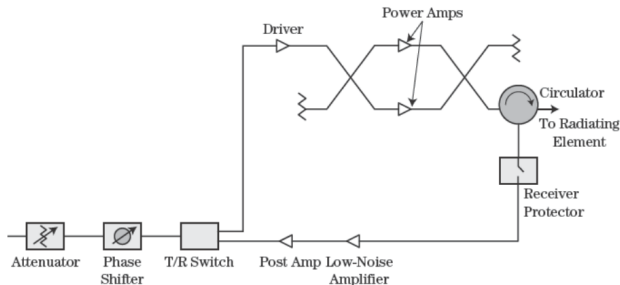


**FIGURE 10-16** ■  
Example T/R module  
architecture.

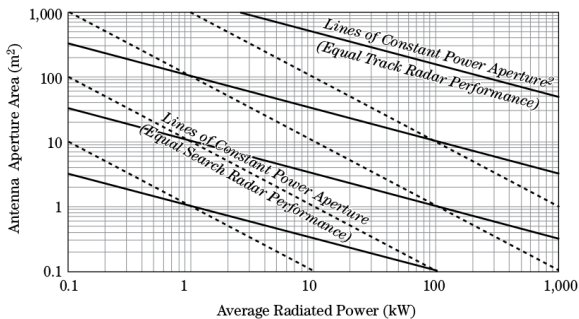- ▶ Attenuator control of receive gain.
- ▶ Phase shifter for beam steering.
- ▶ Circulator improves match to antenna.
- ▶ Receiver is protected from high power by switch.

# Trade-off power-aperture

**FIGURE 10-17** ■  
Aperture area and radiated power for constant  $PA$  and  $PA^2$ .




Constant  $P_t A_e =$  search radar.

Constant  $P_t A_e^2 =$  track radar.

## Solid state active-aperture arrays

Curve for fixed  $P_t A_e G \sim P_t A_e^2$ .

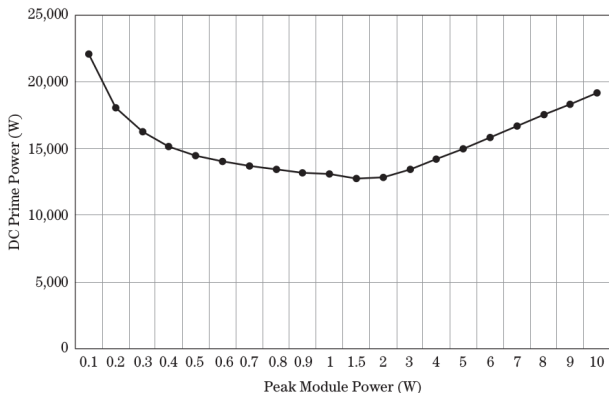

**FIGURE 10-18** ■ Example phased array radar prime power requirement as a function of peak module power for a given level of power-aperture-gain product.

At low module transmit power (large aperture), receive-side is dominating DC prime power, increasing as aperture increases.

At high module transmit power, DC prime power needs to increase to sustain increased transmit power.

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

**Modulators and power supplies**

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation


Receiver noise power

Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions

# Pulse forming network

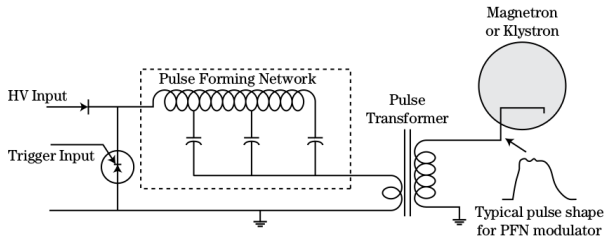


**FIGURE 10-21** ■  
Simplified diagram  
of a PFN modulator.

The pulse forming network creates a pulse with intended pulse length, modulating an RF power source. The trailing edge of the pulse may not be well defined, since it is based on the discharge characteristics of the PFN.

► Discussion

# Active-switch modulator


**FIGURE 10-22** ■  
Simplified diagram  
of an active switch  
modulator.

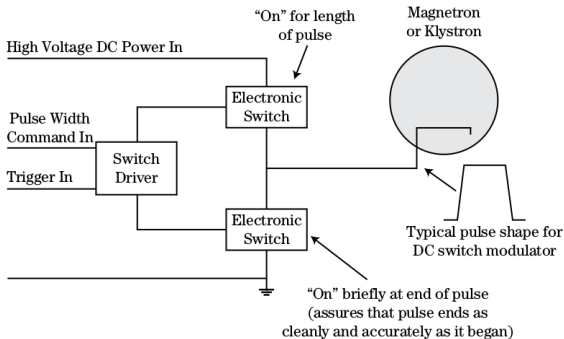

To have both leading and trailing edges well defined, on- and off-switches can be employed. Solid state switches provide fast switching, but may require stacking in series to handle high voltage.




# Power supplies

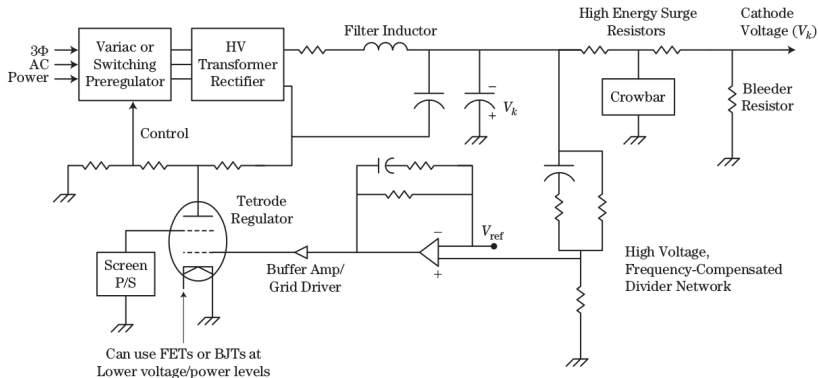

**FIGURE 10-23** ■ Typical high voltage power supply for a radar transmitter.

Not all parts of this schematic are explained in the book. Do not worry too much, it is quite specialized knowledge.

# Power supplies, active aperture

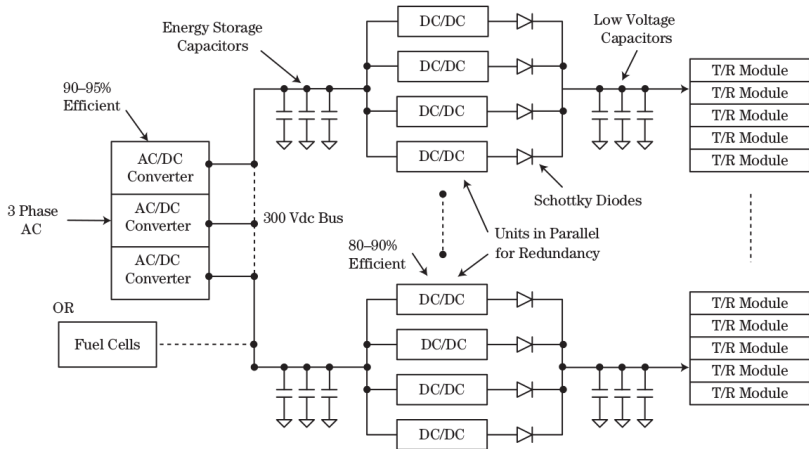

**FIGURE 10-25** ■ An active aperture power supply configuration.

The parallel architecture of an active array promotes distribution of the power supply across the array as well.

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation


Receiver noise power

Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions


# Radar Spectrum Engineering Criteria (RSEC)

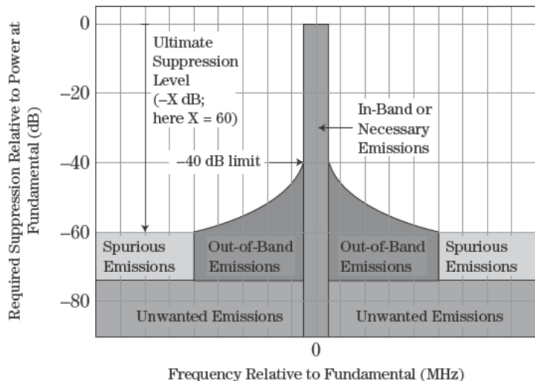

**FIGURE 10-26** ■ Various signal domains considered by the RSEC.

There are regulations for the spectral emission from radars.

# Radar Spectrum Engineering Criteria (RSEC)

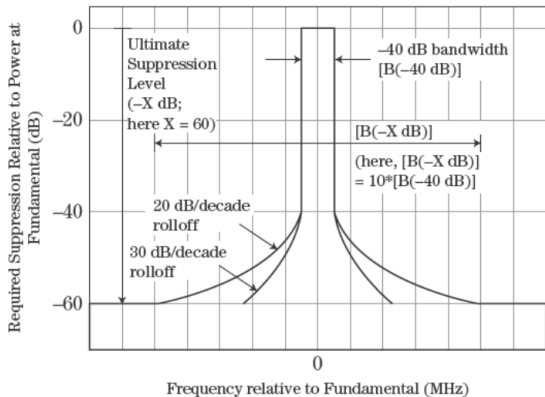


**FIGURE 10-27** ■  
Generic RSEC  
emissions box.

There are regulations for the spectral emission from radars.

# Radar Spectrum Engineering Criteria (RSEC)


**FIGURE 10-28** ■

Figure shows a measured emission within the RSEC box. At about 3050 MHz the system exceeds the allowable limits for the subject group.

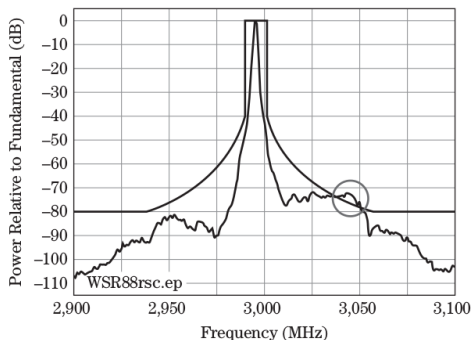

Breach of regulations at 3 050 MHz.

# Spectral purity

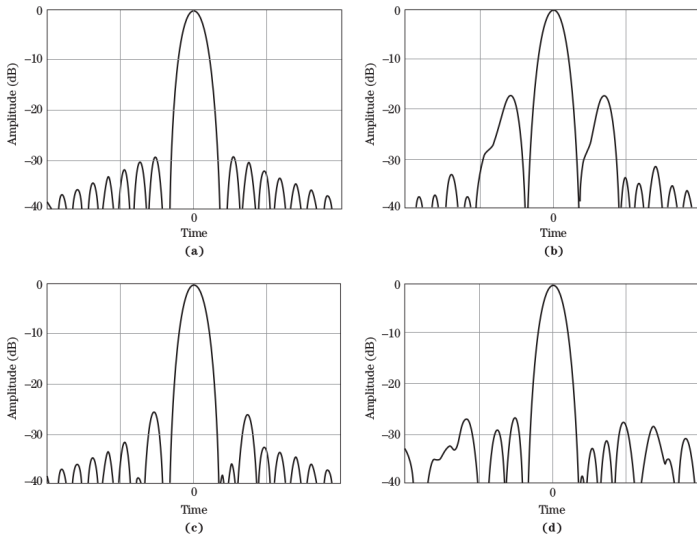

**FIGURE 10-29** ■ Time sidelobe response with intrapulse modulation errors. (a) Idealized response with no intrapulse modulation error. (b) 3 cycles of 10 degrees rms sinusoidal modulation error. (c) 3 cycles of 2 degrees rms sinusoidal modulation error. (d) 10 degrees random modulation error.

# Operational considerations

---

## Reliability

- ▶ High operating temperature and voltages reduce life time.
- ▶ Increased risk for failure when concentrating to few sources.
- ▶ Temperature sensors and power control may prevent failure.
- ▶ Highly parallel systems provide high redundancy.

Heat can be removed in essentially three ways:

- ▶ Normal air-convection currents (low-power devices)
- ▶ Forced-air cooling
- ▶ Liquid cooling

## Safety issues

- ▶ High power: overvoltage, overcurrent.
- ▶ X-rays, material dependent wavelengths, lead shielding.
- ▶ Hazardous materials used, many are toxic.
- ▶ Strong RF field may ignite electro-explosive devices.
- ▶ Tissue heating from RF exposure.



# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation

Receiver noise power

Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation

Receiver noise power


Receiver dynamic range

Analog-to-digital data conversion


## 3 Conclusions

# Radar receivers

**FIGURE 11-1** ■  
General receiver  
functions.

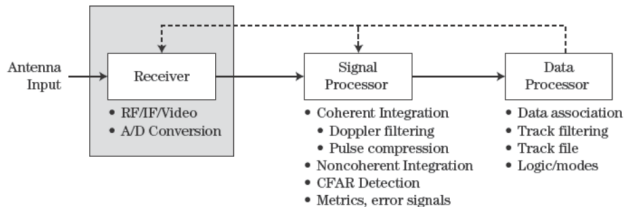

**FIGURE 11-2** ■  
Major receiver  
elements.

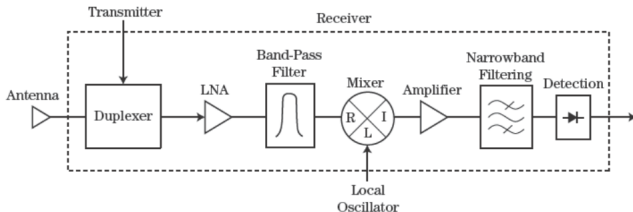

Receivers typically provide down-conversion of the received signal, amplification, and filtering.

# Receiver types

---

Receiver types discussed in the book include

- ▶ Crystal video receivers (rectifier)
- ▶ Superregenerative receivers
- ▶ Homodyne receivers (mixing with transmitted signal)
- ▶ Superheterodyne receivers (mixing with LO)
- ▶ Digital receivers (digitization of received signal)
- ▶ Instantaneous frequency measurement receivers
- ▶ Channelized receivers (polarization, I/Q, monopulse etc)

## Different frequencies


---

A number of frequencies are used in describing receivers (in decreasing amplitude):


- ▶ RF = radio frequency, carrier wave
- ▶ LO = local oscillator, reference inside radar
- ▶ IF = intermediate frequency,  $RF - LO$
- ▶ VF = video frequency, baseband

# Crystal video receivers

---

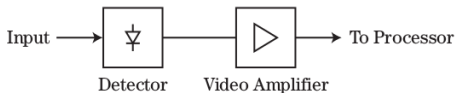

**FIGURE 11-3** ■  
Crystal video receiver.

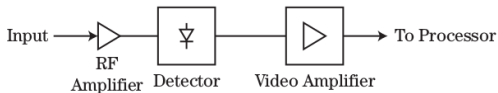


**FIGURE 11-4** ■  
Modified crystal video receiver.

Detects the amplitude envelope of the radar signal, incoherent as it does not preserve phase information.

# Homodyne receivers

---


**FIGURE 11-5** ■  
Homodyne receiver.

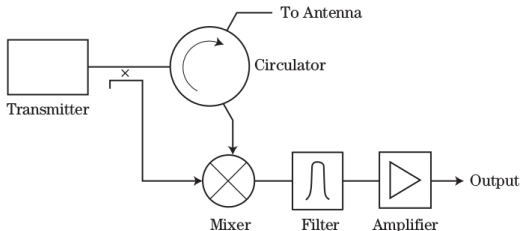

Uses the transmitted signal as reference, requires the transmitter to be on while receiving.

# Superheterodyne receivers

**FIGURE 11-6** ■  
Generic  
superheterodyne  
receiver  
configuration.

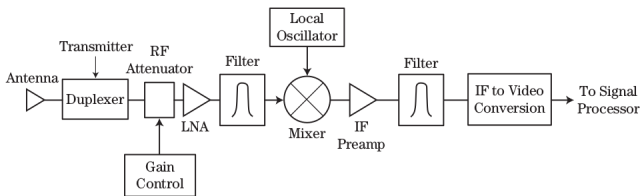

“Super” means LO frequency can be tuned, often to follow the transmit RF. The gain control of the attenuator can be used to reduce sensitivity to near targets, and improve dynamic range. Bandpass filters remove unwanted mixer products and out-of-band signals.



# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation


Receiver noise power

Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions

# RF preselection

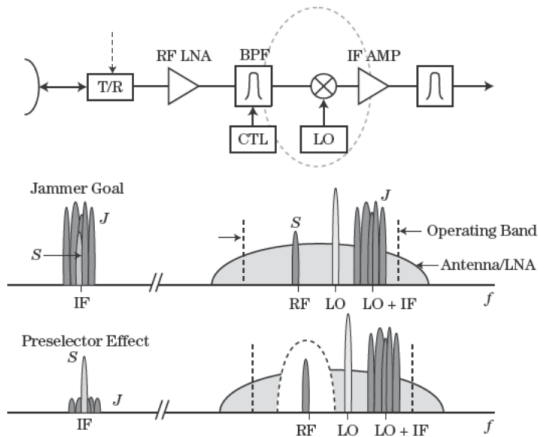


**FIGURE 11-7 ■**  
Effects of  
preselection on  
rejection of jammer  
signals.

Filtering the RF can reduce sensitivity to jammers. No effect if the jammer is exactly at the RF.

## Mixer products

---

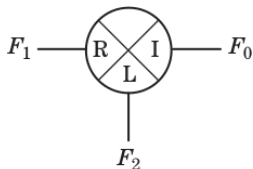

**FIGURE 11-10** ■

Mixer model.

The output of the mixer can be described as

$$I_0 = F(V) = a_0 + a_1V + a_2V^2 + a_3V^3 + \dots + a_nV^n + \dots$$


With two different frequencies,  $V = V_1 \sin(2\pi f_1 t) + V_2 \sin(2\pi f_2 t)$ , the output will have frequencies at all combinations

$$mf_1 + nf_2, \quad m, n = 0, \pm 1, \pm 2, \dots$$


Typically,  $f_1 - f_2$  is desired, and  $f_1 + f_2$  (and others) need to be rejected.

# Multiple downconversions

**FIGURE 11-8** ■  
Single  
downconversion  
process.

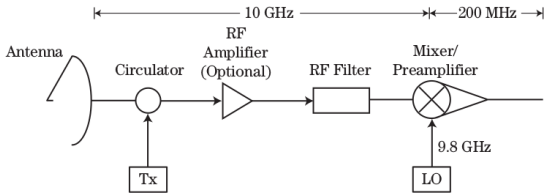

**FIGURE 11-9** ■  
Double  
downconversion  
process.

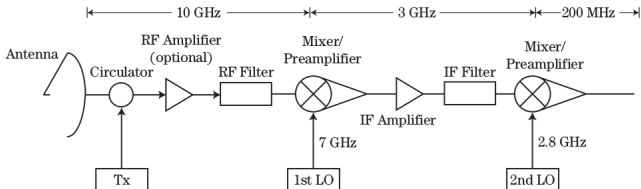

Several frequency stages can help the design of filters. The extra stages make it easier to design the filters, since intermodulation products are far apart. Example:  $2 \cdot 7 - 10 = 4$ ,  $2 \cdot (10 - 7) = 6$ .

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

**Demodulation**

Receiver noise power

Receiver dynamic range

Analog-to-digital data conversion


## 3 Conclusions

# Diode and square-law detectors

---


**FIGURE 11-11** ■

Basic diode detector.

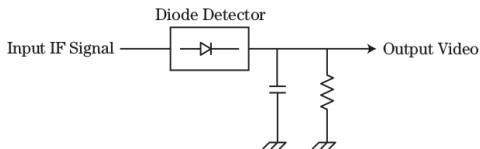


**FIGURE 11-12** ■

Square law detector.

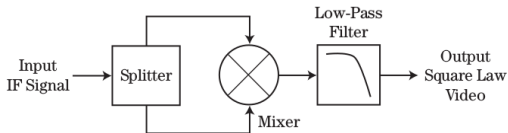


The RF signal can be converted to video based on amplitude or square amplitude. Affects the probability distributions used in detection theory.

# Log amplifier

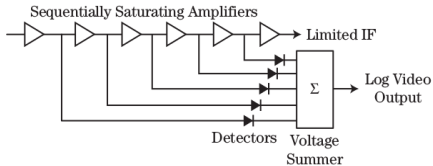


**FIGURE 11-13** ■  
Log amplifier block diagram.

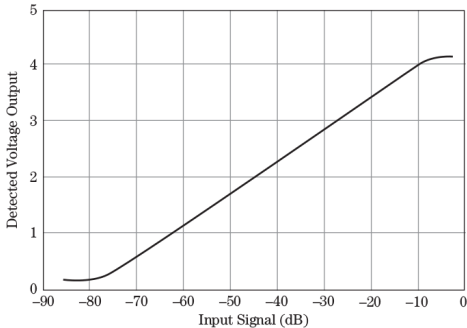

**FIGURE 11-14** ■  
Typical log amplifier output characteristic.

Provides a linear response over large dynamic range in dB scale.

# Coherent demodulation (I/Q)

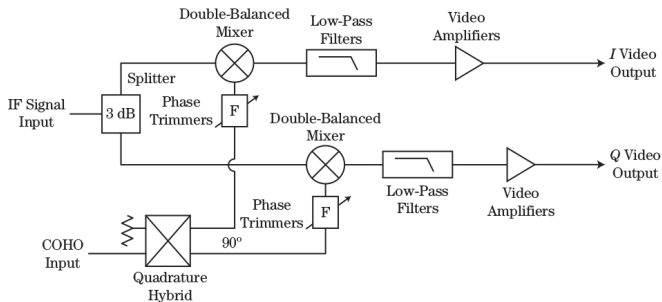

**FIGURE 11-16** ■  
Circuit for analog  
coherent I and Q  
processing.

Mixing with two signals, one in-phase (I) and one in quadrature (Q), makes it possible to keep phase information in the downconverted signal. The analytic signal is

$$a = I + jQ = Ae^{j\phi}$$

with amplitude  $A = \sqrt{I^2 + Q^2}$  and phase  $\phi = \arg(I + jQ)$ .



# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation

**Receiver noise power**

Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions

## Signal to noise ratio and noise figure

---

The signal to noise ratio is given by the radar range equation (note there is a  $\lambda^2$  factor missing in the book's equation (11.9))

$$\text{SNR} = \frac{P_t G^2 \lambda^2 \sigma}{(4\pi)^3 k T_0 B_n F L_s R^4}$$

The noise figure of the  $n$ :th amplifier stage is

$$F_n = \frac{S_{\text{in}}/N_{\text{in}}}{S_{\text{out}}/N_{\text{out}}} = \frac{1}{G_n} \frac{N_{\text{out}}}{N_{\text{in}}}$$

The overall noise figure is then given by Friis' formula (terms of  $-1$  missing in book's equation (11.11))

$$F = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$$

The noise bandwidth  $B_n$  is often taken as the final IF bandwidth.

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation

Receiver noise power


**Receiver dynamic range**

Analog-to-digital data conversion

## 3 Conclusions

# Compression point, intercept point


**FIGURE 11-20** ■  
Receiver distortion  
versus input power  
intercept point.

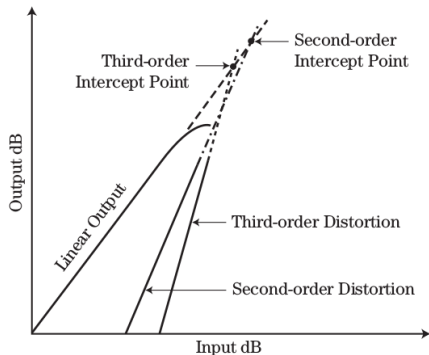

The desired linear output of the amplifier is compromised by saturation and nonlinearities.


► Discussion

# Improving receiver dynamic range using STC

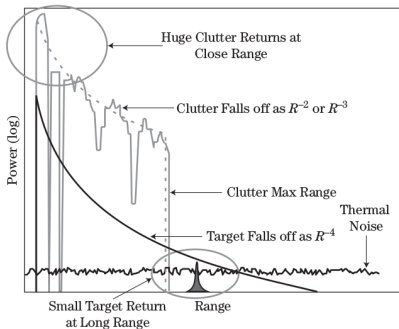

**FIGURE 11-21** ■  
Return signal  
amplitudes from  
targets and clutter.

**FIGURE 11-22** ■  
Sensitivity time  
control attenuation.

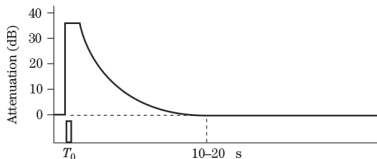

By introducing attenuation at early times, strong responses from near-range objects and clutter do not compromise dynamic range.

# Outline

---

## 1 Transmitters

Transmitter configurations and parameters

Power sources and amplifiers

Modulators and power supplies

EM transmitter impacts and operational considerations

## 2 Receivers

Receiver types

Major receiver functions

Demodulation

Receiver noise power


Receiver dynamic range

Analog-to-digital data conversion

## 3 Conclusions

# Typical ADC configuration

**FIGURE 11-23** ■  
Typical ADC  
configuration.

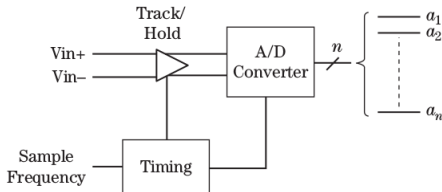

The track/hold circuit samples the signal and keeps its output constant until the analog to digital conversion is performed. The signal is then

$$V_a = V_{FS} \left( \sum_{i=1}^n a_i 2^{-i} \right) + q_e$$

where  $V_{FS}$  is the full-scale voltage of the ADC, and  $q_e$  is the quantization error.

# Examples of ADC:s

**TABLE 11-1** ■ Sample of Analog-to-Digital Converters

Part No.	Manufacturer	Bits	Sampling Speed Msamples/sec	SFDR <sup>a</sup> dBc	SNR dB
ADC083000	National Semiconductor	8	3,000	57	45.3
MAX19692	Maxim	12	2,300	68@1.2 GHz	NS
AT84AS004	Atmel	11	2,000	55	51
ADC081500	National Semiconductor	8	1,500	56	47
Model 366	Red Rapids <sup>b</sup>	2/8	1,500	57	47
TS860111G2B	Atmel	11	1,200	63	49 <sup>c</sup>
ADC10D1000	National Semiconductor	10	1,000	66	57
MAX5890	Maxim	14	600	84@16 MHz	NS
MAX5888	Maxim	16	500	76@40 MHz	NS
Model 365	Red Rapids <sup>b</sup>	2/14	400	84	70
ADS62P49	Texas Instrument	14	250	85	73
LTC2208	Linear Technology	16	130	83	78
AD9446	Analog Devices	16	110	90	81.6

Note: NS, not specified.

<sup>a</sup>Spurious-free dynamic range.

<sup>b</sup>Dual sampler.


<sup>c</sup>Noise power ratio.

The ADC used in the lab was capable of about 100 000 samples/s (about 12 000 samples/s claimed using python).



# Dynamic range of ADC:s

**FIGURE 11-24** ■  
Dynamic range of a  
signal-following  
ADC.

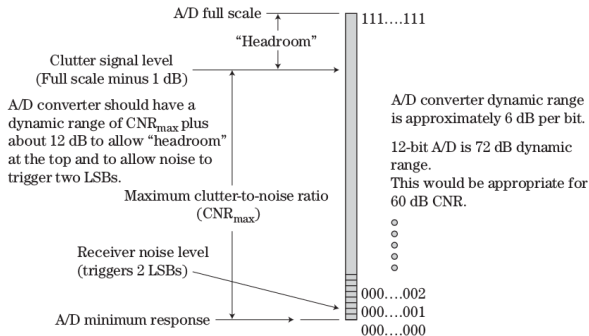

The full dynamic range of the ADC is not attainable, due to headroom to maximum level, and noise level.

# Outline

---

## 1 Transmitters

- Transmitter configurations and parameters

- Power sources and amplifiers

- Modulators and power supplies

- EM transmitter impacts and operational considerations

## 2 Receivers

- Receiver types

- Major receiver functions

- Demodulation

- Receiver noise power

- Receiver dynamic range

- Analog-to-digital data conversion

## 3 Conclusions

# Conclusions


---

- ▶ Transmitters:
  - ▶ Two families of power sources: vacuum electronic devices, and solid state devices.
  - ▶ Three major components: 1) oscillator/power amplifier, 2) modulator, 3) power supply.
  - ▶ Incoherent (random startup) or coherent (reproducible startup).
  - ▶ Concentrated or distributed feed in array antennas.
- ▶ Receivers:
  - ▶ Incoherent and coherent receivers.
  - ▶ Demodulation: incoherent, coherent (I/Q).
  - ▶ Noise power: noise figure, multiple stages, bandwidth.
  - ▶ ADC: dynamic range reduced by clutter signal and noise level.

# Discussion

---

**FIGURE 10-3** ■  
Free-running  
oscillator-based  
transmitter.

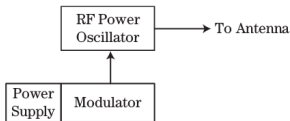


Why would the above configuration be deemed “incoherent”?

◀ Go back

# Discussion

---

**FIGURE 10-3** ■  
Free-running  
oscillator-based  
transmitter.

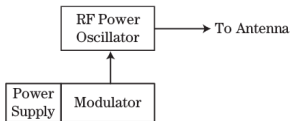


Why would the above configuration be deemed “incoherent”?

Answer: The only thing we can do with the RF power oscillator is to turn it on or off using the modulator, but the phase is out of control.

[◀ Go back](#)


# Discussion

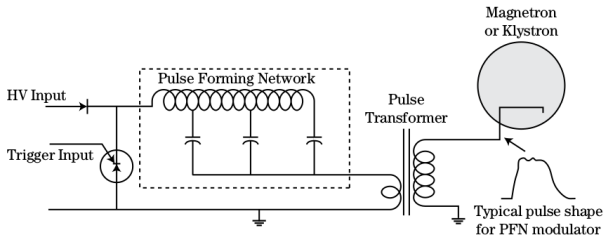

**FIGURE 10-21** ■  
Simplified diagram  
of a PFN modulator.

Why does the PFN produce two flanks (and not just one) of the RF pulse after the trigger input drains the energy from the PFN?

# Discussion

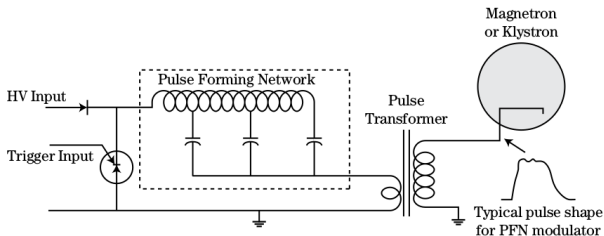

**FIGURE 10-21** ■  
Simplified diagram  
of a PFN modulator.

Why does the PFN produce two flanks (and not just one) of the RF pulse after the trigger input drains the energy from the PFN?

Answer: The pulse transformer only reacts to time-varying currents. At the trigger input instance, the PFN is drained of energy and the pulse starts. Some time later, the PFN is again fully charged and no current is going through the transformer, putting a stop to the RF pulse.

# Discussion

---

Why is it important to down-convert the received signal (remove the carrier frequency)?

◀ Go back



# Discussion

---


Why is it important to down-convert the received signal (remove the carrier frequency)?

Answer: Without down-conversion, we put extremely high requirements on the AD sampler circuit. At a lower IF or video frequency, these requirements can be considerably relaxed.

[◀ Go back](#)

# Discussion


**FIGURE 11-20** ■  
Receiver distortion  
versus input power  
intercept point.

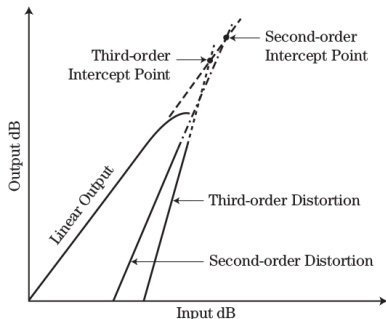

Is it possible to measure the intercept point directly, that is, setting the input dB to one certain value and read off the output dB corresponding to the intercept point?

# Discussion

**FIGURE 11-20** ■  
Receiver distortion  
versus input power  
intercept point.

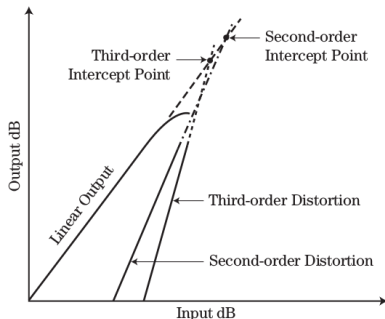

Is it possible to measure the intercept point directly, that is, setting the input dB to one certain value and read off the output dB corresponding to the intercept point?

Answer: No, the very concept of an intercept point is an asymptotic property which is never attained in a real system.